
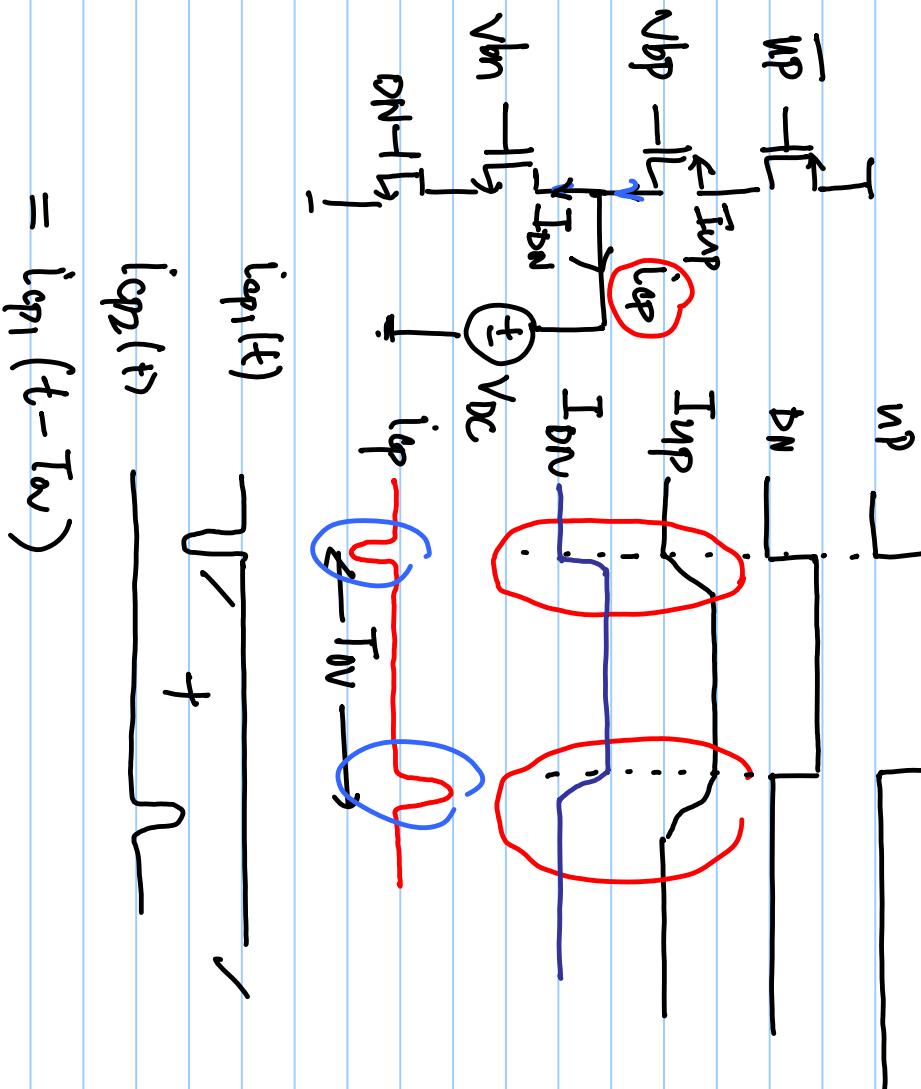


Lecture #37Charge-pump
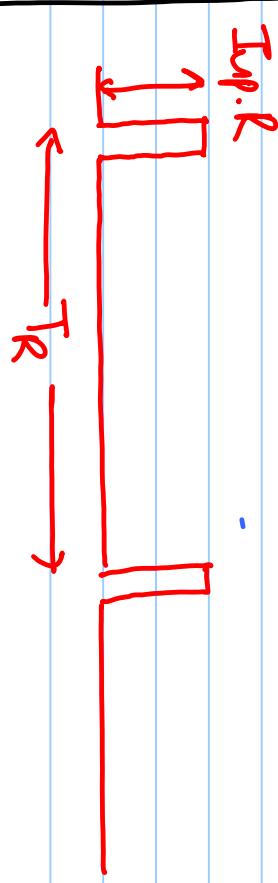
$$i_{cp} = \frac{V_{CH}}{R} - (I_{DN} - I_{UP}) R$$



$$V_{CH} = a_0 + \sum a_n \cos(n\omega_k t) + b_n \sin(n\omega_k t)$$

$$i_{cp1}(t) = \int_0^T a_n \cos(n\omega_k t) dt$$

$$i_{cp2}(t) = \int_0^T b_n \sin(n\omega_k t) dt$$

$$= i_{cp1}(t - T_R)$$

$$\frac{\text{Imp.R}}{m\omega_R} \int_0^{T_{os}} \sin(m\omega_R t) dt = \frac{a_m}{2} \int_0^{T_R} 1 - \cos(2m\omega_R t) dt$$

$$\frac{\text{Imp.R}}{m\omega_R} \sin(m\omega_R T_{os}) = \frac{a_m}{2} \cdot T_R$$

$$a_m = \frac{2}{T_R} \underbrace{\frac{\text{Imp.R}}{m\omega_R} \sin\left(m \cdot \frac{2\pi}{T_R} \cdot T_{os}\right)}_{\frac{2\pi}{T_R}}$$

$$a_m = \frac{1}{m\pi} \times \frac{\text{Imp.R}}{T_R} \sin\left(m \cdot \frac{2\pi}{T_R} \cdot T_{os}\right) \quad \Rightarrow \quad a_1 = \frac{\text{Imp.R}}{\pi} \sin(\phi_{os})$$

$$\frac{\text{Imp.R}}{m\omega_R} \left[-\cos(m\omega_R t) \right]_0^{T_{os}} = \frac{b_m}{2} \int_0^{T_R} 1 + \cos(2m\omega_R t) dt$$

$$\frac{I_{up,R}}{m\omega_R} \left[1 - \cos(m\omega_R T_{us}) \right] = \frac{b_m}{2} \cdot T_R$$

$$b_m = \frac{1}{m\pi} I_{up,R} \left[1 - \cos(m\omega_R T_{us}) \right]$$

$$V_{ctr1} = V_{ctr10} + a_0 + a_1 \cos(\omega_R t)$$

$$f_{vco} = k_{vco} (V_{ctr10} + a_0 + a_1 \cos(\omega_R t))$$

$$V_{out} = \sin \left(2\pi \underbrace{k_{vco}(V_{ctr10} + a_0)t + \int 2\pi k_{vco} a_1 \cos(\omega_R t) dt}_{= \sin(\omega_0 t - \frac{2\pi k_{vco} a_1}{\omega_R} \sin(\omega_R t))} \right)$$

$$\beta = \frac{2\pi k_{vco}}{\omega_R} a_1 = \underbrace{\frac{2\pi k_{vco}}{\omega_R} \cdot \frac{I_{up,R}}{\pi} \sin(\Phi_R)}_{\beta}$$

$$\text{Ref. Spur} = +20 \log_{10} \left(\frac{2\pi K_{vo} \cdot \text{Imp.R} \sin(\phi_{os})}{W_R \cdot f_R} \right)$$



$$= 20 \log_{10} \left(\frac{\text{Mag. of spur}}{\text{Mag. of correct}} \right)$$

$$= 20 \log_{10} \left(\frac{K_{vo} \cdot \text{Imp.R}}{W_R} \sin(\phi_{os}) \right)$$

$$\left[\text{dB} \right]$$


$$= 20 \log_{10} \left(\frac{f_{BW}}{2\pi f_R} \sin(\phi_a) \right) + 20 \log_{10} \left(\frac{f_{12}}{f_R} \right)$$

$$\left[\text{dB} \right]$$

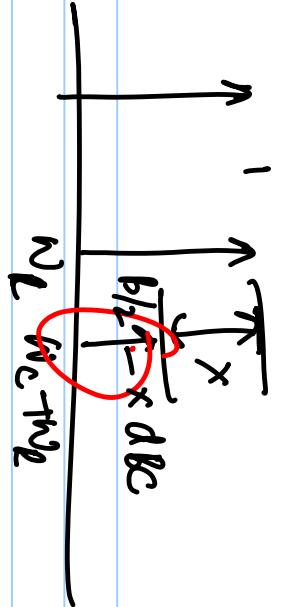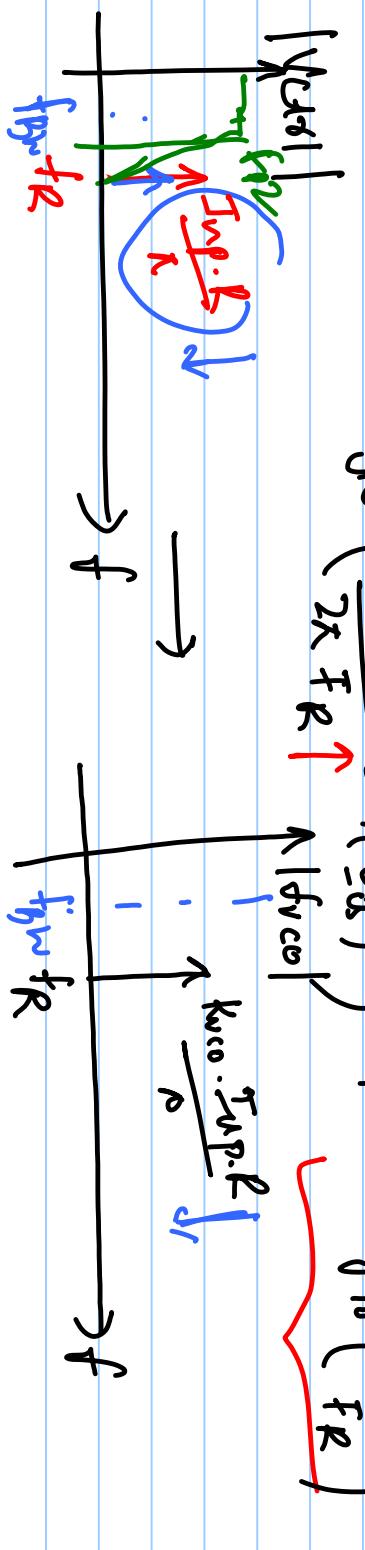

Source-switched

drain-switched

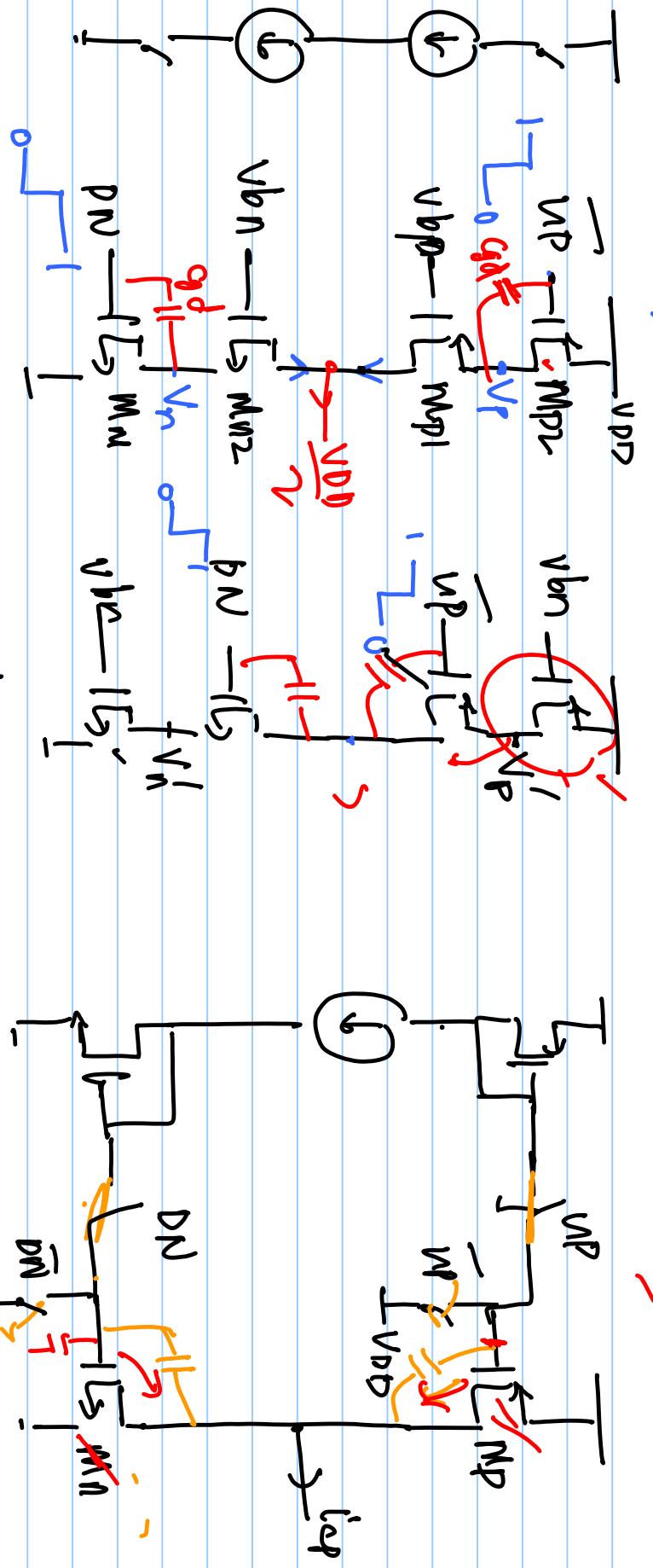

OFF state: $V_h = V_{bp} - |V_{tp}|$

$$V_p = V_{bp} + |V_{tp}|$$

ON state: $V_h = 0$

$$V_p = V_{bp}$$

OFF state: $V_h' = 0$

$$V_p' = V_{DD}$$

ON state: $V_h' =$

$$V_p' =$$

