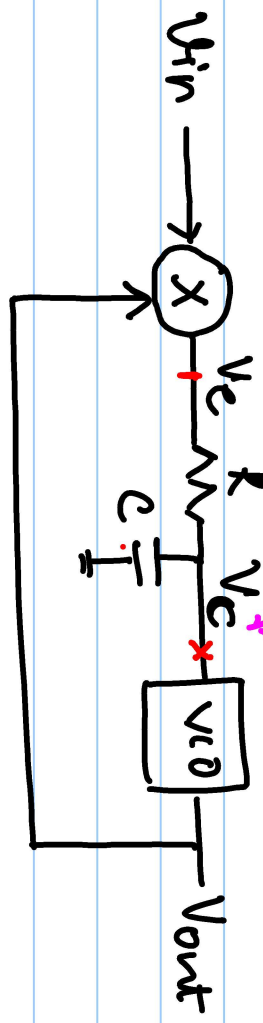


Lecture # 8

$V_e = V_p$

$V_e = \int_{-\infty}^{\infty} I \cdot V_e' \equiv \frac{1}{T_i} \int dt$



at $t=0$ $\Delta\omega(0) = \omega_{in} - \omega_{free}$; $V_c = 0$

if $\Delta\omega(0) > K_{PD}K_{VCO}$


$$\frac{\Delta\omega(0)}{K_{PD}K_{VCO}} > 1$$

$$V_c = \frac{1}{2} \sin(\Delta\omega(0) \cdot t)$$

$$\phi_{err}(t) = \Delta\omega(0) \cdot t$$



$$\omega_{out} = \omega_{free} + K_{VCO} \cdot V_c$$
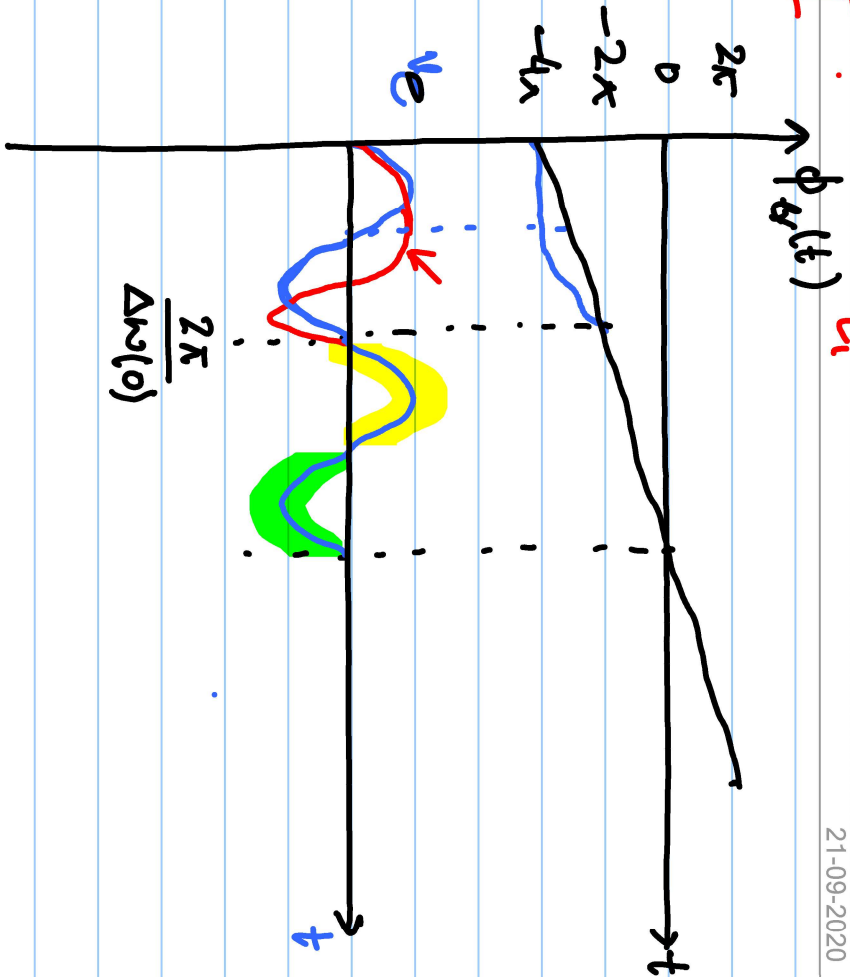
$$\dot{\phi}_{err} = \Delta\omega(0) - K_{VCO} \cdot V_c$$



V_c is small $\Rightarrow \frac{d\phi_{err}}{dt}$ is small

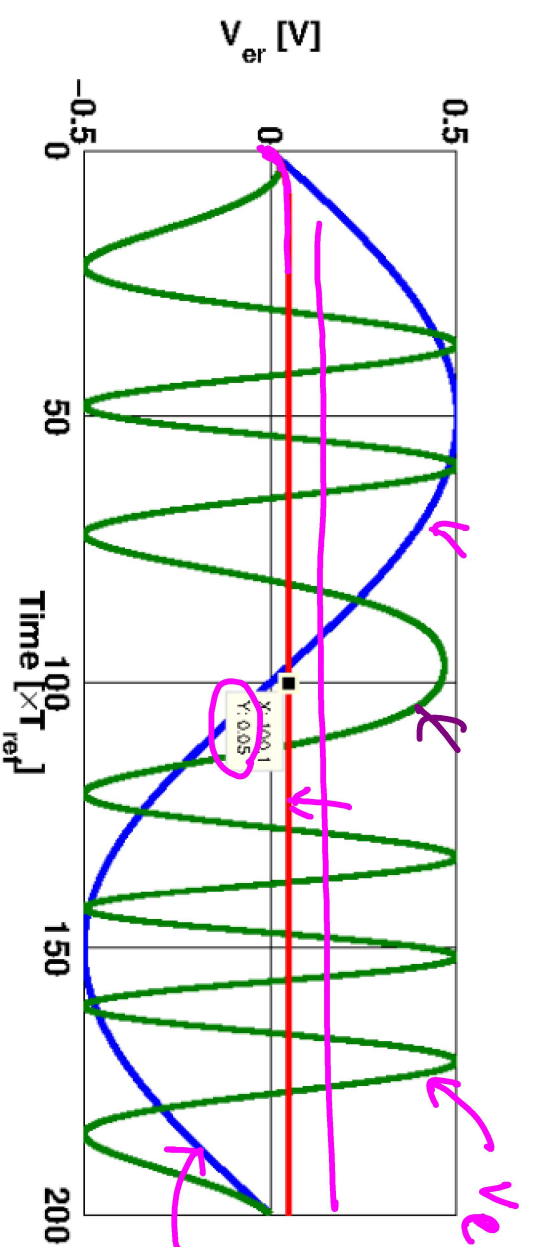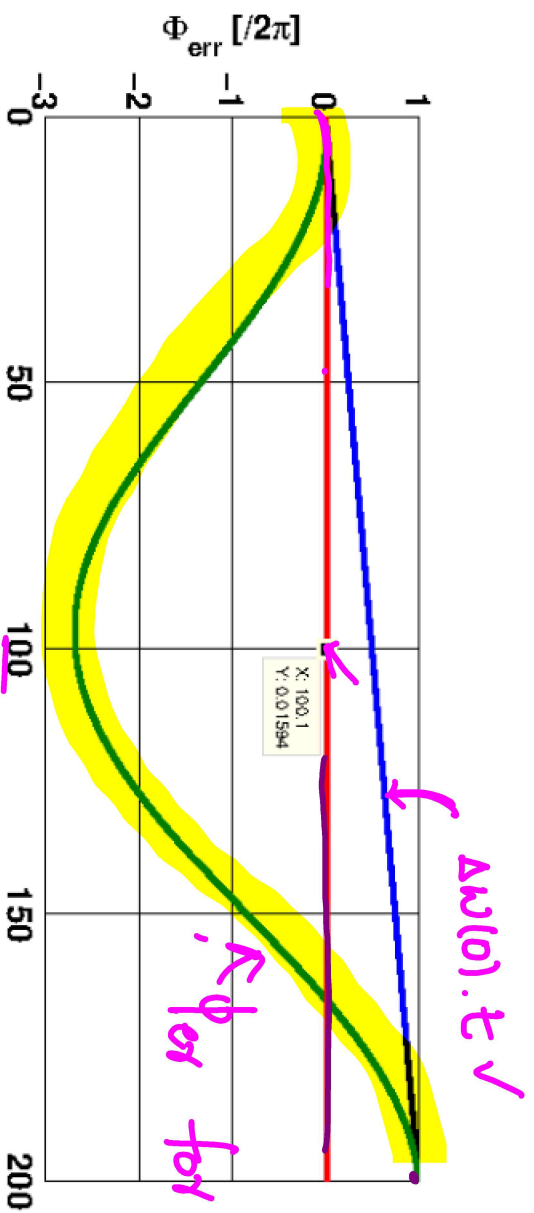V_c is large $\Rightarrow \frac{d\phi_{err}}{dt}$ is large.



$$\Delta\omega(0) = 28 \times 5 \text{ MHz}$$


$$K_{\phi D} = 100 \text{ MHz/V}$$

$$\Delta\omega(0) \leq \frac{1}{2} \times 100 = 50 \text{ MHz}$$


$$V_c = \frac{1}{2} \sin(\Delta\omega(0) \cdot t)$$


$$V_c \text{ for } V_c = \frac{1}{2} \sin(\Delta\omega(0) \cdot t)$$
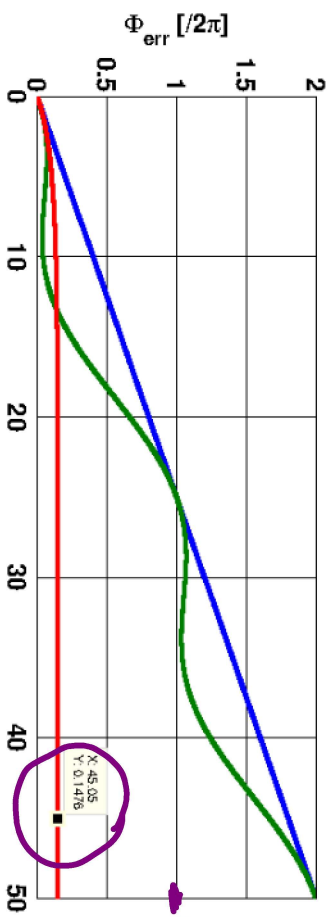
$$V_c = \frac{1}{2} \sin(\Delta\omega(0) \cdot t)$$




2x

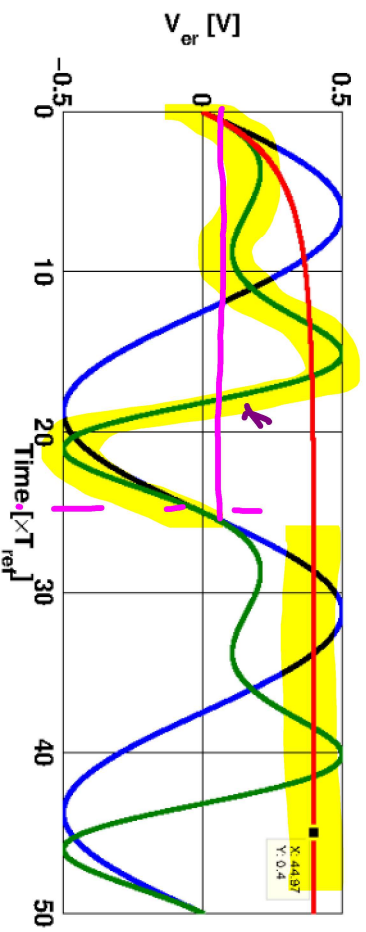

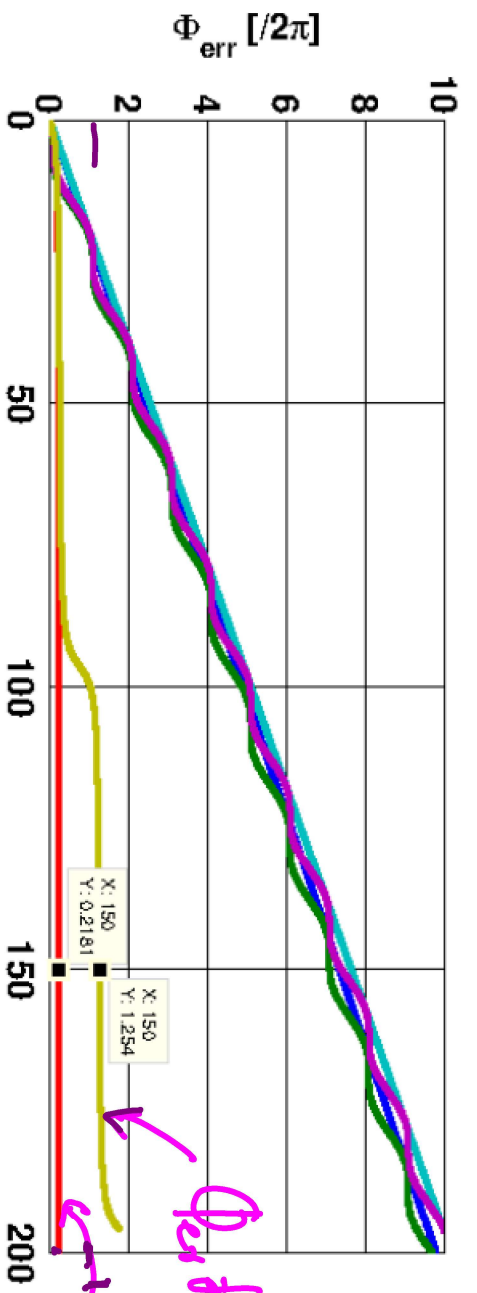


$\Delta f = 51 M$

ϕ_{err} for $\Delta f(0) = 49 M$

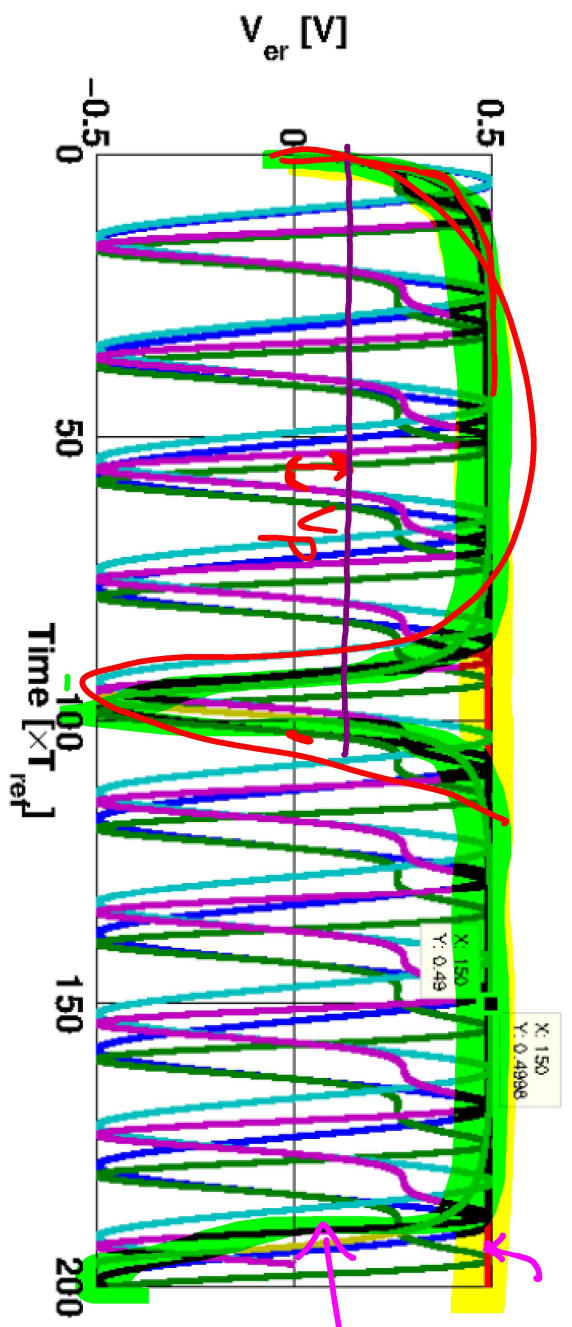

V_e for $\Delta f(0) = 49 M$

V_e for $\Delta f(0) = 51 M$

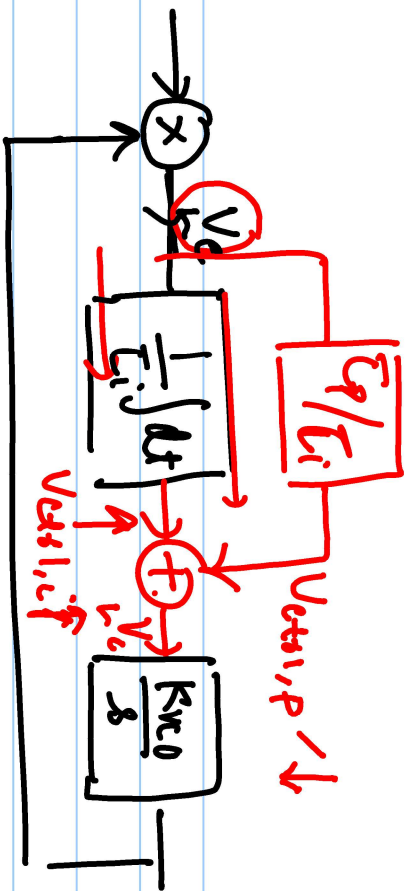


$$V_c = \frac{1}{T_i} \int V_e dt$$

$$\text{at } t=0, \quad V_c = \frac{1}{T_i} \int_0^t \frac{1}{2} \sin(\Delta\omega(0) \cdot t) dt$$

$$\bar{V}_c = 0$$
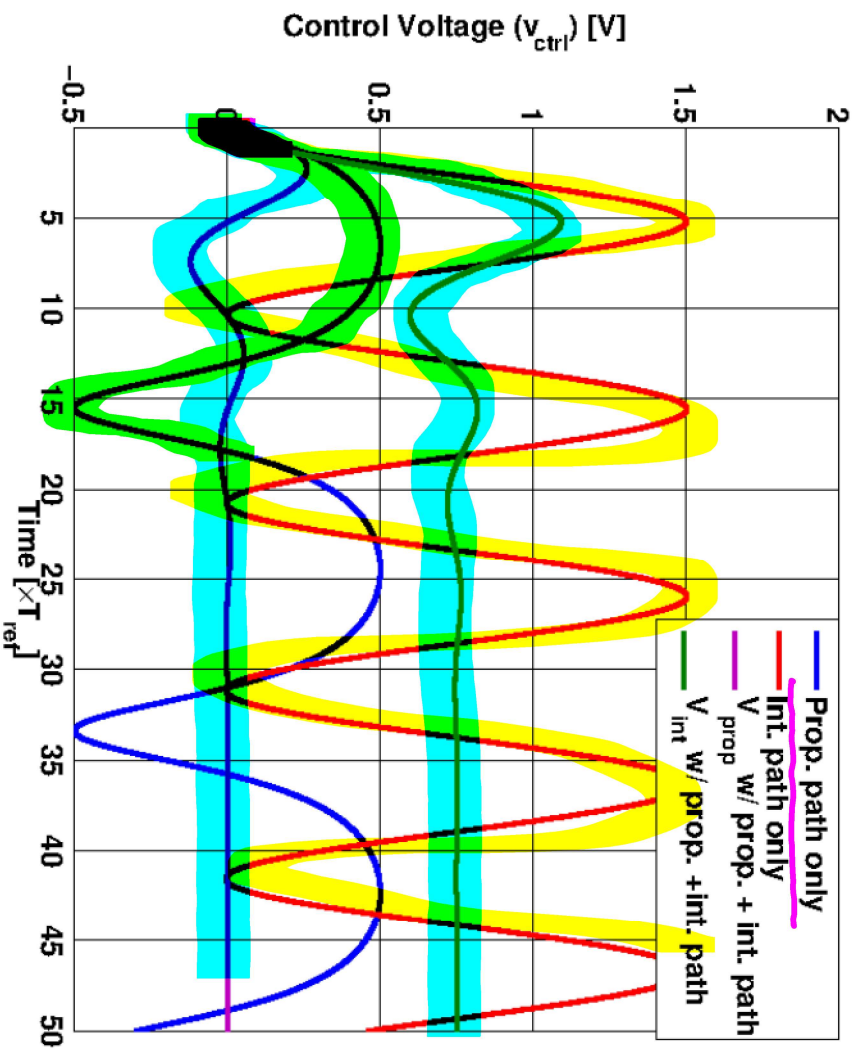
$$M_0 = M_{free} + K_{vc0} \cdot \bar{V}_c$$



$$V_c = V_{ctrl,p} + V_{ctrl,i}$$