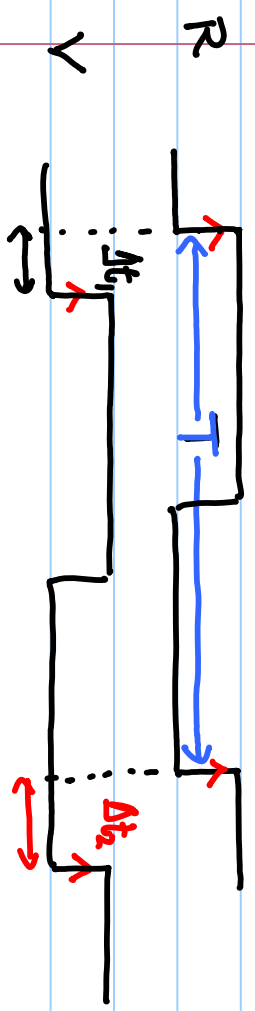


Lecture #12

Digital PD





$$\phi_{ex}(kT) = 2\pi \cdot \frac{\Delta t_{k+1}}{T}$$

$$\phi_{ex}(0) = 2\pi \cdot \frac{\Delta t_1}{T}$$

$$\phi_{ex}(1 \cdot T) = 2\pi \cdot \frac{\Delta t_2}{T}$$

Exclusive-OR based PD

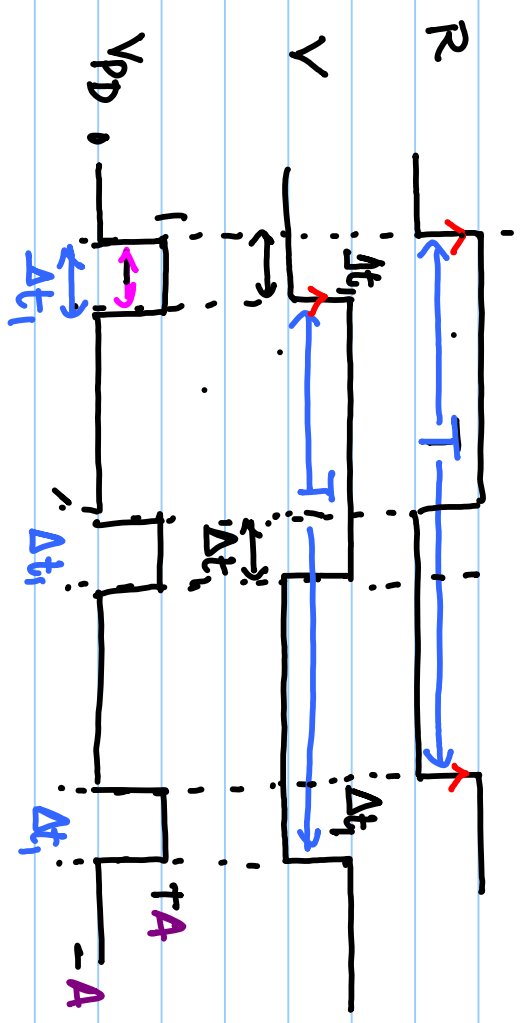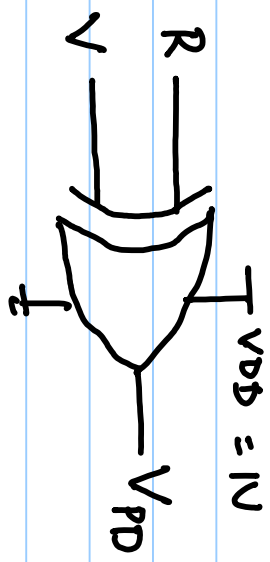

$$\overline{V_{PD}} = 1 \times \frac{\Delta t_1}{T/2} = 2 \cdot \frac{\Delta t_1}{T}$$



$$= \frac{2}{2\pi} \cdot 2\pi \cdot \frac{\Delta t_1}{T} = \frac{1}{\pi} \phi_{ex}$$

$$\bar{V}_{PD} = \frac{1}{\kappa} \phi_{ex} \quad \Bigg| \quad \bar{V}_{PD} = \frac{\Delta t_1 \cdot A - \left(\frac{T}{2} - \Delta t_1\right) A}{T/2}$$

$$= \frac{2A}{T} (2\Delta t_1 - T/2) = A \left(4 \cdot \frac{\Delta t_1}{T} - 1\right)$$


$$= A \left(\frac{2}{\kappa} \quad 2\kappa \cdot \frac{\Delta t_1}{T} - 1\right)$$
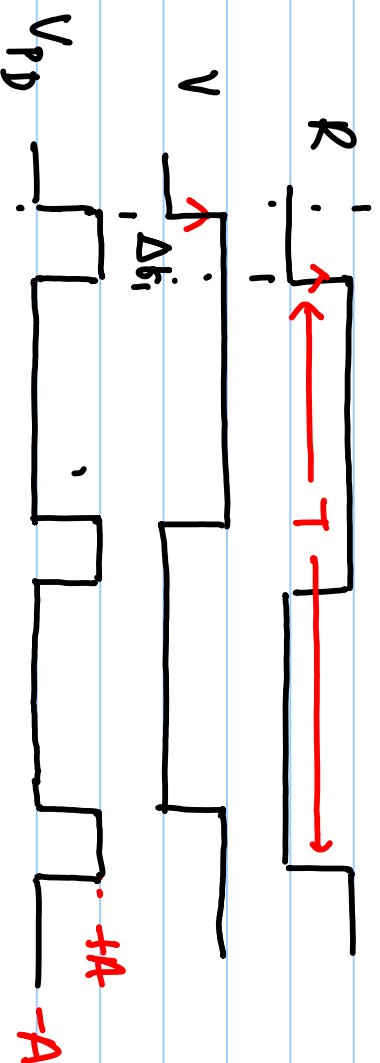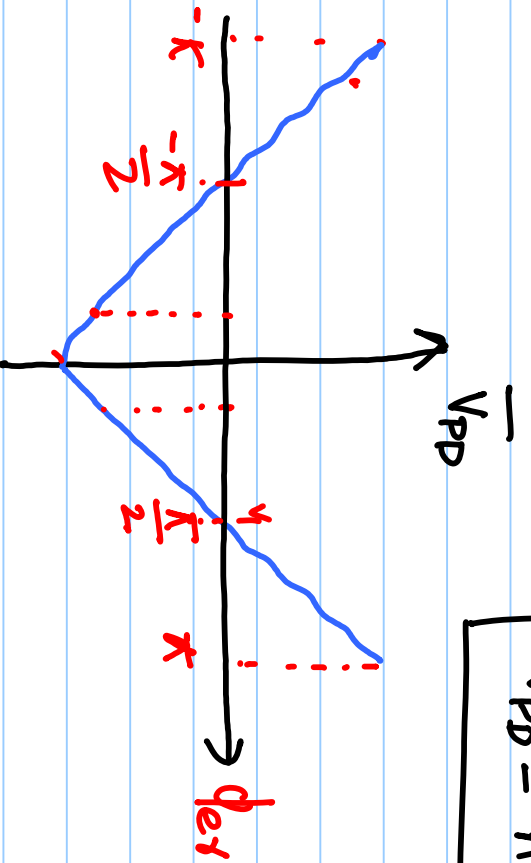
$$\boxed{\bar{V}_{PD} = A \left(\frac{2}{\kappa} \phi_{ex} - 1\right)}$$




\bar{V}_{PD} is a linear fun. of $\phi_{ex} \in [0, \kappa]$
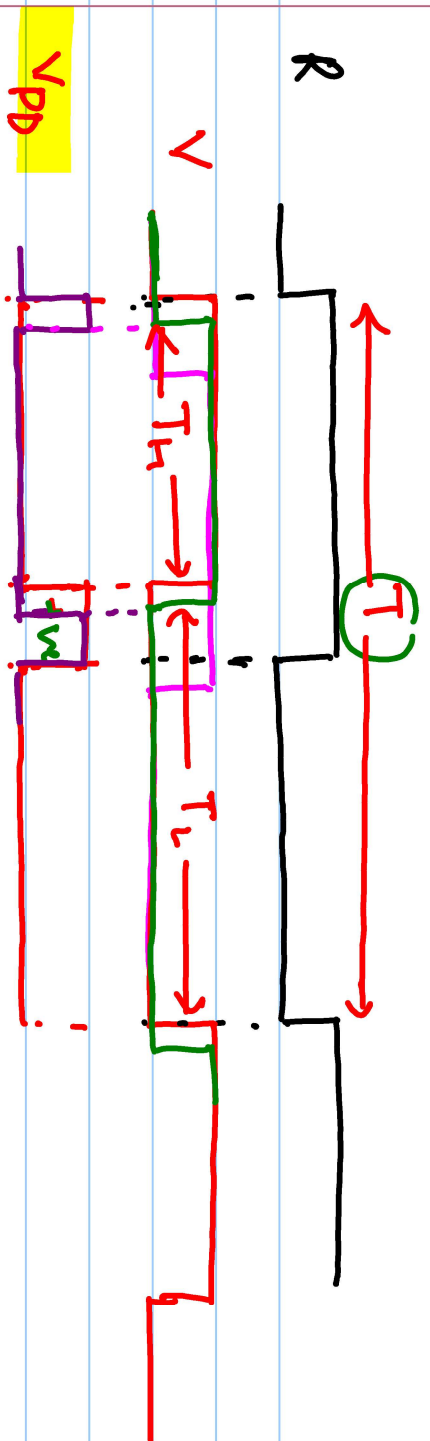
$$\frac{d\bar{V}_{PD}}{d\phi_{ex}} = \frac{2A}{\kappa}$$


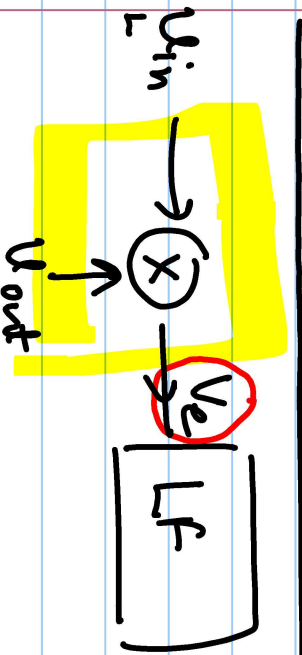
$$D = \frac{T_H}{T_H + T_L} = \frac{T_H}{T}$$





$$u_{in} = \sin(\omega_0 t)$$

$$u_{out} = \cos(\omega_0 t - \phi_{e1})$$




$$V_e = \frac{1}{2} [\sin(2\omega_0 t - \phi_{e2}) + \sin(\phi_{e2})]$$
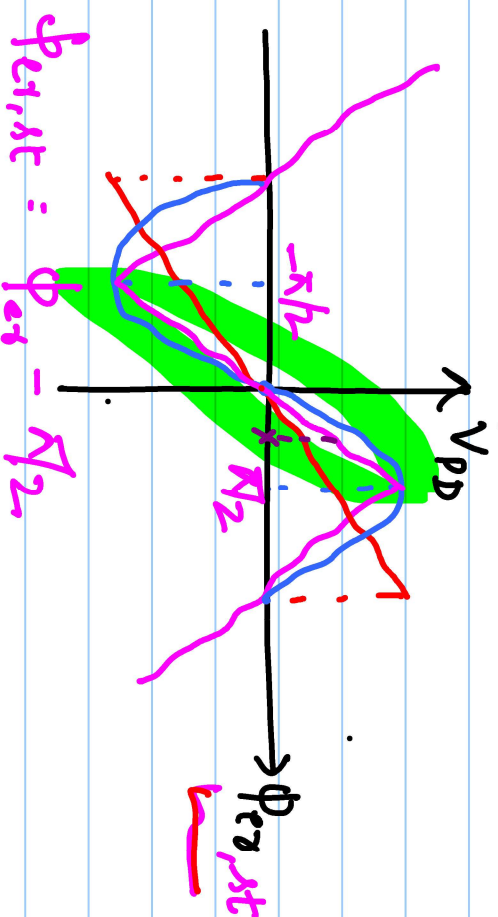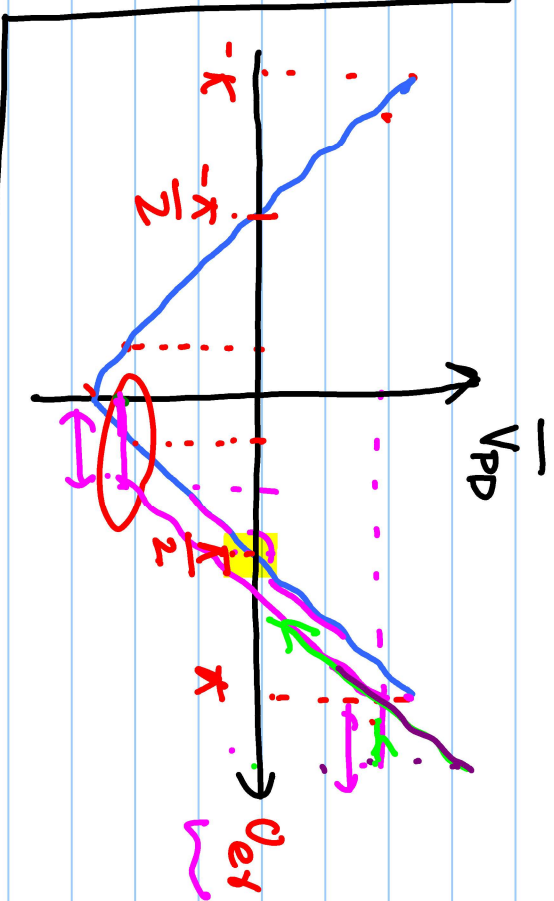
$$V_e = 0 \Rightarrow \sin(\phi_{e2}) = 0$$



2-state Phase Detector.

S-R flip-flop.

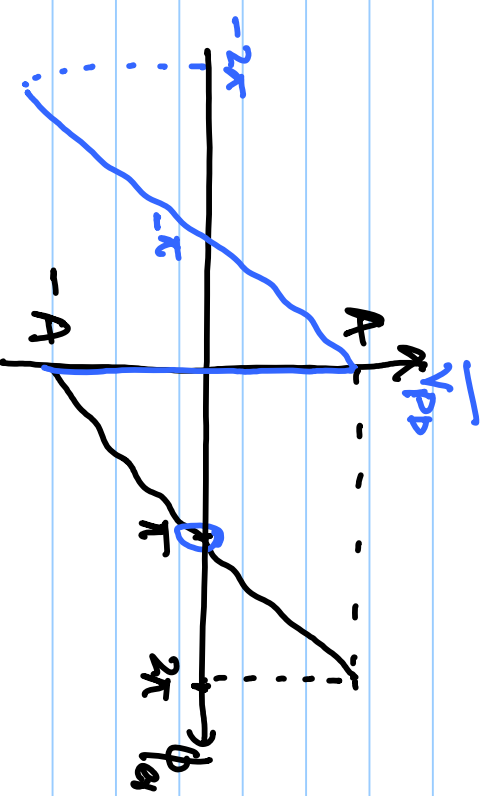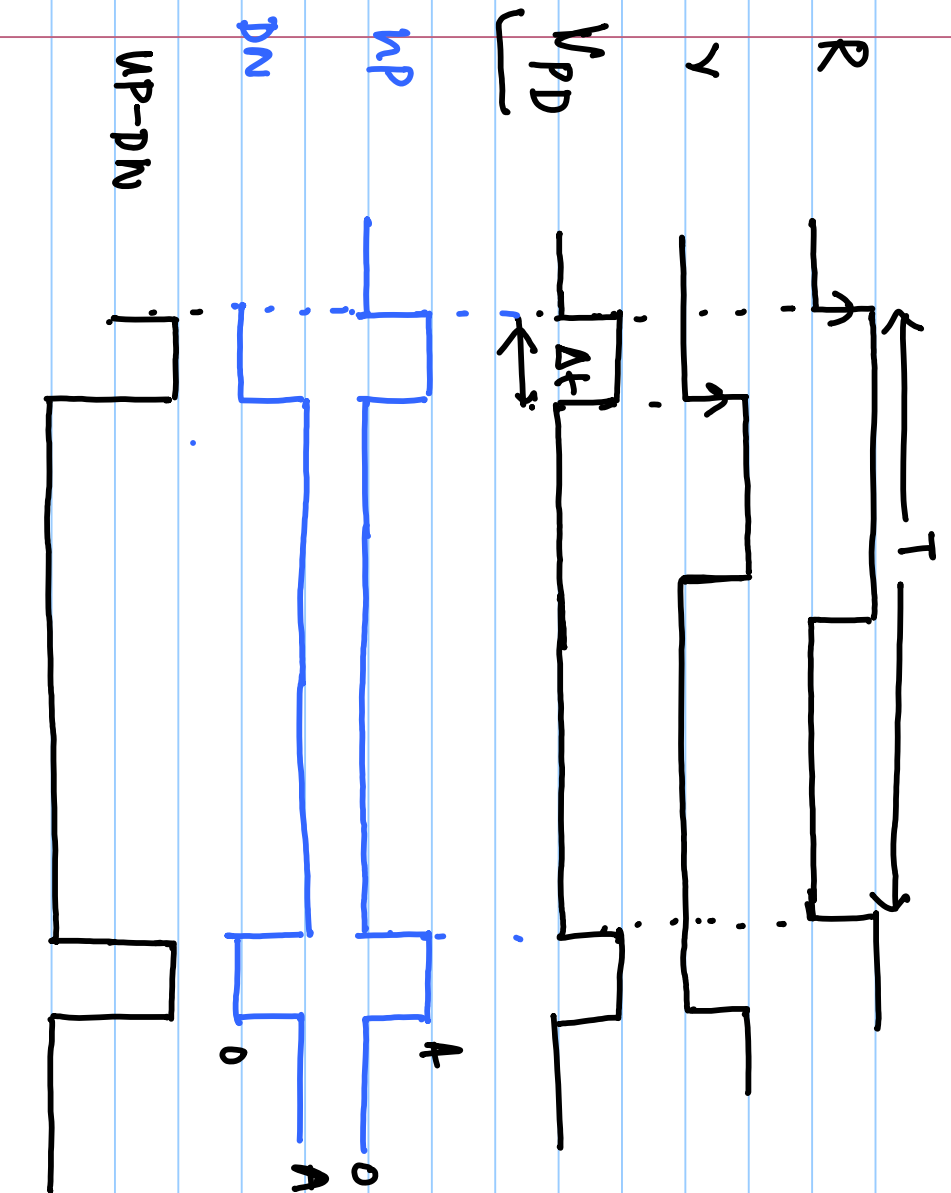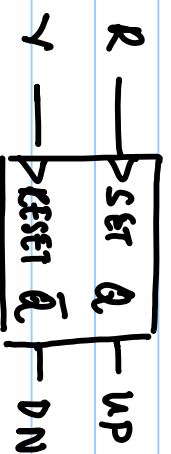

$$\overline{V_{PD}} = \frac{\overline{WP-DN} - \overline{DN}}{T} = \frac{\Delta t \cdot A - (T - \Delta t) \cdot A}{T}$$

$$\text{Gain} = \frac{d\overline{V_{PD}}}{d\phi_{err}} = \frac{A}{\pi}$$

$$\overline{V_{PD}} = A \left(\frac{2\Delta t}{T} - 1 \right)$$

$$\overline{V_{PD}} = A \left(\frac{1}{\pi} \phi_{err} - 1 \right)$$