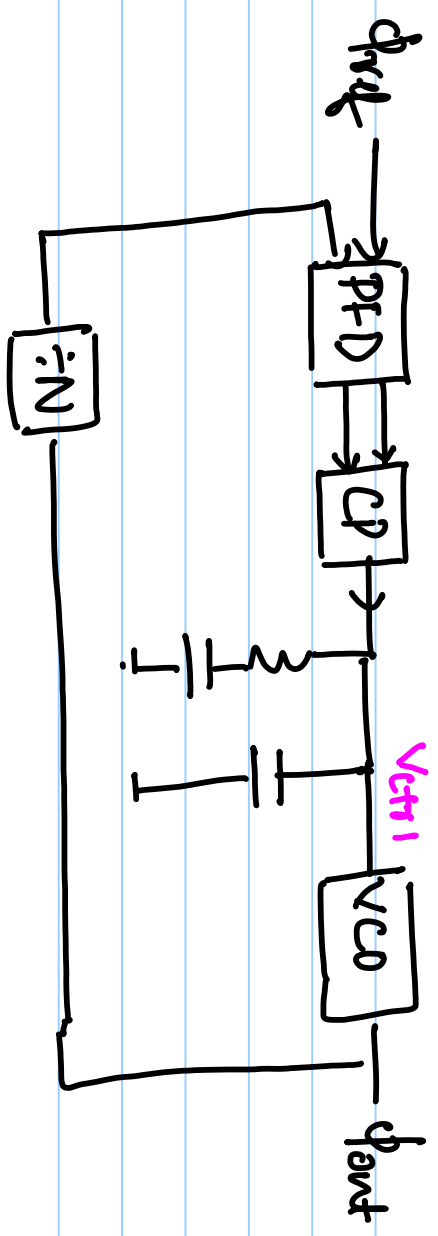




Lecture #24

- PLL @ block-level
- Behavioral Simulations : Noise, loop-gain.



- Clock @ fout using freq.
- Minimum jitter $\sigma_{\phi_{out}}$
- Minimum power cons.
- Ref. spur

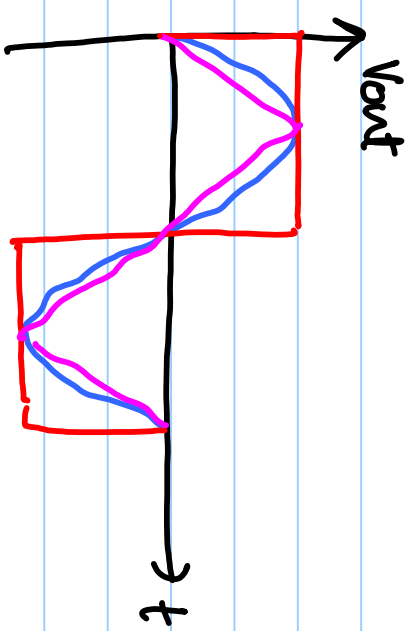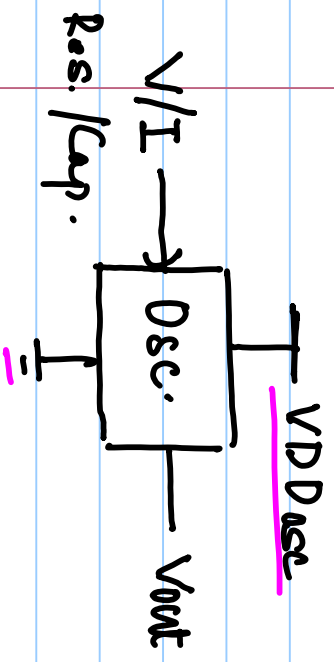Voltage Controlled (Oscillator) : Current Controlled



Crystal Oscillators.


$$|\square| \rightarrow V_{out} (f_{out})$$

- low frequency.

- excellent freq. stability. $\left(\frac{\Delta F}{F_{osc}} \times 10^6 \right) \text{ (ppm)} = 10 - 100 \text{ ppm}$

- excellent phase noise

- can't be integrated on chip.

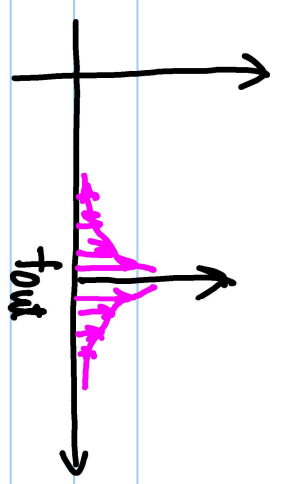


Tuned Oscillators (LRC)

- Clapp / Colpitts / Hartley oscillators ✓

- consume large area.

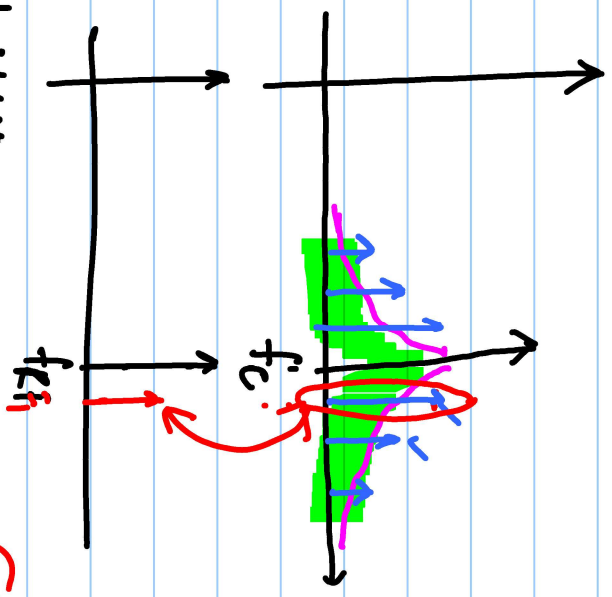- Good phase noise, moderate frequency stability.





Ring Oscillator

- Moderate phase noise

- Small area.



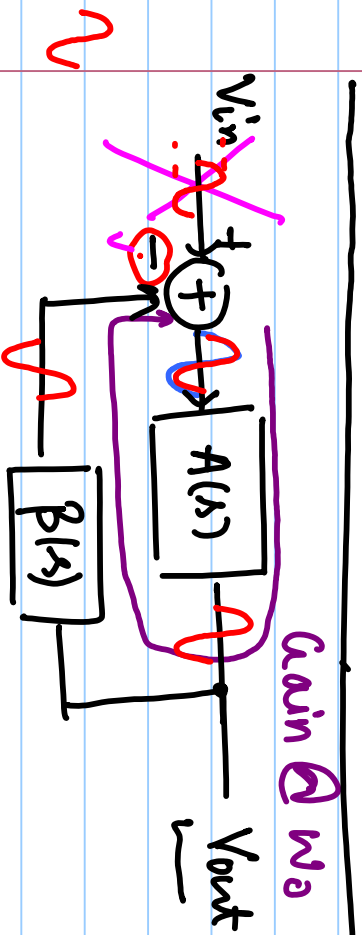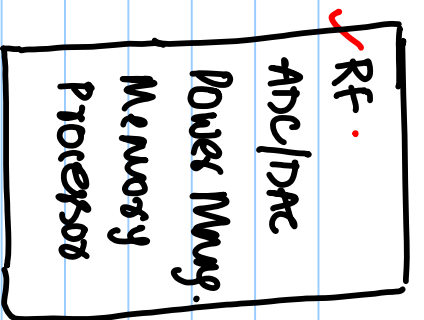

Gain @ $\omega_0 = 1$ and phase @ $\omega_0 = 180^\circ \Rightarrow |A(s)B(s)|_{\omega=\omega_0} = 1$


$$\frac{V_{out}}{V_{in}} = \frac{A(s)}{1 + A(s)B(s)} = H(s)$$

$$\angle A(s)B(s)_{\omega=\omega_0} = 180^\circ$$


Above system is not stable if poles are in R.H.P

Above system is stable if poles in L.H.P

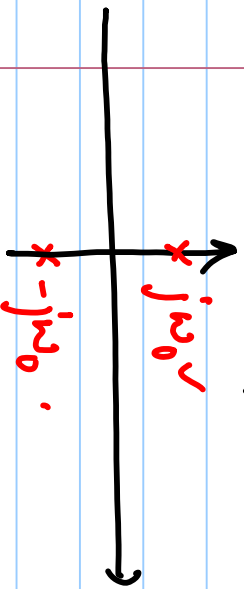
What happens if poles are on $j\omega$ axis.


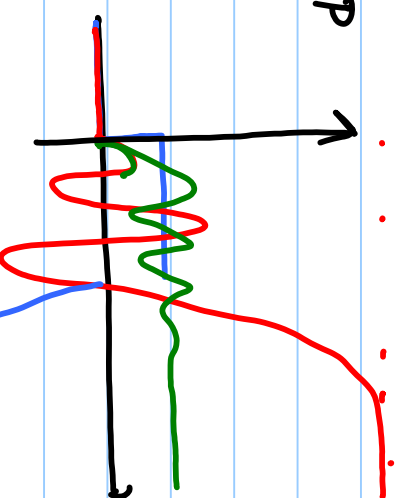
$$H(s) = \frac{1}{(s + j\omega_0)(s - j\omega_0)} = \frac{1}{s^2 + \omega_0^2}$$





$$H(s) = \frac{1}{s^2 + \omega_0^2}$$

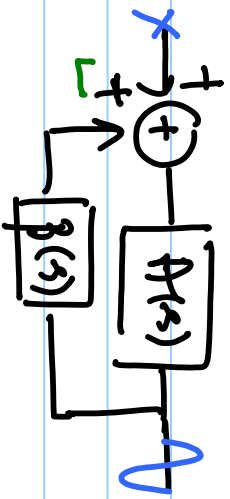

$$L(s) = A(s) \beta(s)$$

$$|L(j\omega)| \Big|_{\omega=\omega_0} = 1$$
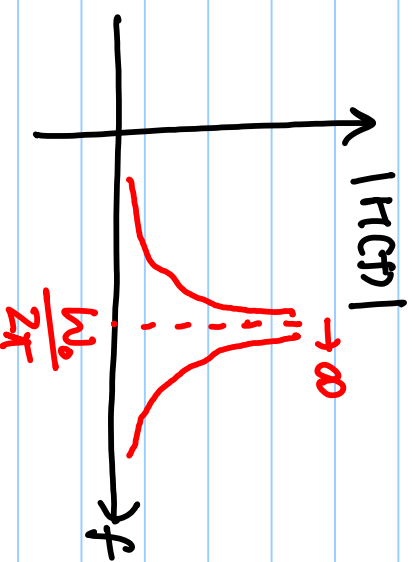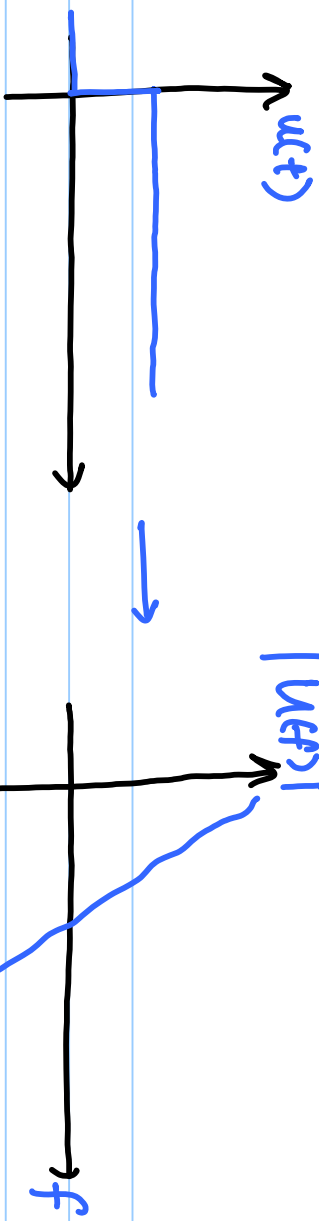
$$\delta(L(j\omega_0)) = 2\pi \checkmark$$



- Sustained oscillations. ✓
- closed loop poles on jw axis.

