

Max.  $V_{op} = V_{DD}$


min.  $V_{op} = V_{DD} - I_b \cdot R$

$I_b R$


Swing,  $\Delta V = I_b \cdot R$

$f_{osc} \propto \frac{1}{R}$

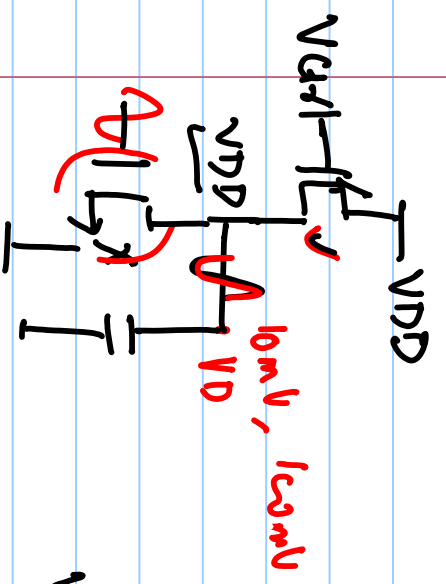
$f_{osc} \uparrow \Rightarrow R \downarrow \Rightarrow \Delta V \downarrow$



$$R = \frac{1}{\mu_p C_{ox} \frac{W}{L} (V_{DD} - V_{thp} - |V_{tp}|)}$$

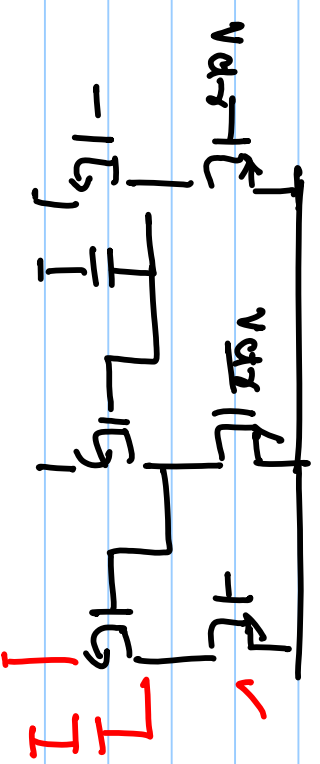

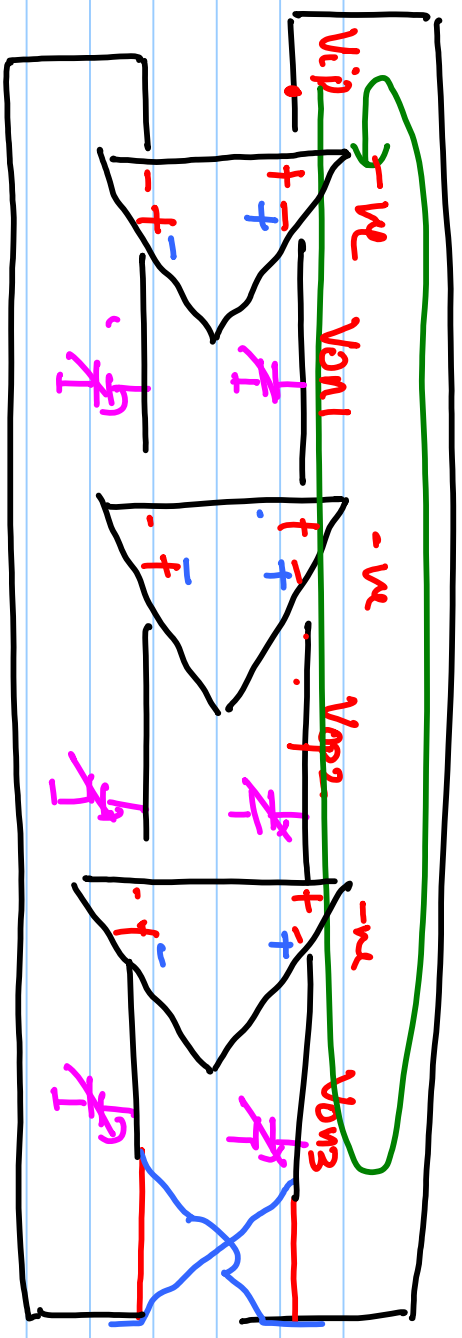CML:  $V_{DD} - \Delta V$  to  $V_{DD}$   
 Or 0 to  $\Delta V$   
 CMOS: 0 to  $V_{DD}$



-  $I_D$  } Mos-Cap }  
 Diode }  
 Min-cap. }  
 Mem-cap }




$f_{osc} \uparrow \Rightarrow R \downarrow$

$$\Delta V = \underline{I_D \cdot R \downarrow}$$

$$\boxed{V_{DD} - V_{ref}} = \underline{I_b \cdot R}$$
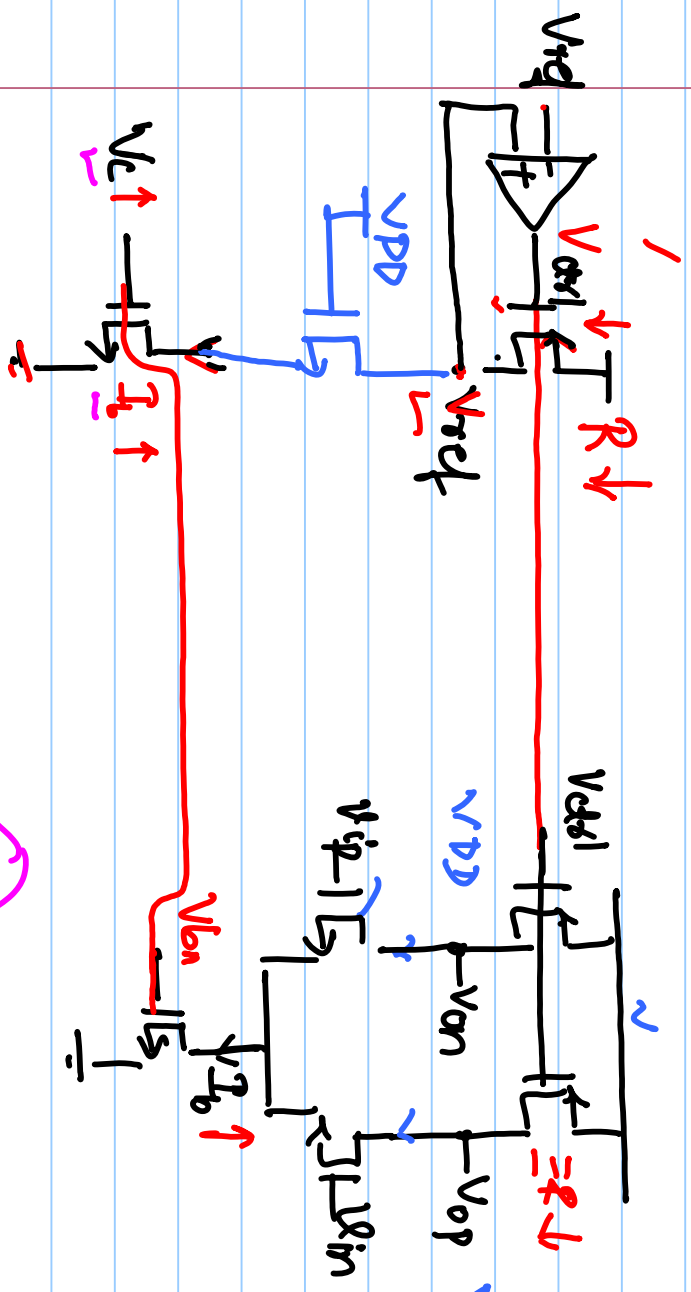
$$\Delta V = V_{DD} - (V_{DD} - V_{ref}) = V_{ref}$$



$$f_{osc} \propto \frac{1}{R_{on} C} \propto \frac{I_b}{(V_{DD} - V_{ref}) C}$$




$$\Delta f_{osc} \propto \underline{g_m (\Delta V_c)}$$

$$\underline{(V_{DD} - V_{ref}) C}$$

$\Delta I_b = g_m \Delta V_c$  if Non-linear  $\Rightarrow$

$$\left| \frac{\Delta f_{osc}}{\Delta V_c} \right| \text{ non-linear.}$$

Bias for Osc.

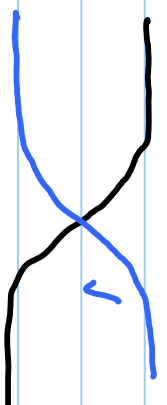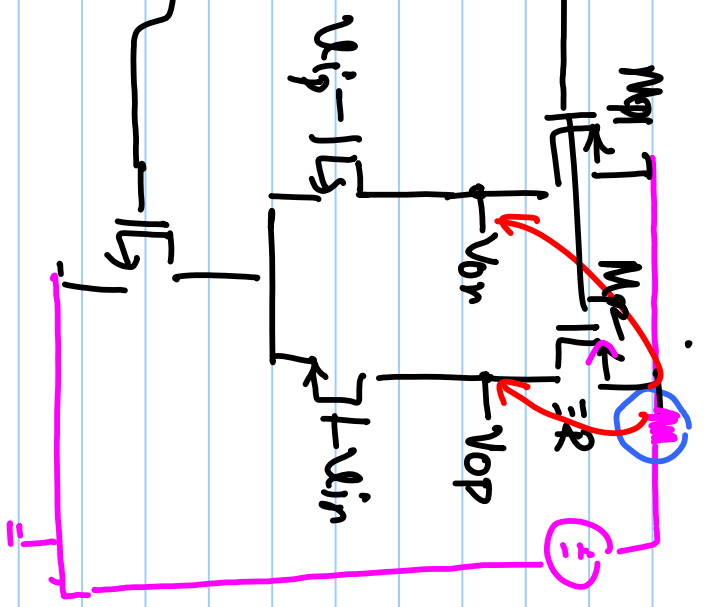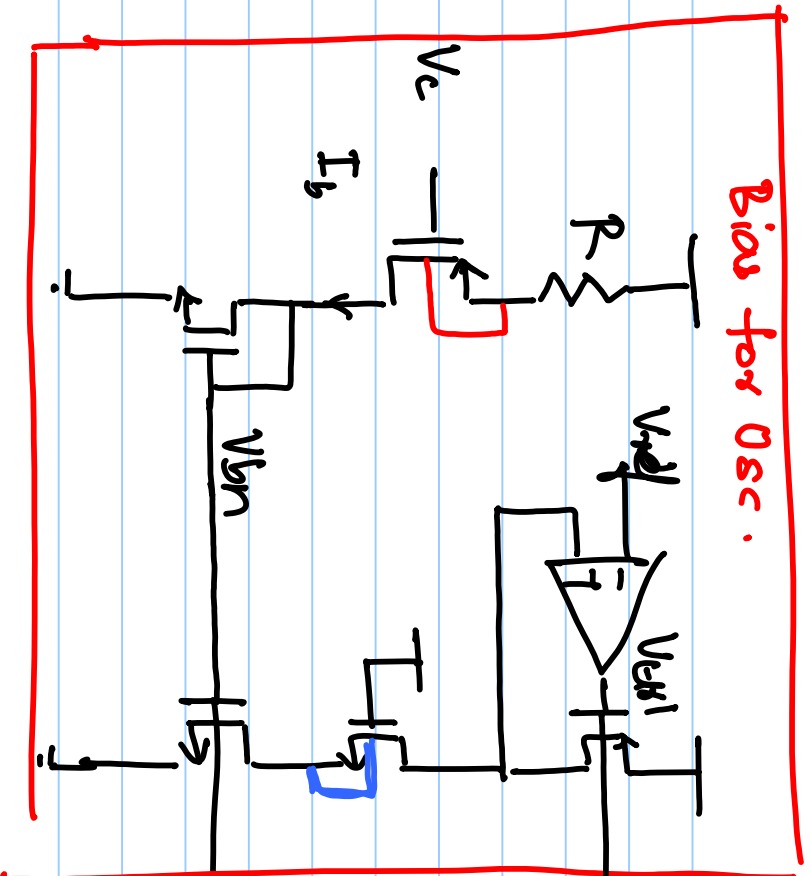

$$\Delta I_b = \frac{\Delta V_c}{R} = \left(\frac{1}{R}\right) \Delta V_c$$

$$V_{op} = V_{DD} - \left(\frac{I_b}{2} + \Delta I_b\right) \cdot R (V_{D1}, I_{D2})$$

$$V_{on} = V_{DD} - \left(\frac{I_b}{2} - \Delta I_b\right) R (V_{D1}, I_{D2})$$

$$|V_{op} - V_{on}| = \underline{\underline{2 \cdot \Delta I_b \cdot R}}$$

Power Supply Rejection Ratio (PSRR)

$$V_{GS1} - V_{th} \rightarrow I_{D1} = I_{D2} = I_{R}$$

