

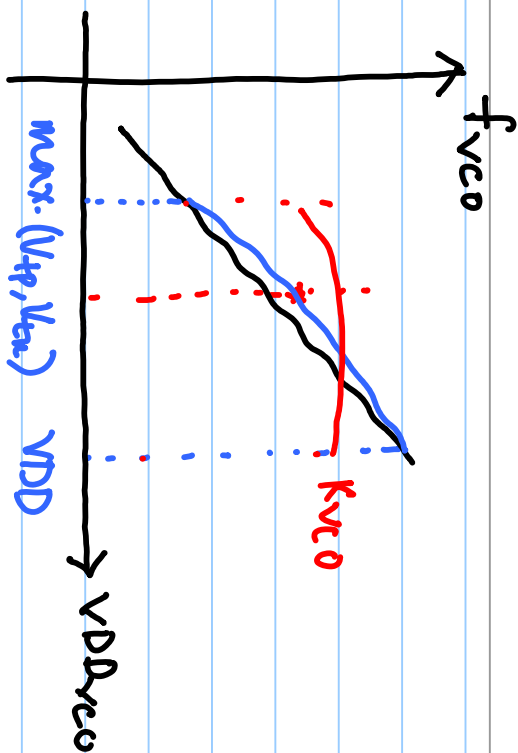
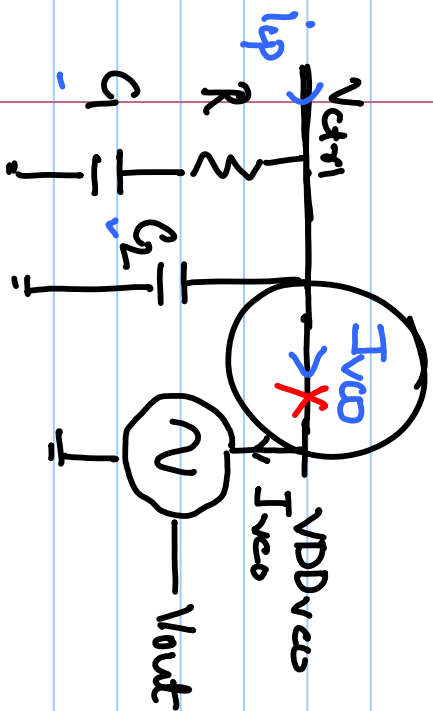



Lecture #31

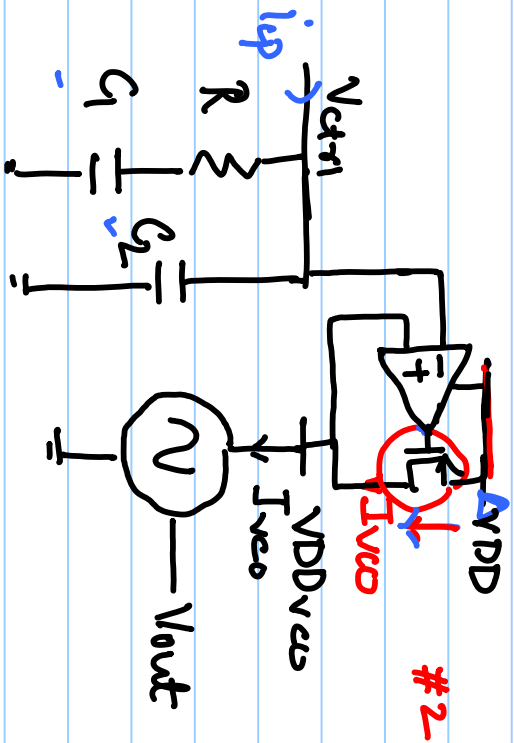
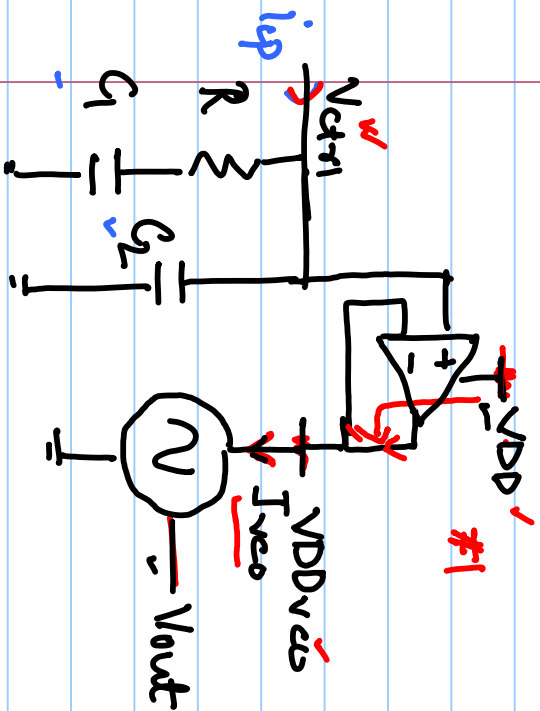
$$K_{vco} = \frac{d(f_{vco})}{d(V_{DD_{vcs}})}$$




VDD ≡

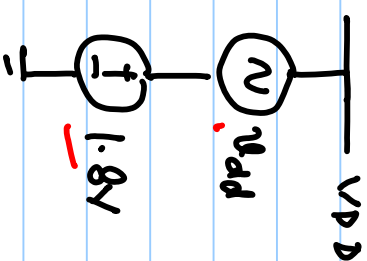


$$\frac{\Delta V_{DD_{vco}}(s)}{V_{DD}(s)} \times \frac{\Delta \phi_{out}}{\Delta V_{DD_{vco}}(s)} = \frac{\Delta \phi_{out}(s)}{V_{DD}(s)} \quad \checkmark$$

(Power Supply Rejection Ratio) (PSRR)

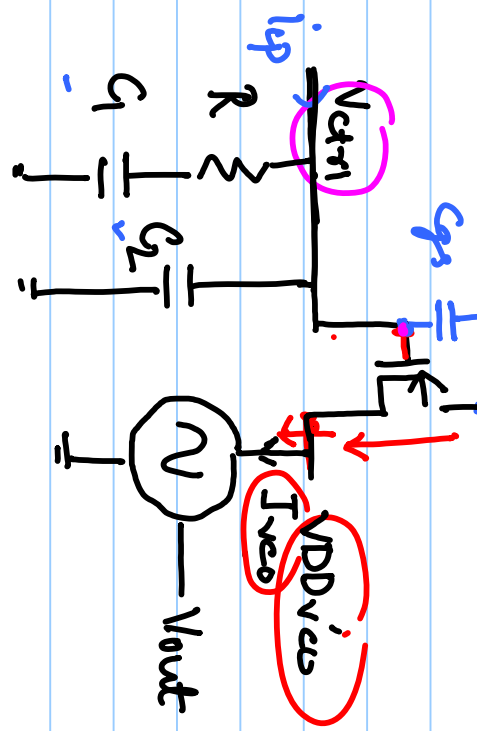
#3 $0.5V = (V_{GS1} - V_{thn})$
 $V_{DD} = 1.8$


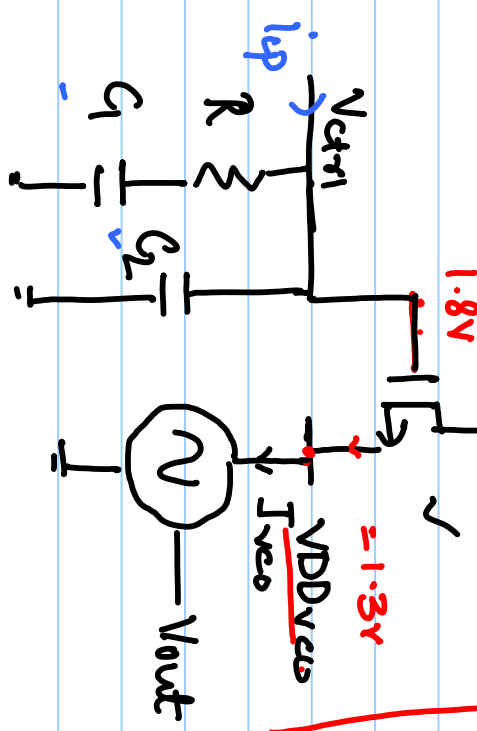
#4 $V_{DD} = 1.8V$
 $V_{GS} = 1.3V$
 $\frac{\Delta V_{DD, V_{CO}} (s)}{\Delta V_{GS1} (s)}$



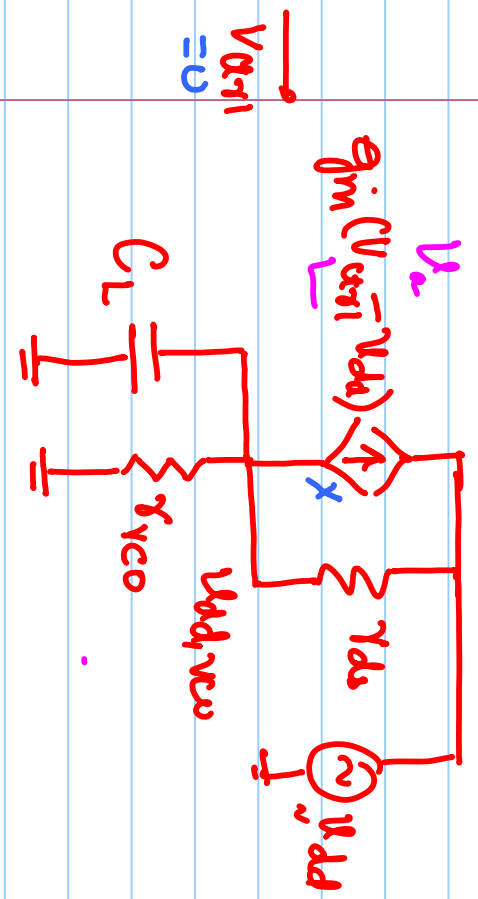
$$V_{DD, V_{CO}} \left(\frac{1}{r_{DS}} + \frac{(1 + sC_2 r_{CO})}{r_{CO}} \right) = V_{DD} \left(g_m + \frac{1}{r_{DS}} \right)$$



$$\frac{V_{DD, V_{CO}}}{V_{DD}} = \frac{(1 + g_m r_{DS})}{(r_{CO} + r_{DS} + sC_2 r_{CO} r_{DS})}$$

$$\frac{V_{DD, V_{CO}}}{(r_{CO} || \frac{1}{sC_2})} = \frac{V_{DD} - V_{DD, V_{CO}}}{r_{DS}} + g_m V_{DD}$$
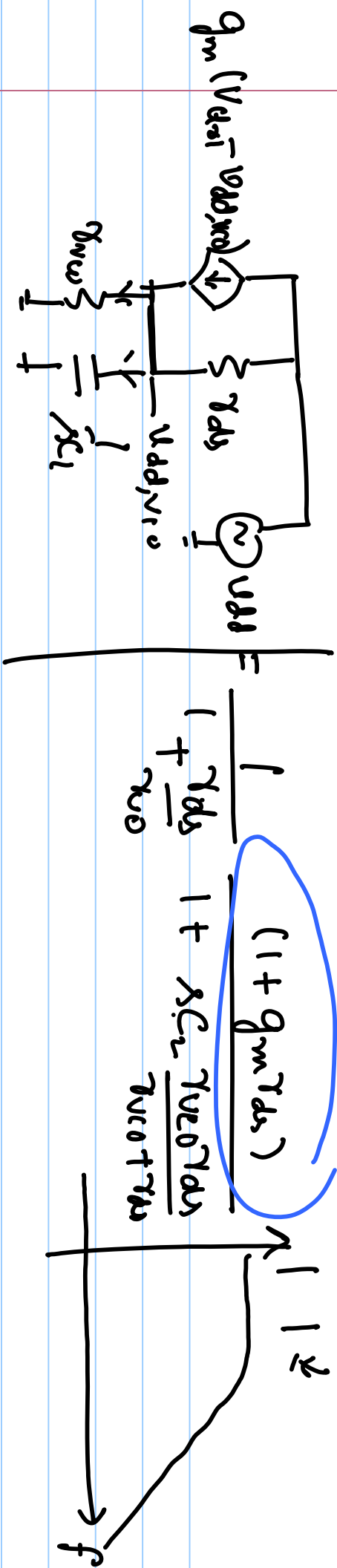
$$= \frac{1}{1 + \frac{r_{DS}}{r_{CO} + r_{DS}}} \frac{1 + g_m r_{DS}}{(1 + \frac{sC_2 r_{CO} r_{DS}}{r_{CO} + r_{DS}})}$$






$$\frac{V_{DD, V_{GS2}} (1 + sC_L r_{V_{GS2}})}{r_{V_{GS2}}} = \frac{V_{DD} - V_{DD, V_{GS2}}}{r_{ds}} - g_m V_{DD, V_{GS2}}$$

$$V_{DD, V_{GS2}} \left(\frac{1}{r_{ds}} + \frac{1}{r_{V_{GS2}}} + g_m + sC_L \right) = \frac{V_{DD}}{r_{ds}}$$

$$\frac{V_{DD, V_{GS2}}}{V_{DD}} = \frac{1}{r_{ds}} \frac{1}{\left(\frac{1}{r_{ds}} + \frac{1}{r_{V_{GS2}}} + g_m \right)} \frac{1}{1 + sC_L} \frac{1}{\left(\frac{1}{r_{V_{GS2}}} + \frac{1}{r_{ds}} + g_m \right)}$$
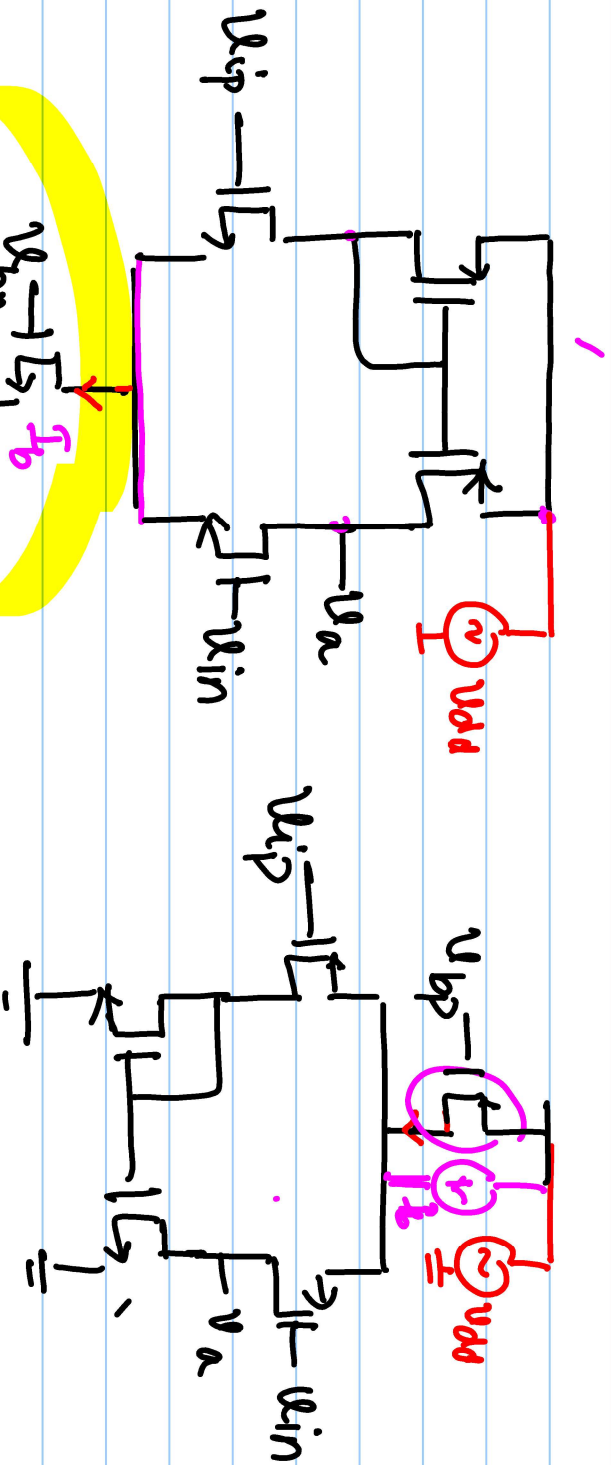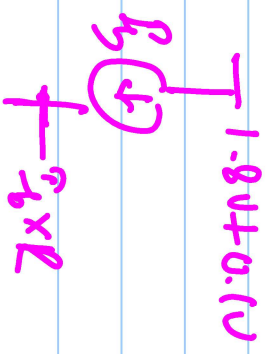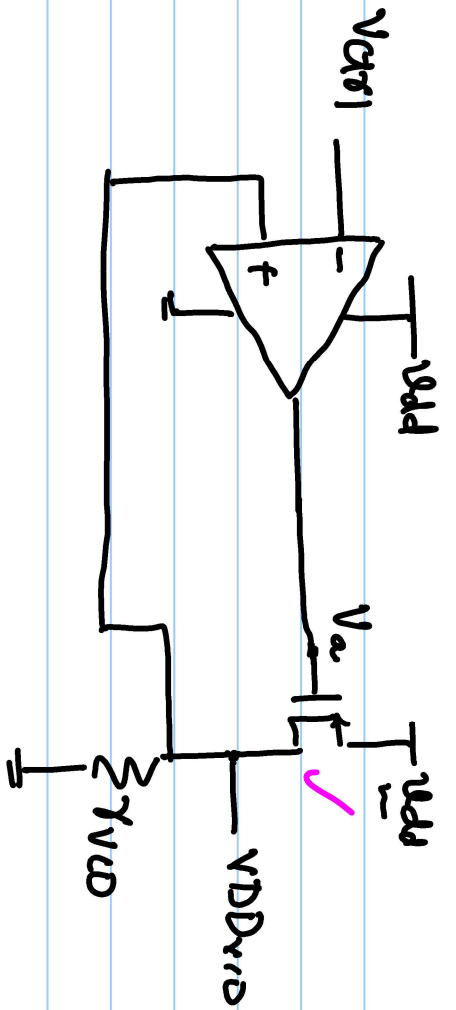
$$= \frac{1}{1 + \frac{r_{ds}}{r_{V_{GS2}}} + g_m r_{ds}} \frac{1}{1 + \frac{sC_L r_{V_{GS2}} r_{ds}}{r_{V_{GS2}} + r_{ds}}} \frac{1}{1 + \frac{g_m r_{ds} r_{V_{GS2}}}{r_{V_{GS2}} + r_{ds}}}$$



$$\frac{V_a}{V_{DD}} = 1$$

$$\frac{V_a}{V_{DD}} = 0$$

