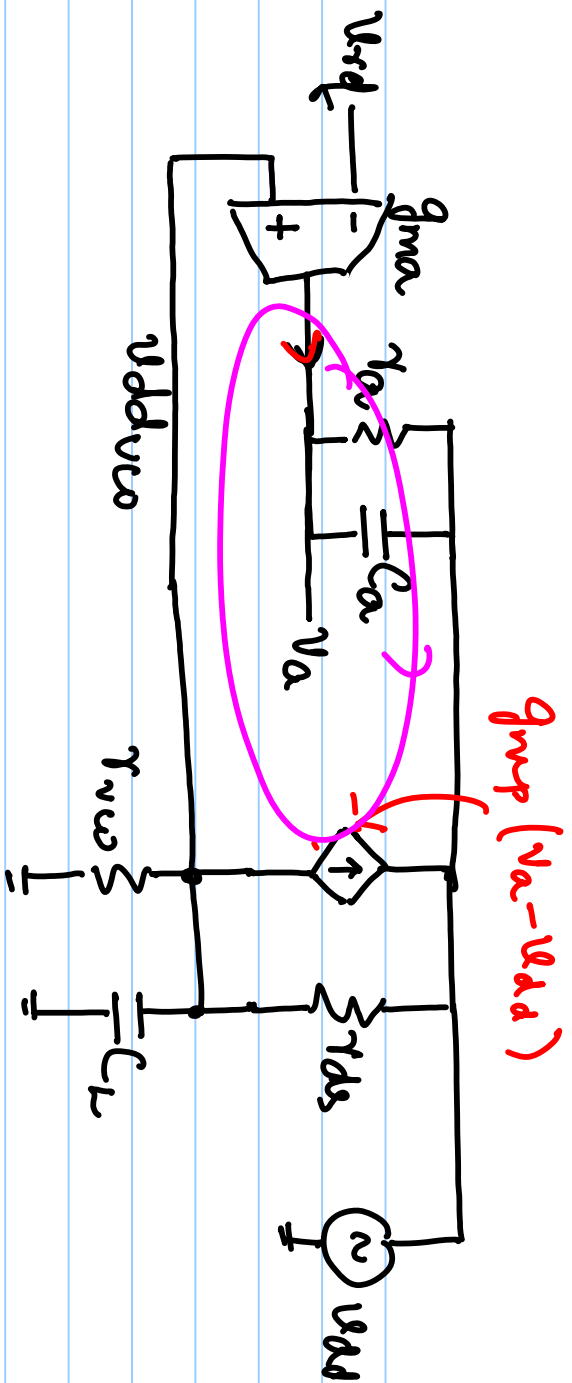


$$\frac{v_{ds}}{v_{gs}} = \frac{1}{1 + \frac{r_{ds}}{r_{L||D}}} \quad \left((1 + g_m r_{ds}) v \right) \quad \left| \quad \frac{v_o}{v_{gs}} = 0 \right.$$

$$\frac{v_{ds}}{v_{gs}} = \frac{1}{1 + \frac{r_{ds}}{r_{L||D}}}$$

$$\frac{v_o}{v_{gs} - v_{gs}} = \frac{g_m r_a}{1 + s C_a r_a}$$

$$A_a = g_m r_a \quad \left| \quad \omega_a = \frac{1}{C_a r_a} \right.$$



$$\frac{V_{DDV_{in}}}{V_{ref}} = \frac{L_n}{1+L_n}$$

$$\left[\frac{(V_{DDV_{in}} - V_{ref}) g_{m1} r_n}{1+sC_{a1}r_n} \right] g_{mp} \times \frac{\overbrace{(r_{DS1} r_{DS})}^{r_L} \times \frac{1}{sC_L}}{(r_{DS1} r_{DS}) + \frac{1}{sC_L}} = -V_{DDV_{in}}$$

$$\underbrace{g_{m1} r_n g_{mp} r_L}_{L_n} \frac{(V_{DDV_{in}} - V_{ref})}{(1+sC_{a1}r_n)(1+sC_Lr_L)} = -V_{DDV_{in}}$$

$$(V_{DDV_{in}} - V_{ref}) L_n = -V_{DDV_{in}} \Rightarrow \frac{V_{DDV_{in}}}{V_{ref}} = \frac{L_n}{1+L_n}$$

$$\frac{U_{dd} v_{in}}{v_{ref}} = \frac{A_a A_b}{1 + \frac{1}{\beta} \frac{1}{\omega_a \omega_b}} = \frac{1}{1 + \frac{1}{\beta} \frac{1}{\omega_a \omega_b}}$$

$$= \frac{1}{1 + (1 + \beta / \omega_a) (1 + \beta / \omega_b)}$$

$$= \frac{A_a A_b}{A_a A_b \left(\frac{\omega_a^2}{\omega_a \omega_b} + \beta \left(\frac{1}{\omega_a} + \frac{1}{\omega_b} \right) + (1 + A_a A_b) \right)}$$

$$\boxed{s_1} = - \left(\frac{1}{\omega_a} + \frac{1}{\omega_b} \right) \approx - (\omega_a + \omega_b)$$

$$\boxed{s_2} = - \frac{1 + A_a A_b}{\frac{1}{\omega_a} + \frac{1}{\omega_b}}$$

$s_1 \gg s_2$

$$ax^2 + bx + c = 0$$

$$x_1 + x_2 = -\frac{b}{a} \quad \checkmark$$

$$x_1 x_2 = \frac{c}{a}$$

$$x_1 \gg x_2 \quad \checkmark$$

$$\Rightarrow x_1 + x_2 \approx x_1 = -\frac{b}{a}$$


$$-\frac{b}{a} \times x_2 = \frac{c}{a}$$

$$x_2 = -\frac{c}{b} \quad \checkmark$$

$$\omega_a \ll \omega_L$$

$$s_1 \approx -\omega_L \checkmark$$

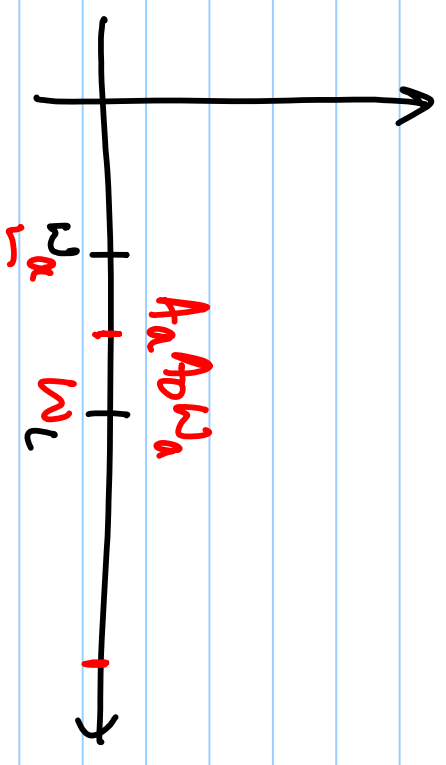
$$s_2 \approx -\underbrace{A_a A_D}_{\omega_a} \omega_a$$




$$\omega_L \ll \omega_a \checkmark$$

$$s_1 \approx -\omega_a$$
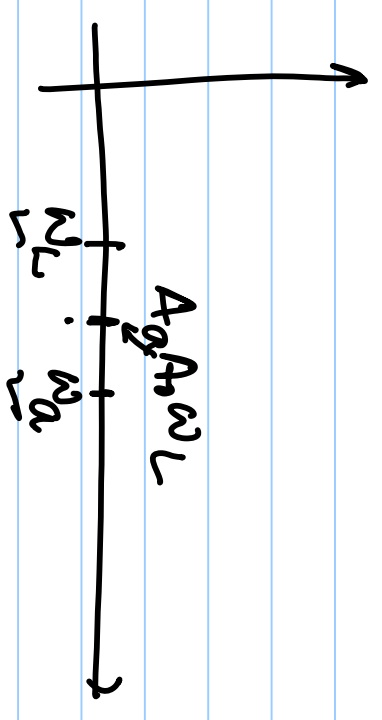
$$s_2 \approx -\underbrace{A_a A_D}_{\omega_L} \omega_L$$


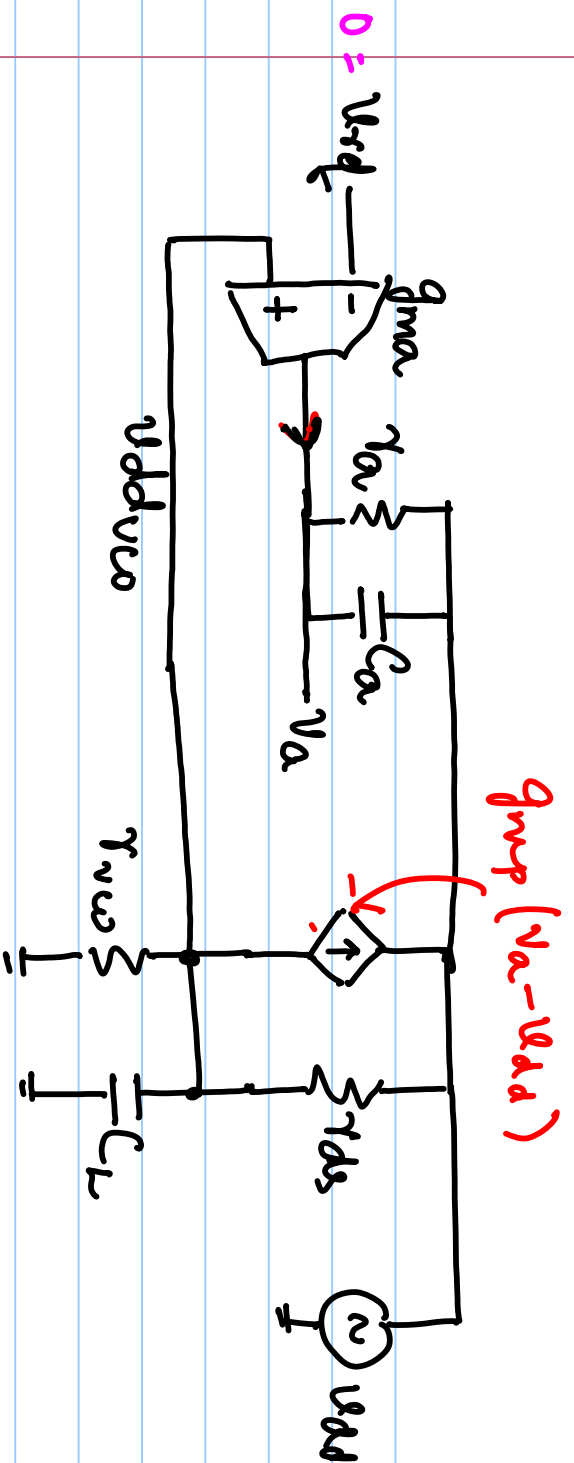
$$k_{w_1} = \frac{r_{op}}{2\pi} \frac{(1+sR_e r_c)}{(1+sR_c C_2)} \frac{1}{s(1+\tau_2)} \frac{1}{(1+s/\omega_{reg})} \frac{2\pi K_{vco}}{s} \approx \frac{1}{N}$$



$$g_m v_{in} = \frac{v_{out} - V_{DD}}{(r_{\pi} \parallel r_{e})} \quad (1)$$

$$\frac{v_{out} - V_{DD}}{r_{e}} - g_m (v_{out} - V_{DD}) = \frac{v_{in}}{(r_{\pi} \parallel r_{e})} \quad (2)$$

$$\frac{v_{out}}{v_{in}} = \frac{S_{V_{DD}} \left(1 + \frac{r_{\pi}}{r_{e}}\right)}{\left(1 + \frac{r_{\pi}}{r_{e}}\right) \left(1 + \frac{r_{\pi}}{r_{L}}\right) + A_{v} A_{\beta}}$$

$$S_{vdd} = \frac{r_{vco}}{r_{vco} + r_{ds}}$$


$$\frac{S_{vdd}}{A_a A_o}$$

$$\omega_a \ll \omega_L$$

$$\omega_L, A_a A_o \omega_a$$

$$\omega_L \ll \omega_a \checkmark$$

$$\omega_a, A_a A_o \omega_L$$

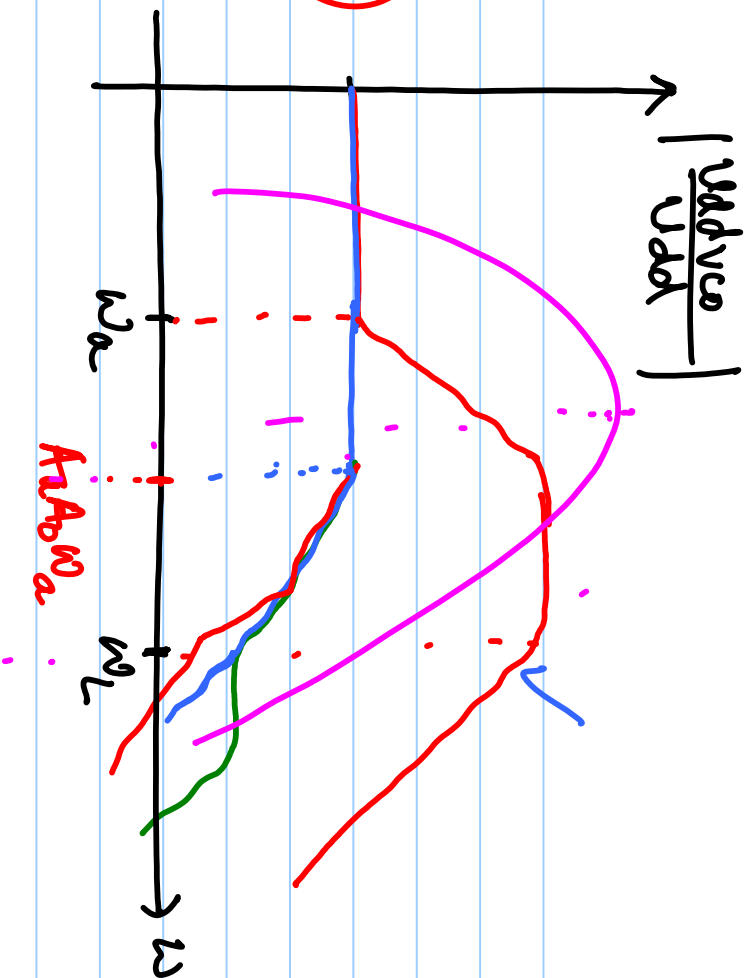

$$\omega_L A_a A_o \omega_L$$

$$\omega_a = \frac{1}{r_a C_a}$$

$$C_a \uparrow = C_{amp} \uparrow + C_{gg} \uparrow (n)$$

$$\omega_L = \frac{1}{(r_{vco} \parallel r_{ds}) C_L \uparrow}$$

$$r_{vco} = \frac{1.5V}{1.5mA}$$

$$= 1k\Omega$$

$$\frac{\phi_{out}}{U_{ddvco}} = \frac{2\pi K_{vco} / s}{1 + k_{a-pLL}}$$

$$= \frac{1}{1 + k_{a-pLL}} \approx \frac{2\pi K_{vco}}{s}$$

