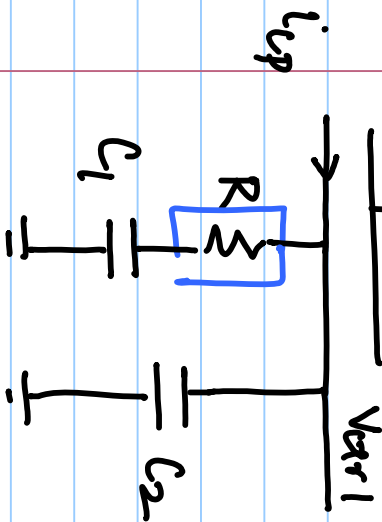


lecture # 41

Loop filter




$$\frac{V_{err1}}{i_{cp}} = \frac{1}{sC_2} \parallel \left(R + \frac{1}{sC_1} \right)$$

$$= \frac{(1+sRC_1) \times \frac{1}{sC_2}}{sC_1 \left(R + \frac{1}{sC_1} \right) + \frac{1}{sC_2}} = \frac{(1+sRC_1) / s^2 C_1 C_2}{C_2 + sRC_1 C_2 + C_1}$$

$$= \frac{1}{s(C_1 + C_2)} \quad \checkmark$$
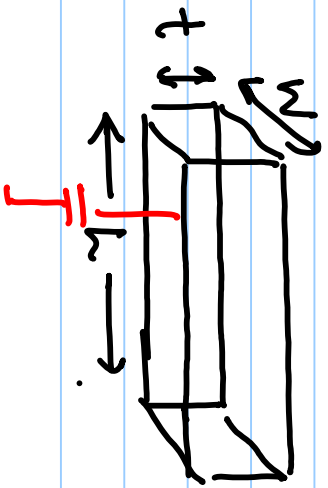
$$\omega_z = \frac{1}{RC_1}, \quad \omega_p = \frac{1}{RC_1 C_2}$$



$$R = \rho \frac{l}{w \times t} = \frac{\rho}{t} \frac{l}{w} = R_{sh} \frac{l}{w}$$

(sq/d)


$$L_u = \frac{I_{cp} (1+sRC_1)}{2s (C_1+C_2)} \frac{1}{(1+s \frac{RC_1}{C_1+C_2})} \frac{2\pi k_{vco}}{sN} v$$


$$\omega_n \approx \frac{I_{cp} \cdot R \cdot k_{vco}}{N} \frac{C_1}{C_1+C_2}$$

$$I_{cp} \propto \frac{1}{R}$$

$$\left. \begin{aligned} & |L_u(\omega_n)| = 1 \\ & \frac{I_{cp} \omega_n R C_1}{\omega_n^2 (C_1+C_2)} \frac{k_{vco}}{N} = 1 \end{aligned} \right\}$$

$$I_0 = \frac{V_{ref}}{R}$$

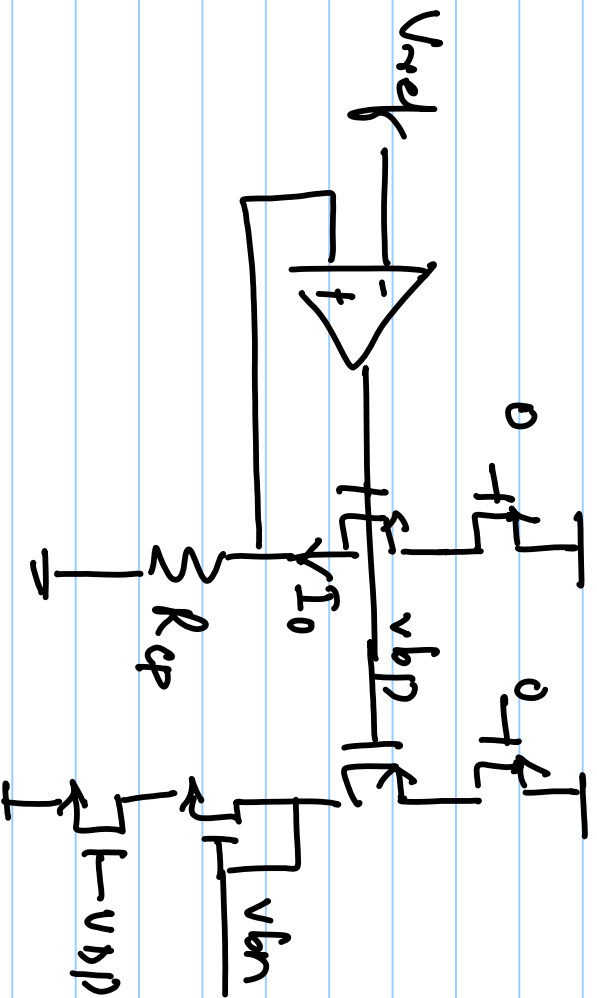

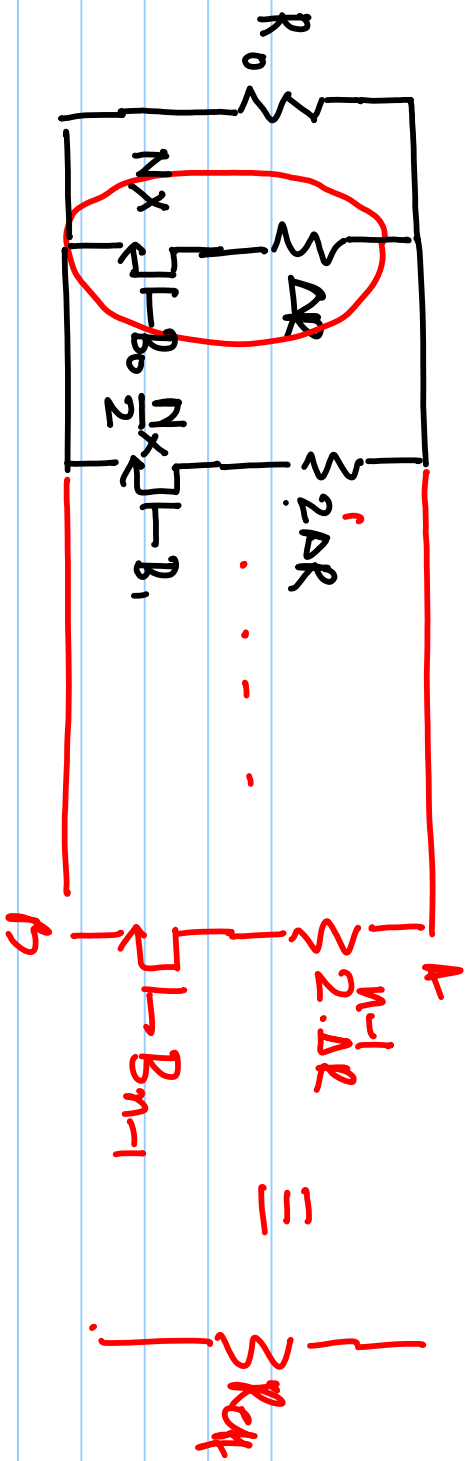

$$R_{eff} = \frac{1}{\frac{1}{R_0} + \frac{B_0}{\Delta R} + \frac{B_1}{2 \cdot \Delta R} + \dots}$$


for Max. variation $\pm 30\%$


$$R_{nom} = \frac{1}{\left(\frac{1}{R_{0,max}} + \frac{1}{\Delta R_{max}} + \frac{1}{2 \Delta R_{avg}} + \dots + \frac{1}{2^{(n-1)} \cdot \Delta R_{avg}} \right)}$$

for min. variation -30%

$$R_{nom} = \frac{1}{R_{0,min}}$$

$$\Delta R = R_{nom} - R_{eff}$$

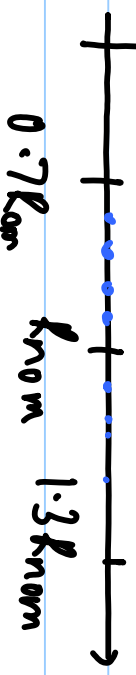

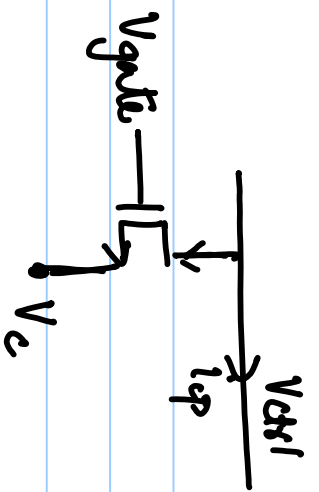

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th} - \frac{V_{DS}}{2}) V_{DS} \right]$$

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[(V_{gate} - V_c - V_{th}) (V_{gate} - V_c) - \frac{(V_{gate} - V_c)^2}{2} \right]$$

$$(V_{gate} - V_c) < (V_{gate} - V_c) - V_{th}$$

$$V_{gate} < V_{gate} - V_{th}$$

Voltage coefficient, $V_c = \frac{1}{R} \cdot \frac{\partial R}{\partial V_{DS}} =$


$$R(V) = R(V_0) \left[1 + 10^{-6} \kappa C_1 (V - V_0) + 10^{-6} \kappa C_2 (V - V_0)^2 \right]$$

$$R = \frac{V_{DS}}{I} = \frac{1}{\mu_n C_{ox} \frac{W}{L} \left(V_{gs} - V_{th} - \frac{V_{DS}}{2} \right)}$$

$$\frac{\partial R}{\partial V_{DS}} = \frac{1}{\mu_n C_{ox} \frac{W}{L}} \left(\frac{-1}{(V_{gs} - V_{th} - \frac{V_{DS}}{2})^2} \right) \times \frac{-1}{2}$$


$$\frac{1}{R} \frac{\partial R}{\partial V_{gs}} = \frac{1}{2(V_{gs} - V_{th} - \frac{V_{DS}}{2})}$$

Capacitors

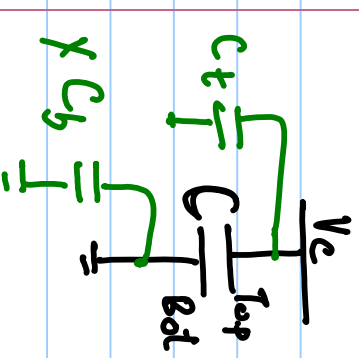

$$C = \frac{\epsilon_{ox}}{t_{ox}} wL$$

$C_b > C_t$

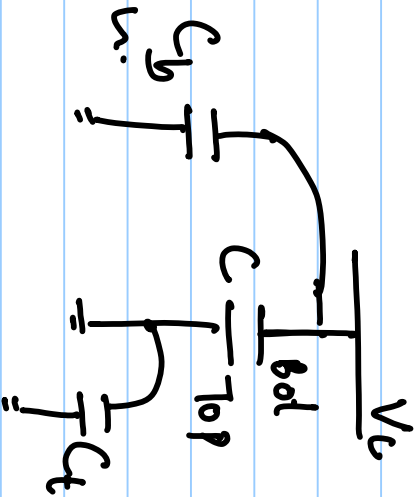

1-2 fF/ μm^2



p-sub.

