
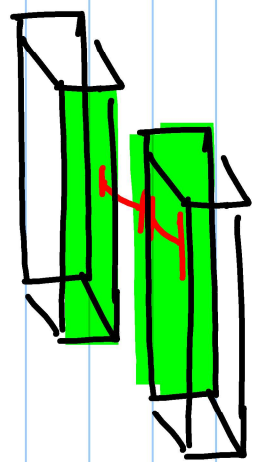



Lecture # 42

Loop-filter

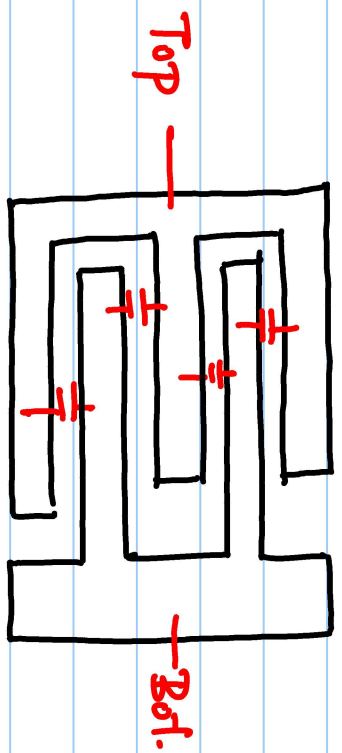


$$\phi_m = f\left(\frac{C_1}{C_2}\right)$$

1-2 fF/ μm^2

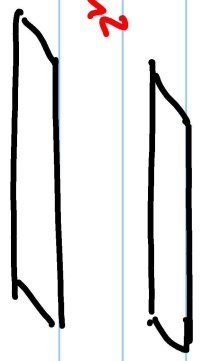


$$\omega_N = \frac{I_{\text{op}} \cdot R_{\text{Kvco}}}{N} \frac{C_1}{C_1 + C_2}$$





_____ P-sub _____

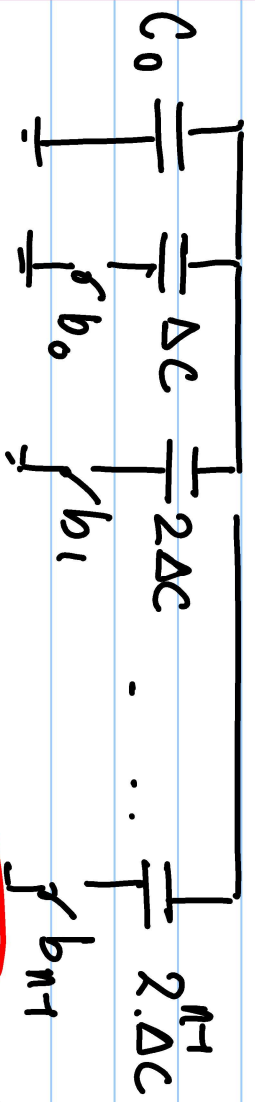


$$C_{\text{tot}} = C_0 + b_0 \cdot \Delta C + b_1 \cdot 2 \cdot \Delta C + \dots + b_{N1} \cdot 2 \cdot \Delta C$$

V_{cv}
 V_{cv}
10-12 fF/ μm^2

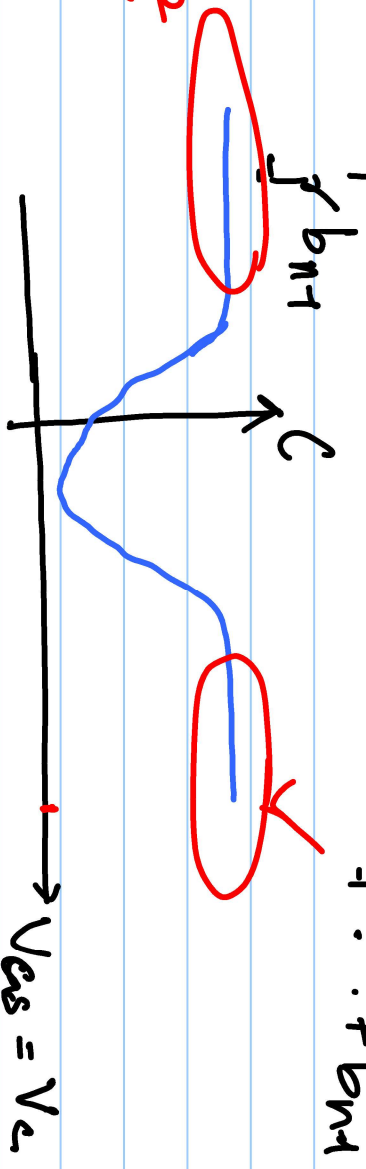

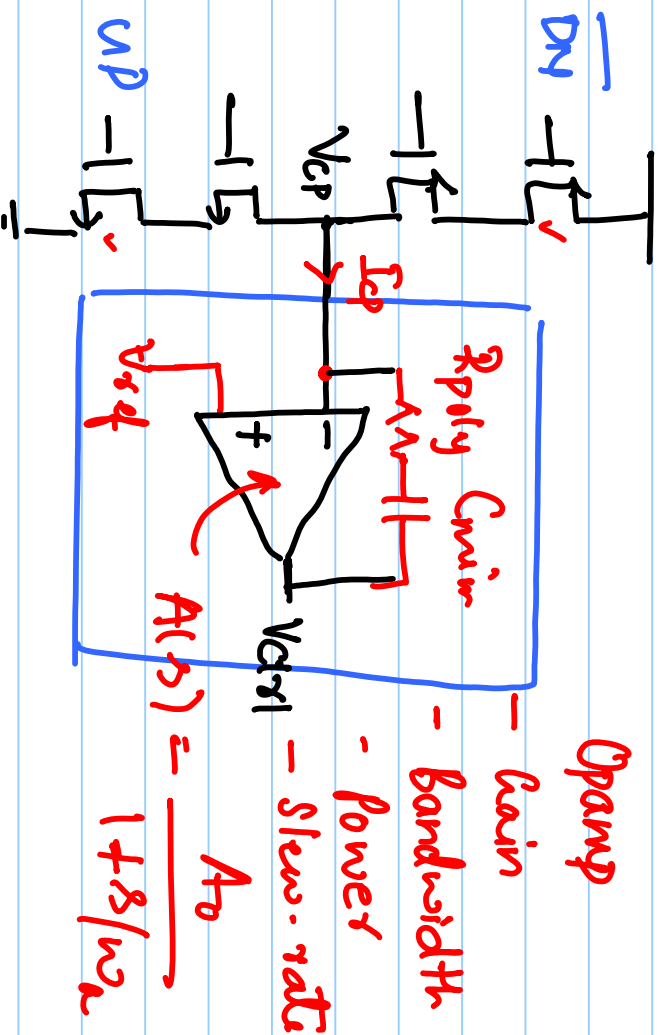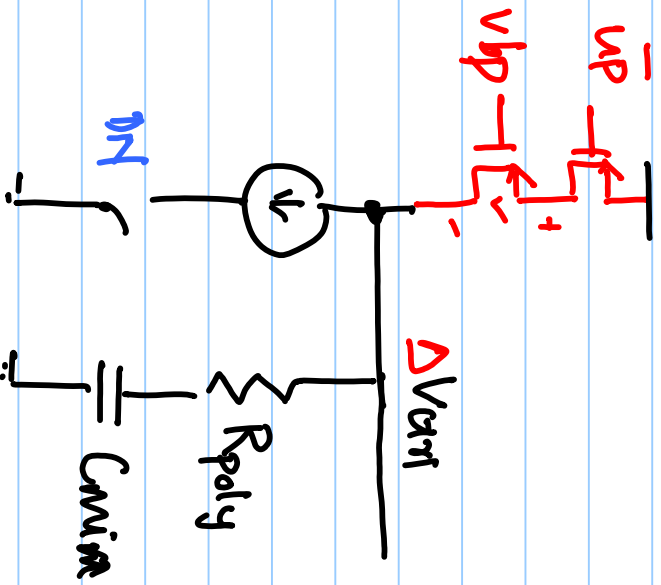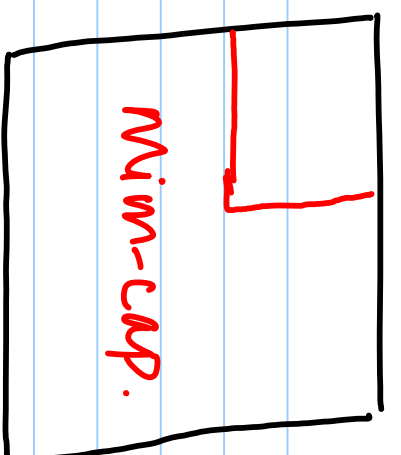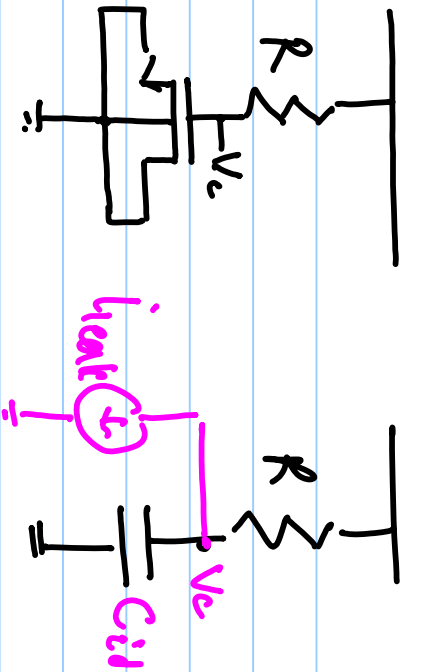
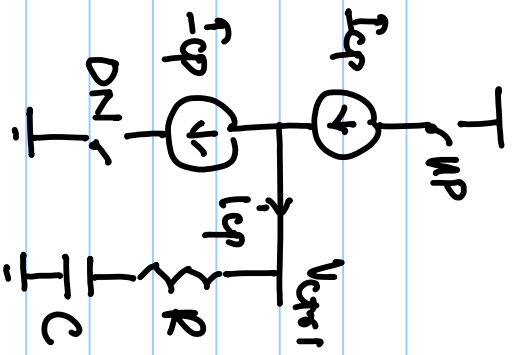
$$\frac{V_{drl}}{I_{dp}} = \ominus \left(R_{poly} + \frac{1}{sC_{min}} \right)$$



$$V_{ctrl}(s) = I_{cp}(s) \left(R + \frac{1}{sC} \right)$$

$$V_{ctrl}(t) = i_{cp} \cdot R + \frac{1}{C} \int i_{cp} \cdot dt$$

$$= \underbrace{i_{cp1}}_{V_p} \cdot R + \frac{1}{C} \int \underbrace{i_{cp2}}_{V_E} dt$$

$$V_{ctrl}(s) = I_{cp1} \cdot R + \frac{1}{sC} I_{cp2}$$


$$= \frac{I_{cp2}}{sC} \left(1 + \frac{I_{cp1}}{I_{cp2}} sRC \right)$$

$$\frac{V_{ctrl}}{I_{cp2}} = \frac{1}{sC} \left(1 + sRC \left(\frac{I_{cp1}}{I_{cp2}} \right) C \right) = \frac{1}{sC} \left(1 + sRC(K_G) \right)$$

$$M_Z = \frac{1}{R \left(\frac{I_{cp1}}{I_{cp2}} \right) C_1} = \frac{1}{RC_0} \Rightarrow \frac{I_{cp1}}{I_{cp2}} C_1 = C_0$$

$$\Rightarrow \frac{I_{cp1}}{I_{cp2}} > 1$$

$$M_Z = \frac{1}{RC_0}$$

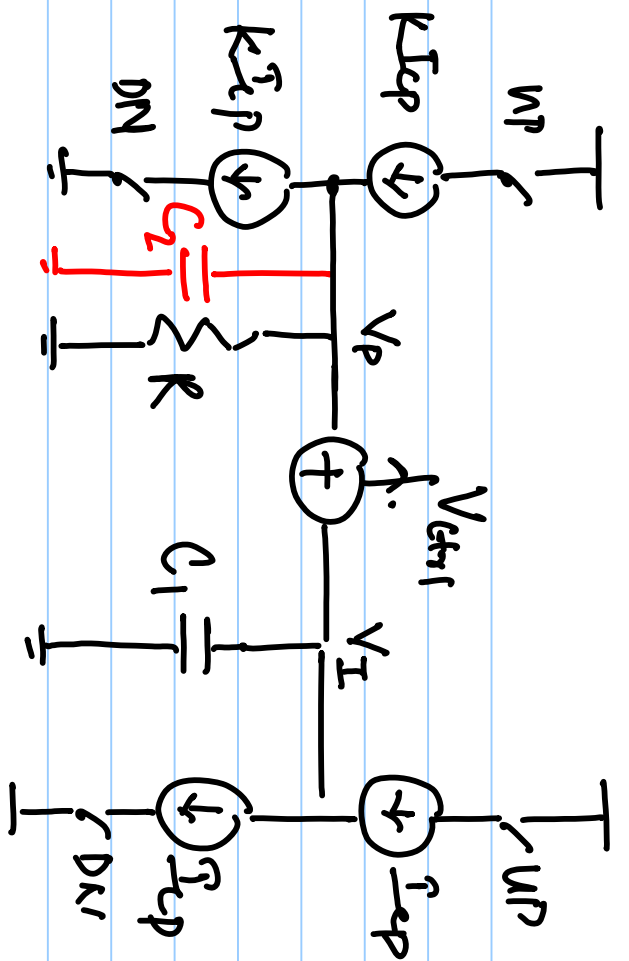

$$V_{th1}(s) = \frac{kI_{cp} R}{1+sRC_2} + \frac{I_{cp}}{sC_1}$$

$$\begin{aligned} \frac{V_{th1}(s)}{I_{cp}} &= \frac{k \cdot R \cdot sC_1 + 1 + sRC_2}{sC_1 (1 + sRC_2)} \\ &= \frac{1 + sR(kC_1 + C_2)}{sC_1 (1 + sRC_2)} \end{aligned}$$



$$\frac{V_{th1}}{I_{cp}} = \frac{1+sRC_1}{\left(1+s\frac{RC_1C_2}{C_1+C_2}\right)}$$


$$\omega_z = \frac{1}{RC_1}$$

$$\omega_z = \frac{1}{R(kC_1 + C_2)}$$



$$\omega_p = 0, \frac{1}{RC_2}$$
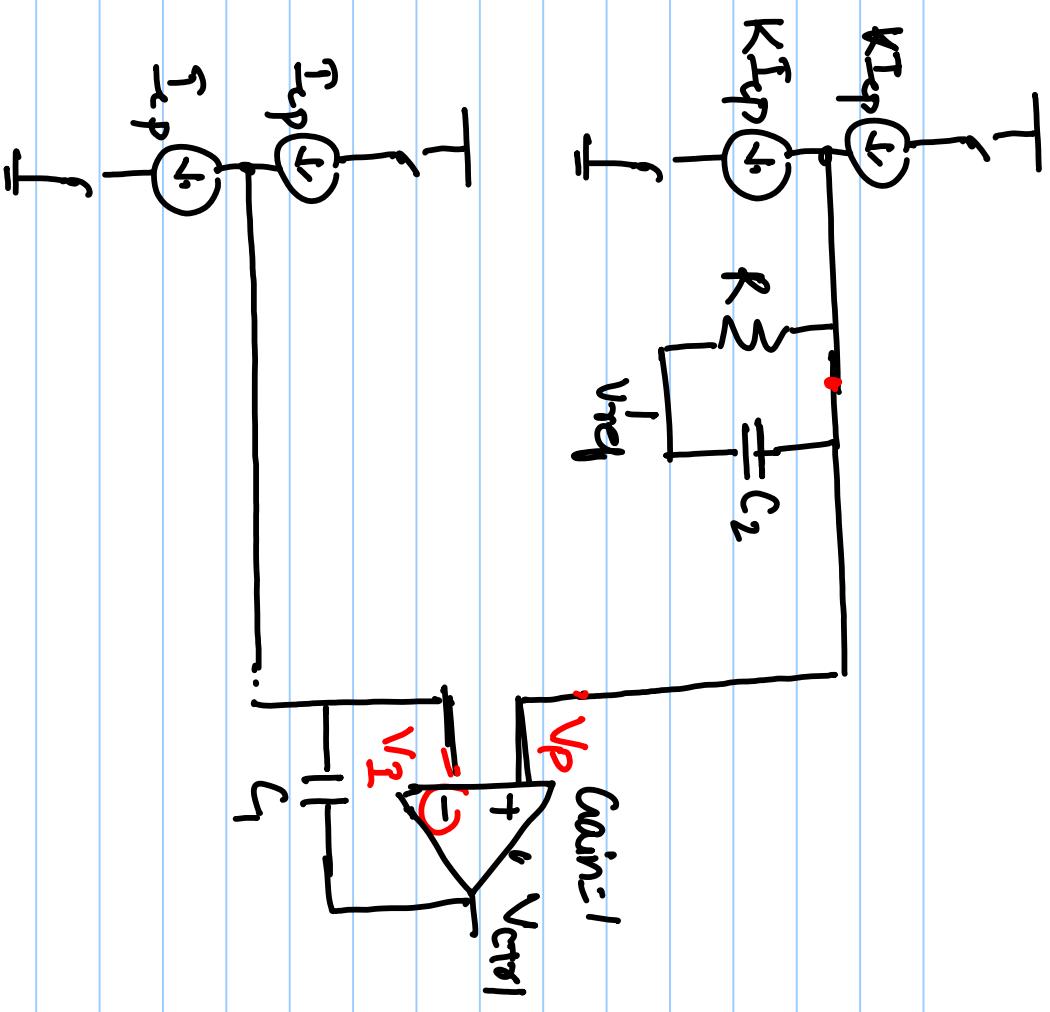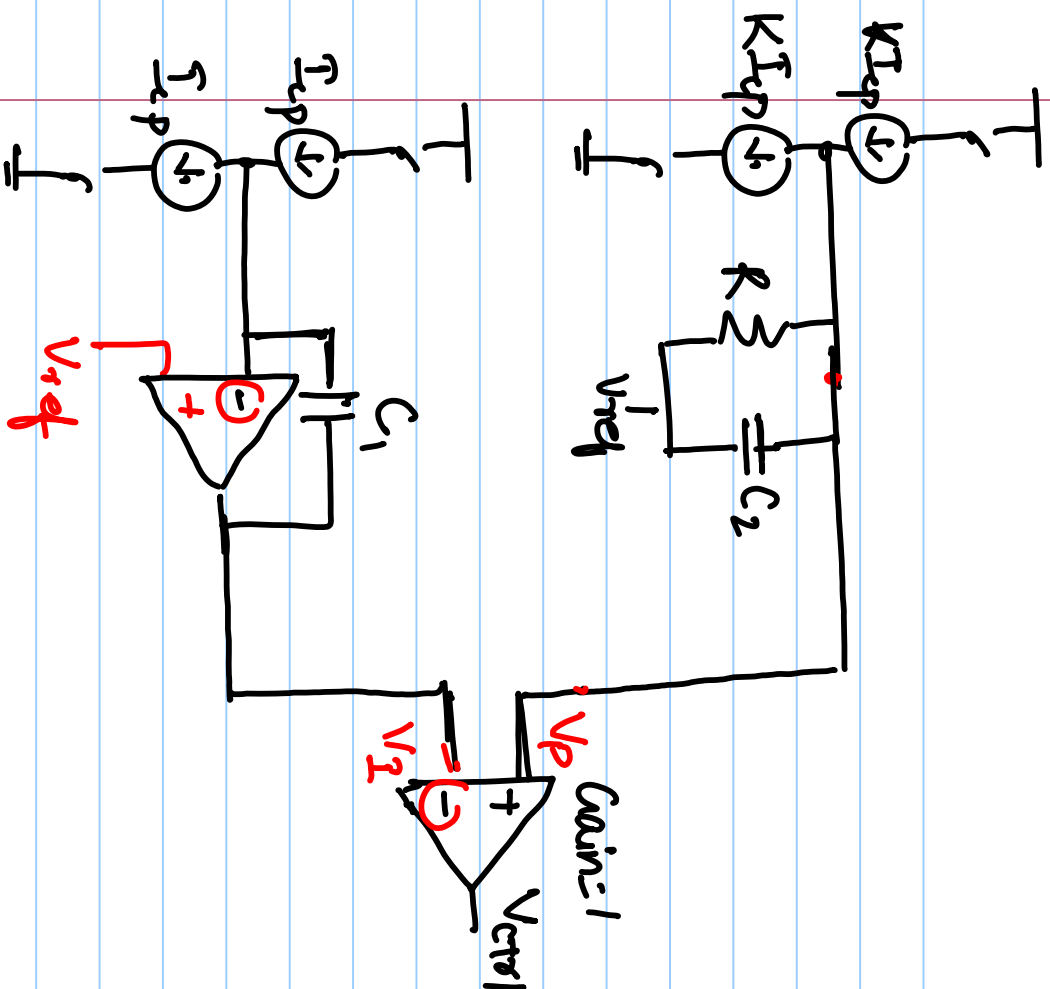
$$\omega_p = 0, \frac{1}{RC_1C_2} \frac{1}{C_1+C_2}$$





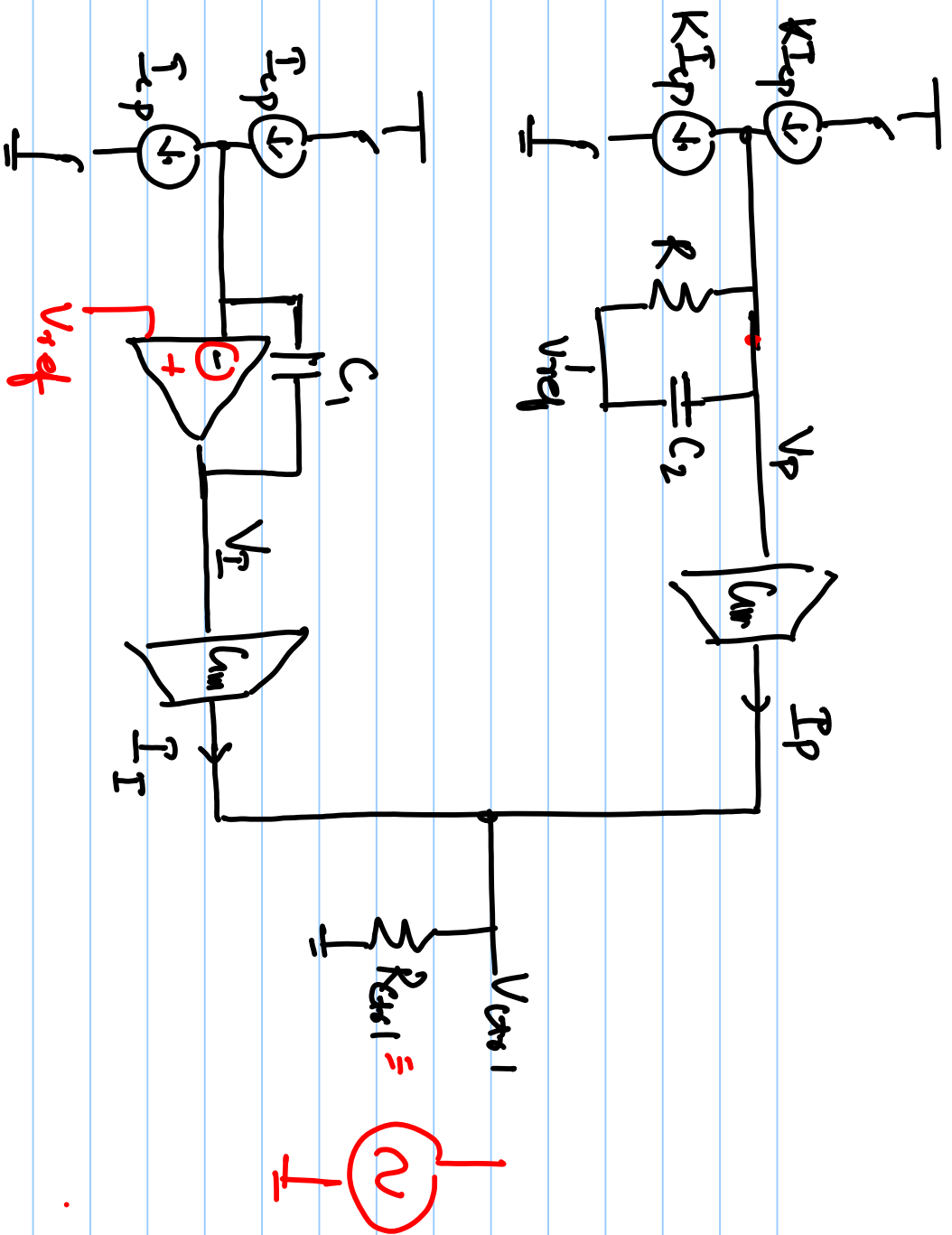

Dual Path Loop Filter (DPLF)

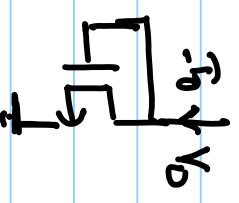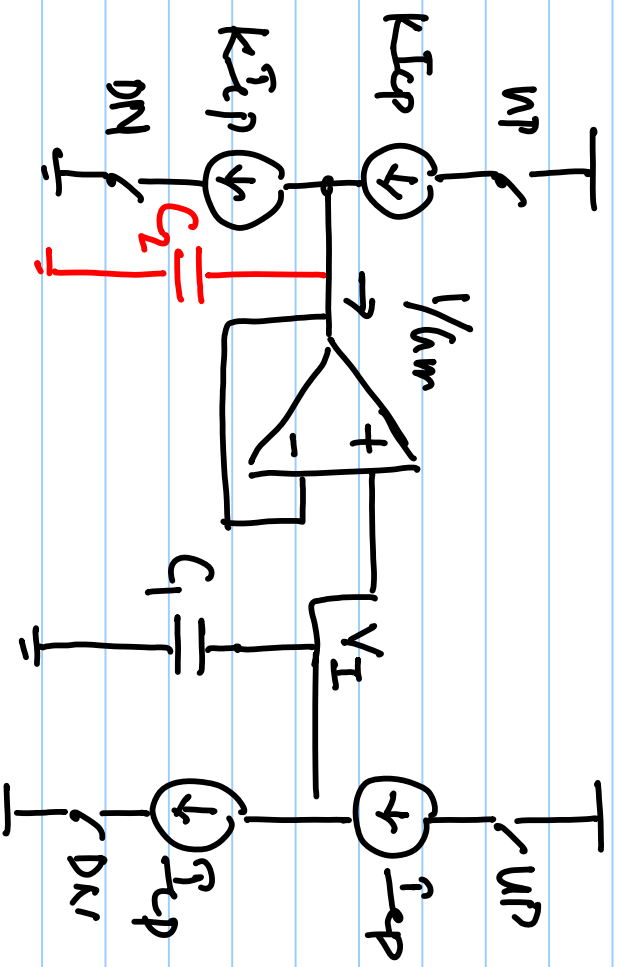
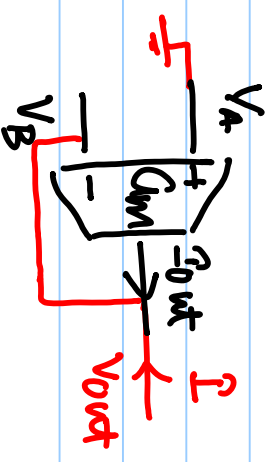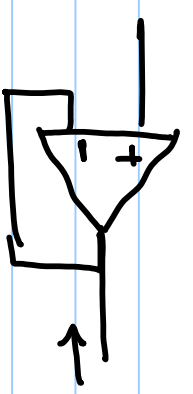
$$R = \frac{1}{g_m} = \frac{\Delta V_0}{\Delta I_0}$$



$$I_{out} = C_{gm} (V_A - V_B)$$

$$I = -C_{gm} (0 - V_{out})$$

$$\frac{V_{out}}{I} = \frac{1}{C_{gm}}$$