
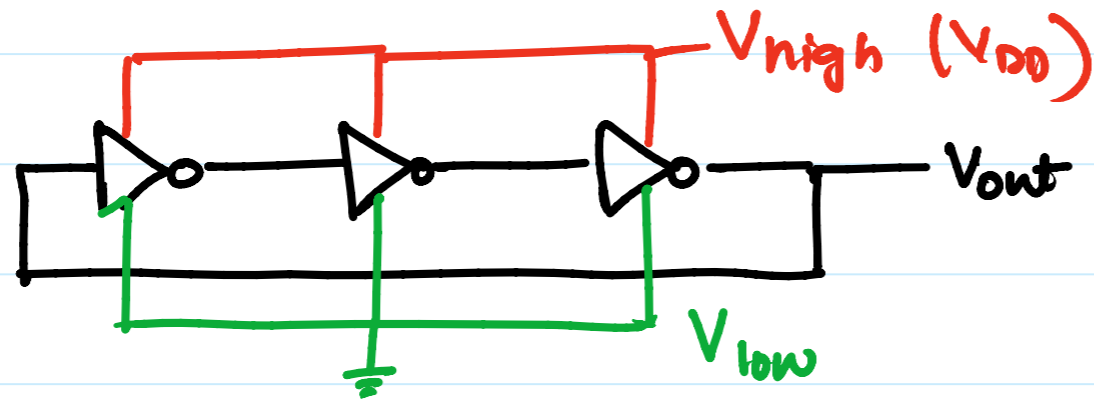



Oscillators.

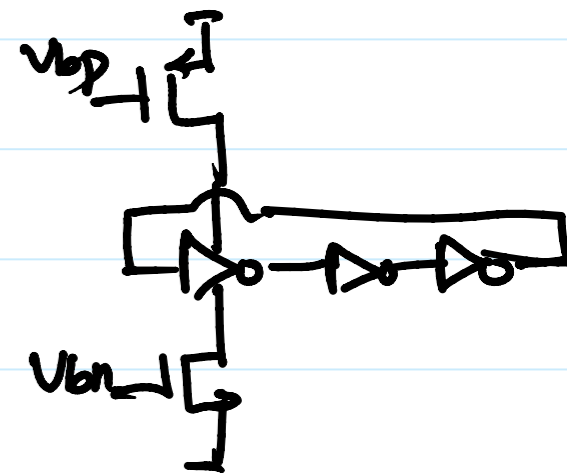

- High swing oscillator
- Tuning clock freq:
 - a) Change control voltage (V_{high})
 - b) Current starved inverters
 - c) Vary capacitive load for inverters.




a) & (c) or (b) & (c)

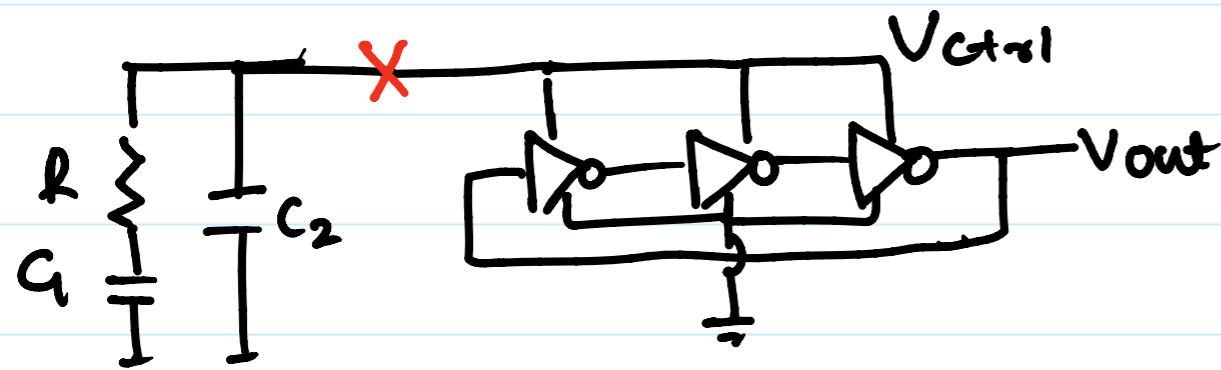

$$f_{out} = f(V_{ctrl}) \approx K_{VCO} [Hz/V]$$

Pros: Power scales w/ frequency

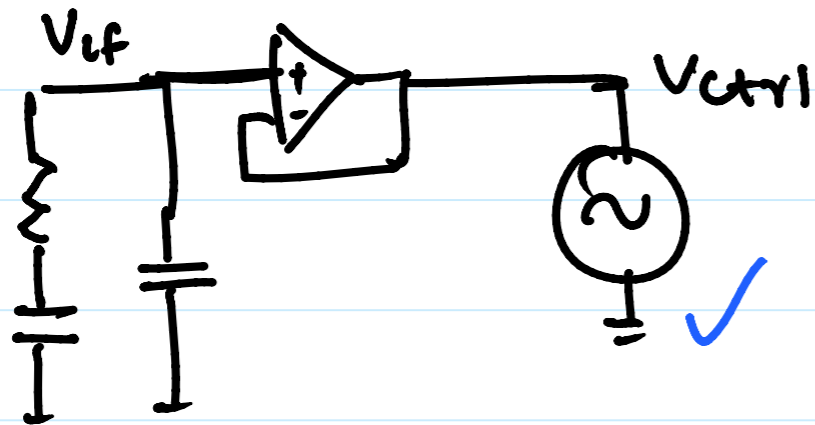
Cons: Loads the loop-filter \Rightarrow Charge-pump operates w/ input offset



- No current drawn from loop filter
- Static current consumption increases.



$$\frac{V_{ctrl}(s)}{V_{lf}(s)} = 1$$



- output swing is limited by opamp

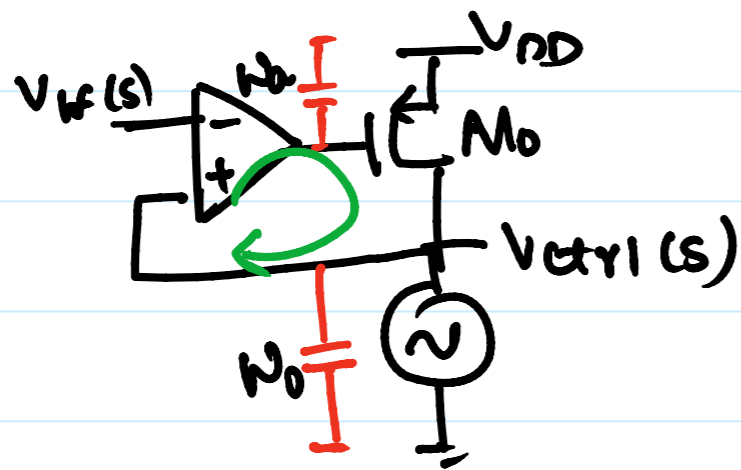


- Reduced opamp static power consumed
- $0 \leq V_{ctrl} \leq V_{DD} - V_{OV, M0}$

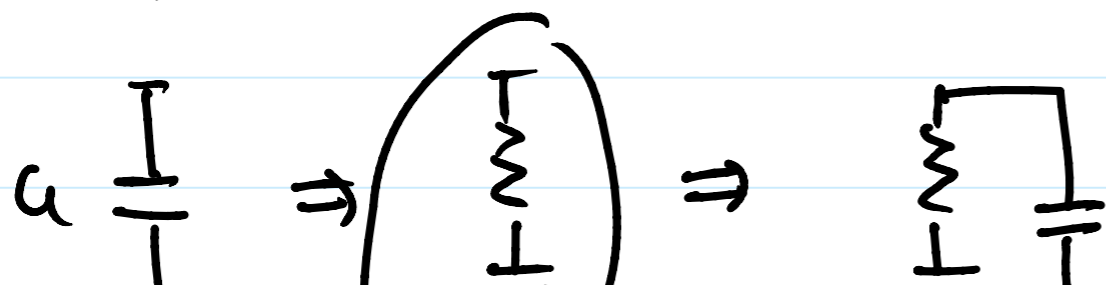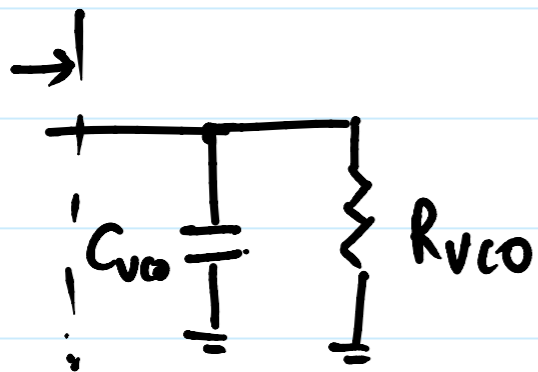- Regulation bandwidth for VCO $> 5\omega_{pu}$






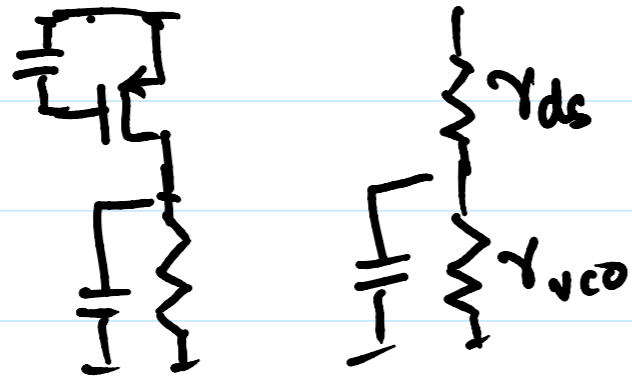
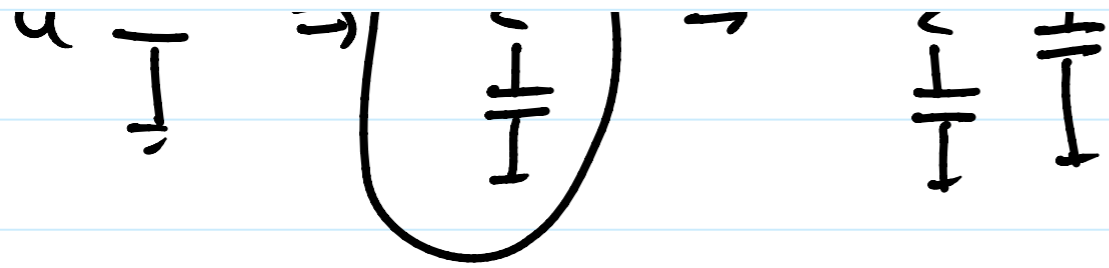


Power Supply Noise in Ring PU

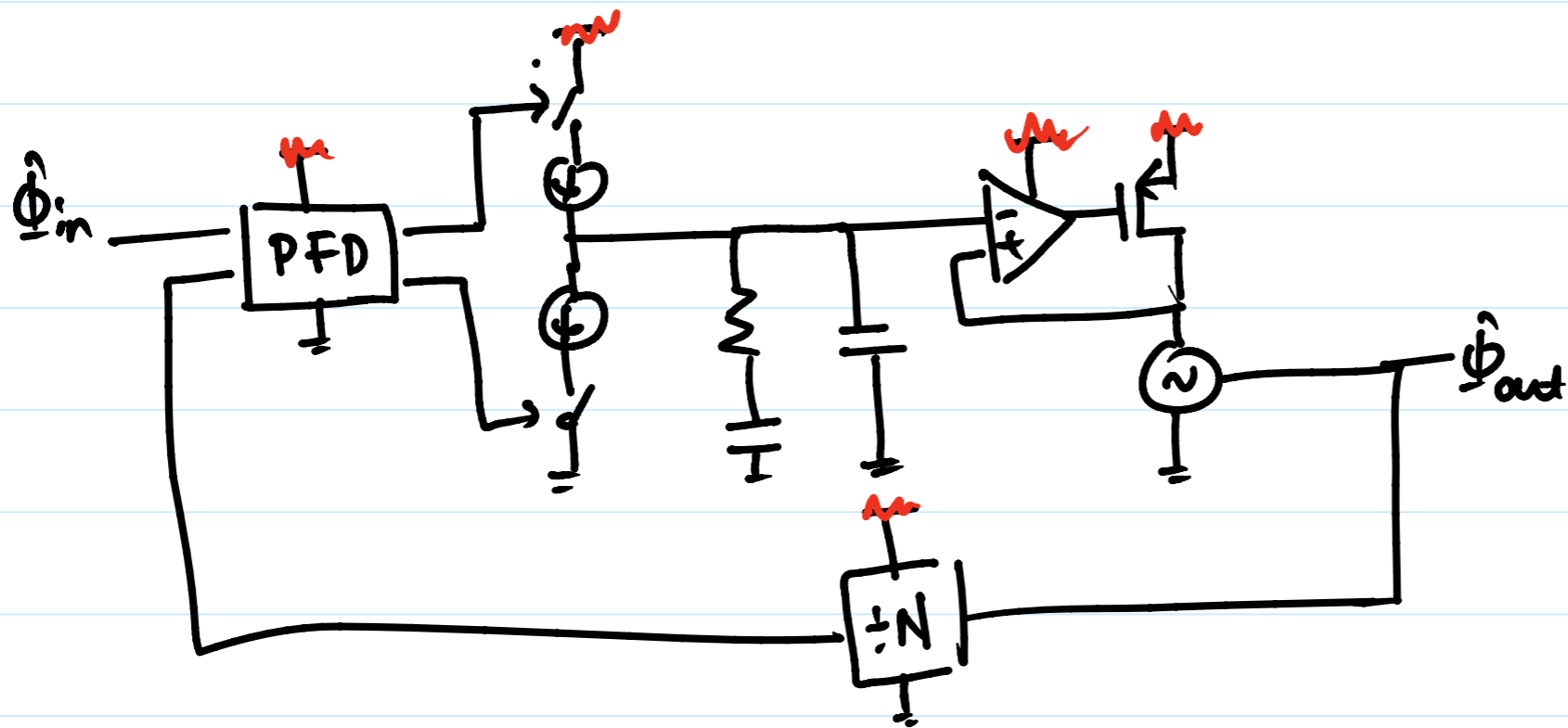
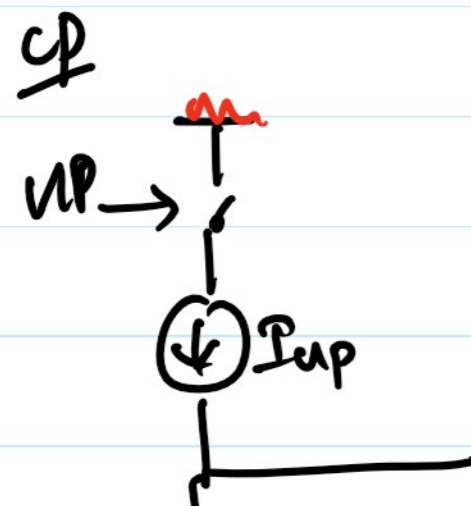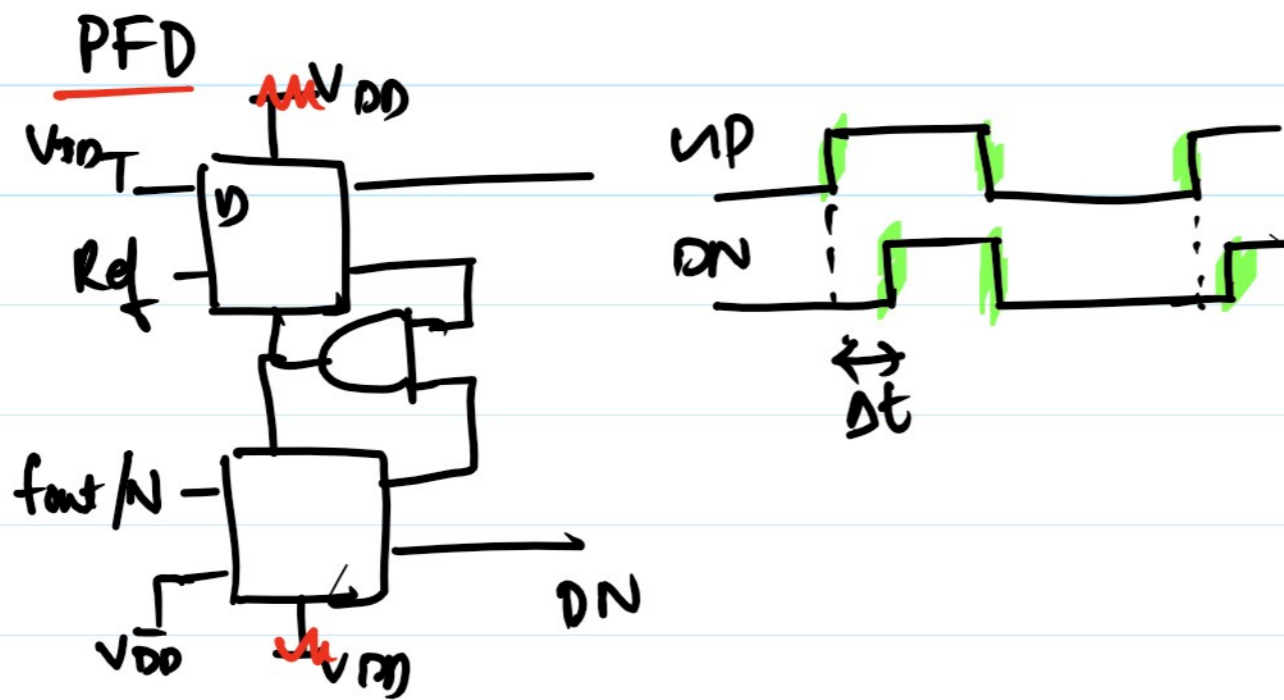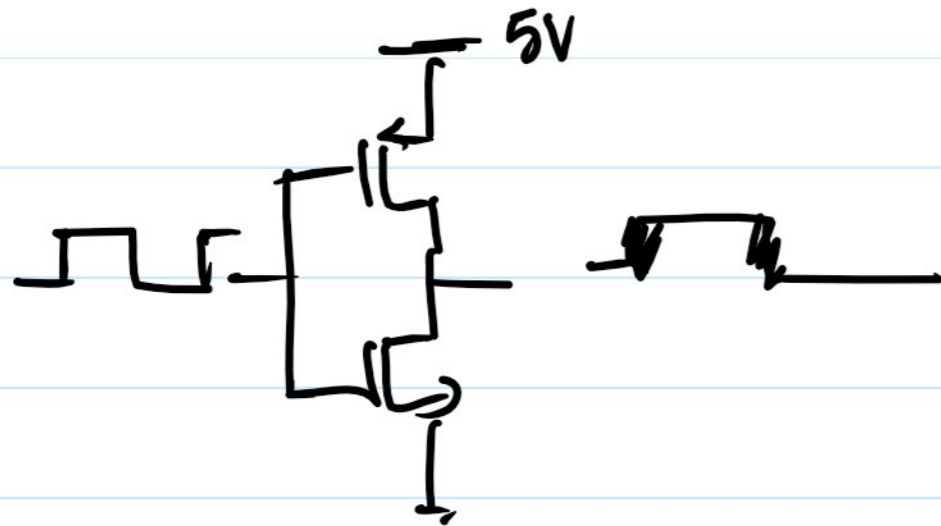
$$\text{Power Supply Noise Ratio (PSNR)} = 20 \log_{10} \left(\frac{\Delta T_i / T}{\Delta V_{DD}} \right)$$



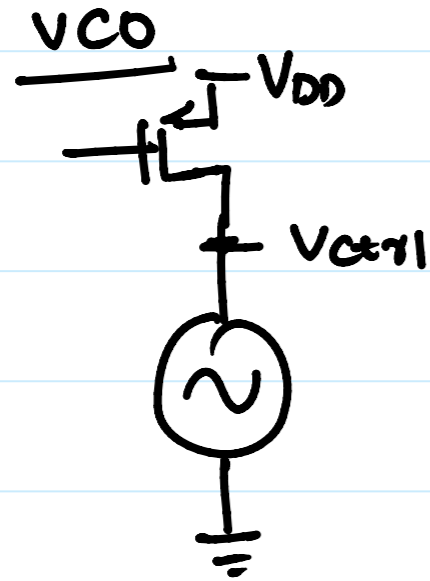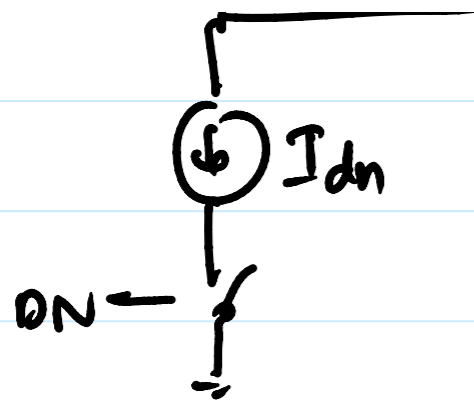

$$\frac{V_{ctrl}(s)}{V_{DD}(s)} = K_{VDD}$$

$$N_{out} = K_{VCO} V_{ctrl} = K_{VCO} V_{ctrl,io} + K_{VCO} \cdot K_{VDD} V_{dd,n}$$

$$\Delta\Phi = K_{VCO} \cdot K_{VDD} \int V_{dd,n} dt$$

$$= K_{VCO} \cdot K_{VDD} \cdot A_{VDD} \int \sin(\omega_{nt}) \cdot dt$$

$$= K_{VCO} \cdot K_{VDD} \cdot \frac{A_{VDD}}{\omega_n} \cos(\omega_{nt})$$

$$PSNR [dB] = 20 \log_{10} \left[\frac{K_{VCO} \cdot K_{VDD}}{\omega_n \cdot 2\pi} \right]$$