

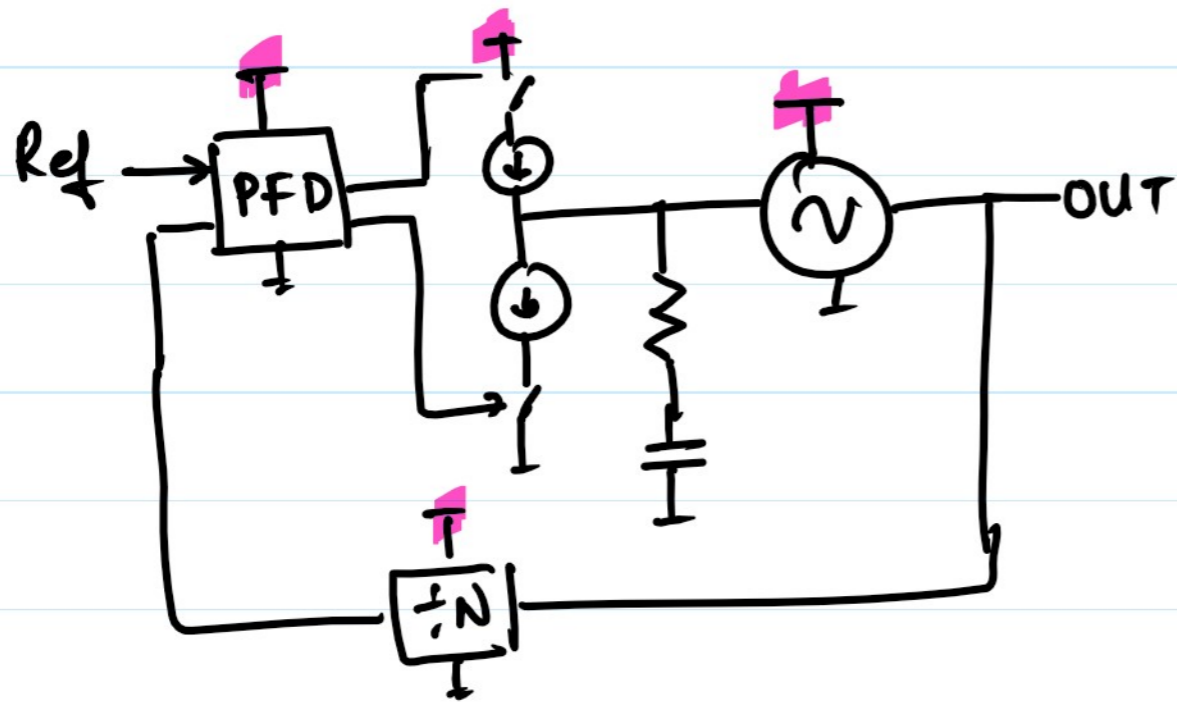
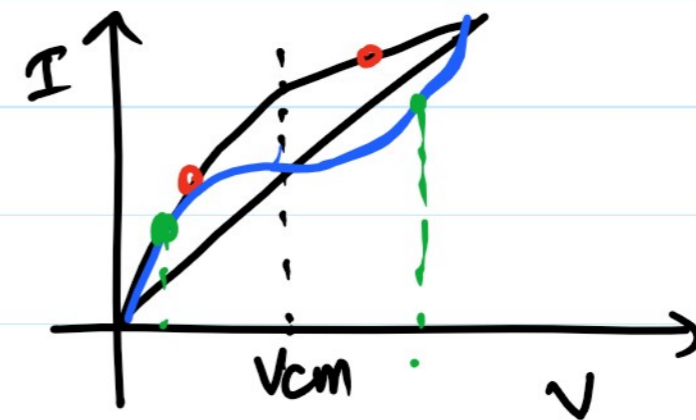



Power Supply Rejection in PLL

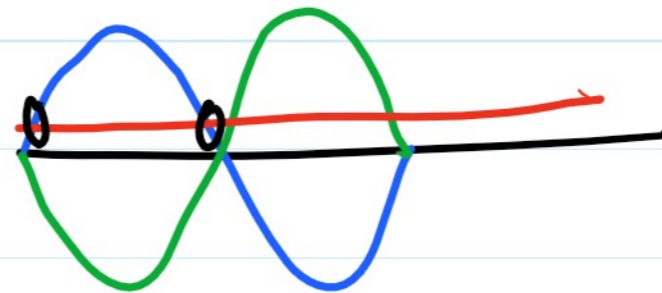

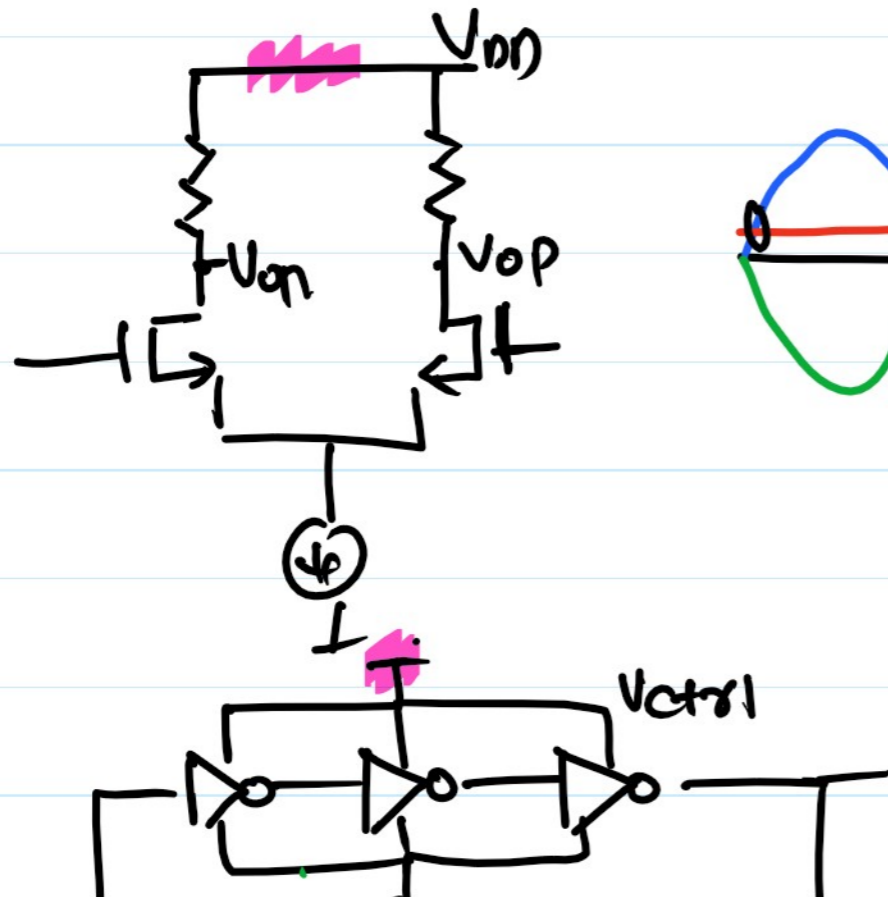Power Supply Noise Rejection, $PSNR [dB] = 20 \log_{10} \left(\frac{\Delta T / T}{\Delta V_{dd}} \right)$





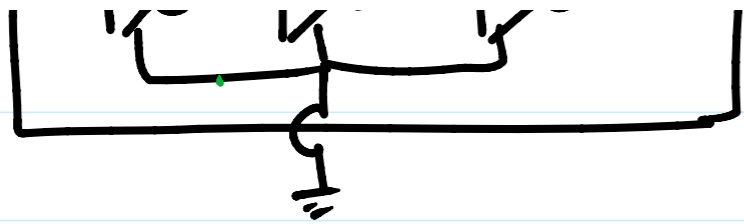$f_{out} = K_{vco} \cdot V_{ctrl}$
 $f_{out}(t) = K_{vco} V_{dd} + K_{vco} \psi_1$






$$f_{out}(t) = K_{vco} V_{dd} + K_{vco} \varphi_{dd}$$



$$\phi_{out}(t) = 2\pi \int f_{out} dt$$

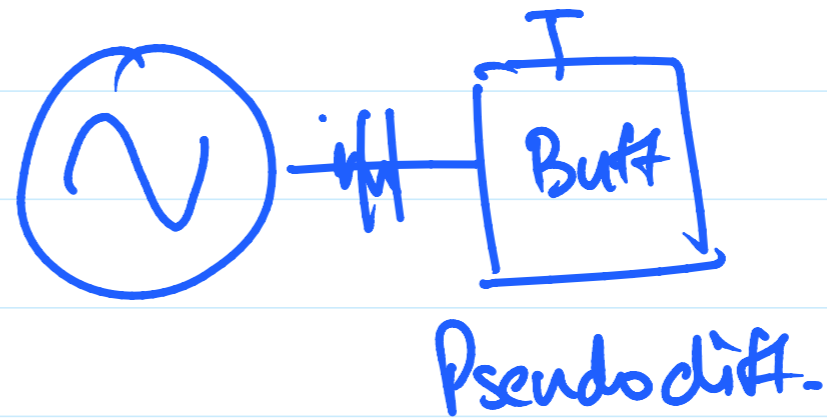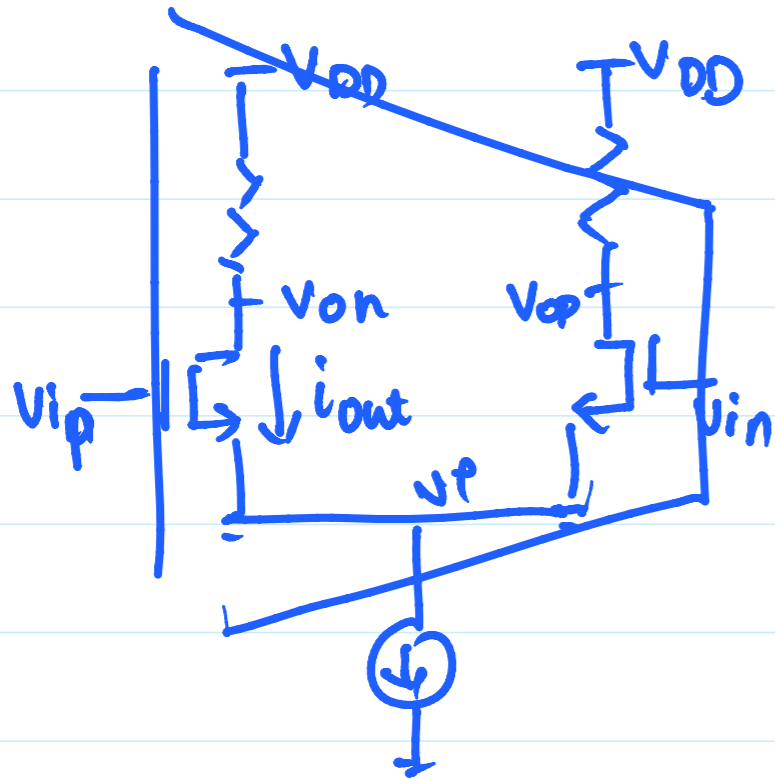

Supply regulation in ring oscillators

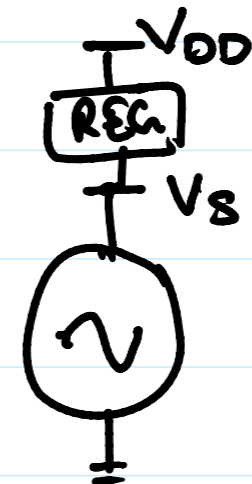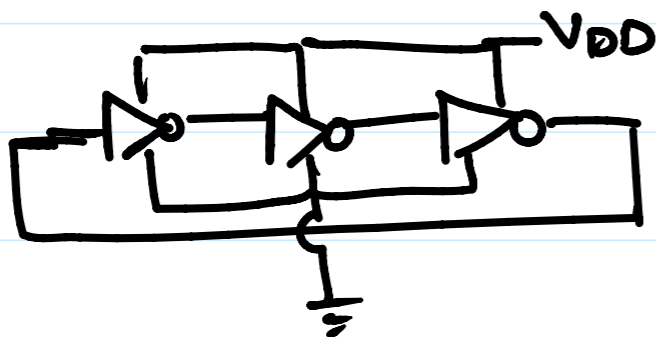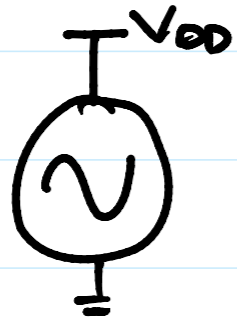


Output of ...

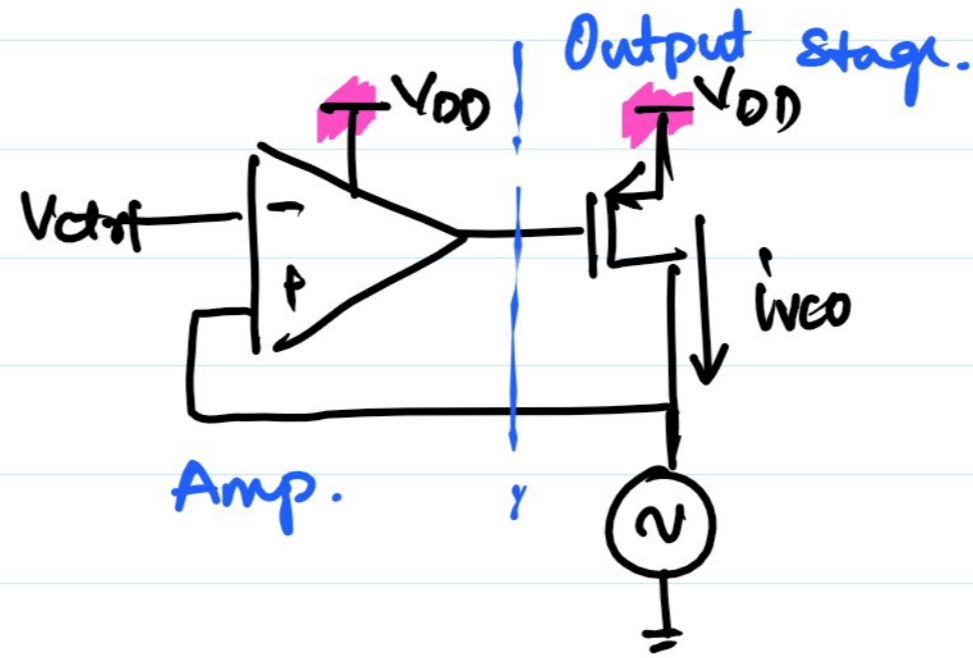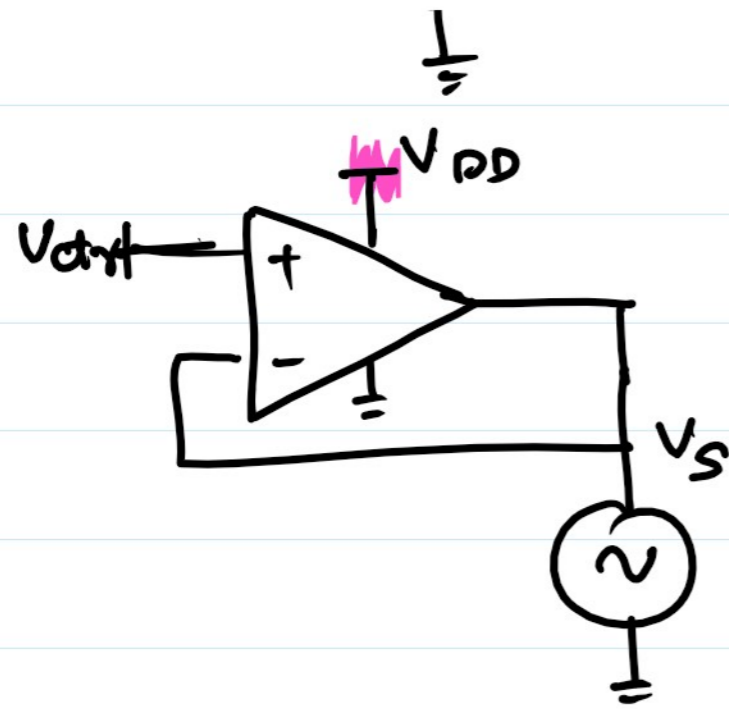


Output Stage.

- 1.) PMOS o/p
- 2.) NMOS o/p

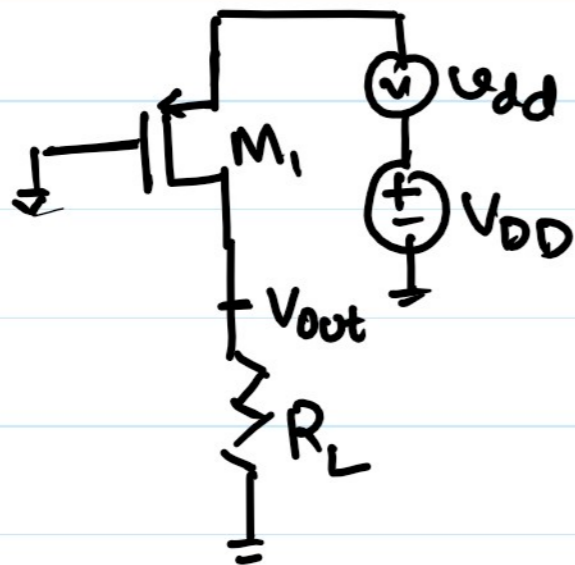


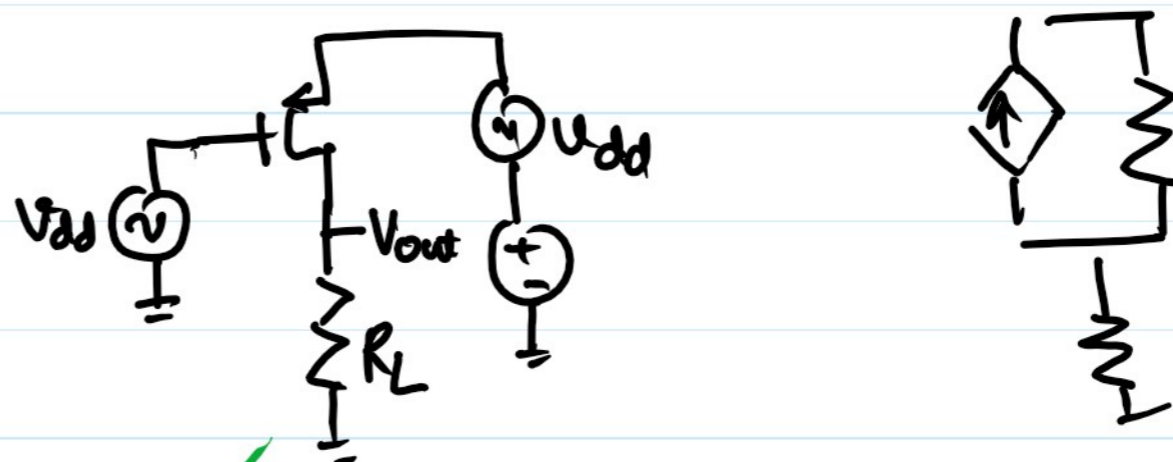
$$\frac{V_{out}(s)}{V_{dd}(s)} = g_{m1} (\gamma_{ds1} \parallel R_L)$$



$$\frac{V_{out}(s)}{V_{dd}(s)} = \frac{R_L}{R_L + \gamma_{ds1}}$$

$V_{dd}(s)$

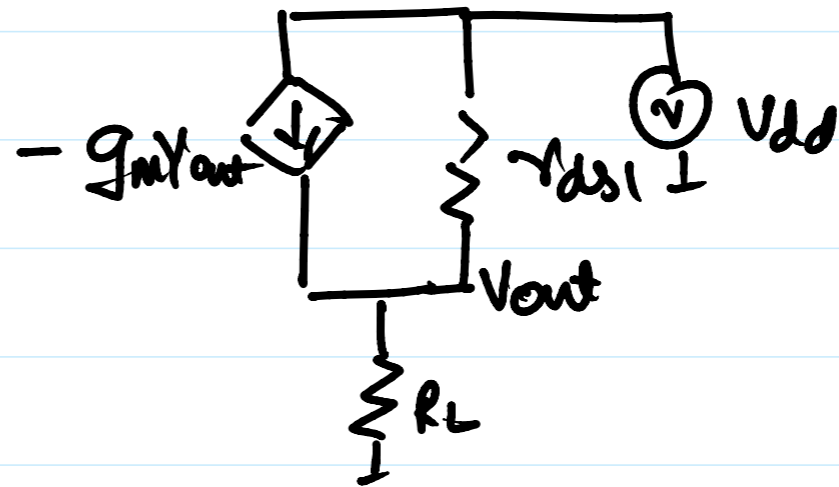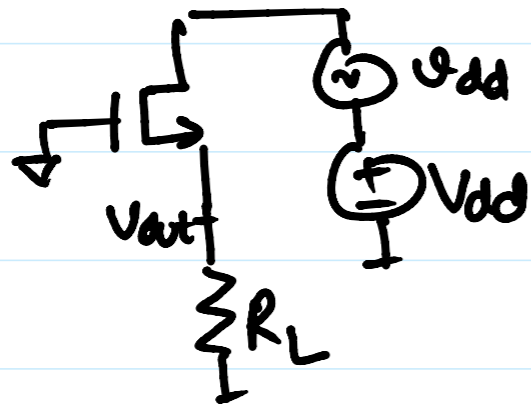
Ideal $\gamma_{ds} \rightarrow \infty \Rightarrow$ lower $V_{out} \Rightarrow$ lower fout



$$\frac{V_{out}(s)}{V_{dd}(s)} \approx \frac{1}{g_m \gamma_{ds1}}$$

$$-g_m v_{out} + \frac{V_{dd} - v_{out}}{\gamma_{ds1}} = \frac{v_{out}}{R_L}$$
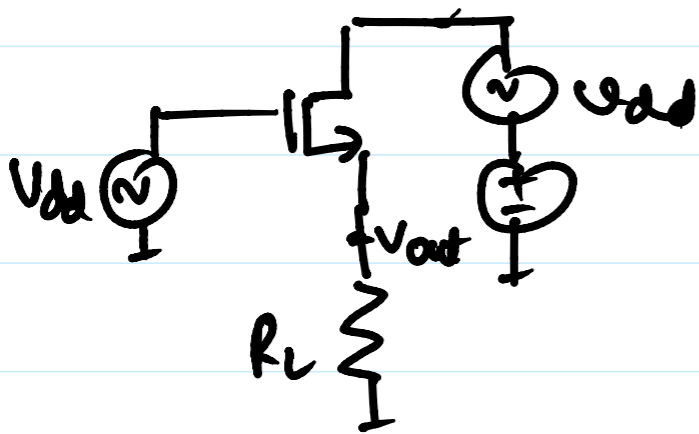
$$v_{out} \left(\frac{1}{\gamma_{ds1}} + \frac{1}{R_L} + g_m \right) = \frac{V_{dd}}{\gamma_{ds1}}$$




$$g_m (V_{dd} - v_{out})$$

$$\frac{V_{out}(s)}{V_{dd}(s)} \approx 1$$

$$\frac{V_{out}(s)}{V_{dd}(s)} \approx 1$$


Amplifier stage.

NMOS i/p stage

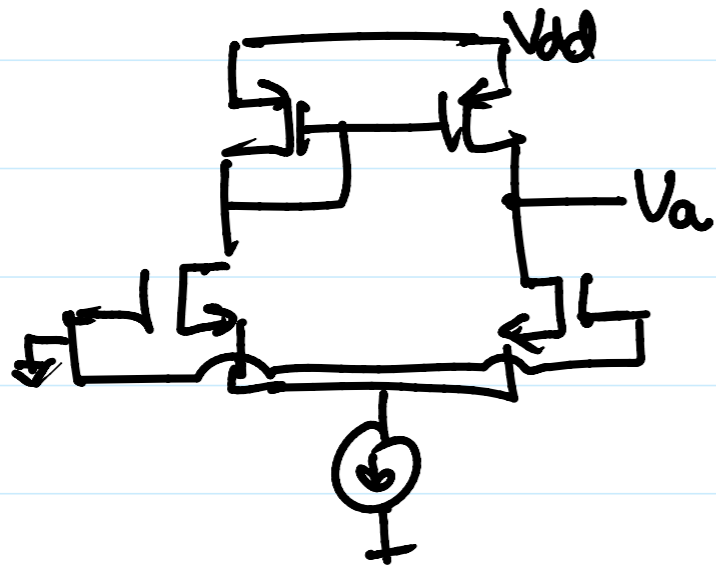



$$\frac{V_a(s)}{V_{dd}(s)} = 1$$

PMOS i/p stage

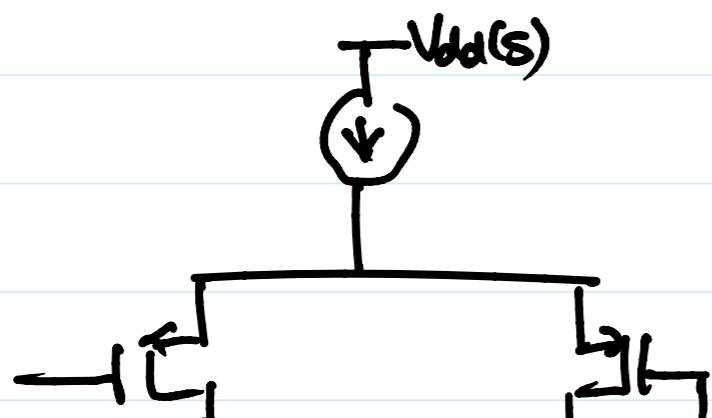

$$\frac{V_a(s)}{V_{dd}(s)} \approx 0$$


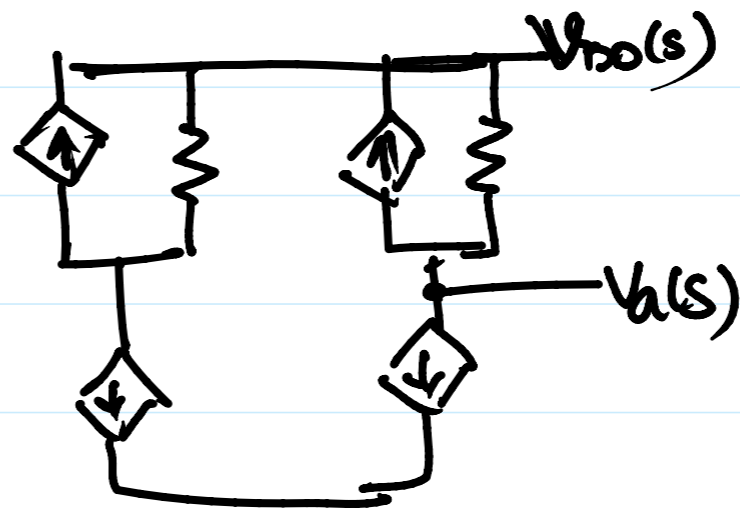


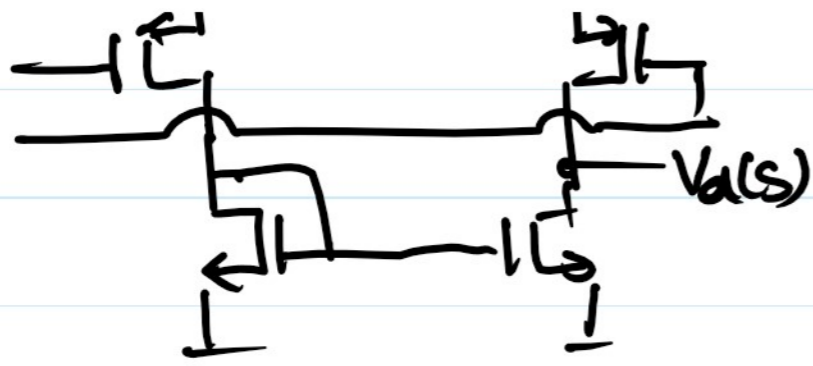

$$\frac{V_a(s)}{V_{dd}(s)} \approx 0$$



Amp. stage + o/p stage

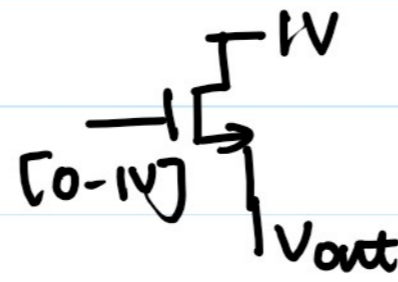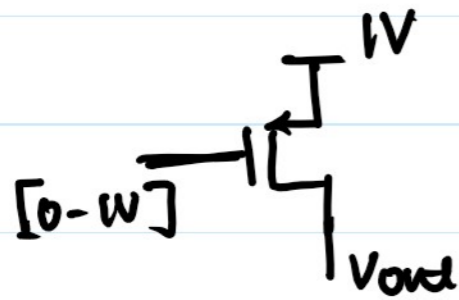
- 1) NMOS i/p amp. + PMOS o/p stage ✓
- 2) NMOS i/p amp + NMOS o/p stage
- 3) PMOS i/p amp + PMOS o/p stage
- 4) PMOS i/p amp + NMOS o/p stage. ✓



$$V_{out,max} = V_{DD} - V_{ov}$$
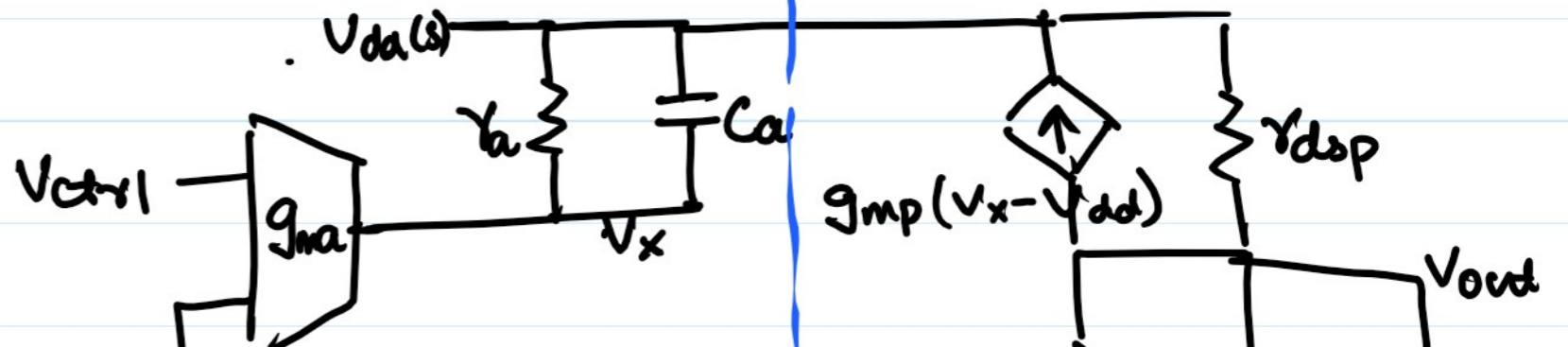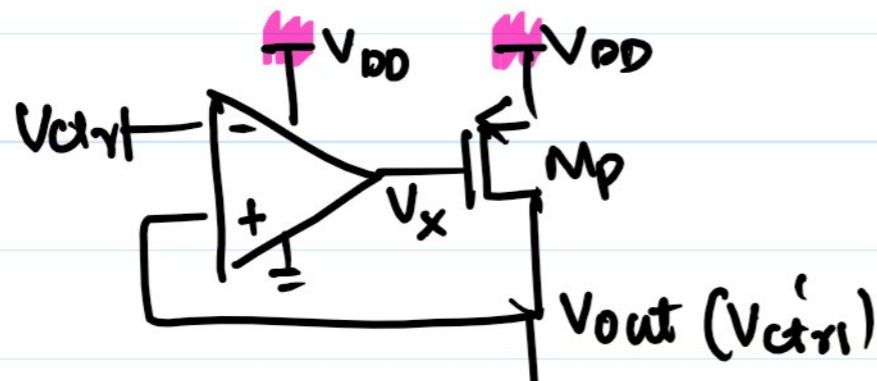
$$V_a - (V_{DD} - V_{ov}) - V_T = V_{ov}$$



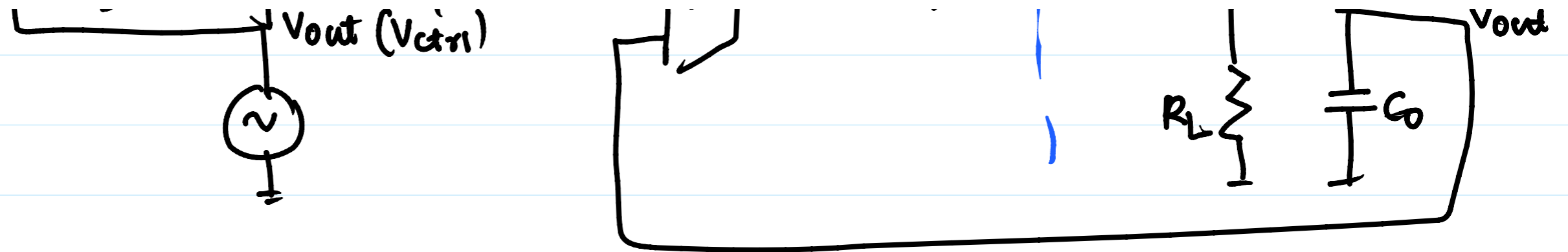


$$\frac{V_{out}(s)}{V_{dd}(s)} = \frac{S_{vdd}}{\left(1 + \frac{s}{\omega_0}\right) \left(1 + LC_{reg}\right)} = \frac{S_{vdd} \left(1 + s/\omega_a\right)}{\left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_0}\right) + A_o A_a}$$

$$S_{vdd} = \frac{R_L}{R_L + Y_{dep}}, \quad \omega_0 = \frac{1}{(Y_{dep} \parallel R_L) C_o}$$

$$LC_{reg} = \frac{A_a A_o}{\left(1 + \frac{s}{\omega_0}\right) \left(1 + \frac{s}{\omega_a}\right)}; \quad A_a = g_{ma} \gamma_a, \quad A_o = g_{mp} (Y_{dep} \parallel R_o)$$

$$\omega_a = \frac{1}{\gamma_a C_c}$$

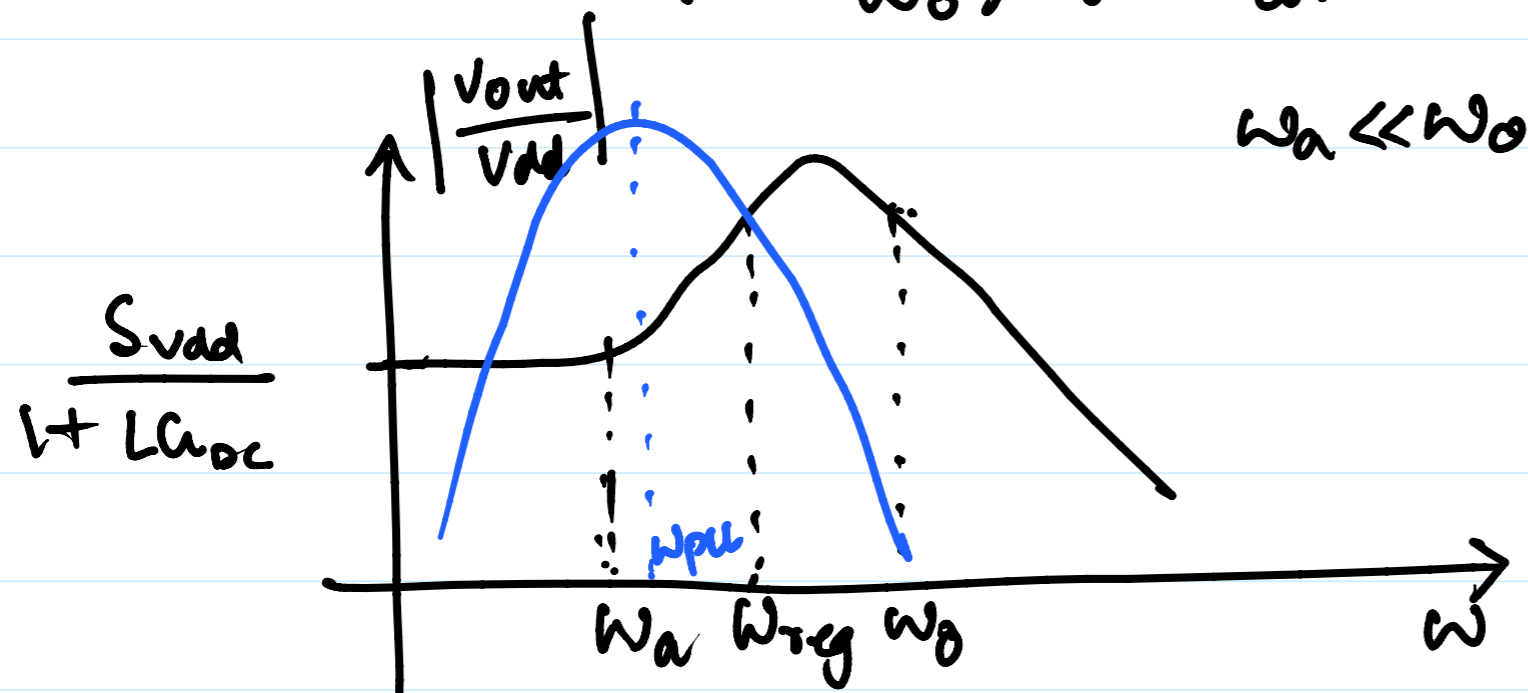

$$\frac{\Phi_{out}}{V_{ctrl}(s)} = \frac{K_{vco}}{s} \frac{1}{1 + LC_{pi}}$$