
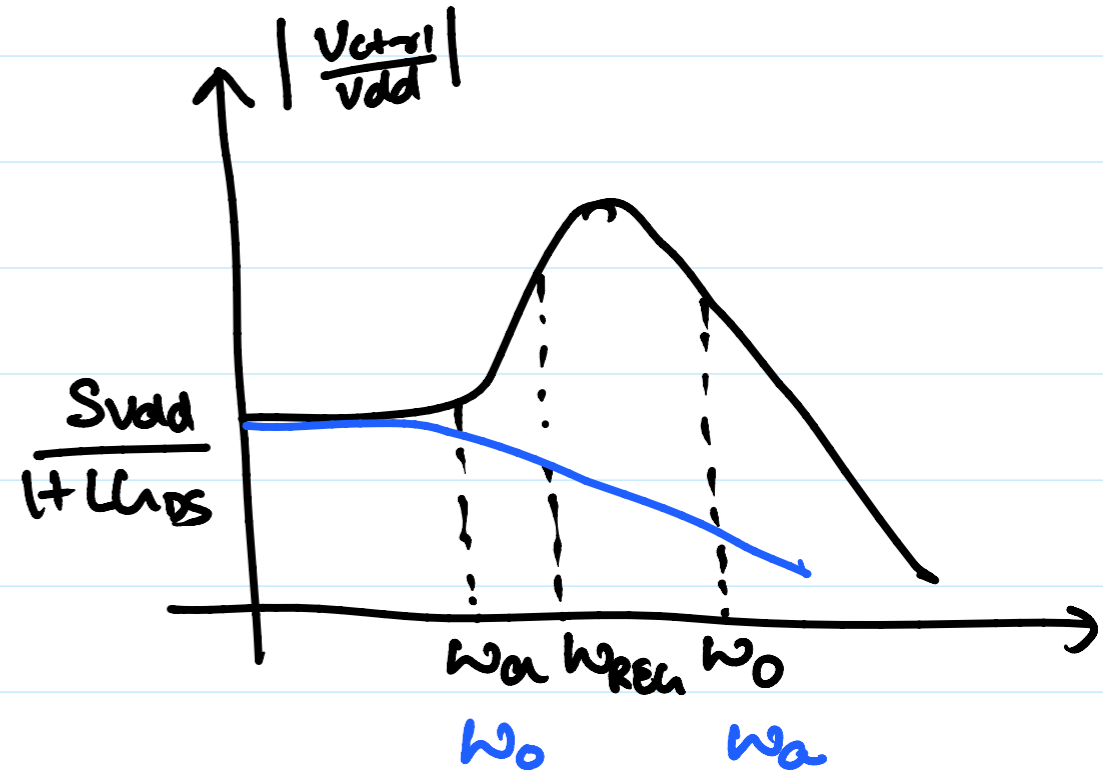
 



PSRR in PLLs.

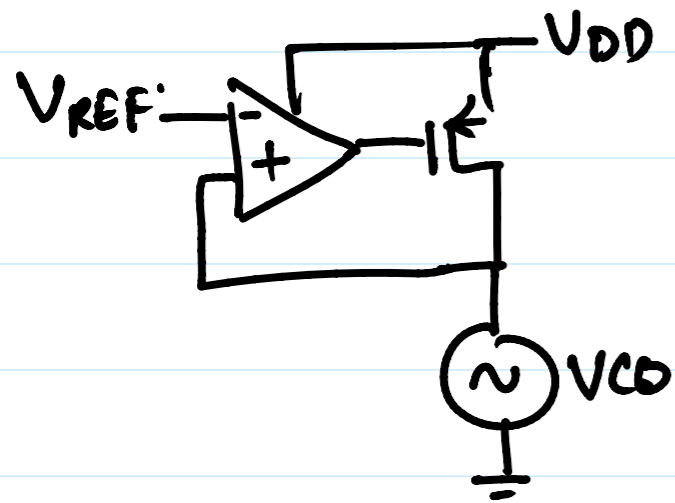


$$\frac{V_{ctrl}(s)}{V_{dd}(s)} = \frac{S_{vdd}}{\left(1 + \frac{s}{\omega_0}\right) \left(1 + LG(s)\right)}$$

$$LG(s) = \frac{A_a A_o}{\left(1 + \frac{s}{\omega_a}\right) \left(1 + \frac{s}{\omega_0}\right)}$$
 
$$\omega_a = \frac{1}{\gamma_{oa} C_a}, \quad \omega_0 = \frac{1}{(\gamma_{dsp} \parallel R_L) C_o}$$



 
$$\frac{V_{ctrl}(s)}{V_{dd}(s)} = \frac{S_{vdd}}{1}$$



$$\frac{V_{ctrl}(s)}{V_{DD}(s)} = \frac{\Delta V_{DD}}{(1 + s/\omega_0)(1 + Ls/\omega_{reg})}$$
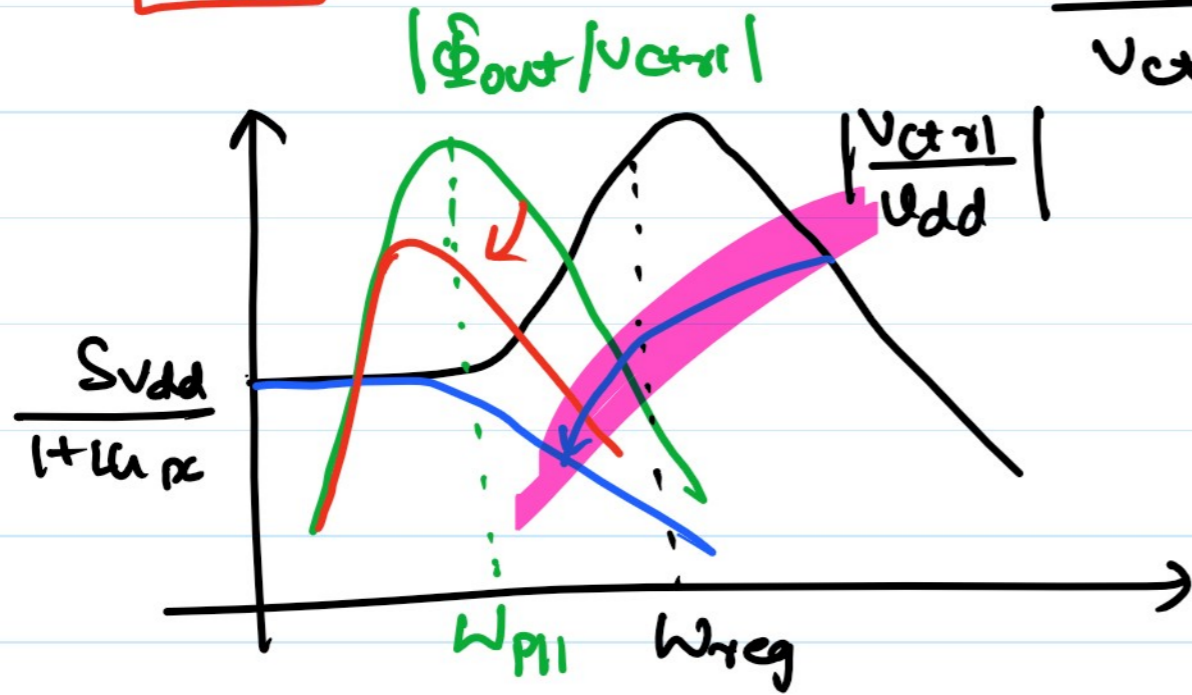
$$\frac{\Phi_{out}(s)}{V_{ctrl}(s)} = \frac{K_{VCO}}{s} \frac{1}{1 + Ls/\omega_{reg}}$$



$$\frac{\Phi_{out}(s)}{V_{DD}(s)} = \frac{V_{ctrl}(s)}{V_{DD}(s)} \times \frac{\Phi_{out}(s)}{V_{ctrl}(s)}$$

$$L_{C_{reg}}(s) = \frac{I_{cp}}{s^2(C_1 + C_2)} \frac{1}{2\pi} K_{VCO} \frac{(1 + s/\omega_z)}{(1 + s/\omega_{p3})} \times \left(\frac{1}{1 + s/\omega_{reg}} \right)$$

w/o reg.
w/ reg.


For better PSRR

- a) $\omega_{PII} < \omega_{reg} \Rightarrow$ large power in reg.
- b) $\omega_0 < \omega_a$ for regulator \Rightarrow large capacitor, lower PU bandwidth
- c) lower PLL bandwidth \Rightarrow increase in VCO noise

c) Lower PLL bandwidth \Rightarrow Increase in VCO noise.

Techniques to improve PSRR




1) NMOS as current source.

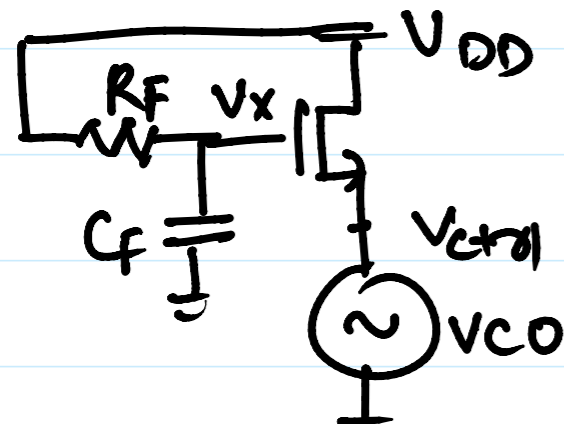


$$\frac{V_x}{V_{DD}} = \frac{1}{1 + sC_F R_F}$$

$$\omega_F = \frac{1}{C_F R_F}$$

  
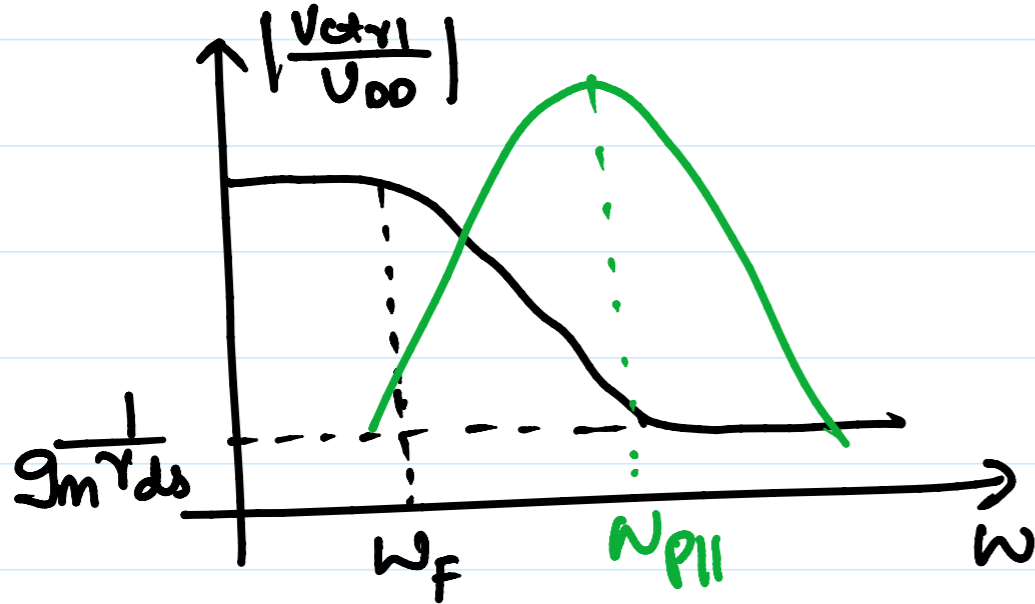
For better PSRR ; $\omega_F \ll \omega_{PII}$



 

Cascaded Regulators

b)

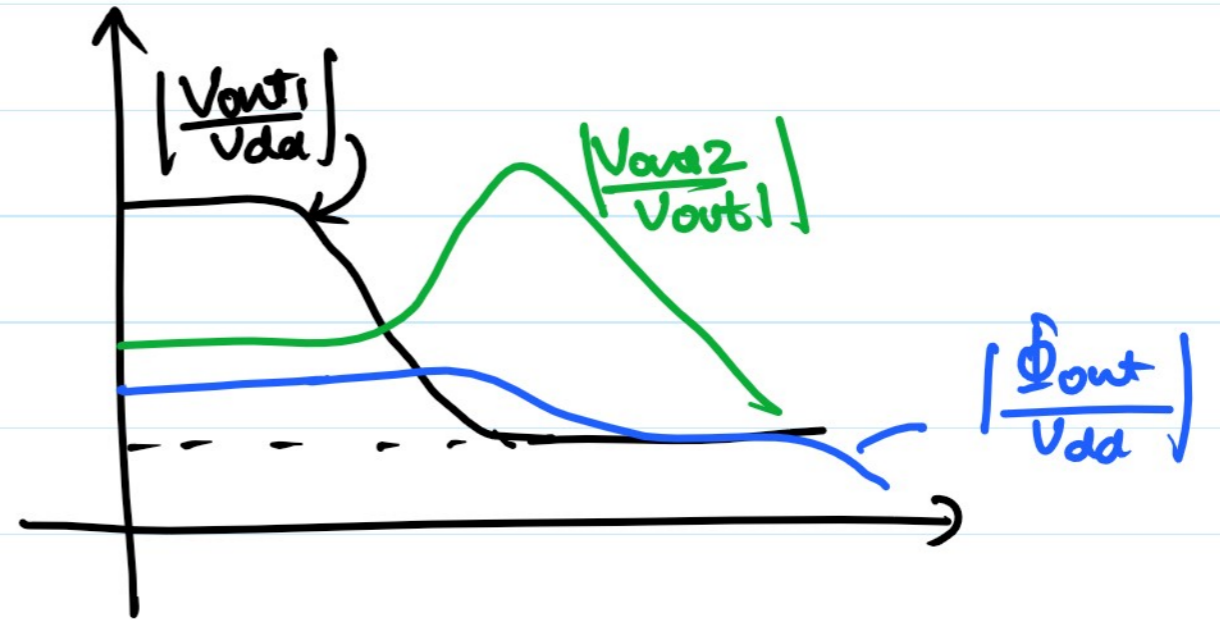
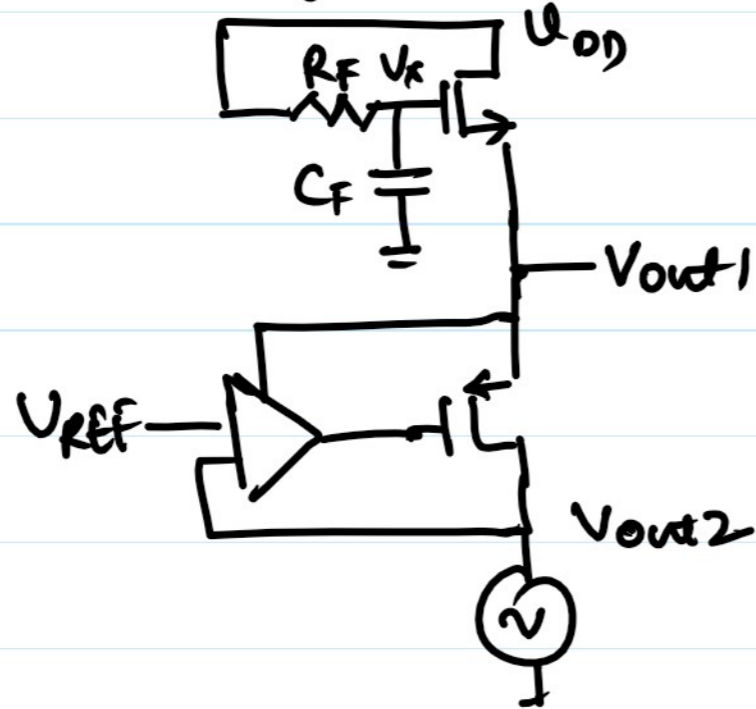






Cons: Larger headroom for regulator

In a given CMOS technology

Regular V_t , low V_t , high V_t , Native.

c) Replica-biased LDO

  

   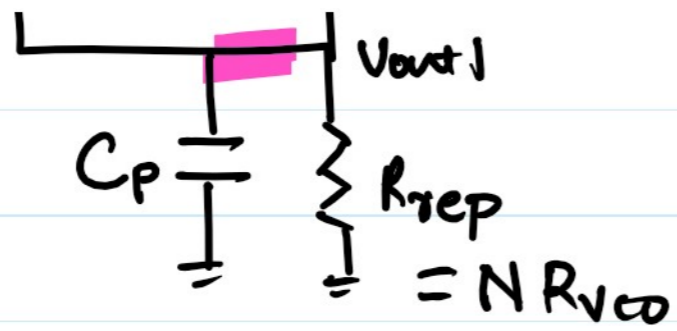

Remarks
 - Mismatch between M_n and M_p degrade PSRR

