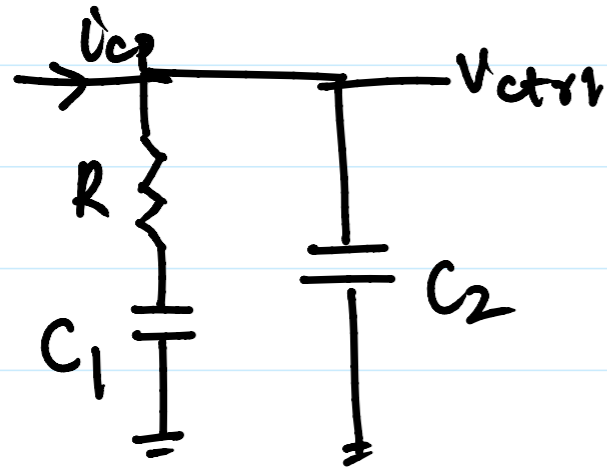



Loop Filter.




- Resistor
- Capacitors
 - Parallel plate Cap.
 - Fringe cap. using metal in same layer.

Ex. 100 pF \rightarrow $\frac{100 \times 10^{-12}}{2 \times 10^{-15}} = 50\,000 \mu\text{m}^2$

$0.5 - 2.0 \text{ fF}/\mu\text{m}^2$

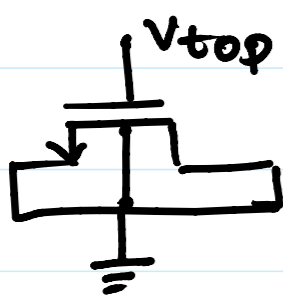


Active Capacitor

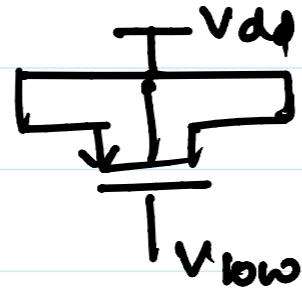


nMOS cap.

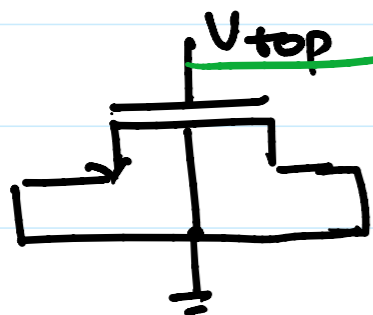$V_{top} \quad 0.1 \rightarrow 1.0$
 $1 \text{ fF}/\mu\text{m}^2 \rightarrow 12 \text{ fF}/\mu\text{m}^2$



Cap. i_{leak}


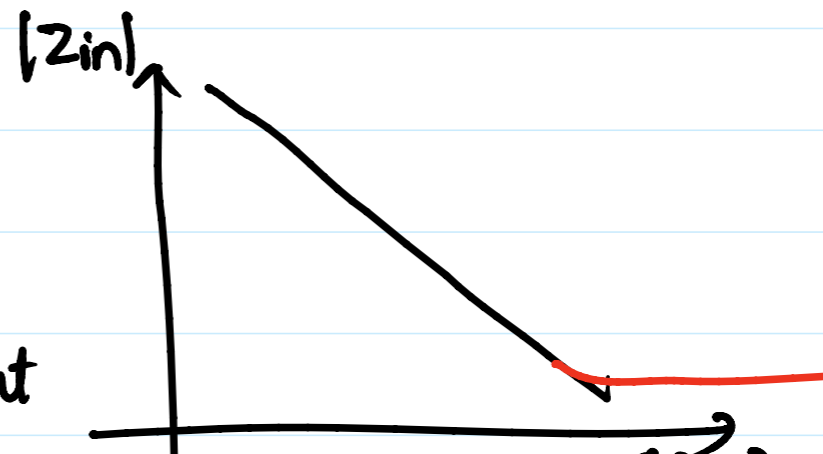
- $10 \text{ fF}/\mu\text{m}^2$
- ✓ leakage current
- Series resistor
- Voltage dependent



- Voltage dependent





$$Z_{in} = \frac{1}{sC}$$

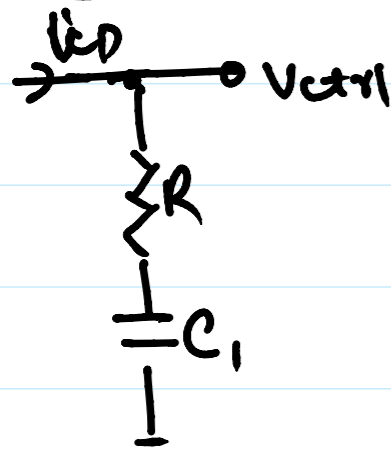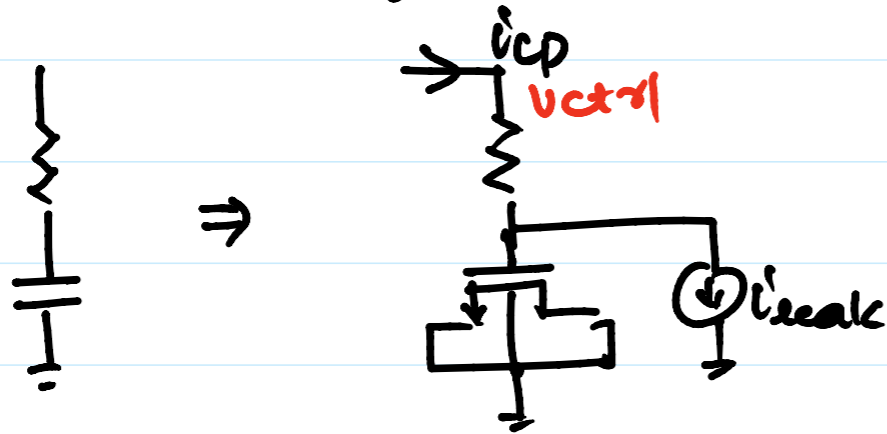

$$Z_{in} = R + \frac{1}{sC}$$
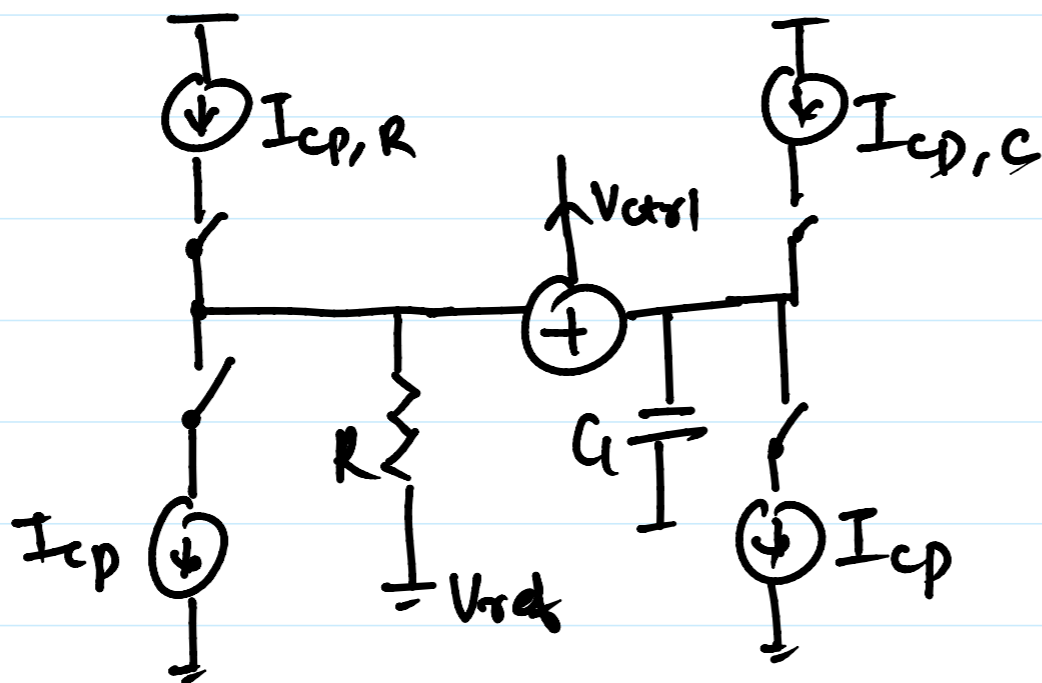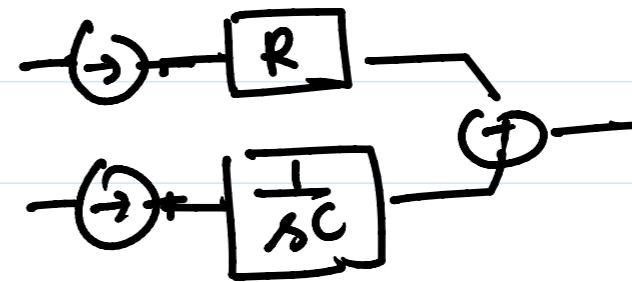
$$V_{ctrl} = \underbrace{i_{cp} (R)} + \underbrace{\frac{i_{cp}}{sC}}$$



- Mismatch in I_{cp} in R & C
- linearity of summer
- more hardware.

Dual-path loop filter

$$V_{ctrl} = I_{cp,R} \cdot R + I_{cp,C} \times \frac{1}{sC}$$

$$= \frac{I_{cp,C}}{sC} \left[1 + sC \cdot R \frac{I_{cp,R}}{I_{cp,C}} \right]$$



$$\frac{I_{cp}}{sC} [1 + sRC]$$




$$\omega_z = \frac{1}{RC}$$

$$\omega_z = \frac{1}{RC \underbrace{\frac{I_{cp,R}}{I_{cp,C}}}_{C_{eff}}}$$

$$V_{ctrl} \Big|_{\frac{I_{cp,R}}{10} = I_{cp,C} = I_{cp}} = \frac{I_{cp}}{sC} [1 + sRC \cdot 10]$$
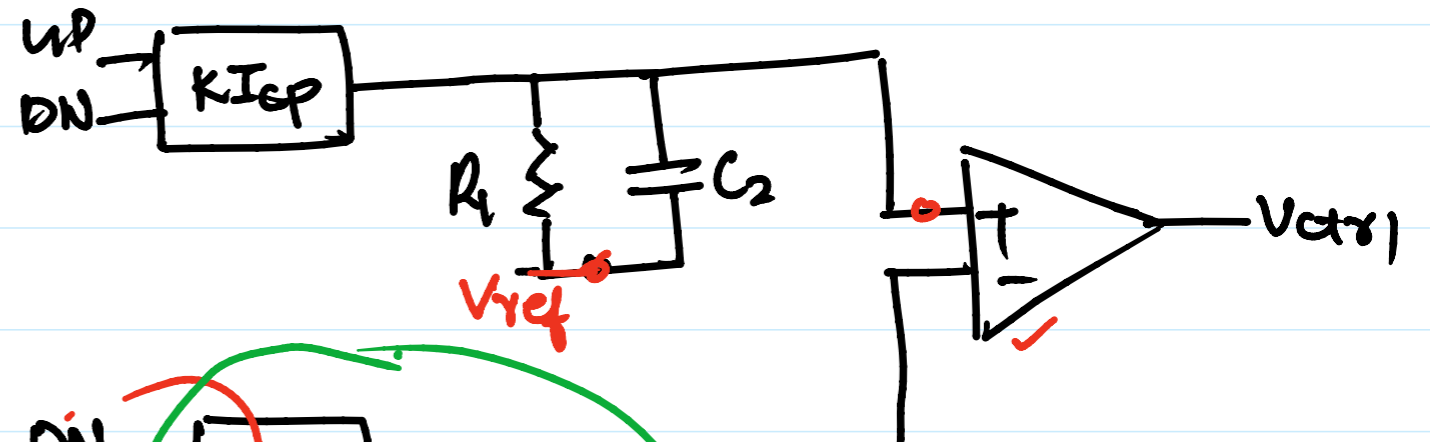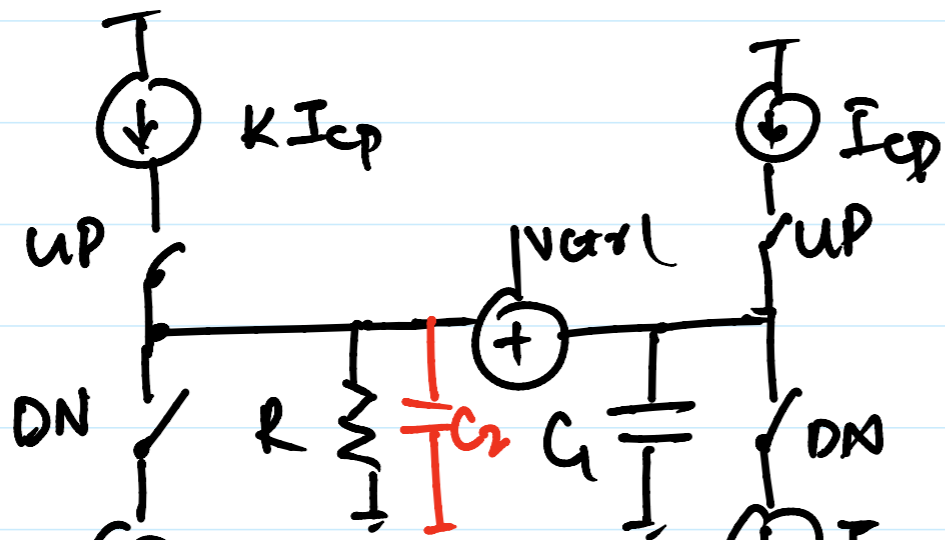
$$\omega_z = \frac{1}{10 \cdot R \cdot C}$$






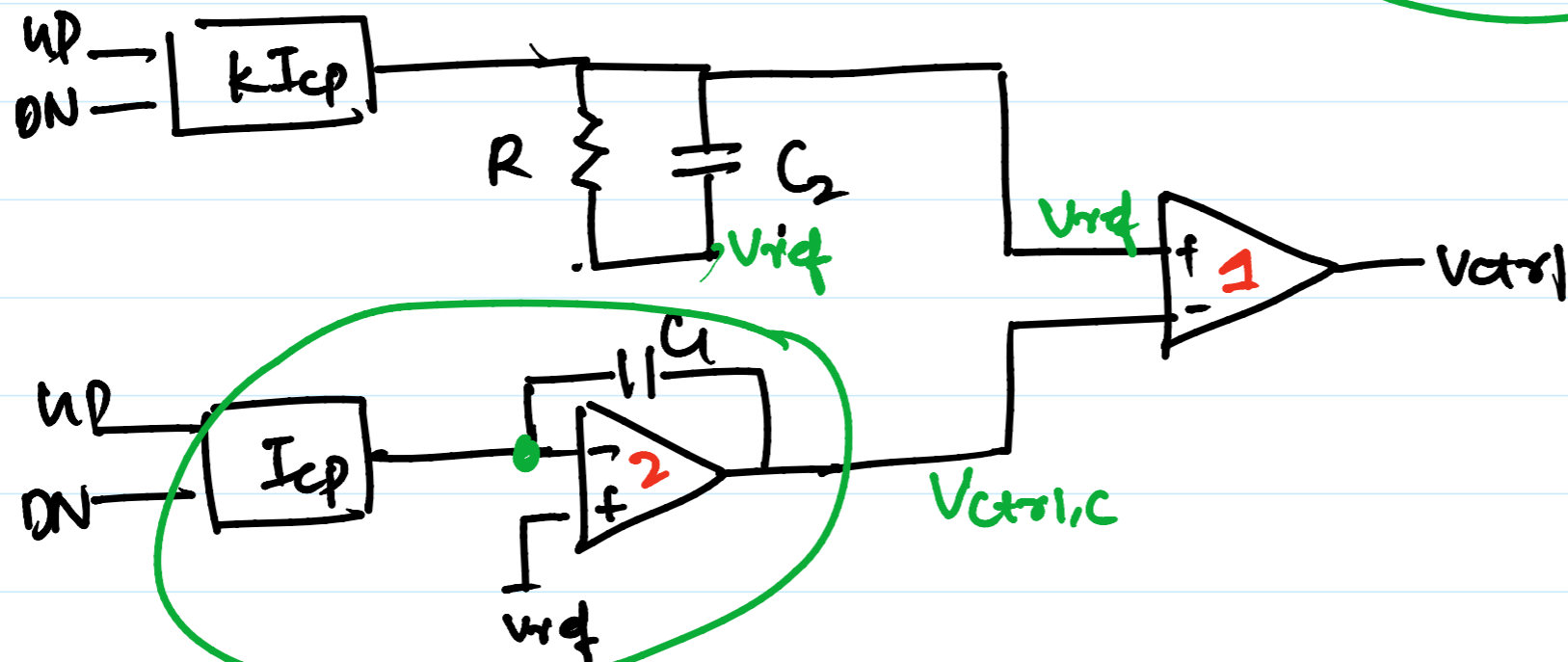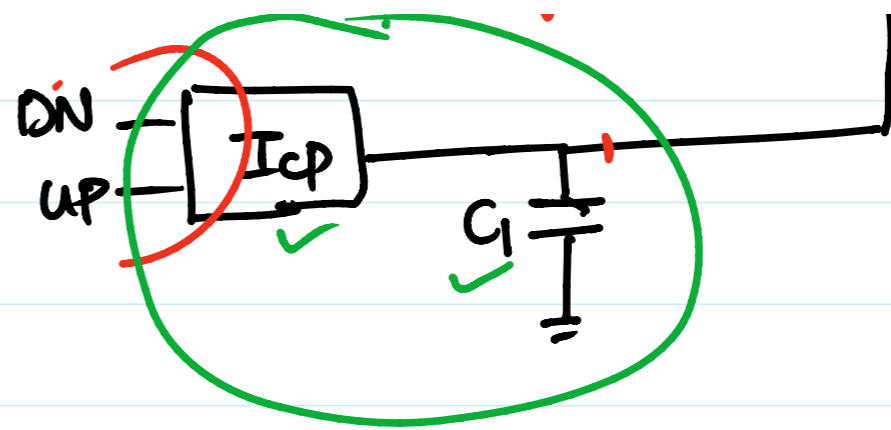
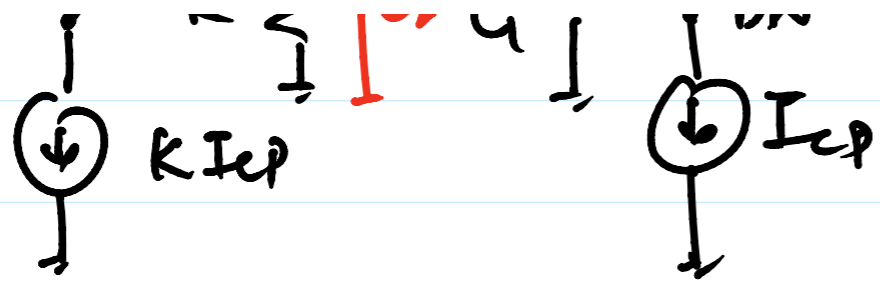


— Two Opamps

Added noise & non-linearity of opamp.

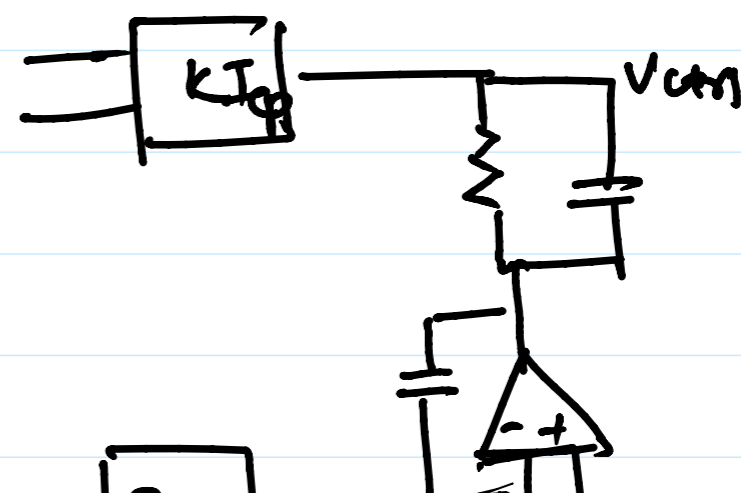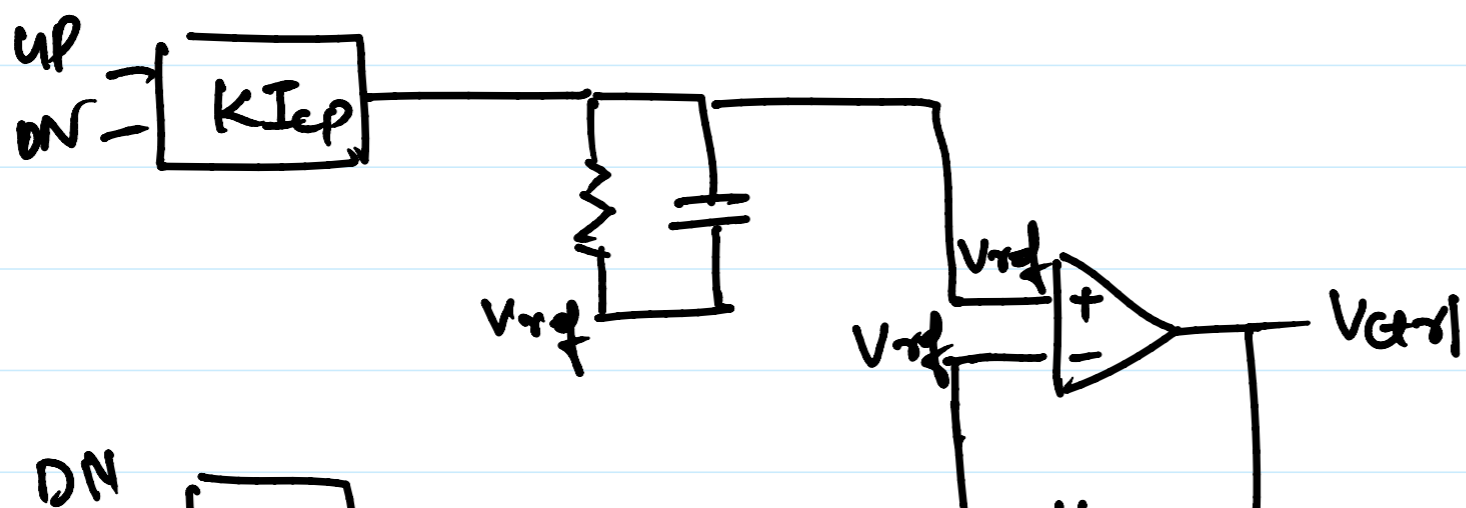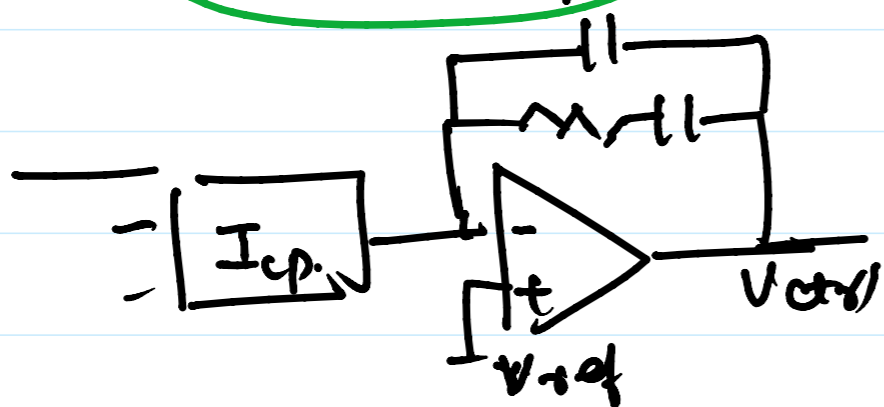— Channel length modulation in CP is negligible (0)



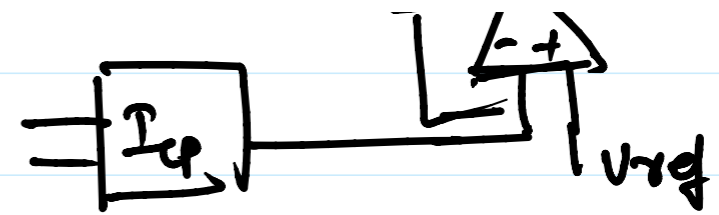
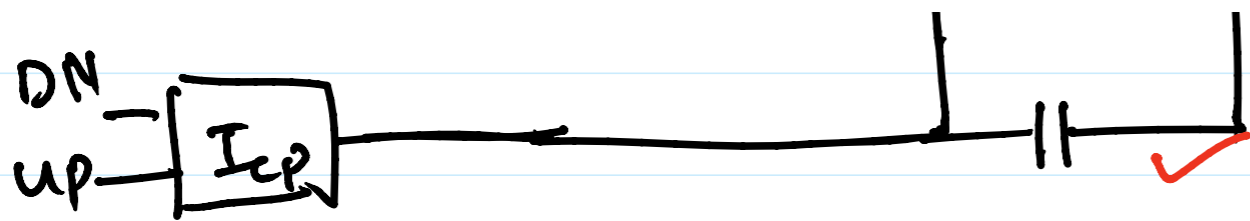



$$V_{ctrl} = K I_{cp} \times \frac{R}{1 + sC_2 R} + I_{cp} \cdot \frac{1}{sC_1}$$

$$= \frac{I_{cp}}{(1 + sC_2 R) sC_1} [sRKC_1 + 1 + sC_2 R]$$

$$= \frac{I_{cp}}{sC_1} \frac{1 + sR(C_2 + KC_1)}{1 + sC_2 R}$$
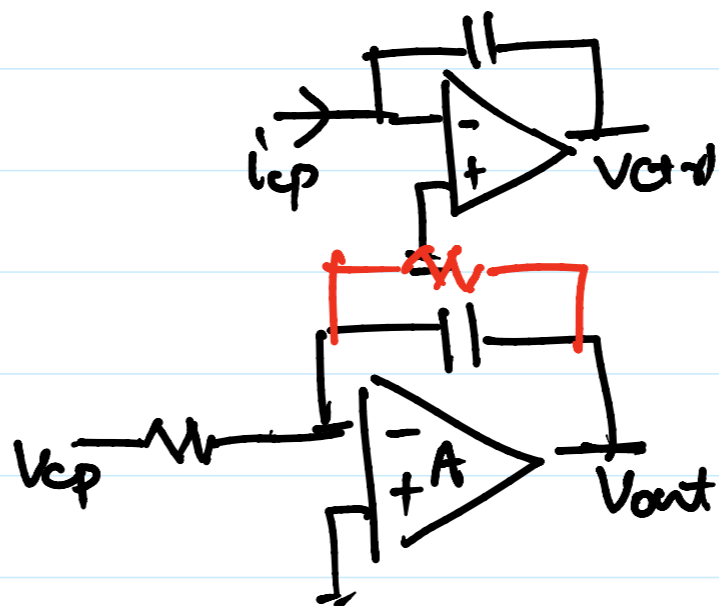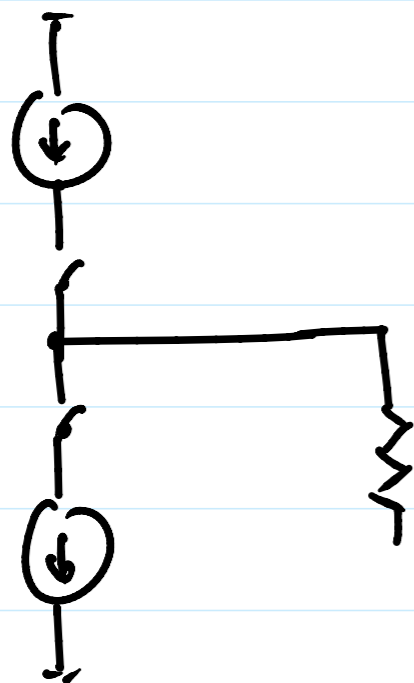
$$\frac{I_{cp}}{sC_1} \frac{(1 + sRC_1)}{(1 + s \frac{RC_1 C_2}{C_1 + C_2})}$$





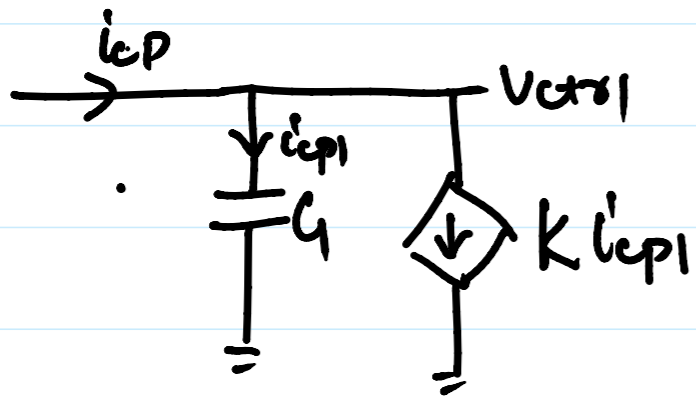

$$i_{cp} = i_{cp1} + k i_{cp1} = (1+k) i_{cp1}$$

$$V_{ctr1} = \frac{i_{cp1}}{sC} = \frac{i_{cp}}{s(1+k)C}$$
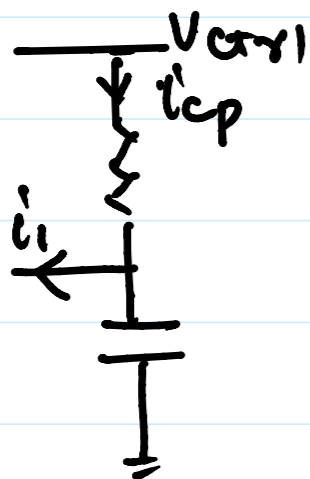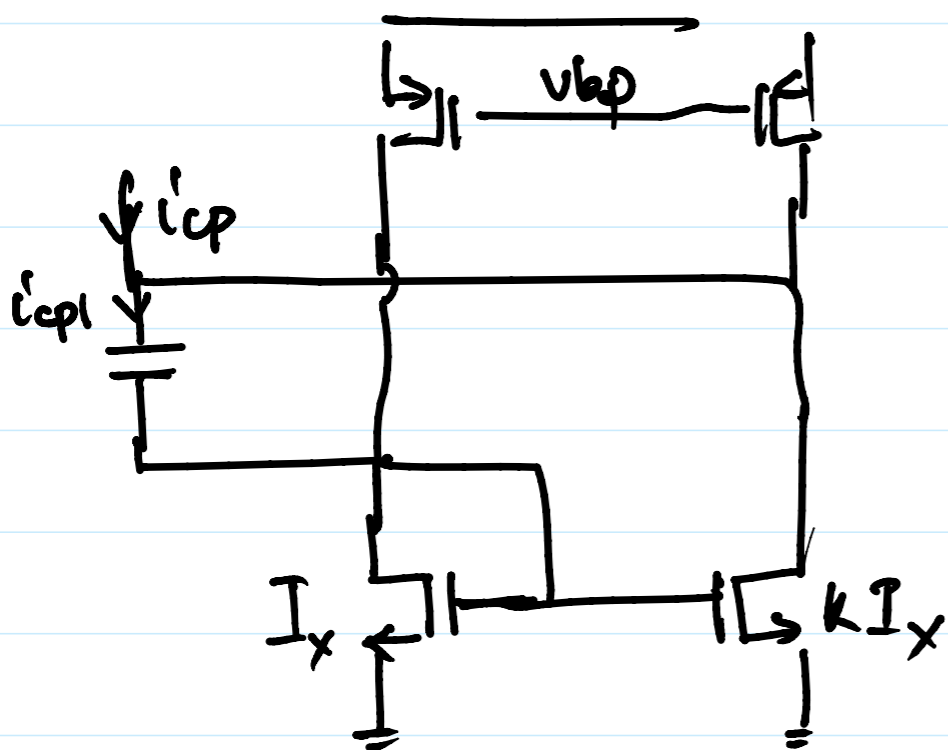
$$\frac{V_{ctr1}}{i_{cp}} = \frac{1}{s(1+k)C}$$




$$V_{ctr1} = i_{cp} R + (i_{cp} - i_o) \frac{1}{sC}$$


$$= \frac{i_{cp}}{sC} \left[sRC + \left(1 - \frac{i_o}{i_{cp}}\right) \right]$$

$$= \frac{i_{cp} \left(1 - \frac{i_o}{i_{cp}}\right)}{sC} \left[1 + \frac{sRC}{1 - \frac{i_o}{i_{cp}}} \right]$$
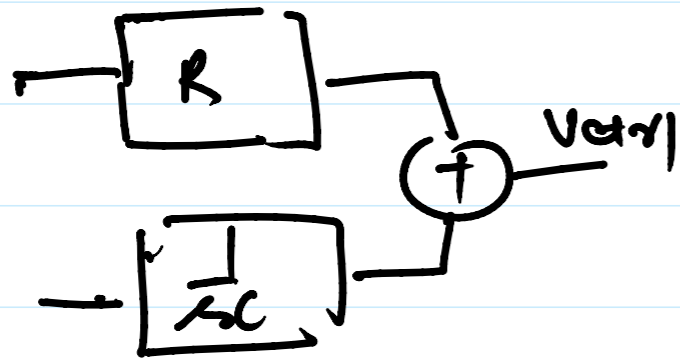
$$\frac{i_{cp}}{sC} \left[1 + \frac{sRC}{\left(1 - \frac{i_1}{i_{cp}}\right)} \right]$$


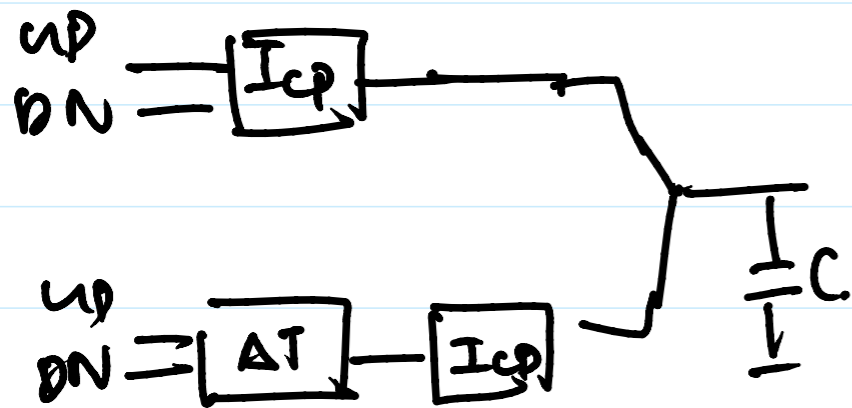
$$\left(R + \frac{1}{sC} \right) i_{cp} = V(s)$$



$$V(s) = I_{cp} \left[1 + e^{-s \cdot \Delta T} \right] \frac{1}{sC}$$

$$= \frac{I_{cp}}{sC} \left[1 + 1 - s \cdot \Delta T \right]$$

$$= \frac{I_{cp} \cdot 2}{sC} \left[1 - \frac{s \cdot \Delta T}{2} \right]$$