
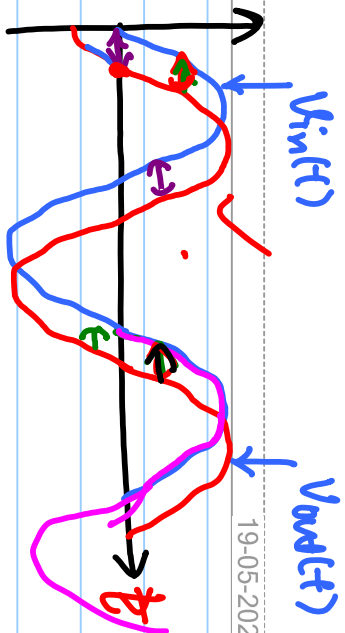


lecture # 3

Oscillator

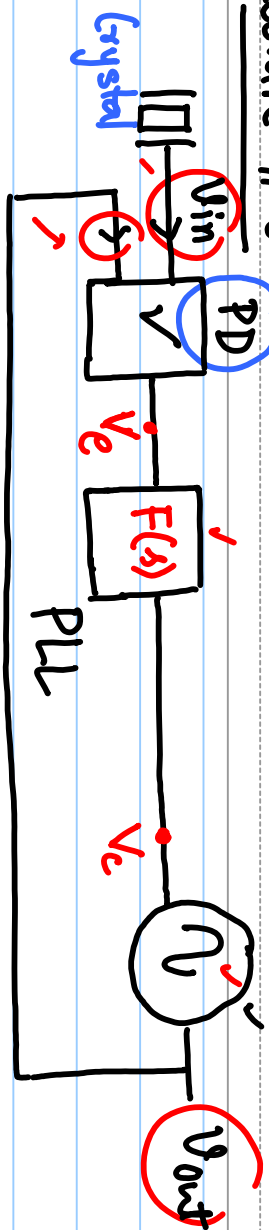

$$V_{in}(t) = A_{in} \sin(\omega_{in} t)$$

$$V_{out}(t) = A_{out} \sin(\omega_{out} t) - \pi/4$$

$$= A_{out} \sin(\omega_0 t + \phi(t))$$

$$\phi_{in}(t) - \phi_{out}(t) = (\omega_{in} - \omega_0)t - \phi(t)$$

$$\phi_{er}(t) = (\omega_{in} - \omega_0)t - \phi(t) = \pi/4$$

Once PLL is locked.

$$\omega_{in} = \omega_{out}$$

$$\frac{d\phi_{er}(t)}{dt} = 0$$

$$\phi_{in}(t) = \int \omega_{in} dt = \omega_{in} t$$

$$\phi_{out}(t) = \int \omega_0 dt + \phi(t) = \omega_0 t + \phi(t)$$

Output of phase detector & $\phi_{er}(t)$

$$[\text{Gain of PD}] = V/\text{rad}$$

$$V_c \text{---} \textcircled{N} \text{---} V_{out} = A_{out} \sin(\omega_{out} t)$$


Control voltage, V_c changes the frequency of osc.

$$\omega_{out}(t) = \omega_{free}^{= \omega_{in}} + K_{vco} \cdot V_c(t)$$

free running freq.

of osc, $V_c = 0$
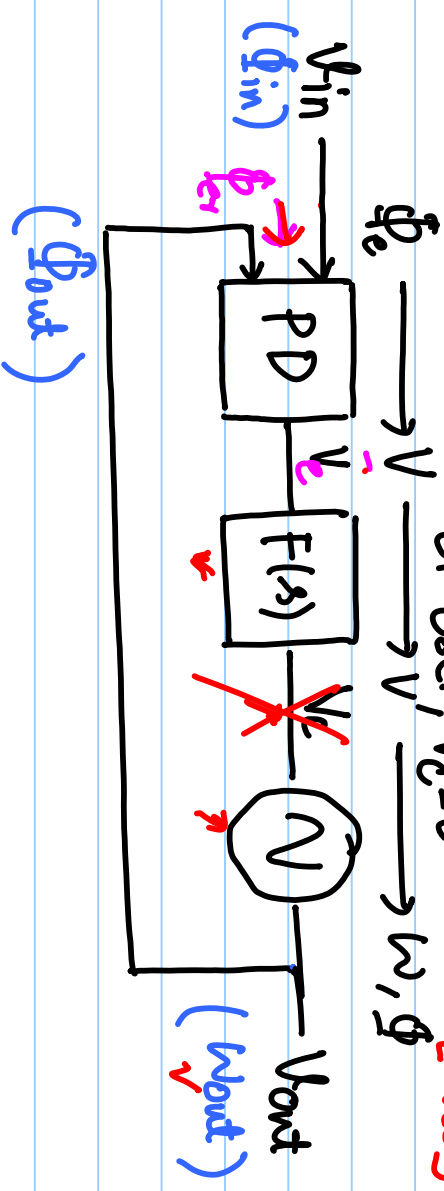
$$[\text{K}_{vco}] = \frac{\text{rad/s}}{\text{V}}$$



Basic Phase Locked Loop

Gain of PD, $K_{PD} = \frac{dV_c}{d\Phi_{in}}$

Gain of osc, $K_{vco} = \frac{d\omega_{out}}{dV_c}$ [rad/s/V]

Loop filter, $\frac{V_c(s)}{V_e(s)} = F(s)$

$$v_{in} = \sin(\omega_{in} t) \checkmark$$

$$v_{out} = \sin(\omega_0 t - \pi/4) = \sin(\omega_{in} t - \pi/4) \checkmark$$

let $t=0$.
 $\omega_{in} = \omega_0$

$$\phi_{ex}(t) = \omega_{in} t - (\omega_{in} t - \pi/4)$$

$$= \pi/4$$

$$\omega_{out}(t) = \omega_{free} + K_{vco} \cdot V_i(t)$$

$$\omega_{out}(t) = \omega_{in} + K_{vco} \cdot \underline{V_c} > \omega_{in}$$


$$= \omega_{in} + K_{vco} \cdot 0 = \omega_{in}$$

$$\checkmark \left. \frac{d\phi_{ex}(t)}{dt} = 0 \right\} \phi_{ex} = 0.$$

$$\checkmark \omega_{out} = \omega_{in}$$

Steady state.


Voltage/Current

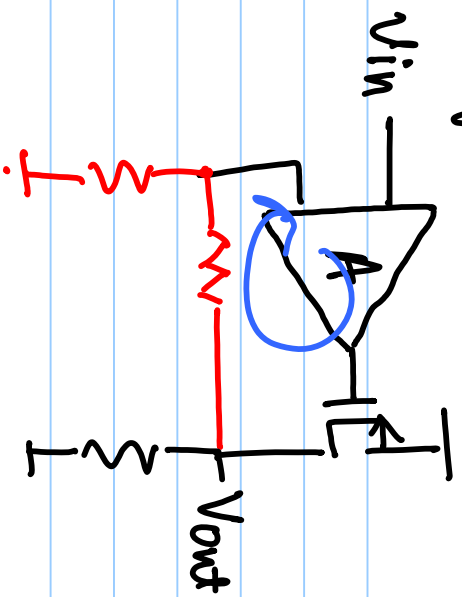

$$V_{out} = V_{in}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = 1$$

Phase / Frequency.

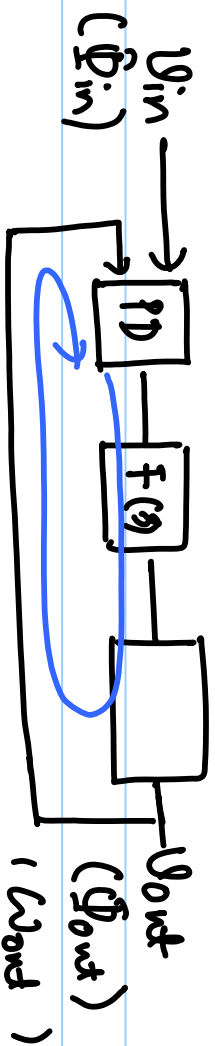


$$\Phi_{out} = \Phi_{in} + K$$

$$M_{out} = N M_{in}, \quad \text{Integer } -N \text{ PLL}$$

$$= (N+K) M_{in}, \quad \text{OR } K < 1$$

$M_{out} = N M_{in}$ \leftarrow Fractional- N PLL.
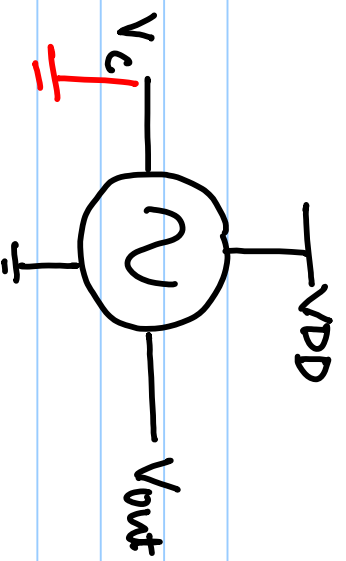
$$H(s) = \frac{\Phi_{out}(s)}{\Phi_{in}(s)}$$




$$V_{out} = \sin(\omega_{free} t + \int K_{vco} \cdot V_c dt)$$


$$\omega_{out}(t) = \omega_{free} + K_{vco} \cdot V_c$$

$$\omega_{out}(t) \Big|_{V_c=0} = \omega_{free}$$

$$\omega_{free} = \omega_{in}$$

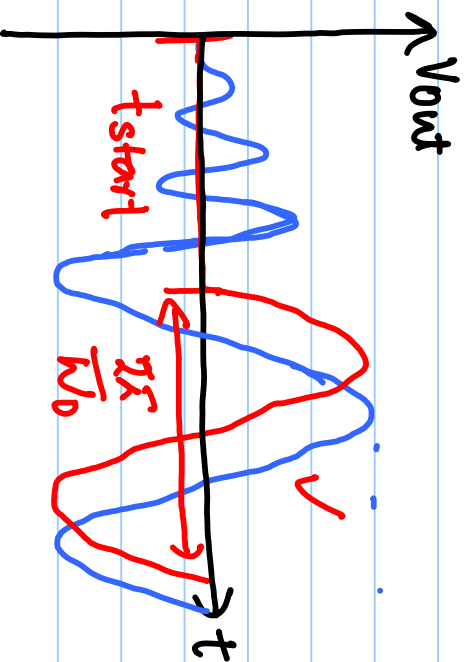

Basic PLL

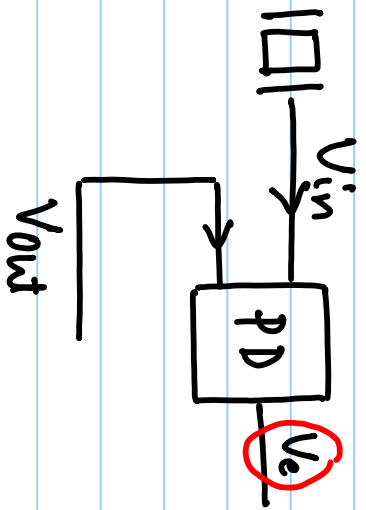


$$V_{in}(t) = A_{in} \sin(\omega_{in} t) \quad \checkmark$$

$$V_{out}(t) = A_{out} \cos(\omega_{free} t + \int K_{VCO} \cdot V_e dt + \phi_{in}(0)) \quad \checkmark$$

$$\phi_{in}(t) = \omega_{in} t \quad \cos(\omega_{free} t)$$

$$\phi_{out}(t) = \omega_{free} t + \int K_{VCO} \cdot V_e dt + \phi_{in}(0)$$
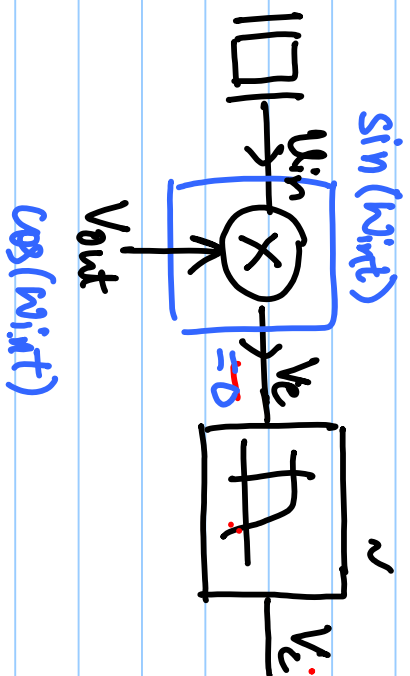
$$V_{in} \times V_{out} = A_{in} \cdot A_{out} \sin(\quad) \cos(\quad)$$




$$2 \sin A \cdot \cos B$$

$$= \sin(A+B) + \sin(A-B)$$

$$= \frac{A_{in} A_{out}}{2} \left[\sin(\underbrace{\omega_{in} + \omega_{free}}_{\text{cos}} t + \int K_{VCO} V_e dt + \phi_{in}(0)) \right. \\ \left. + \sin(\underbrace{\omega_{in} - \omega_{free}}_{\text{cos}} t - \int K_{VCO} V_e dt - \phi_{in}(0)) \right]$$

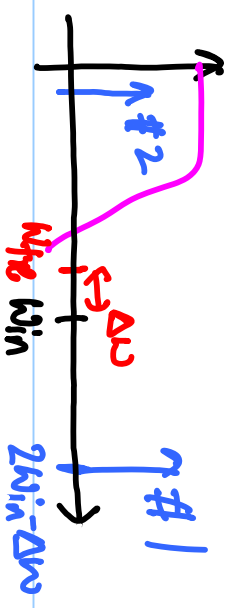For $\omega_{in} - \omega_{free} = \Delta\omega$.




1 : $\frac{A_{in} A_{out} \sin}{2} \left(2\omega_{in} - \Delta\omega t + \int K_{vco} \cdot V_c dt + \phi_{in}(0) \right)$ ✓ Reject

2 : $\frac{A_{in} \cdot A_{out}}{2} \sin \left(\Delta\omega \cdot t - \int K_{vco} \cdot V_c dt - \phi_{in}(0) \right)$ ✓ Retain

$\phi_{in} - \phi_{out} = \Delta\omega \cdot t - \int K_{vco} \cdot V_c dt - \phi_{in}(0)$

$V_c = \frac{A_{in} \cdot A_{out}}{2} \left[\sin(2\omega_{in} - \Delta\omega t + \int K_{vco} \cdot V_c dt + \phi_{in}(0)) + \sin(\Delta\omega \cdot t - \int K_{vco} \cdot V_c dt - \phi_{in}(0)) \right]$ ✗ (Neglect from analysis)

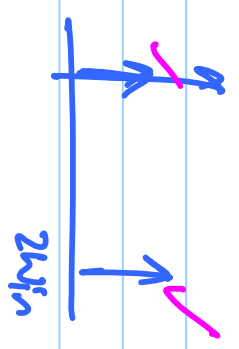
$V_c \approx \frac{A_{in} A_{out}}{2} \sin(\Delta\omega \cdot t - \int K_{vco} \cdot V_c dt - \phi_{in}(0))$ ✓



$V_c = \frac{A_{in} \cdot A_{out}}{2} \sin(\phi_{er}(t))$ ✓

Ideally, $V_c = K_{PD} \phi_{er}$
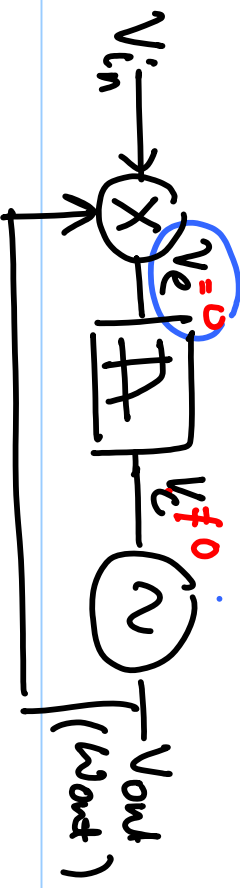
$$V_e = \frac{A_{in} \cdot A_{out}}{2} \sin(\phi_{ex}(t))$$



$$\omega_{out} = \omega_{free} + K_{vco} \cdot V_e$$

at $t=0$ $\Delta\omega=0$, $\phi_{in}(0) = 0$, $\omega_{free} = \omega_{in}$

in steady state or $t \rightarrow \infty$ (dc value)

$$\Rightarrow V_e = 0 \Rightarrow V_e = 0 = () \sin(\phi_{ex})$$

$$\Rightarrow \phi_{ex} = 0$$

Case 2: at $t=0$, $\Delta\omega=0$, $\phi_{in}(0) = -\pi/4$

$$\phi_{ex}(0) = \pi/4$$

In steady state, $V_e = 0 \Rightarrow \sin(\phi_{ex}) = 0 \Rightarrow \phi_{ex} = 0$

Case 3 at $t=0$, $\Delta\omega = 1 \text{ Mrad/s}$, $\phi_{in}(0) = 0$