
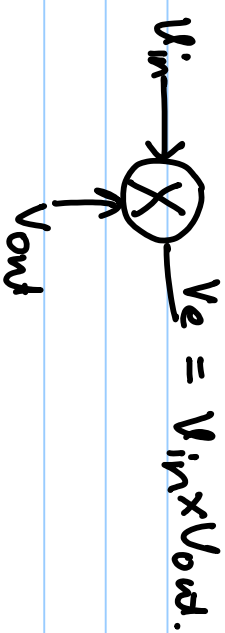


Basic PLL

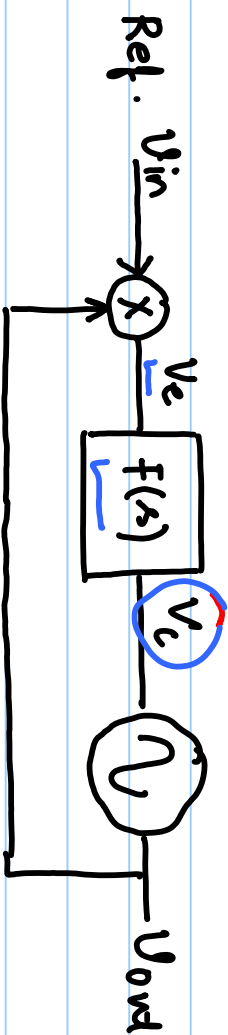

$$V_{in} = A_{in} \sin(\omega_{in} \cdot t)$$

$$V_{out} = A_{out} \cos(\omega_{out} t) = A_{out} \cos(\omega_{free} \cdot t + \int K_{VCO} \cdot V_c dt + \Phi_{out}(0))$$

$$V_e = V_{in} \times V_{out}$$

$$\approx \frac{A_{in} \cdot A_{out}}{2} \sin((\omega_{in} - \omega_{free})t - \int K_{VCO} \cdot V_c dt - \Phi_{out}(0))$$

Case 3: $\omega_{in} - \omega_{free} = \Delta\omega$ $\left| \begin{array}{l} \Delta\omega \text{ is freq. error b/w i/p} \\ \text{freq. and free running freq.} \\ \text{of oscillation} \end{array} \right.$

at $t=0$, $V_e(0) = 0$ so, $\omega_{in} - \omega_{out} = \omega_{in} - \omega_{free} = \Delta\omega$

$$V_e = \frac{A_{in} \cdot A_{out}}{2} \times \sin(\Delta\omega \cdot t - K_{VCO} \int V_c dt) \quad \checkmark \quad \left| \text{let } \Phi_{out}(0) = 0 \right.$$

(or at $t \rightarrow \infty$)


If RL reaches steady state \Rightarrow Finally, $\omega_{out} = \omega_{in}$

$\omega_{free} + K_{vco} \cdot V_c = \omega_{in}$

$\Rightarrow V_c = \frac{\omega_{in} - \omega_{free}}{K_{vco}}$

$V_c = \frac{\Delta\omega}{K_{vco}}$ ✓

$V_c(s) = F(s) \cdot V_e(s)$

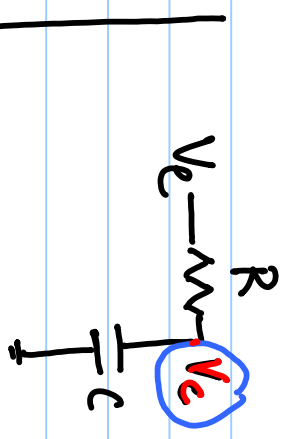

$\frac{V_c}{V_e} = \frac{1}{1+sRC}$

$V_e = V_c$

$\Rightarrow V_c = V_e$

$\frac{\Delta\omega}{K_{vco}} = \frac{A_{in} A_{out}}{2} \sin \left(\Delta\omega \cdot t - \int K_{vco} \cdot V_c \, dt + \Phi_{es} \right)$ ✓

Assume $A_{in} = A_{out} = 1$

$\frac{\Delta\omega}{K_{vco}} = \frac{1}{2} \sin \left((\Delta\omega - K_{vco} \cdot V_c) t + \Phi_{es} \right)$

Φ_{es} : Error in state
steady

$$= \frac{1}{2} \sin(\phi_{es})$$

$$\sin(\phi_{es}) = 2 \cdot \frac{\Delta \omega}{K_{vco}}$$

$$\phi_{es} = \sin^{-1} \left(\frac{2 \cdot \Delta \omega}{K_{vco}} \right)$$

$$V_{out} = \cos(\omega_{out} \cdot t - \phi_{es})$$

$\omega_{in} \downarrow$

at $t=0$

$$V_c = \frac{1}{2} \sin(\Delta \omega \cdot t - \int K_{vco} V_c \cdot dt)$$

$V_c = 0$


$$V_c \approx V_e$$



$$\omega_{out} = \omega_{tra} + K_{vco} \cdot V_c$$

$$= \omega_{tra} + K_{vco} \cdot \frac{1}{2} \sin(\Delta \omega \cdot t)$$

$$V_{out} = \cos(\omega_{tra} + \frac{K_{vco}}{2} \sin(\Delta \omega \cdot t))$$
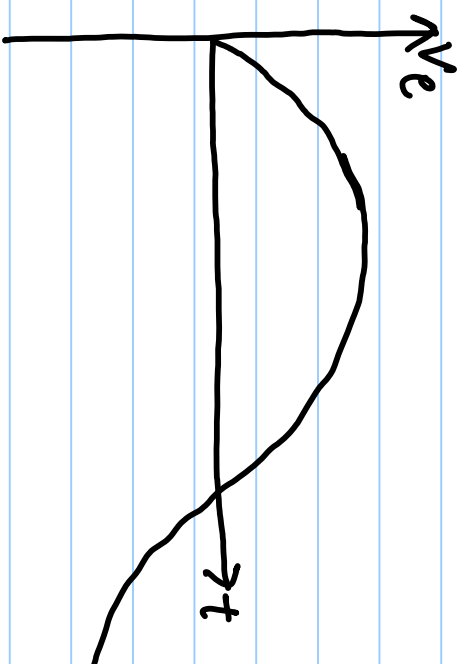
$$\phi_e(t) = (\omega_{in} - \omega_{tra}) t - \int K_{vco} V_c \cdot dt \quad (\text{integral})$$



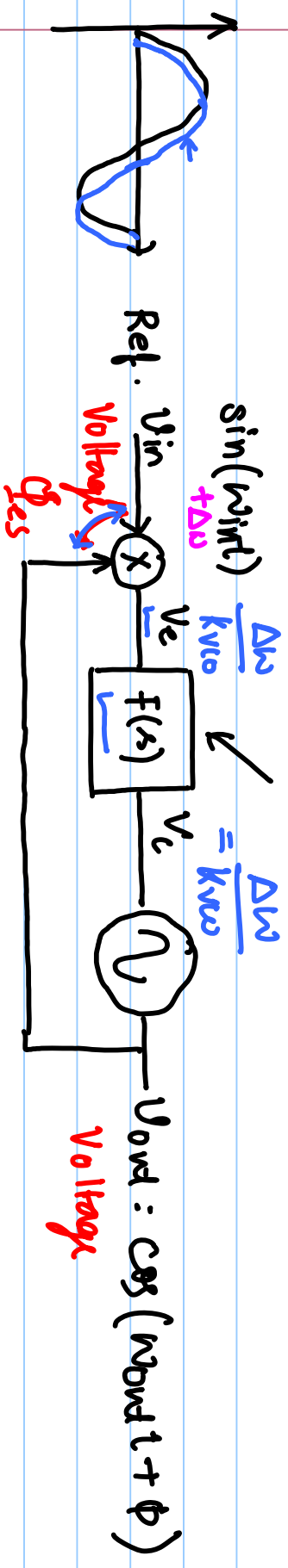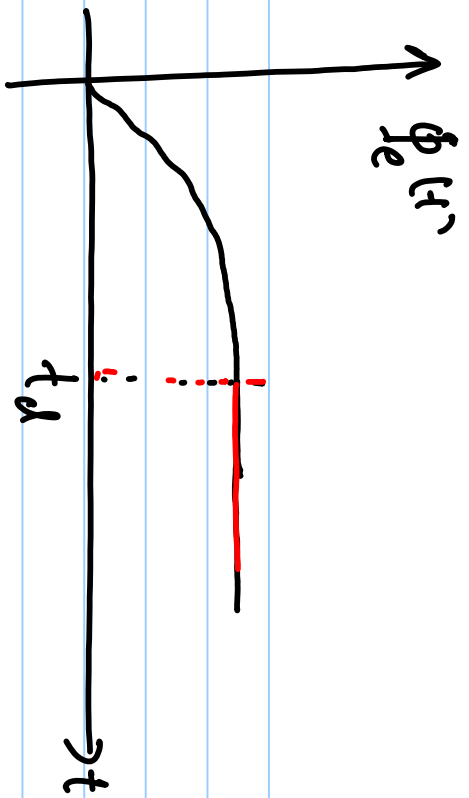

ω_{in} : i/p freq.

ω_{free} : free running freq. osc.



K_{vco} : gain of osc

$$F(s) = \frac{1}{1 + sRC} \quad \checkmark$$

In steady state : $V_e = \frac{\Delta \omega}{K_{vco}}$

$$\frac{1}{2} \sin(\Phi_{es}) = \frac{\Delta \omega}{K_{vco}}$$

$$\hat{\Phi}_{es} = \sin^{-1} \left(\frac{2 \cdot \Delta v_o}{K_{vco}} \right) + \Delta \hat{\Phi}_e \quad \left| \quad v_c = \frac{\Delta \omega}{K_{vco}} + \Delta v_c \right.$$

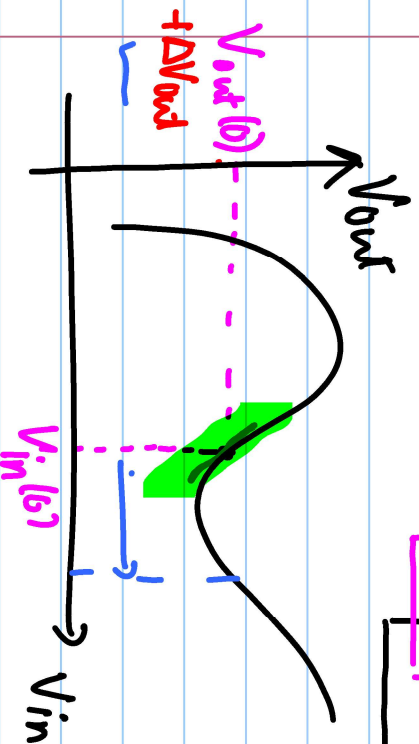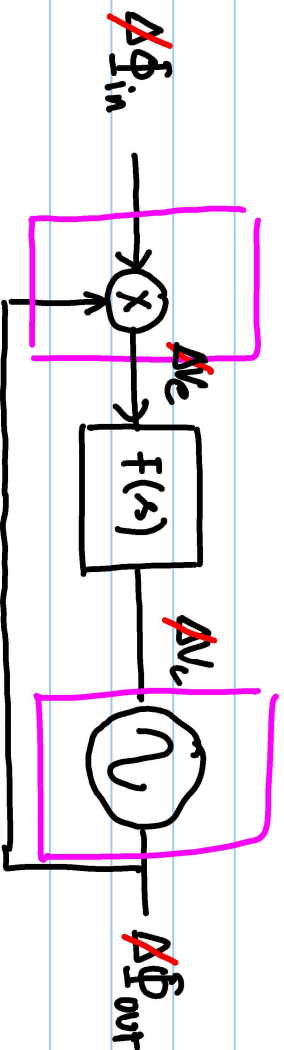

$$v_{out} = f(v_{in})$$

$$\Delta v_{out} = f'(v_{in}) \Big|_{v_{in}=v_{in}(t)} \times \Delta v_{in}$$

$$v_{out} = v_{out}(t) + \Delta v_{out}$$

$$v_{in} = \sin(w_{int}), \quad v_{out} = \cos(w_{out} t + \Phi_{es})$$

$$v_c = \frac{1}{2} \left[\sin(2w_{in} t + \hat{\Phi}_{es}) + \sin(\hat{\Phi}_{es}) \right]$$

$$\underline{V}_c = \frac{1}{2} \sin(\underline{\Phi}_{cs}) \quad \left\{ \begin{array}{l} \text{Changing} \\ \text{Not changing} \end{array} \right.$$

$$-R_{\text{eff}} \underline{V}_c \quad \left\{ \begin{array}{l} \text{Changing!} \\ \text{Not changing} \end{array} \right.$$



$$W_{\text{out}} = W_{\text{free}} + K_{\text{vco}} \cdot V_c$$

$$\underline{\Phi} = \int \omega \cdot dt$$

$$= \int_0^{t_1} \omega_1 dt + \int_{t_1}^{t_2} \omega_2 dt + \dots + \int_{t_n}^{\infty} \omega_n dt$$

$$= \underline{\Phi}_{\text{os}} + \dots$$

$t \gg t_n$

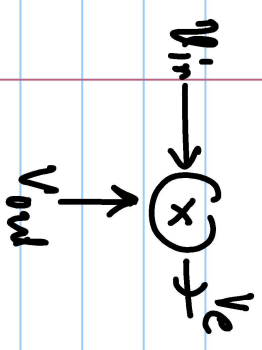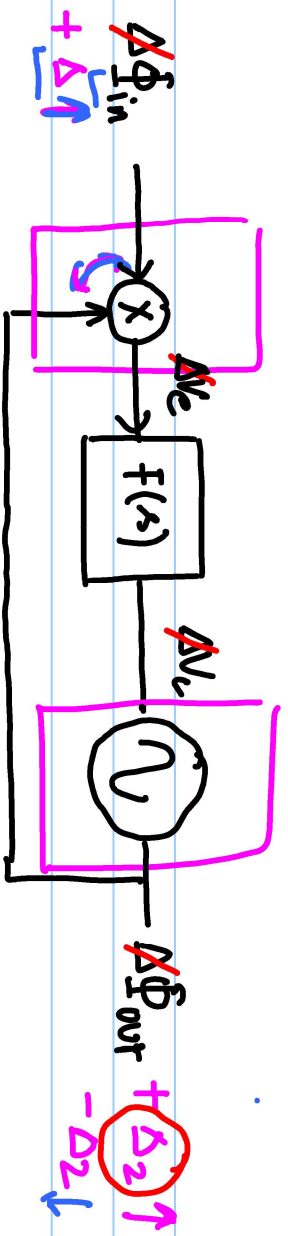

$$V_e \approx \frac{A_{in} \cdot A_{out}}{2} \sin \left(\underbrace{\Delta \omega \cdot t - K_{VCO} \cdot V_c \cdot dt}_{=0} + \Phi_{es} \right)$$


$$\approx \frac{A_{in} \cdot A_{out}}{2} \sin(\Phi_{es}) \quad \left| \begin{array}{l} \Phi_{es} = \Phi_{in} - \Phi_{out} \end{array} \right.$$


$$V_c + \Delta V_c = \frac{A_{in} \cdot A_{out}}{2} \sin(\Phi_{es} + \Delta \Phi_{es})$$

$$K_{PD} = \frac{dV_c}{d\Phi_{es}} = \frac{A_{in} \cdot A_{out}}{2} \cos(\Phi_{es})$$

$$\Delta V_c = K_{PD} \cdot \Delta \Phi_{es}$$

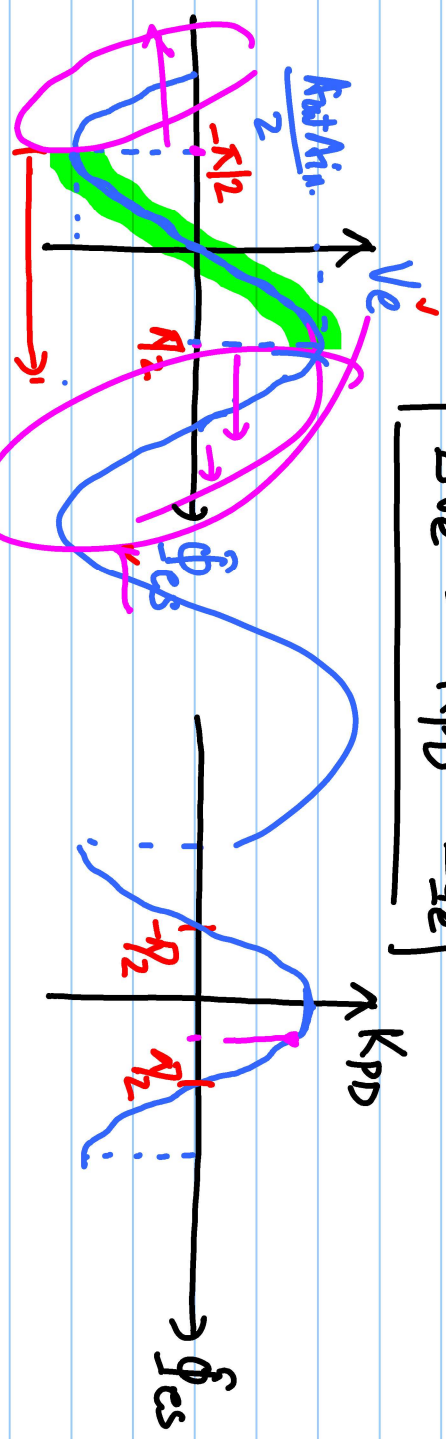
Gain of Phase Detector.
 $[K_{PD}] = V/\text{rad.}$



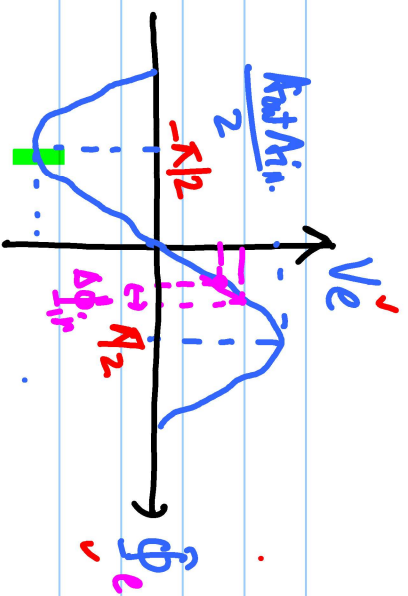


$$\phi_{in} - \phi_{out} = \phi_{es}$$
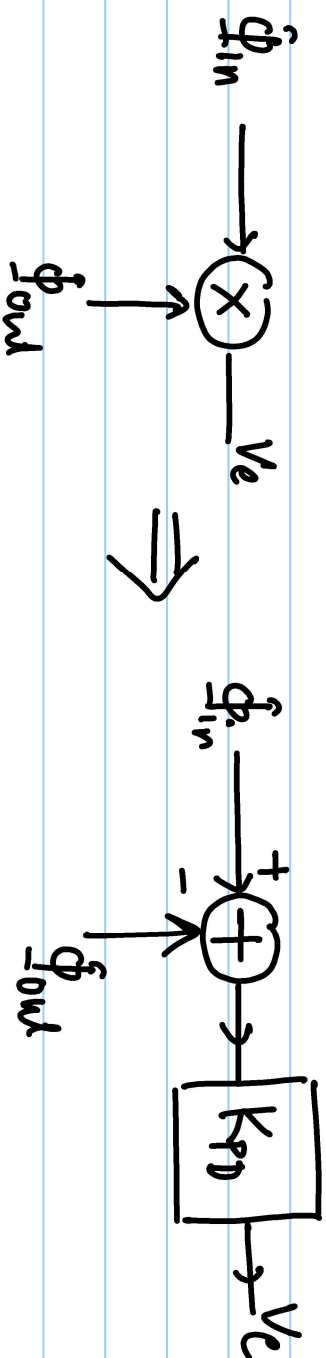
$$\phi_e = (\phi_{in} + \Delta\phi_{in} - \phi_{out}) = \phi_{es} + \Delta\phi_{in}$$




Non-linear

linear.

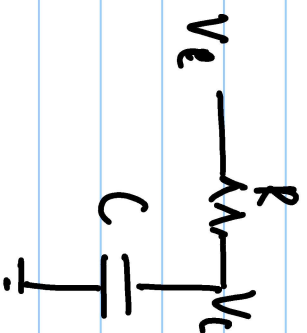

$$\frac{V_c}{V_e} = \frac{1}{sRC + 1}$$

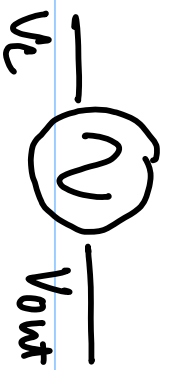$\frac{V_c}{V_e} =$ linear transfer function.



$$V_{out} = \omega_{free} (\omega_{free} \cdot t + \int K_{vco} \cdot V_c \cdot dt)$$

$$\Phi_{out} = \int \omega_{free} + K_{vco} \cdot V_c \cdot dt = \int \omega_{out} \cdot dt$$

$$\Phi_{out} + \Delta \Phi_{out} = \int \omega_{free} + K_{vco} (V_c + \Delta V_c) \cdot dt$$

$$= \int \omega_{free} + K_{vco} \cdot V_c \cdot dt + K_{vco} \int \Delta V_c \cdot dt$$

$$\Delta \Phi_{out} = K_{vco} \int \Delta V_c \cdot dt$$

$$\frac{\Delta \Phi_{out}(s)}{\Delta V_c(s)} = \frac{K_{vco}}{s}$$

