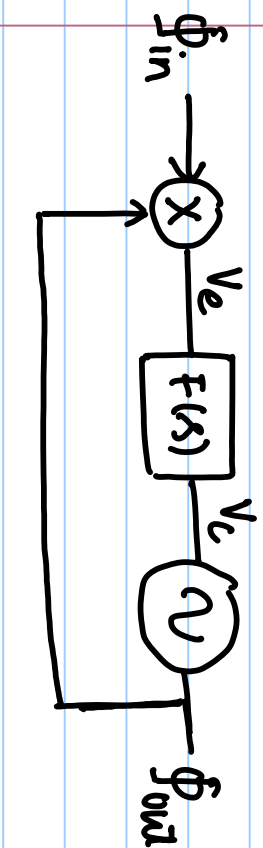


Frequency Acquisition in PLLs



Input freq. ω_{in}

Output freq. $\omega_{out} = \omega_{free}$ at $t=0$.

$\Delta\omega = \omega_{in} - \omega_{free}$

$$F(s) = \frac{1}{1 + s/\omega_p} \cdot \frac{1}{1 + sRC}$$


$\Delta\omega_L \leq K_{VCO} \cdot K_{PD}$

$\dot{\Phi}_e = 0 = \Delta\omega - K_{VCO} \cdot K_{PD} \sin(\Phi_e)$

$\Delta\omega_p \leq K_{VCO} \cdot K_{PD}$

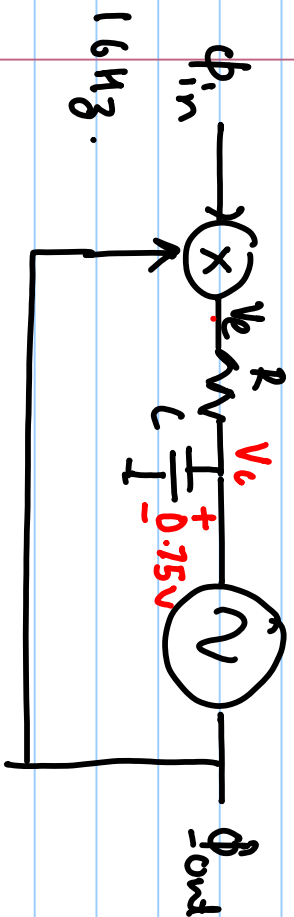1. Lock-in range: $\Delta\omega_L$
w/o cycle slipping
w/o Φ_e exceeding 2π .
2. Pull-in range: $\Delta\omega_p$
w/ or w/o cycle slipping.
3. Hold-in range: $\Delta\omega_H$

✓ $\Delta \omega_H$: max. ($\omega_{in} - \omega_{free}$)



$$\omega_{out} = \omega_{free} + K_{VCO} \cdot V_c$$

$$1.06 \text{ MHz} = 0.925 \text{ MHz} + K_{VCO} \cdot V_c$$

$$V_c = \frac{75 \text{ MHz}}{100 \text{ MHz/V}} = 0.75 \text{ V}$$


$$K_{PD} = 1/2$$

$$\Delta \omega_L = \Delta \omega_P = \underline{150 \text{ MHz}} = \Delta \omega_H$$

$$V_c = \underline{V_c} = \frac{1}{2} \sin(\phi_e) \leq \frac{1}{2}$$

$$V_c = 0.75$$

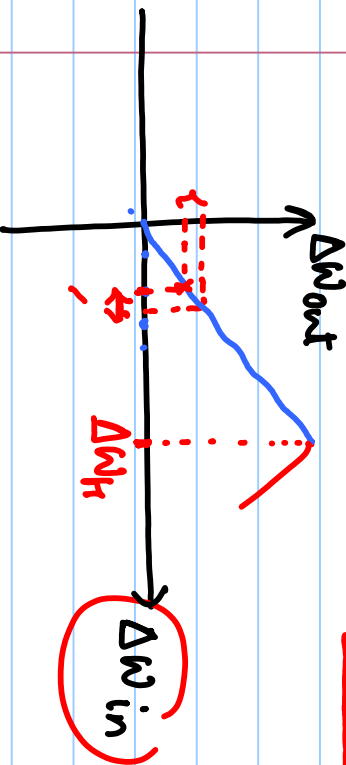
$$\omega_{free} = 925 \text{ MHz} \rightarrow \Delta \omega = \underline{75 \text{ MHz}}$$




$$\Delta \omega_{in} = \omega_{in} - \omega_{in(0)}$$

$$\Delta \omega_{out} = \omega_{out} - \omega_{out(0)}$$

$$\omega_{in(0)} = \omega_{out(0)}$$

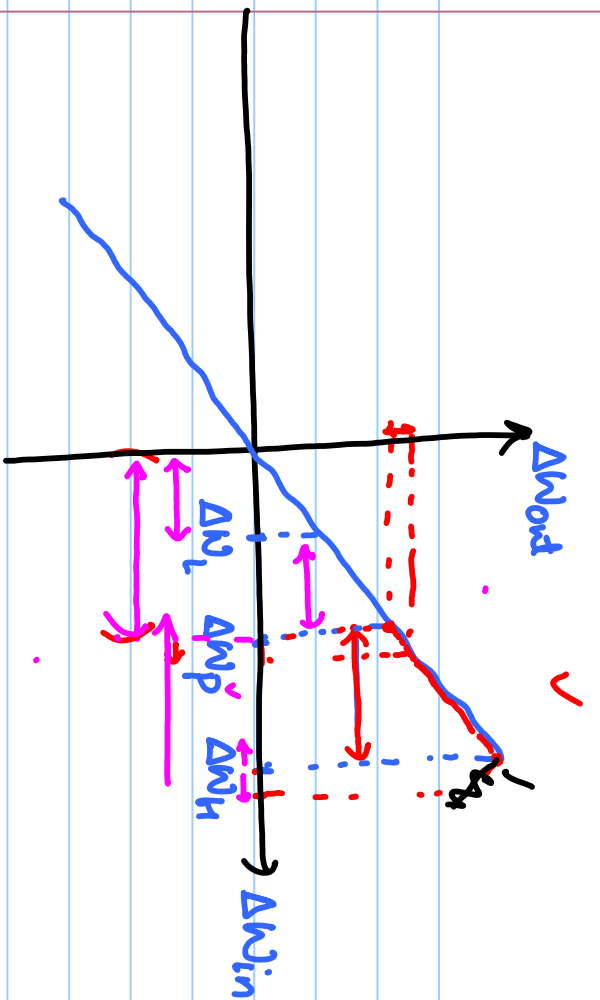

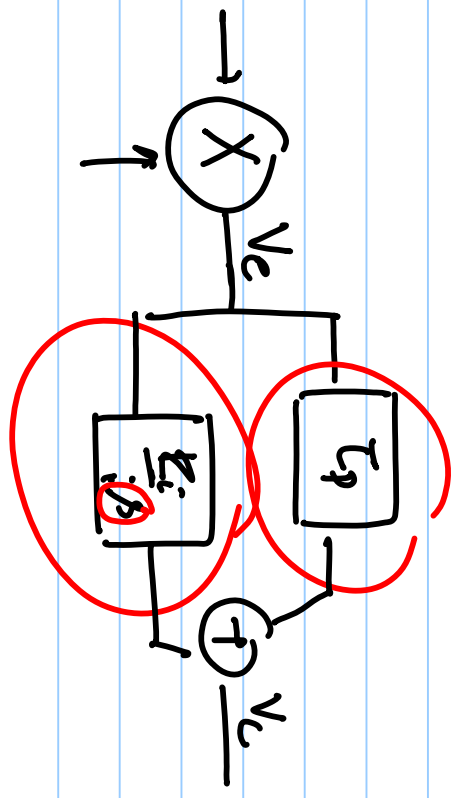
$$\Delta V_H \gg \Delta V_P \approx \Delta V_L$$




Snapshots #1. ΔV_P , $V_i = 0.5V$

Snapshots #2. $V_i = 0.6V$

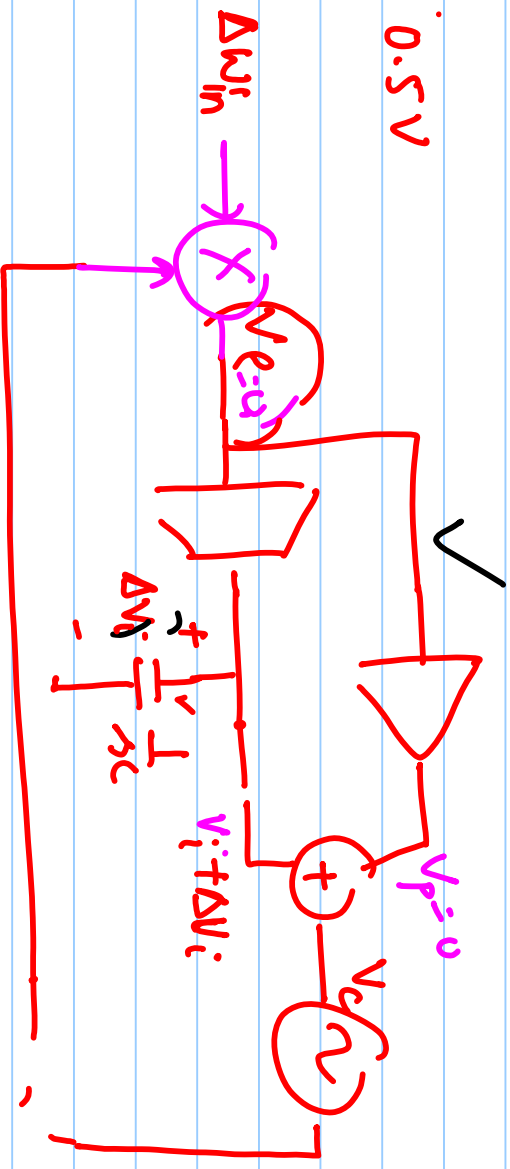

Type-II PLL

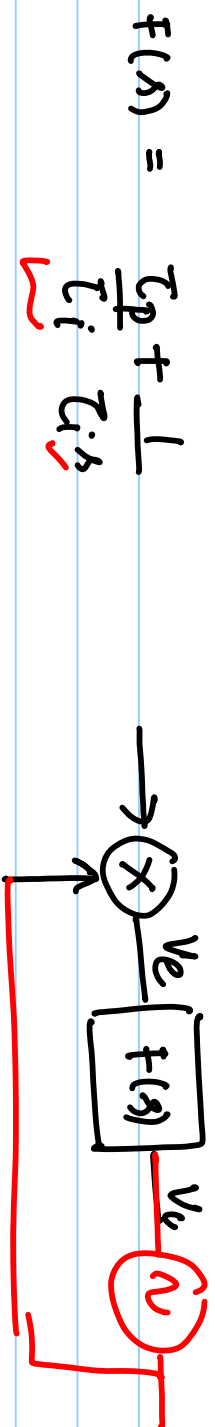

$$F(s) = \frac{T_p + \frac{1}{T_i}}{T_i s}$$

$$V_c(t) = \frac{T_p}{T_i} V_e(t) + \frac{1}{T_i} \int V_e dt$$

$$\begin{aligned} \omega_{out}(t) &= \omega_{free} + K_{VCO} \cdot V_c \\ &= \omega_{free} + K_{VCO} \frac{T_p}{T_i} V_e(t) + \frac{K_{VCO}}{T_i} \int V_e dt \end{aligned}$$

$$V_e = \frac{1}{2} \sin(\Phi_e)$$



$$\Phi_e(t) = \omega_{in} \cdot t - \int \omega_{out} dt$$

$$\begin{aligned} &= (\omega_{in} - \omega_{free}) t - K_{VCO} \frac{T_p}{T_i} \int_0^t \frac{1}{2} \sin(\Phi_e) \cdot dt - \int_0^t \frac{K_{VCO}}{T_i} \int_0^y \frac{1}{2} \sin(\Phi_e) dy \\ &= \underbrace{\Delta\omega(0)} \cdot t - K_{VCO} \cdot \frac{T_p}{T_i} \cdot \frac{1}{2} \int_0^t \sin(\Phi_e) dt - \frac{K_{VCO}}{T_i} \cdot \frac{1}{2} \int_0^t dt \int_0^y \sin(\Phi_e) dy \end{aligned}$$

$$\frac{d\Phi_e(t)}{dt} = 0 \Rightarrow \Phi_e = \Delta\omega(0) - K_{vco} \cdot \frac{C_p}{C_i} \frac{1}{2} \sin(\Phi_e) - \frac{K_{vco}}{C_i} \frac{1}{2} \int_0^t \sin(\Phi_e) dy.$$

$$\Phi_e' = 0$$
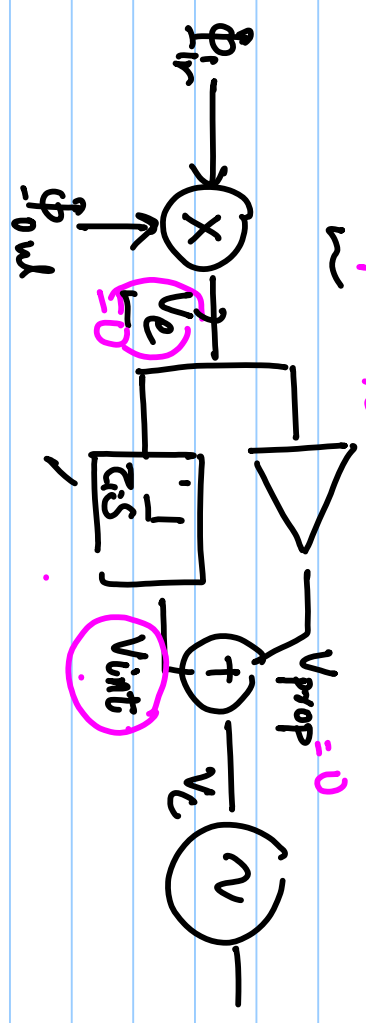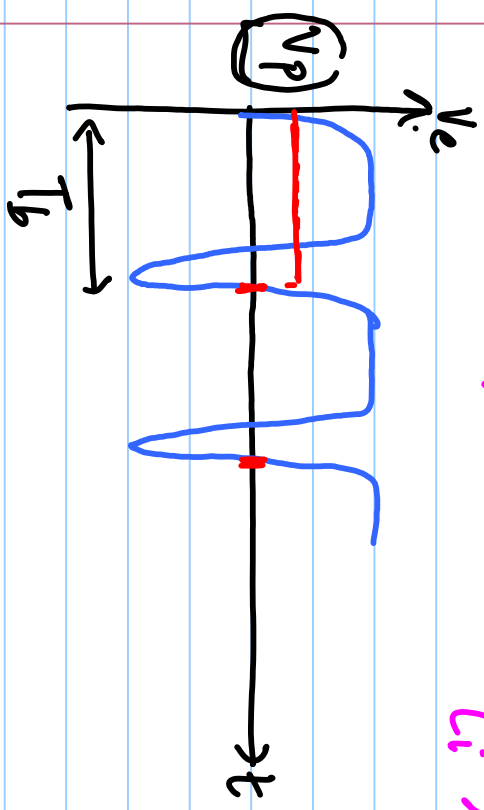
$$\Delta\omega_{in} \leq K_{vco} \cdot \frac{C_p}{C_i} \frac{1}{2} = K_{vco} \cdot K_p \cdot K_{pd}$$



$$\omega_{out} = \omega_{free} + K_{vco} \cdot V_{int}$$

Assume \$V_{int}\$ remains constant for 1-beat period

$$\Delta\omega = \omega_{in} - \omega_{out}$$


$$= \Delta\omega(0) - K_{vco} \cdot V_{int}$$

$$\Delta \Omega = \Delta \Omega(0) - K_{VIO} \cdot \frac{1}{T_i} \int_0^t V_e dt \quad \checkmark$$


$$\checkmark V_p = K_{PD} \left[\frac{\Delta \Omega}{K} - \sqrt{\left(\frac{\Delta \Omega}{K}\right)^2 - 1} \right]$$

$$K = K_{VIO} \cdot K_{PD} F(\omega)$$

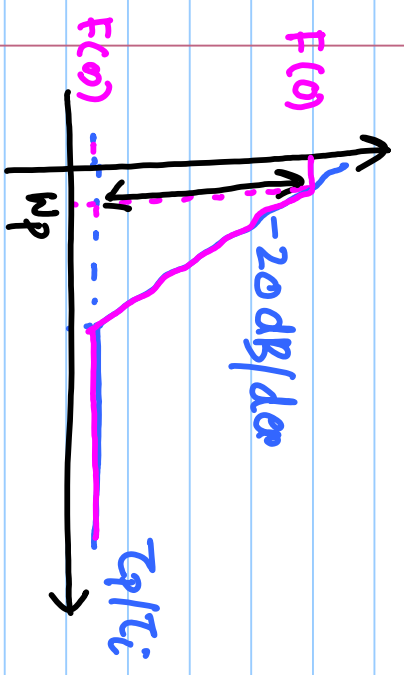✓ $\Delta \Omega = \Delta \Omega - K_{VIO} \cdot V_{int} = 0$


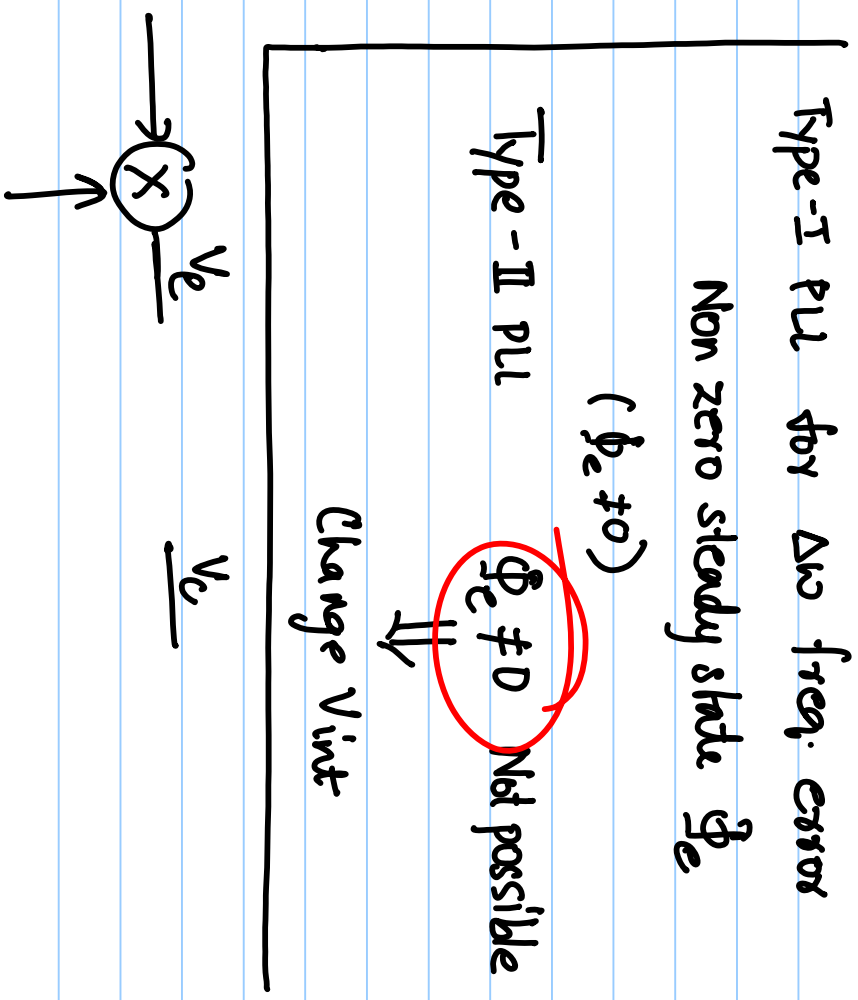
$$F(s) = \frac{T_p}{T_i} + \frac{1}{s T_i}$$



$$V_c(s) = F(\omega) V_e(s) + \frac{F(0)}{1 + s/\omega_p} V_e(s)$$

Integral path gain = $F(0) - F(\omega)$

$$\checkmark \Delta\Omega = \Delta\omega - K_{VCO} (F(0) - F(\omega)) V_p \checkmark$$

$$\left[\Delta\omega = \Delta\omega - K_{VCO} (F(0) - F(\omega)) K_{PD} \left[\frac{\Delta\omega}{K} - \sqrt{\left(\frac{\Delta\Omega}{K}\right)^2 - 1} \right] \right] \checkmark$$

if PLL locks, above eq. should have complex solution.


Roots are complex. if $\Delta\omega < K \sqrt{\frac{2K_{dc}}{K} - 1}$

$$K_{dc} = K_{VCO} K_{PD} F(0)$$

$$K = K_{VCO} \cdot K_{PD} F(\omega)$$

$$\Delta\omega_p < K_{VCO} \cdot K_{PD} F(\omega) \sqrt{\frac{2F(0)}{F(\omega)} - 1}$$

Hold in range.

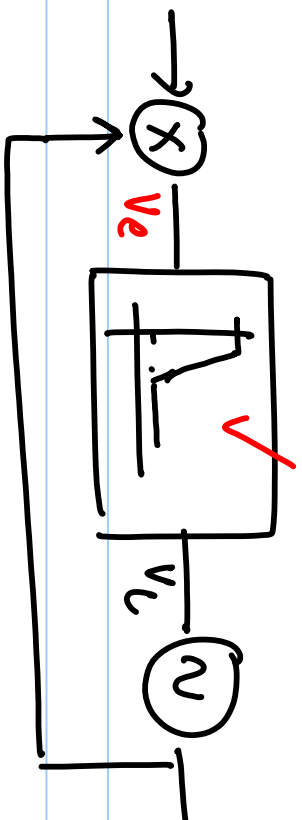

$$V_c = \frac{\Delta \omega_H}{K_{vco}} \checkmark$$

$$V_e = \frac{V_c}{F(10)} = \frac{1}{2} \sin(\Phi_e)$$

$$\sin(\Phi_e) : \frac{2V_c}{F(10)} < 1$$

$$\Rightarrow \frac{2 \Delta \omega_H}{K_{vco} \cdot F(10)} < 1$$

$$\Delta \omega_H < K_{vco} \cdot F(10) \cdot \frac{1}{2}$$

$$\Delta \omega_H < K_{vco} \cdot F(10) K_{pp}$$

$$\Delta \omega_H < K_{vco} \cdot K_{pp} F(10)$$

$$\Delta \omega_p < K_{vco} K_{pp} F(10)$$

$$\sqrt{\frac{F(10)}{F(10)} - 1}$$

$$\Delta \omega_p < K_{vco} K_{pp} \sqrt{F(10) F(10)} < F(10)$$