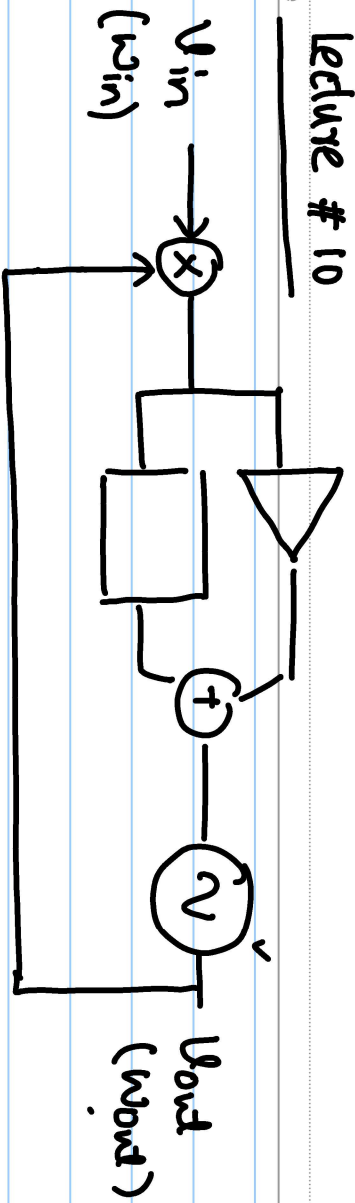




Lecture # 10



$\omega_{out} = \omega_{in}$




$M_{out} = N \omega_{in}$


$M_{out} = 5 \omega_{in}$

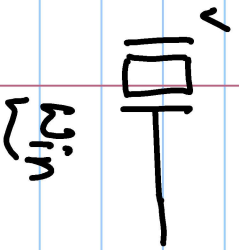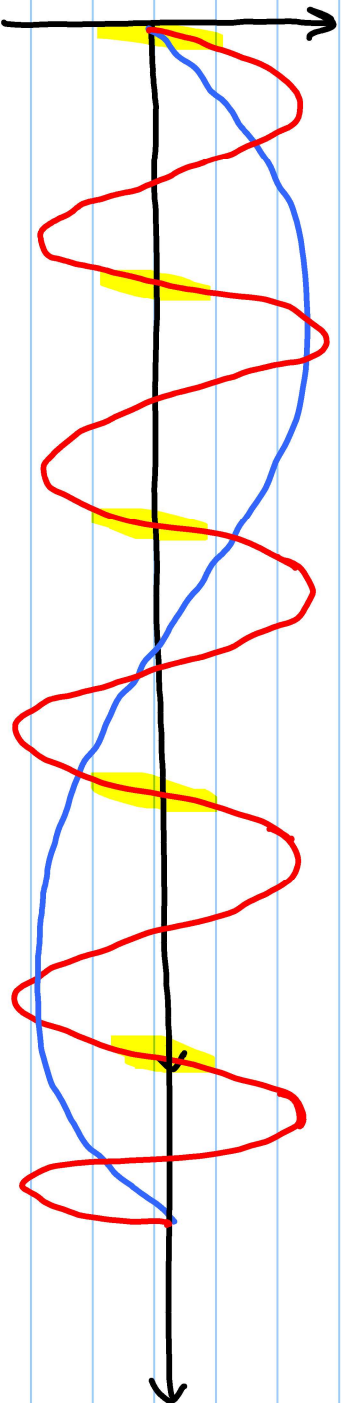


$V_{avg} = 1.0V$

of phases

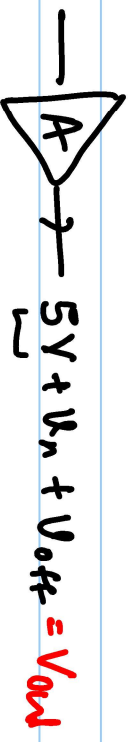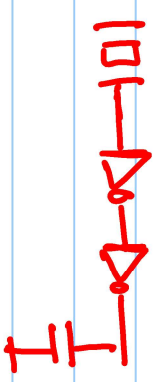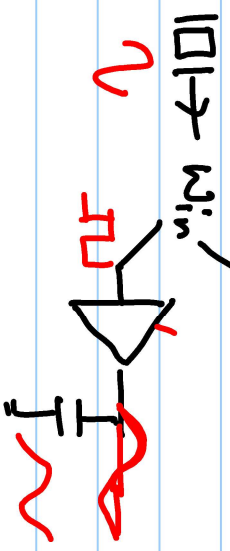

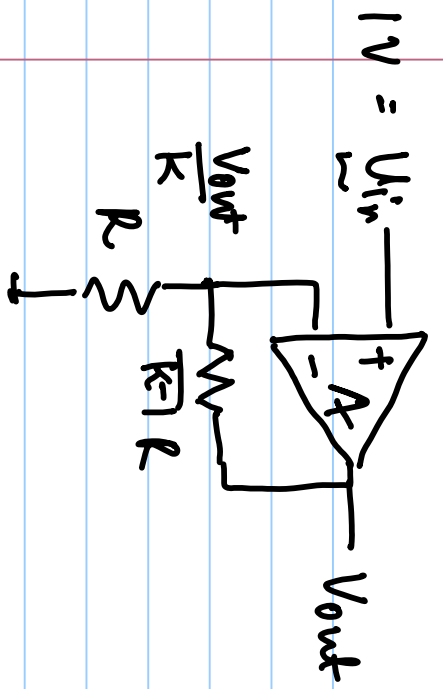

$$\frac{V_{out}}{K} = V_{in}$$

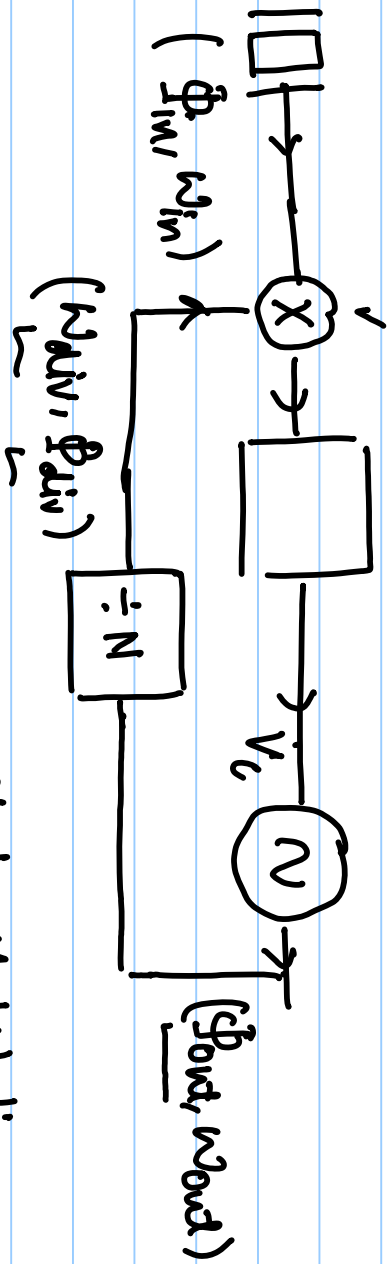

$$w_{out} = 5 w_{in}.$$

Clock-Multiplier.

$$V_{in} = \sin(w_{in} \cdot t)$$

$$\Phi_{in}(t) = w_{in} \cdot t$$

$$V_{out} = \sin(w_{out} \cdot t)$$

$$\Phi_{out} = w_{out} \cdot t$$

$$\Phi_{out} = 5 w_{in} \cdot t$$

$$w_{div} = \frac{w_{out}}{N}$$

$$\Phi_{div} = w_{div} \cdot t$$


$$= \frac{w_{out} \cdot t}{N}$$

$$= \frac{\Phi_{out}}{N}$$



$$w_{div} = w_{in} = \frac{w_{out}}{N}$$

$$\frac{d}{dt} (\Phi_{in} - \Phi_{div}) = 0$$


$$\Rightarrow$$

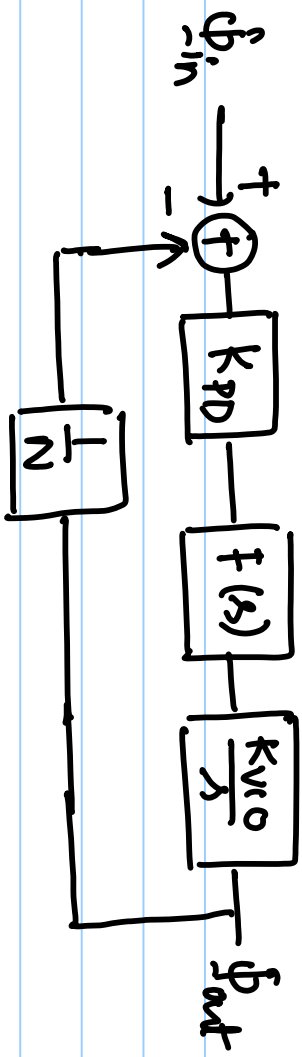
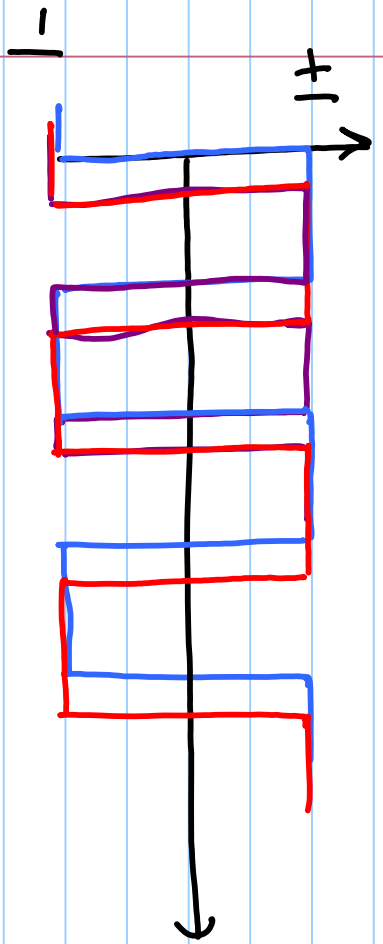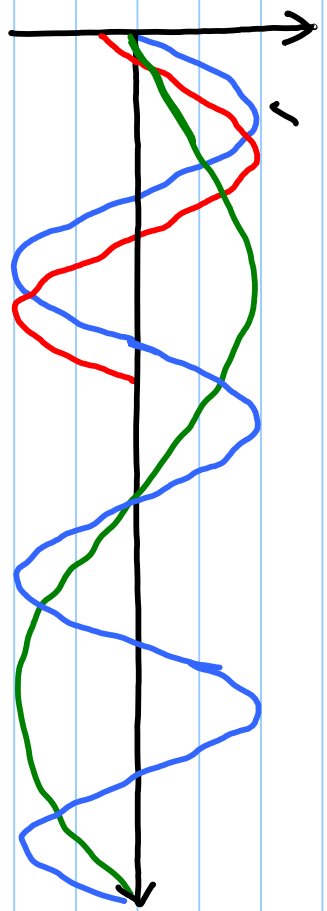
$$K_{Lu} = K_{PD} \cdot F(s) \cdot \frac{K_{VCO}}{s} \cdot \frac{1}{N}$$




$$\Delta\omega_p \rightarrow \infty$$

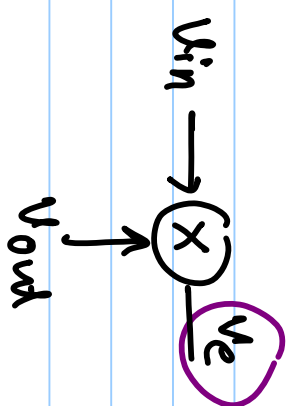


- RF Applications
- MP conversion
- DV conversion (Sinusoidal clock signals)
- LC oscillator
- o/p signals are sine
- clock as a sampling signal!

- Square wave signals
(PFD, DACs)

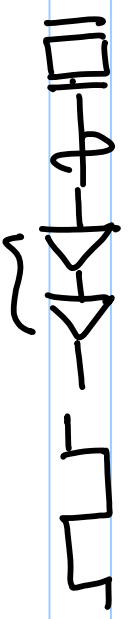

Phase Error Detectors. (PFD)

1. Mixer-based phase error detector

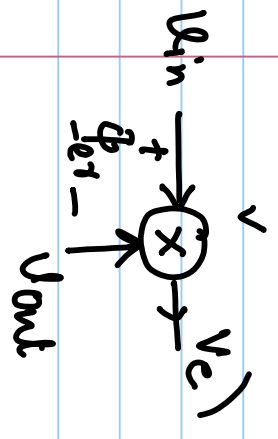

$U_{in} = A_{in} \sin(\omega_{in} t)$



$U_{out} = A_{out} \sin(\omega_{in} t - \Phi_{er}(t))$

$V_e = \frac{A_{in} \cdot A_{out}}{2} [\cos(\Phi_{er}) - \cos(2\omega_{in} t + \Phi_{er})]$

- Range of PFD: $(-\pi/2 \text{ to } \pi/2)$

- Gain of PD

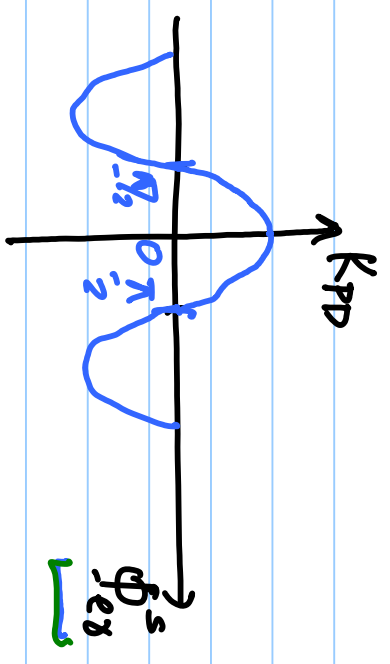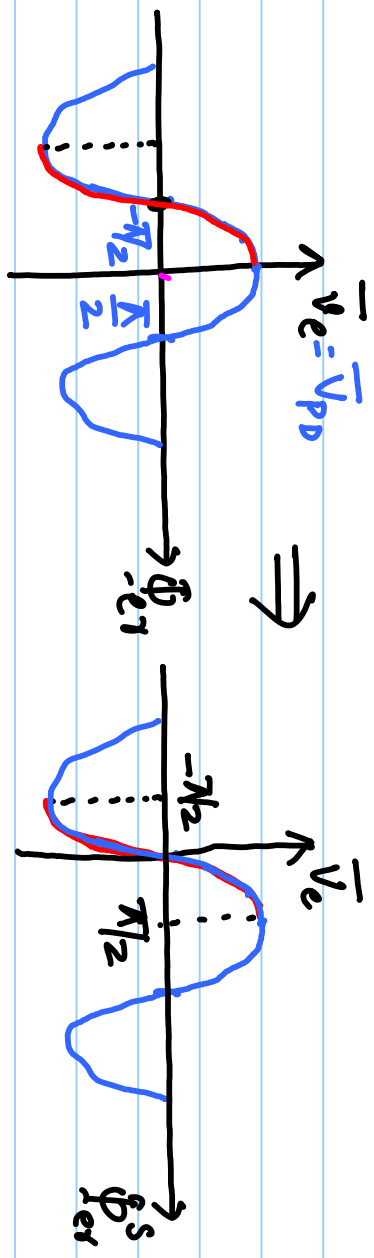Gain of PD $K_{PD} = \frac{dV_e}{d\Phi_e} = -\frac{A_{in} \cdot A_{out}}{2} \sin(\Phi_{er})$



2. Sampler Based Phase Detector.

