

Phase Error Detectors.

Analog PD

- Mixer/multiplier based PD
- Sample & hold based PD ✓


Digital PD


- XOR-based PD
- SR flip flop based 2-state PD
- 3-state PD
- D-flip flop based PD

- linear / non-linear range of Φ_p .

- Gain of PD, $K_{PD} = \frac{d(V_{PD})}{d\Phi_E}$

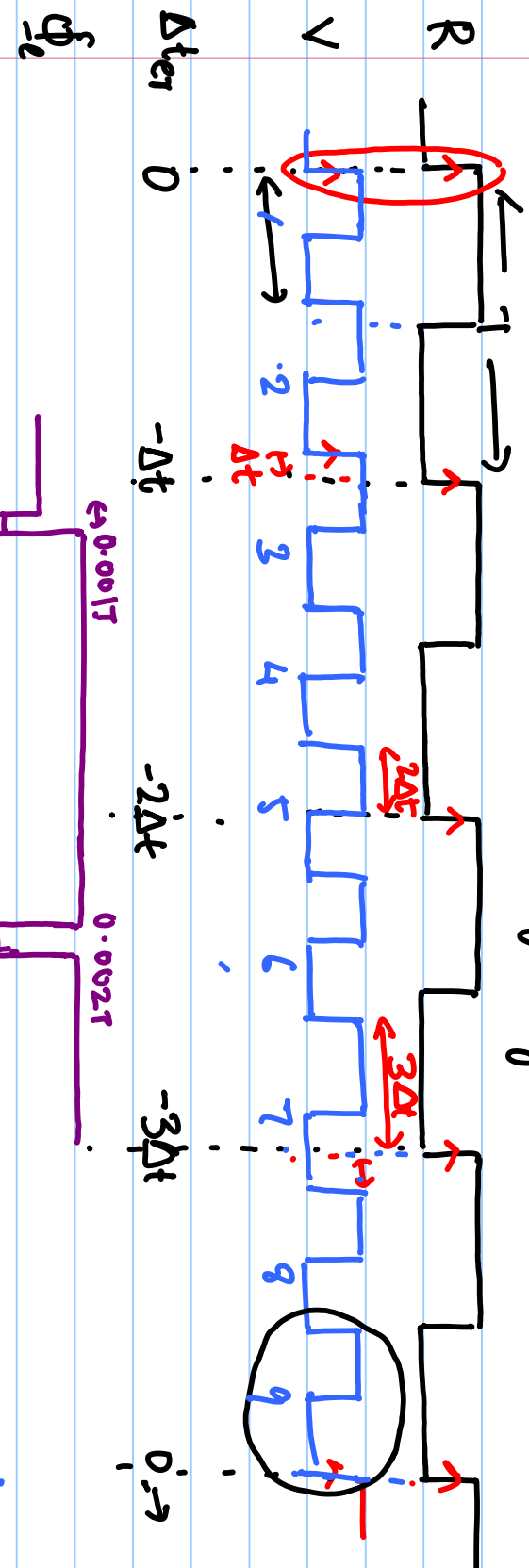Whether we can use PDs as frequency detectors?



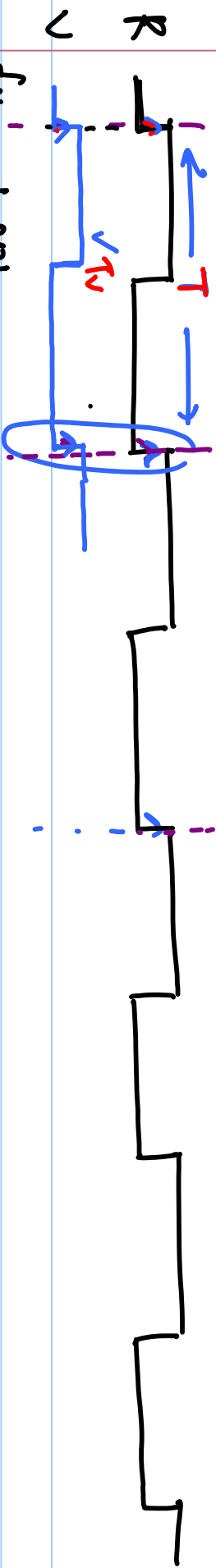


$$\frac{f_V}{f_R} = 1.001$$

$$-0.001T$$

$$-0.002T$$
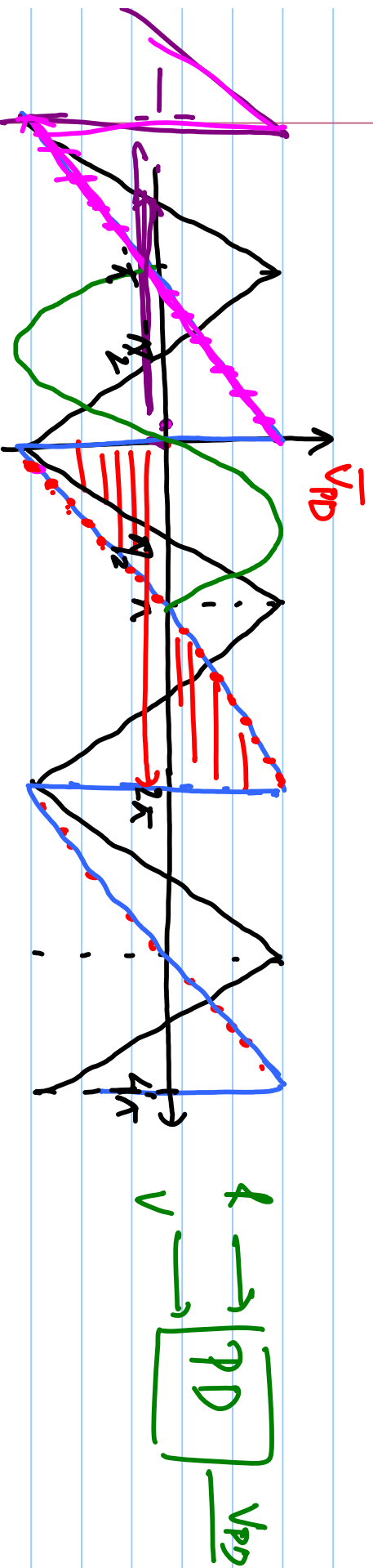
$$\frac{f_V}{f_R} = 2.25 \Rightarrow \frac{T_R}{T_V} = 2.25 \Rightarrow \frac{T_R}{T_V} = \frac{2 \times 25}{9} = \frac{100}{4}$$





Phase error accumulates and edge realign after accumulating 1T.




3-state PFD.

(Phase Frequency Detector)


fLL

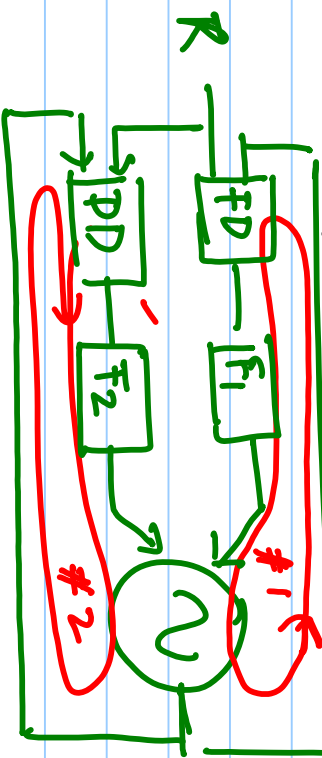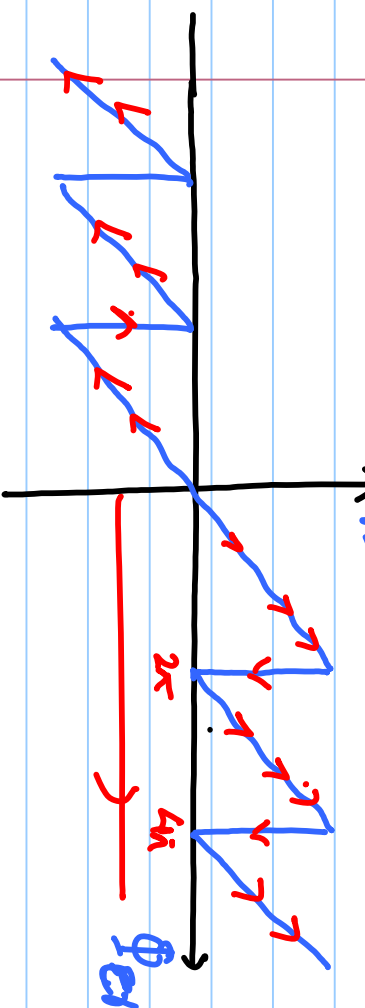


Frequency Transfer Characteristics.

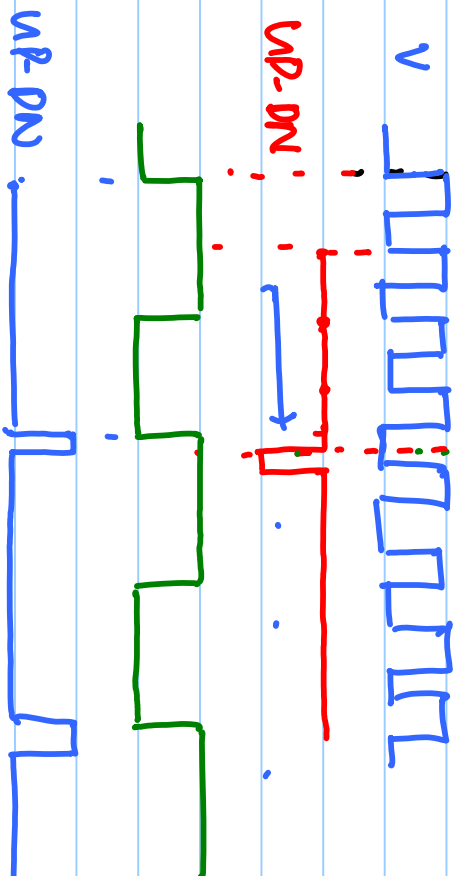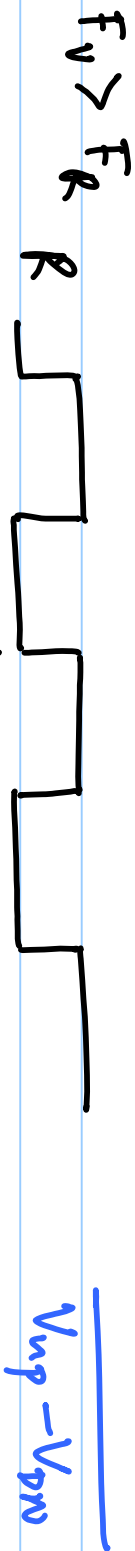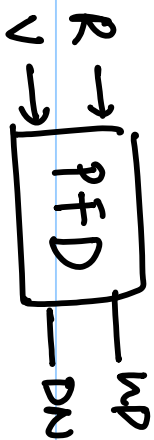
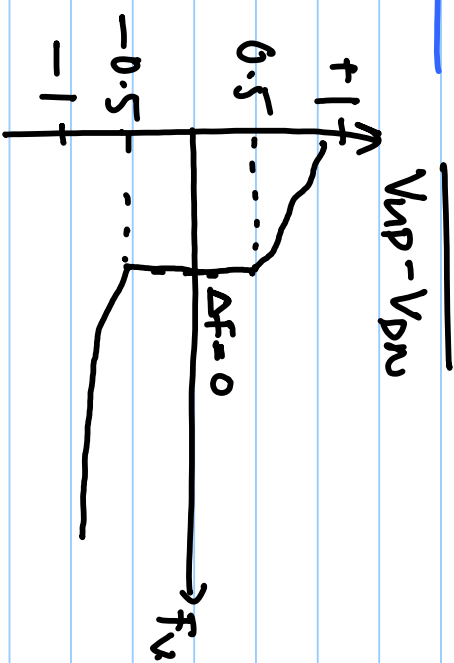
$$\frac{V_{np} - V_{dn}}{V_{np} - V_{dn}} = \begin{cases} 1 - \frac{0.5 F_v}{F_r} & , \text{ if } F_v < F_r \\ \frac{0.5 F_r}{F_v} - 1 & , \text{ if } F_v > F_r \end{cases}$$



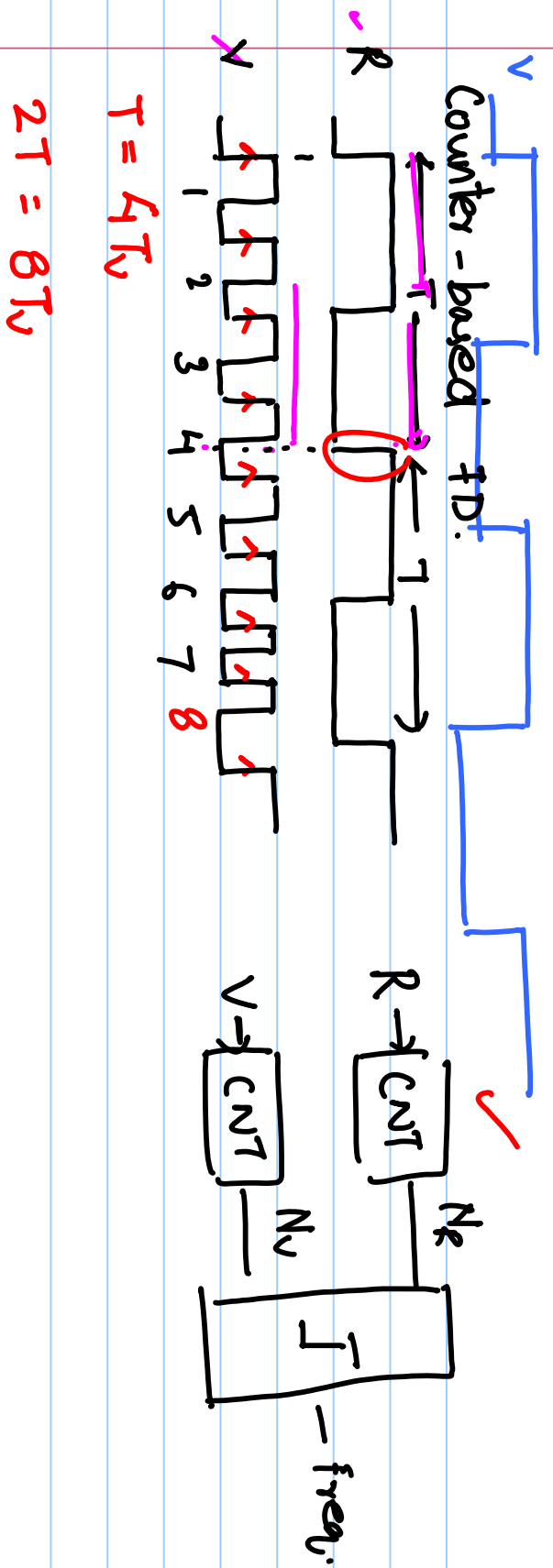




- Larger reference period \Rightarrow o/p freq. more accurately.
- Increase the time for counting of clock periods

$$T_R = 4.25T_V = \frac{17465}{4146} T_V$$

$$41T_R = 17T_V$$
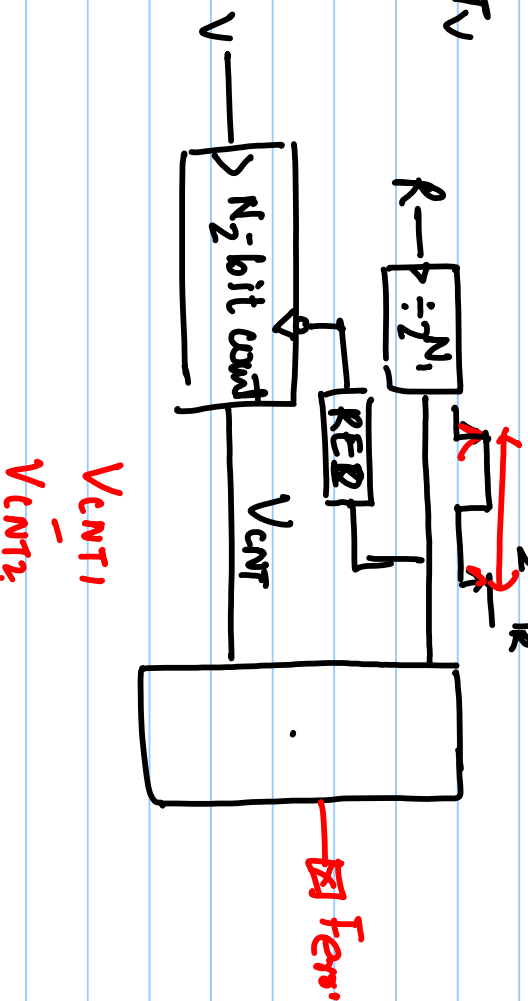
$$F_{err} = \frac{\Delta F}{F_R} \times 10^6 \text{ (ppm)}$$



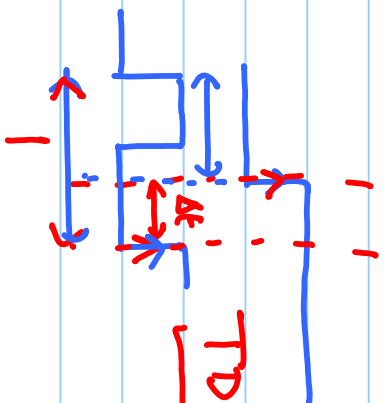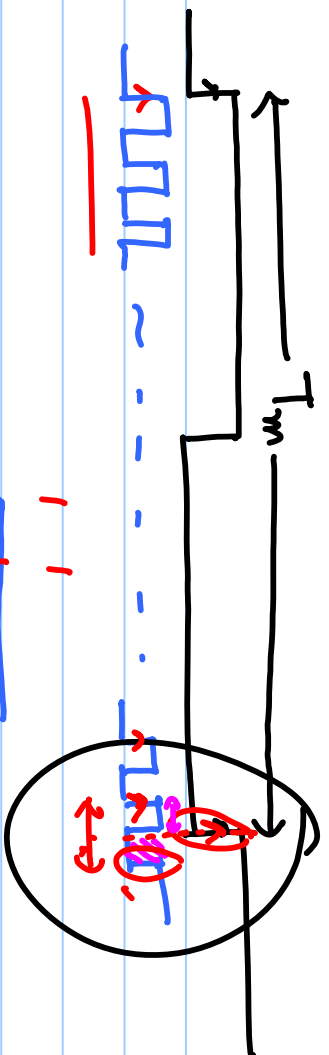

TDC : Time-to-digital converter

