
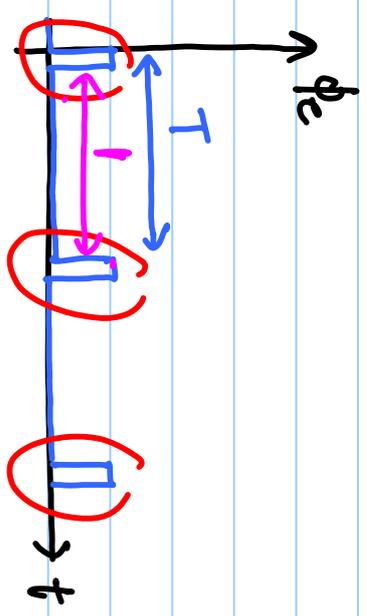


lecture # 17

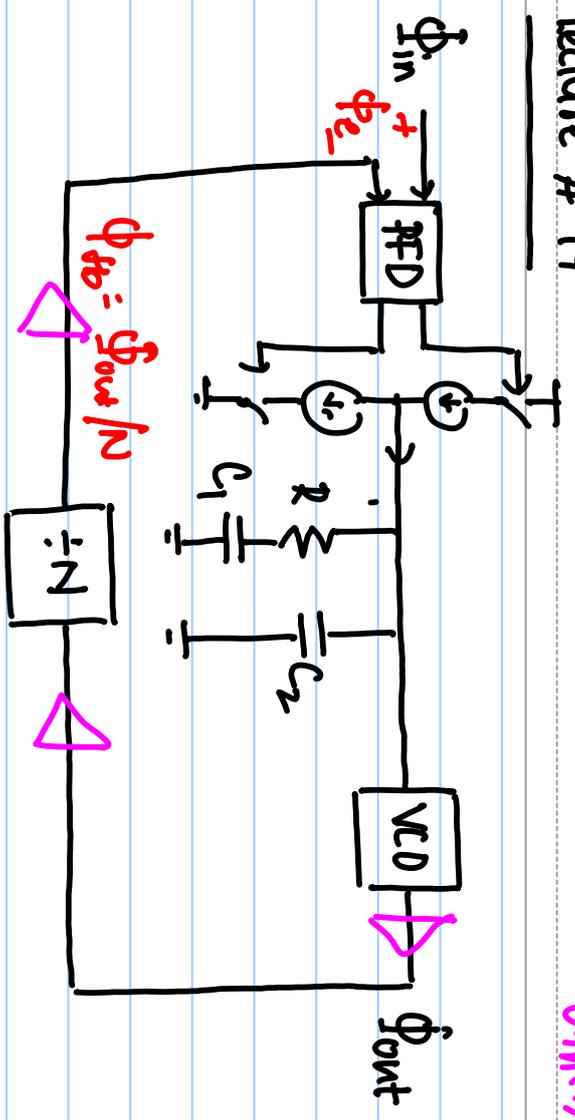$v_{in}(t) \rightarrow v_{in}(H) \rightarrow v_{in}(t - T_d)$



$$G_n(s) = \frac{1}{2\pi} T_{cp} \left\{ (R + \frac{1}{s}) \parallel \frac{1}{sC_2} \right\} \frac{2\pi K_{vco}}{s} \times \frac{1}{N} \times e^{-sT_d}$$

- Given ω_n (open loop) $\approx \omega_{3dB}$ (closed loop) & ϕ_m

$$\frac{C_1}{C_2} = 2 \left(\tan^2 \phi_m + \tan \phi_m \sqrt{1 + \tan^2 \phi_m} \right)$$


$$\omega_2 = \frac{\omega_n}{\sqrt{1 + \frac{C_1}{C_2}}}$$

- Choose R, $C_1 = \frac{1}{\omega_2 R}$

$$\angle L_a = -180^\circ + \tan^{-1} \left(\frac{\omega}{\omega_2} \right) - \tan^{-1} \left(\frac{\omega}{\omega_3} \right) - \tan^{-1} (\omega T_d)$$

$$e^{-sT_d} = \frac{e^{-sT_d/2}}{e^{+sT_d/2}}$$

$$\frac{e^{-sT_d/2}}{1 + sT_d/2}$$

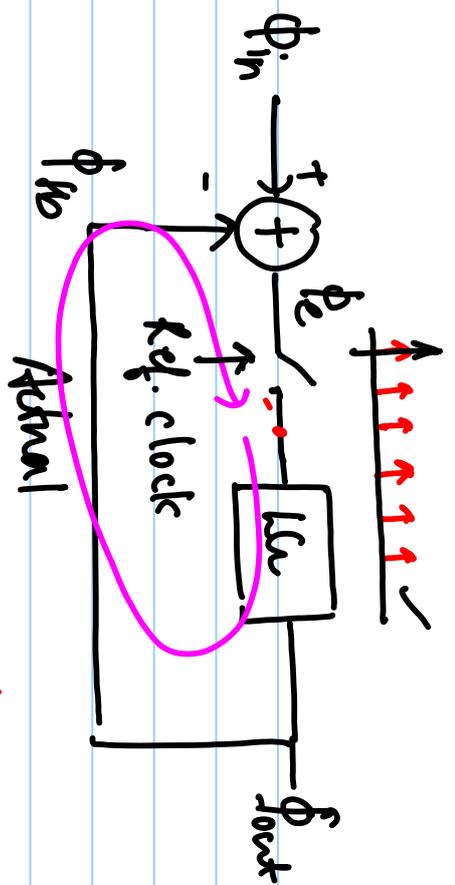

Impulse Invariance Transformation

- Calculate impulse response $k(t)$


- Sample $k(t)$ by periodic

impulse train to get $k_u(nT)$

- $k_u(nT) \xrightarrow{z} k_u(z)$

- Closed loop transfer function

with $k_u(z)$

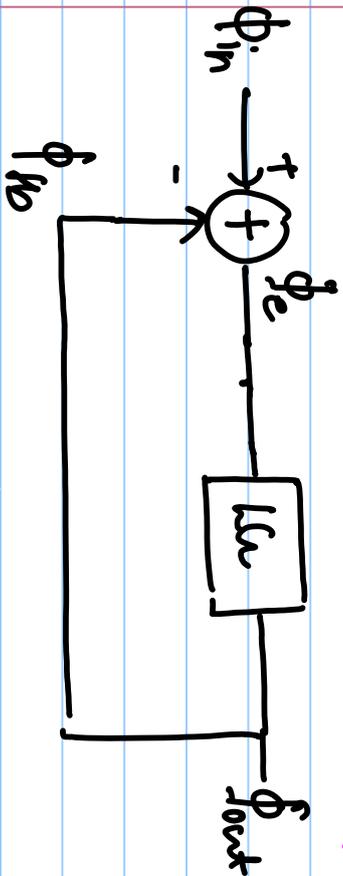

s-domain

z-domain

$k_u(s)$

$k_u(z)$

quite well


- $k_u(s)$ matches $k_u(z)$ for $\frac{f_{ref}}{f_{BW}} \leq 10$ or

$$f_{BW} \leq \frac{f_{ref}}{10}$$

- for higher bandwidth $f_{BW} < \frac{f_{ref}}{2}$, we should use $k_u(z)$.

Sources of Non-linearity

- Non-linearity in charge pump

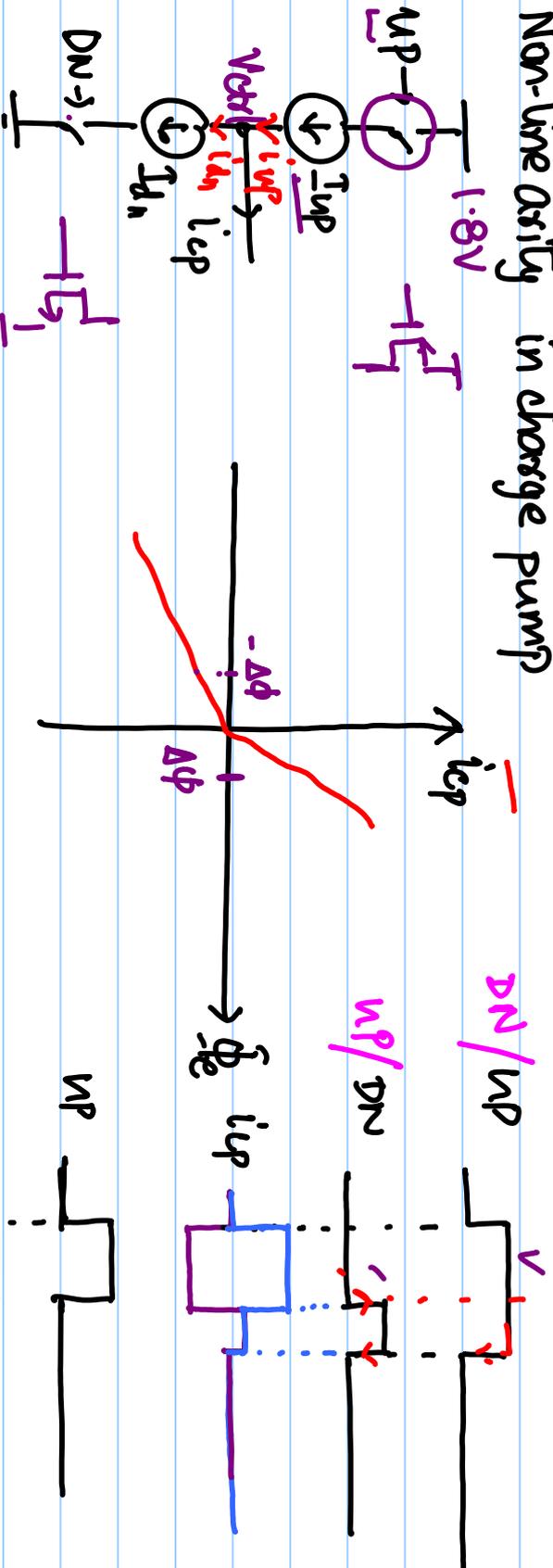


always $I_{mp} = I_{dn} + \Delta I$ static non-linearity

① $V_{gs1} = 0.9V$, $I_{mp} = I_{dn}$

$V_{gs1} = 1.2V$, $I_{mp} < I_{dn}$

$V_{gs1} = 0.6V$, $I_{mp} > I_{dn}$


} dynamic non-linearity.

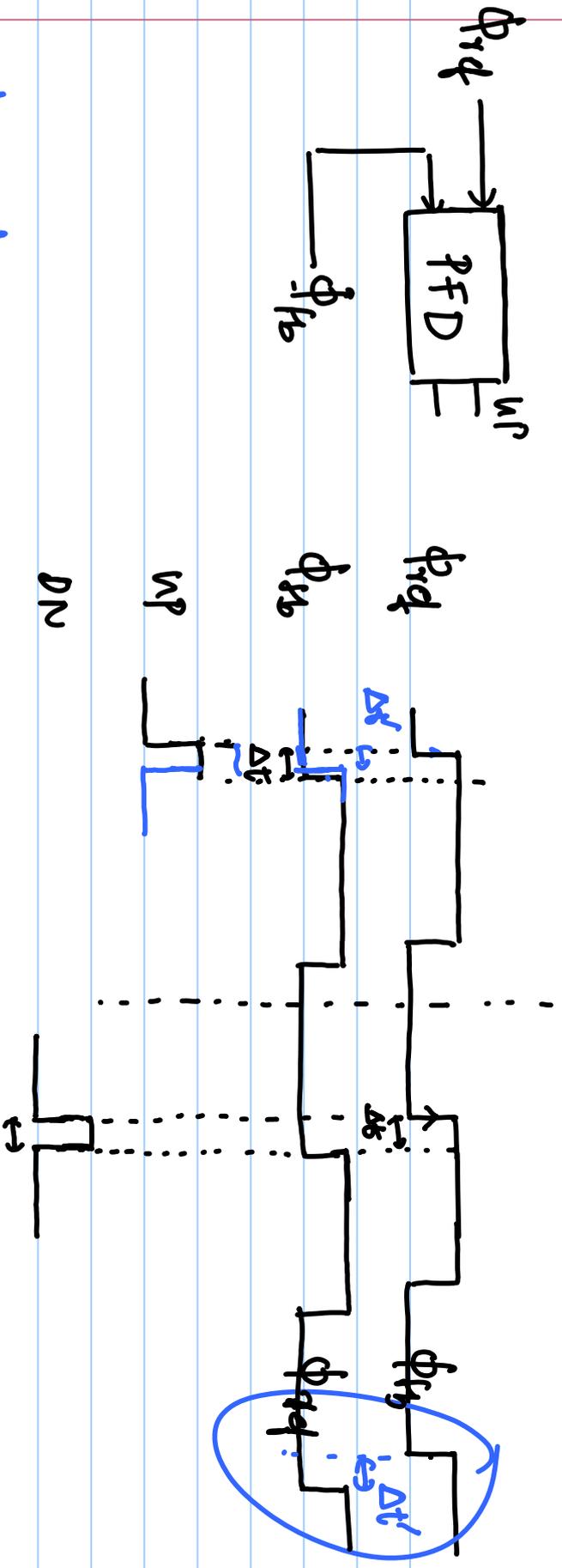

$$\phi_e = \phi_{req} - \phi_{fb}$$

$$y = f(x)$$

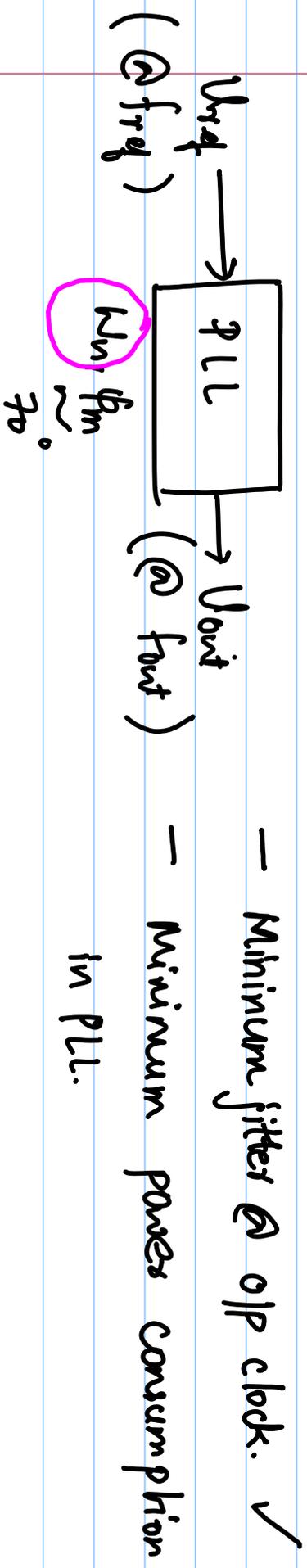- Unity gain frequency (ω_u) & Phase Margin (ϕ_m)



- Minimum jitter @ o/p clock. ✓

- Minimum power consumption in PLL.


- Relationship b/w jitter @ o/p and unity freq. of PLL.

Sources of Noise in PLL


- Extrinsic noise sources. (Peterministic Noise Sources)
 - supply noise
 - substrate noise
 - coupling to unwanted signal
- Intrinsic noise sources (Random)
 - Thermal Noise
 - Flicker Noise.

Basic noise elements


- Resistor

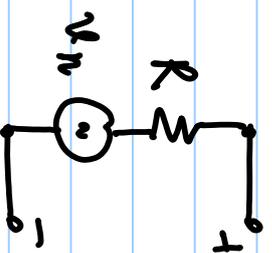
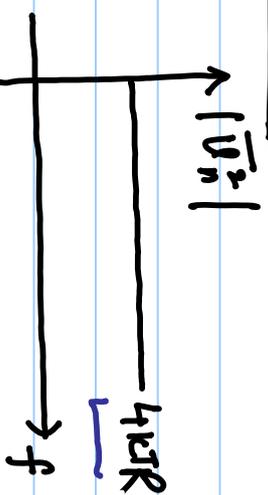
$$\frac{\overline{v_n^2}}{\Delta f} = 4kTR$$



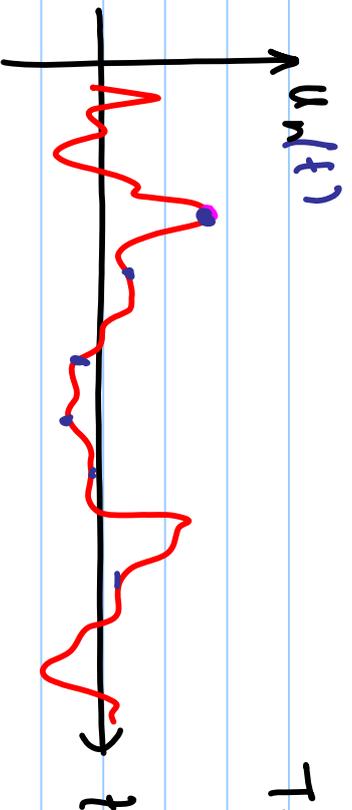k - Boltzmann's constant.
 T - temperature in Kelvin





$$\overline{I_n^2} = \frac{4kTy}{g_m} \int_s^B$$

γ : technology constant

$$\frac{2}{3} < \gamma < 2$$

g_m : transconductance.

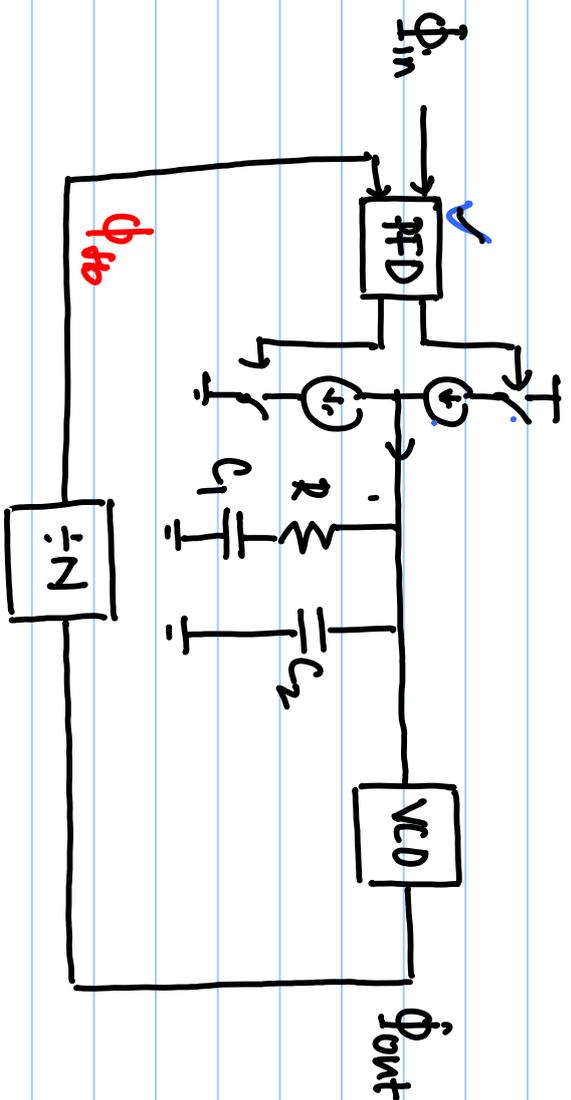

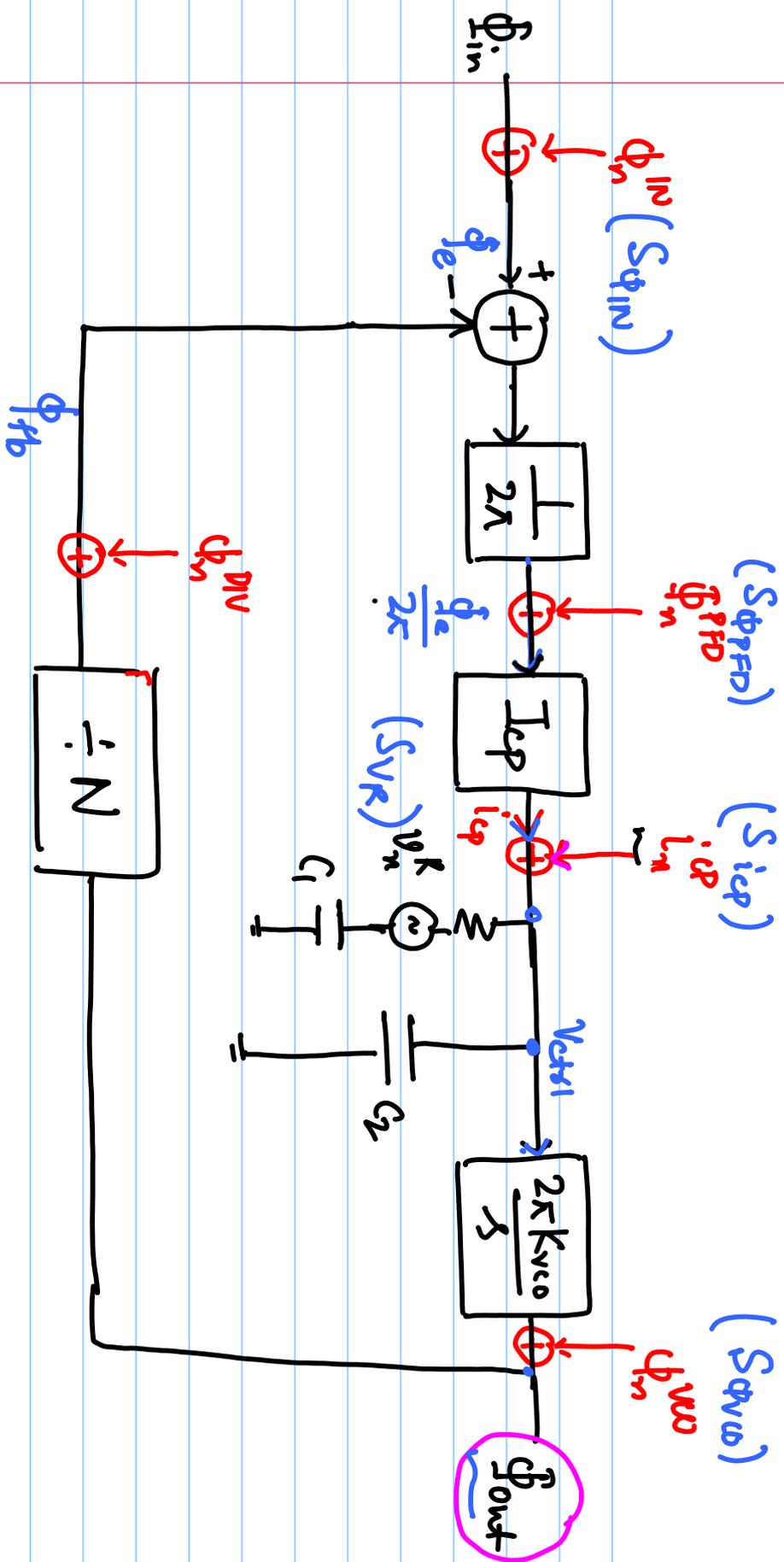


1. Identify all noise sources.

2. Calculate (simulate) the noise power spectral density of each

noise source ($S_i(f)$)

power spectral


Density $S_{\phi}(f)$

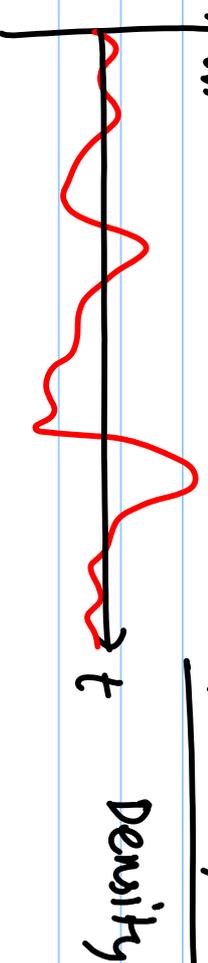

3. Noise transfer function (NTF) for each noise source to the op.

$$NTF = \frac{Y(s)}{X(s)}$$

4. find contribution of each source to the op. $(|NTF_i|^2 \times S_i(f))$

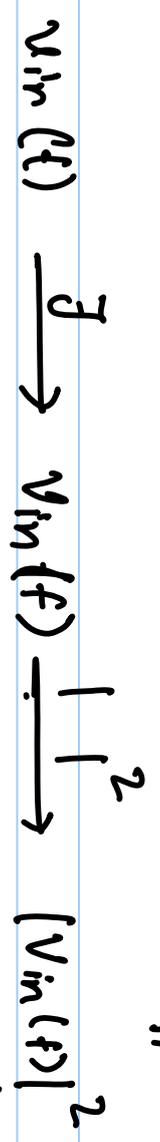

5. $\sum (|NTF_i|^2 S_i(f))$

$$NTF_{IN} = \frac{\phi_{out}}{\phi_{in}} = N \cdot \frac{k_L(s)}{(1+k_L(s))}$$

$$NTF_{PFD} = 2\kappa \cdot \frac{\phi_{out}}{\phi_{in}} = 2\kappa \cdot N \cdot \frac{k_L(s)}{(1+k_L(s))}$$

$$NTF_{CP} = \frac{2\kappa}{I_{CP}} \cdot N \cdot \frac{k_L}{(1+k_L)}$$

$$NTF_{DIV} = \frac{\phi_{out}}{\phi_{in}} = N \cdot \frac{k_L(s)}{(1+k_L(s))}$$

$$NTF_{VCO} = \frac{\phi_{out}}{\phi_{vco}} = \frac{1}{(1+k_L(s))}$$

$$NTF_R = \frac{g_{out}}{V_m^R} = \frac{1/sG_2}{sL_2 + R + \frac{1}{sC_1}} \times \frac{2\pi K_{VCO}}{s} \times \frac{1}{1+L_L}$$

$$= \frac{1/sC_1}{C_1 + sRC_1G_2 + C_2} \quad \frac{2\pi K_{VCO}}{s} \quad \frac{1}{1+L_L}$$

$$\approx \frac{C_1}{C_1 + C_2} \frac{1}{1 + sRC_1G_2} \frac{2\pi K_{VCO}}{s} \frac{1}{1+L_L}$$

