

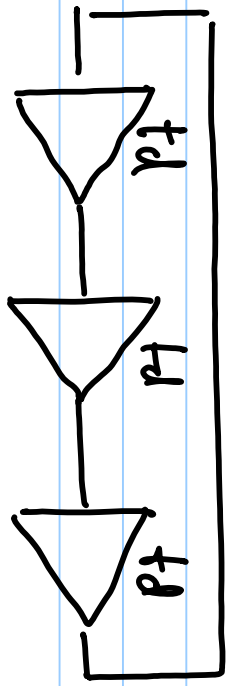
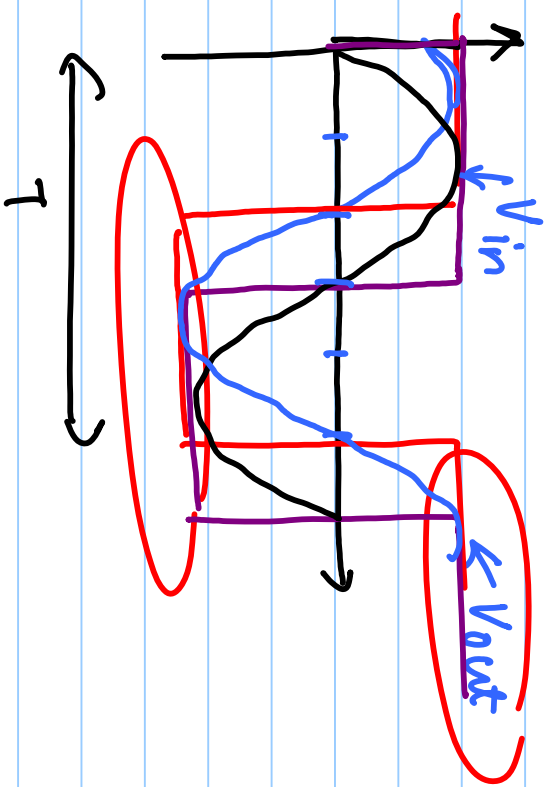


Lecture # 21



Oscillator

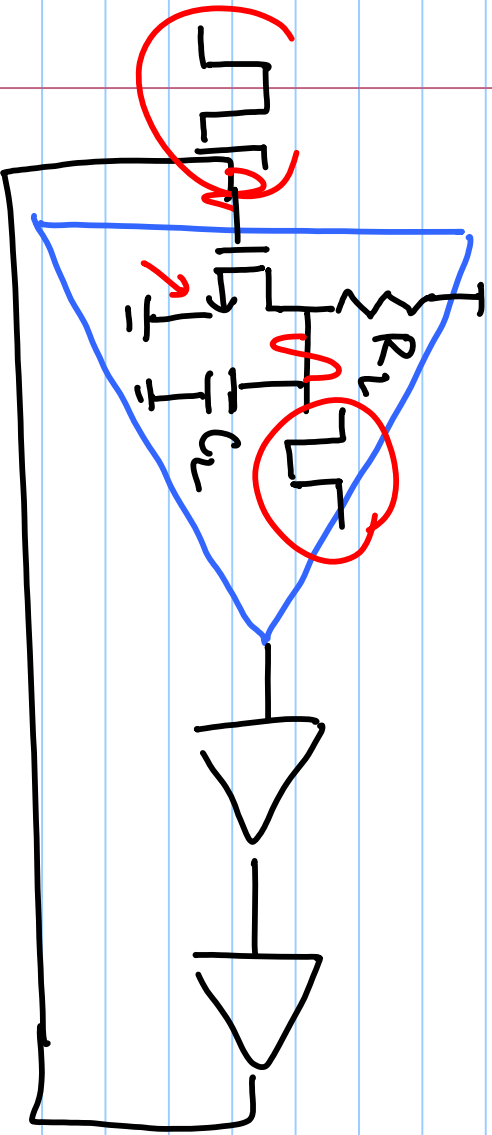
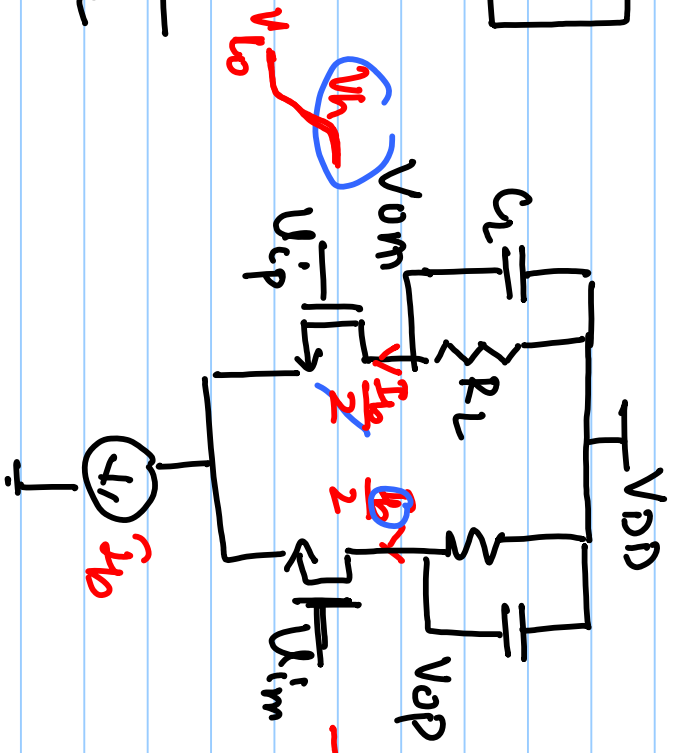
$$\frac{V_{op} - V_{om}}{V_{ip} - V_{im}} = \frac{-g_m R_L}{1 + sR_L C_L}$$



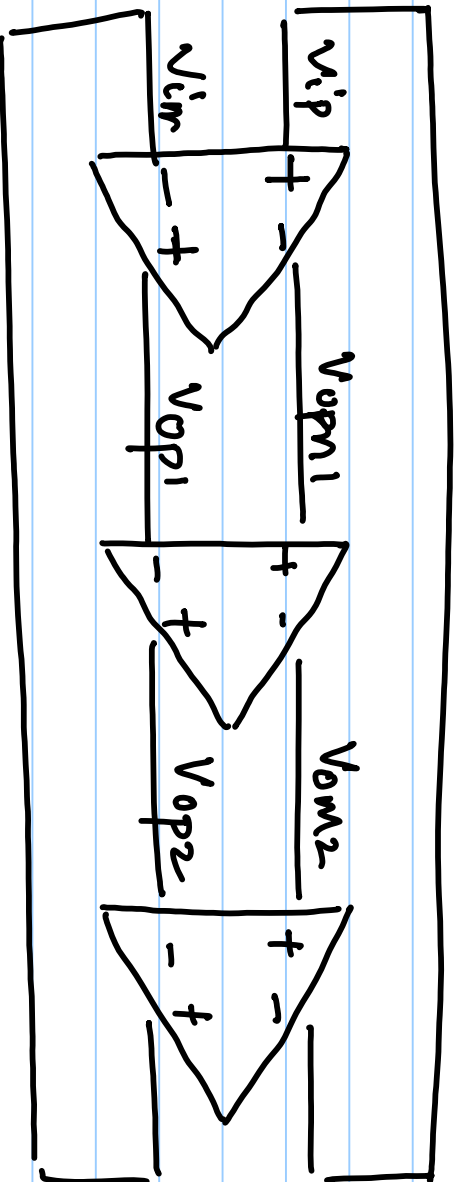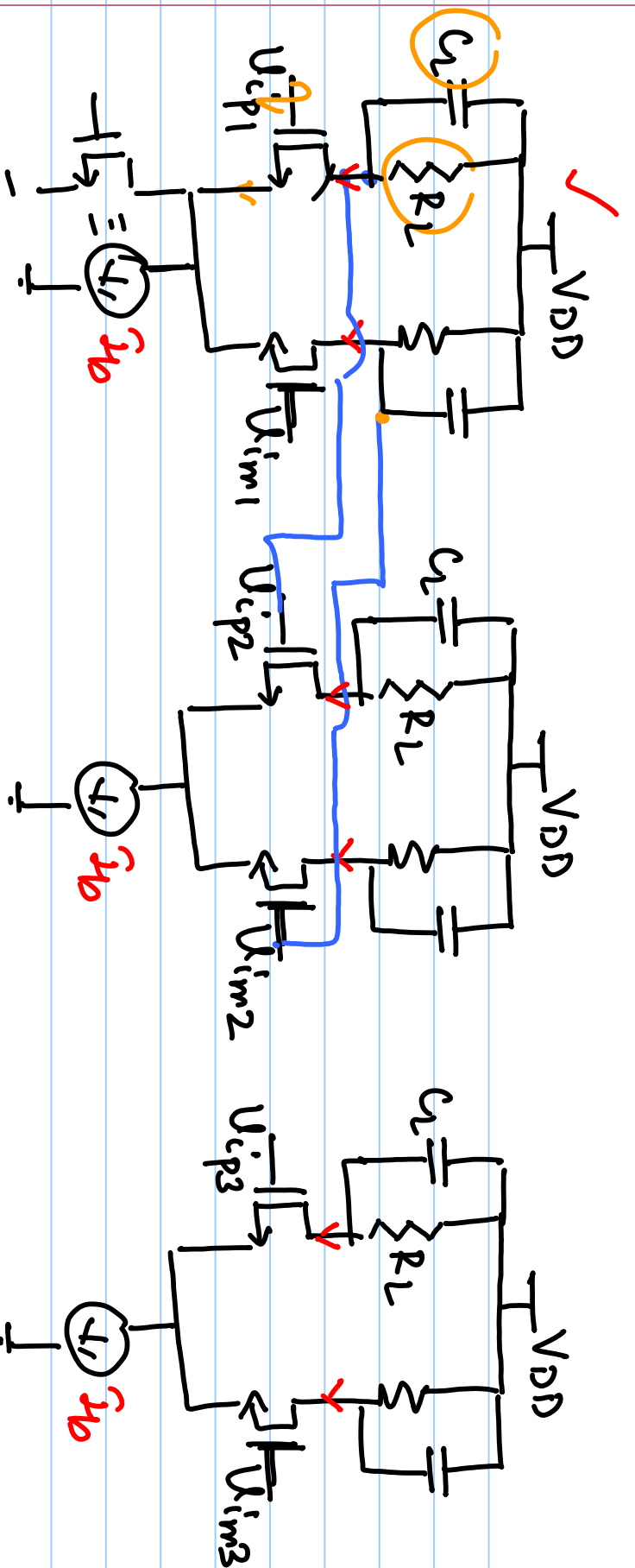$V_{op} = V_{DD}$
 $V_{om} = V_{DD} - I_D R_L$
 $V_{op} - V_{om} = I_D R_L$



$$H(s) = \frac{-g_m R_L}{1 + s k_L C_L} \cdot \frac{-A_0}{1 + s/\omega_p} \cdot \frac{-A_0^3}{(1 + s/\omega_p)^3} \quad k_L = -A_0^3$$

Output Swing = $I_b \cdot R_L$



Oscillator frequency \propto

$$\frac{1}{RLC}$$


- if frequency varies due to PVT variation.
- bring it back to desired


- if I need to change to a new frequency

then need frequency tuning.

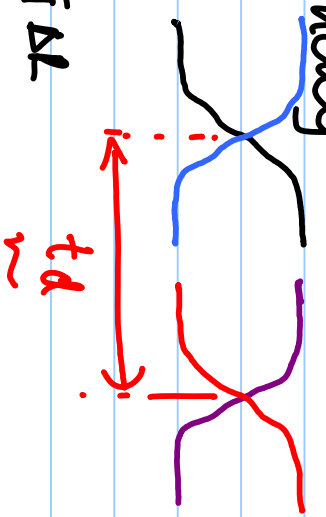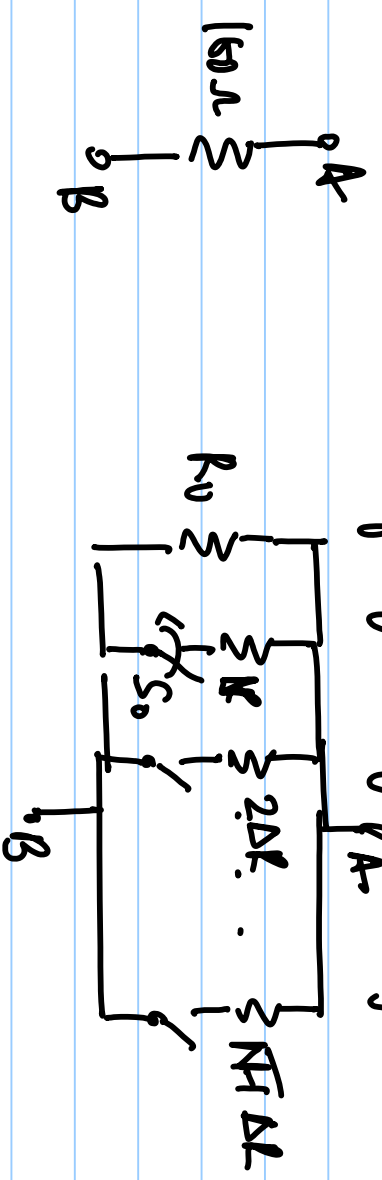
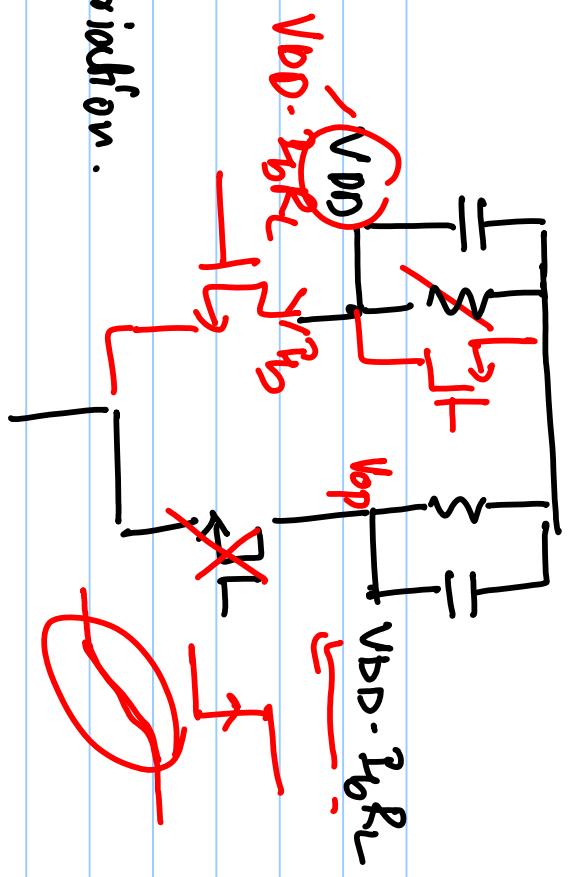
$$\frac{1}{R} = \frac{1}{R_0} + \frac{S_0}{\Delta R}$$



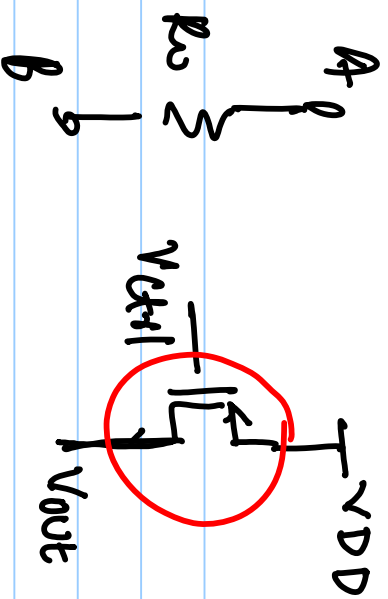

$$V_{GS} - |V_{TP}| > 0$$

$V_{SD} < V_{GS} - |V_{TP}|$ Linear Region.

$$V_{DD} - V_{out} < V_{DD} - V_{GS1} - |V_{TP}|$$

$$V_{GS1} < V_{out} - |V_{TP}| \quad \checkmark$$

$$I_{SD} = \mu_p C_{ox} \frac{W}{L} \left[(V_{GS} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$g_{ds} = \frac{\partial I_{SD}}{\partial V_{SD}} = \mu_p C_{ox} \frac{W}{L} \left[(V_{GS} - |V_{TP}|) - V_{SD} \right]$$

$$R = \frac{1}{\mu_p C_{ox} \frac{W}{L} \left((V_{GS} - |V_{TP}|) - \overset{V_{SD}}{V_{SD}} \right)}$$

$$\frac{V_{SD}}{I_{SD}} = \frac{1}{\mu_p C_{ox} \frac{W}{L} \left((V_{GS} - |V_{TP}|) - \frac{V_{SD}}{2} \right)}$$


$$R = \frac{1}{\mu_{p\text{ox}} \frac{W}{L} \left[V_{DD} - \underbrace{V_{\text{ox1}}}_{\text{red}} - |V_{TP}| \right]} V$$

$$f_{\text{osc}} \propto \frac{1}{R C_L} = \mu_{p\text{ox}} \frac{W}{L} \left[V_{DD} - \underbrace{V_{\text{ox1}} - |V_{TP}|}_{\text{red}} \right] \frac{1}{C_L}$$

$$V_{\text{swing}} = I_b \uparrow R_L \downarrow$$


$\propto R_L$

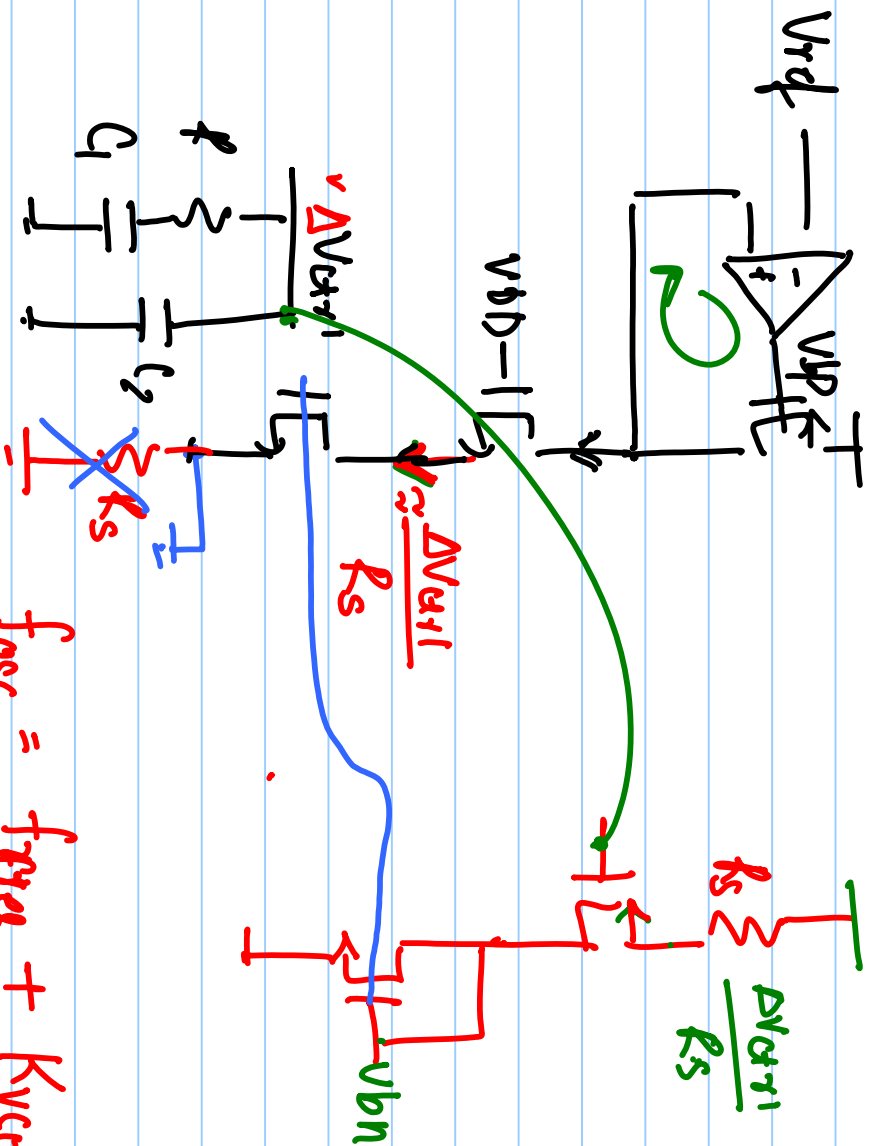- Output freq. increases w/ decrease in R_L
- Output swing decreases w/ decrease in R_L



$$f_{osc} = f_{T_{PMOS}} + K_{V_{GS}} \cdot V_{GS1}$$



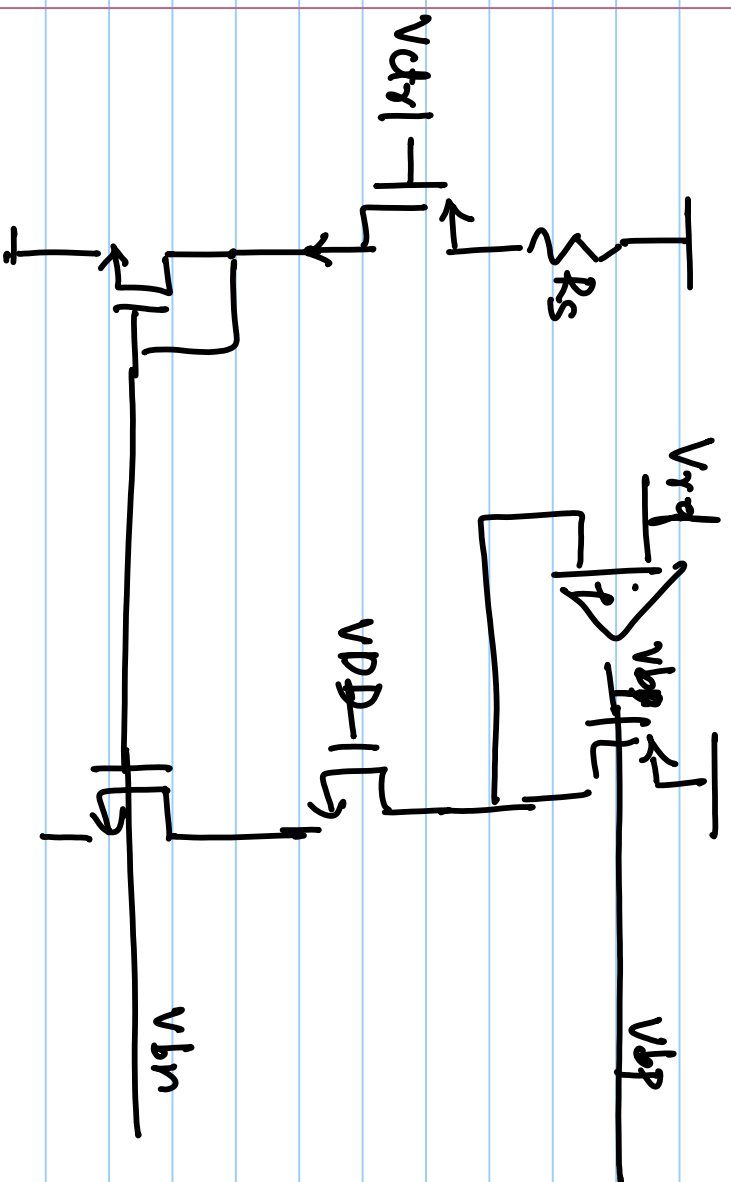
$$\frac{V_{OP}}{V_{GS1}} = f_{T_{PMOS}} + K_{V_{GS}} (\underbrace{V_{GS1(0)} + \Delta V_{GS1}})$$



$$I_{GS1} \approx \frac{V_{GS1}}{R_S}$$

$$f_{osc} \propto \frac{I_{GS1}}{(V_{DD} - V_{GS1})C} = \frac{V_{GS1}}{R_S C (V_{DD} - V_{GS1})}$$

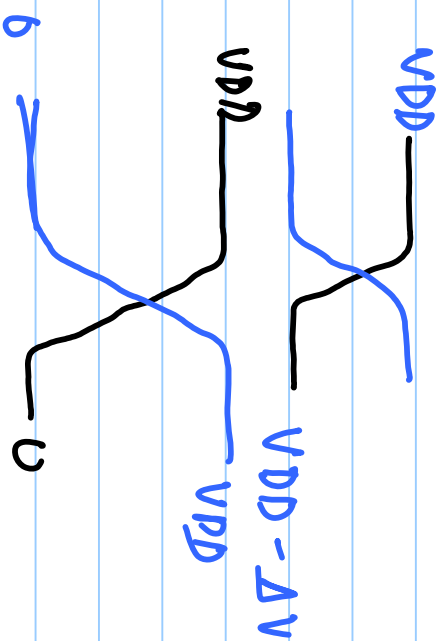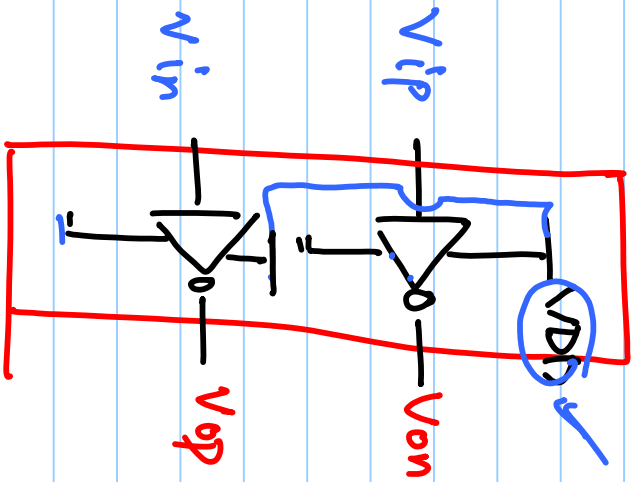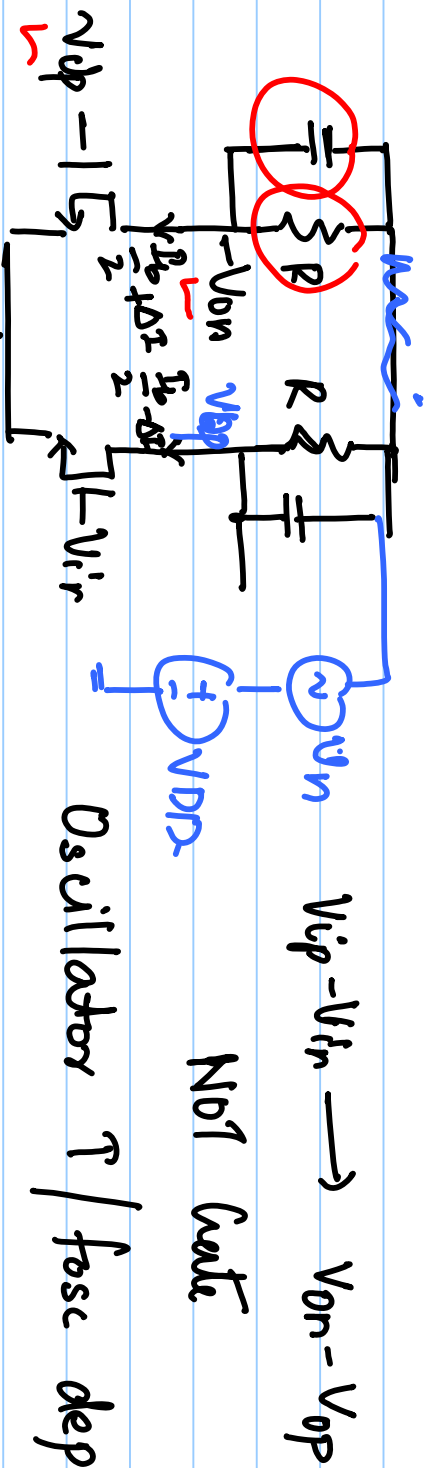
- Amplitude
- Tunable frequency.
- linear voltage-to-frequency conversion.



$$V_{op} = V_{DD} - \left(\frac{I_b}{2} + \Delta I \right) R$$


$$V_{on} = V_{DD} - \left(\frac{I_b}{2} - \Delta I \right) R + U_n$$
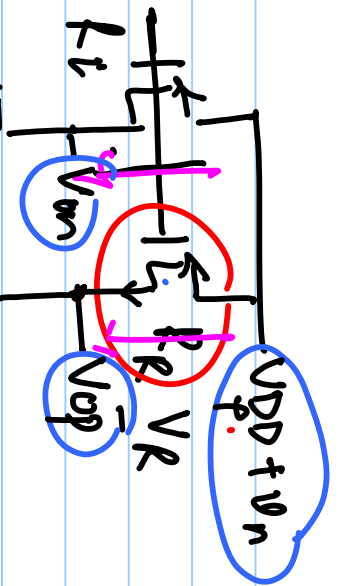
$$V_{op} - V_{on} = 2 \cdot \Delta I \cdot R$$



$$V_{op} = V_{DD+V_n} - \left(\frac{I_p}{2} + \Delta I\right) (R_p) \rightarrow (R_0 + \Delta R)$$
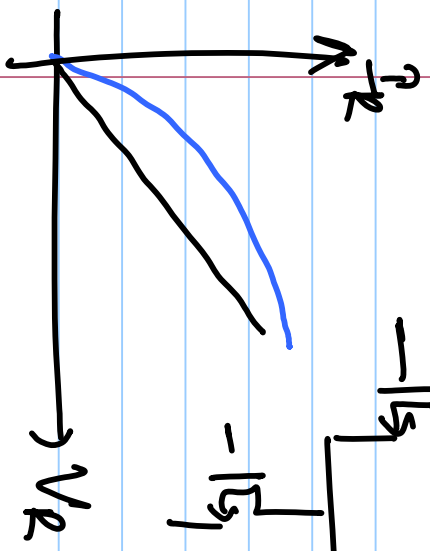
$$V_{on} = V_{DD+V_n} - \left(\frac{I_n}{2} - \Delta I\right) (R_L) \quad (R_0 + \Delta R)$$



$$R_p = \frac{1}{\mu_p C_{ox} \frac{W}{L} \left(\{V_{DD+V_n} - V_{A_{T1}} - |V_{tp}| \} - (V_{DD+V_n} - V_{op}) \right)}$$

$$R_L = \frac{1}{\mu_n C_{ox} \frac{W}{L} \left(\{V_{DD+V_n} - V_{A_{T1}} - |V_{tp}| \} - (V_{DD+V_n} - V_{op}) \right)}$$

