
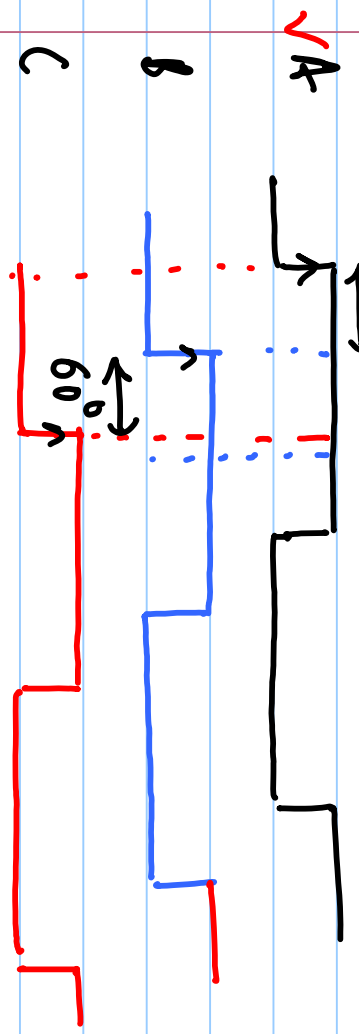


Lecture # 23


Ring Oscillator

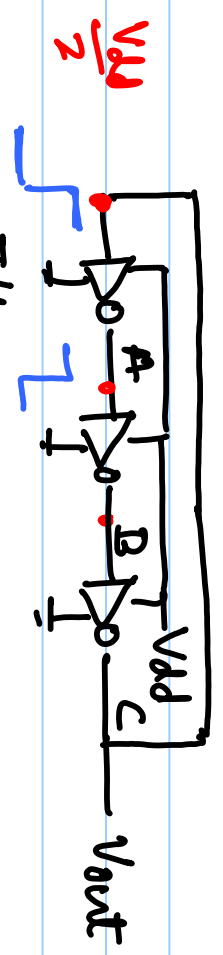


90° phase shifted: $\frac{360^\circ}{2N} V$


$$f_0 = \frac{1}{6t_d} = \frac{1}{3(t_{dp} + t_{dn})}$$








$t_{dp} = t_{dn}$

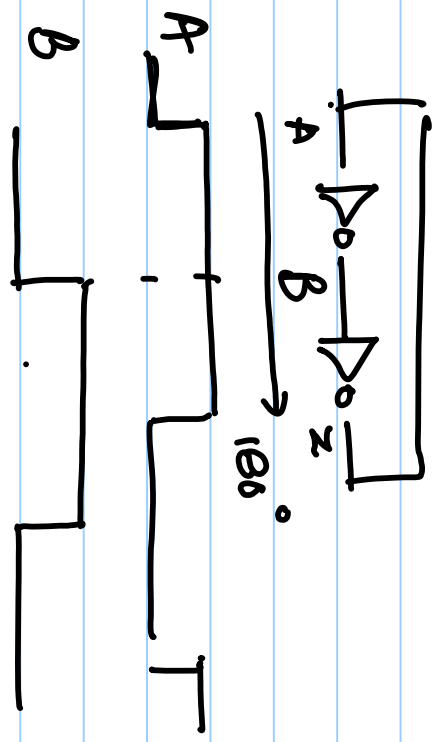


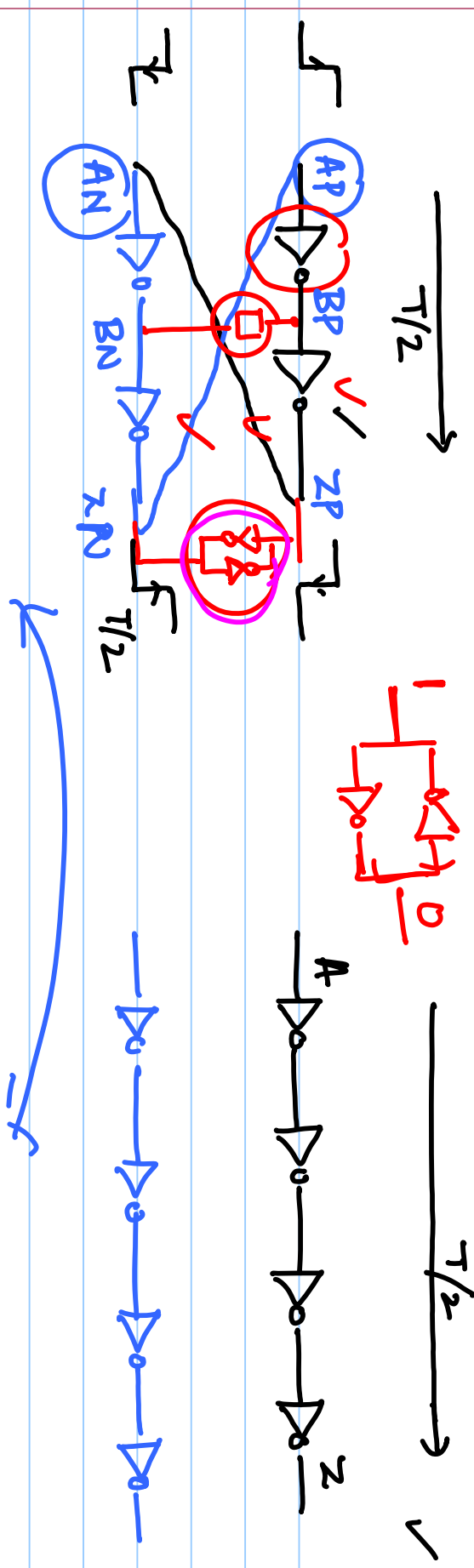

Pseudo-differential Ring Osc.

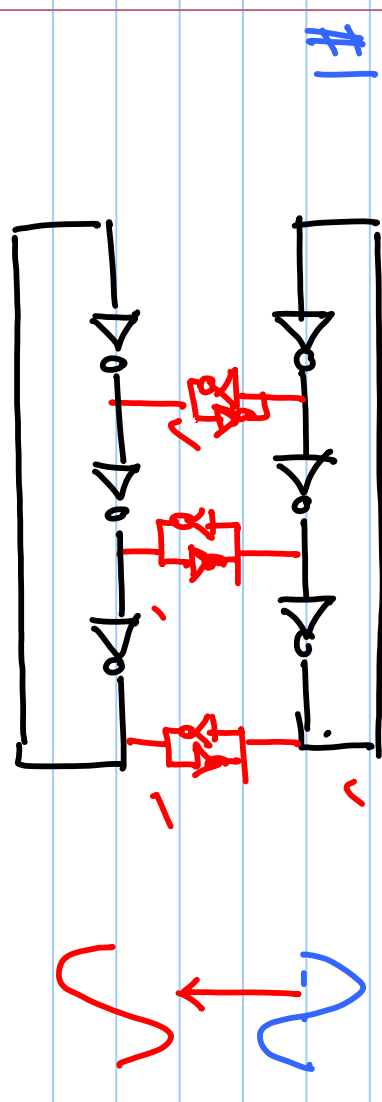


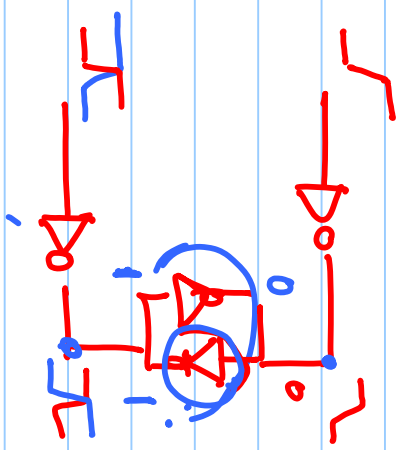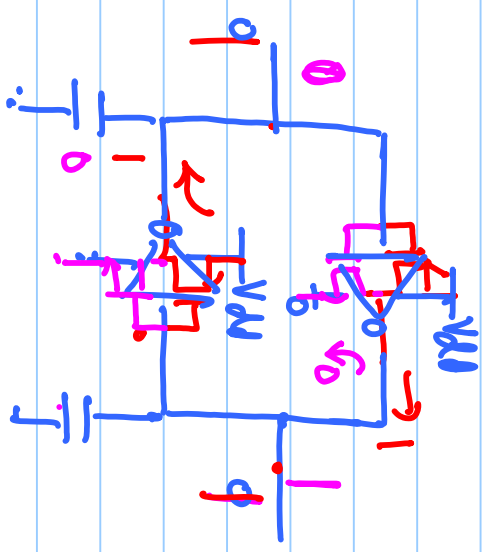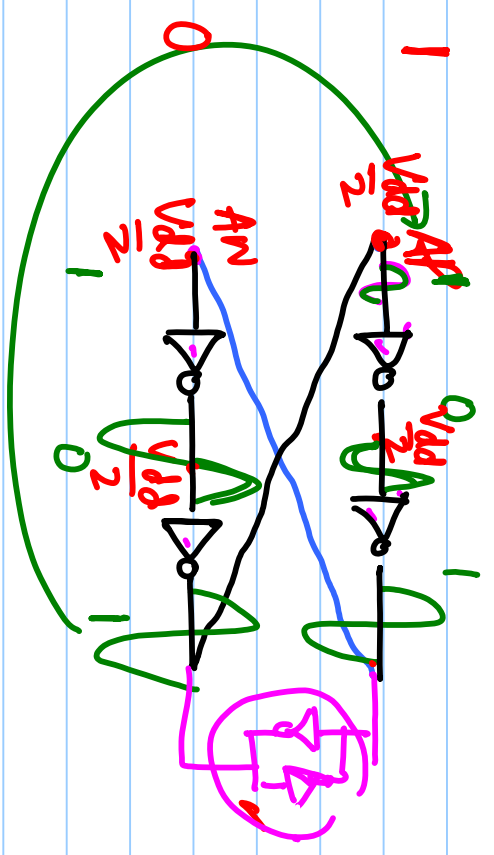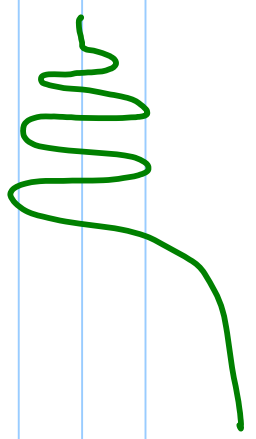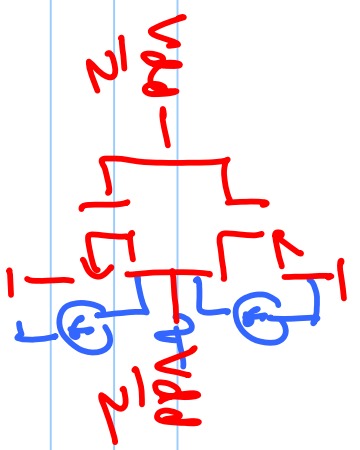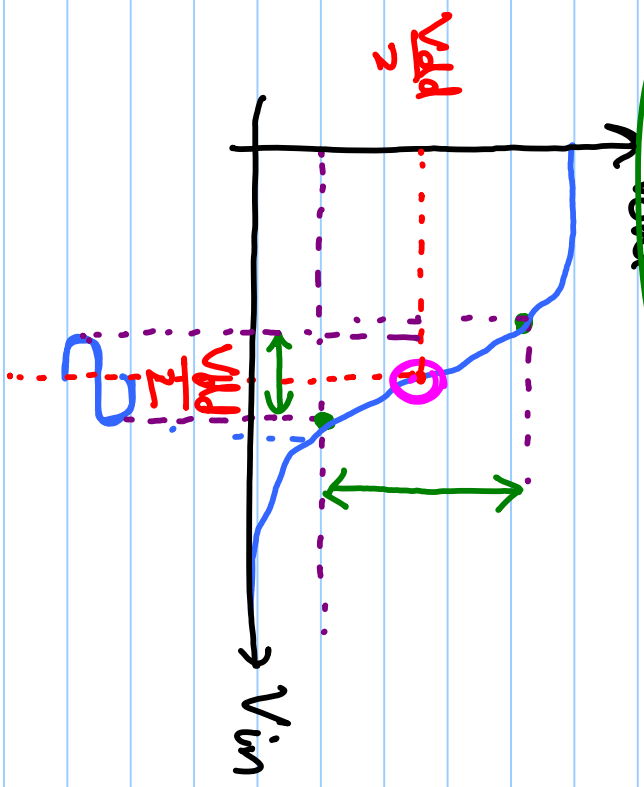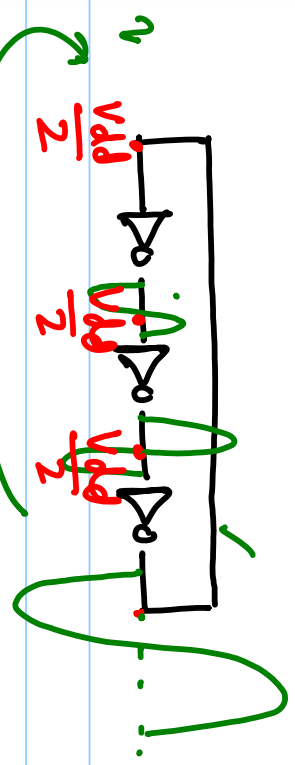


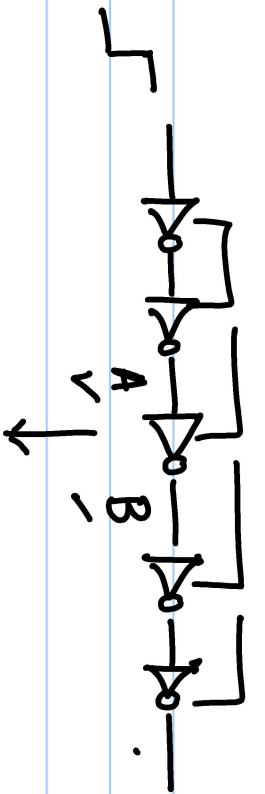


$$t_{d_{rise}} = t_{d_{fall}}$$

$$T = 6 t_d$$

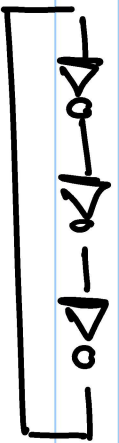

$$A_P = A_N$$

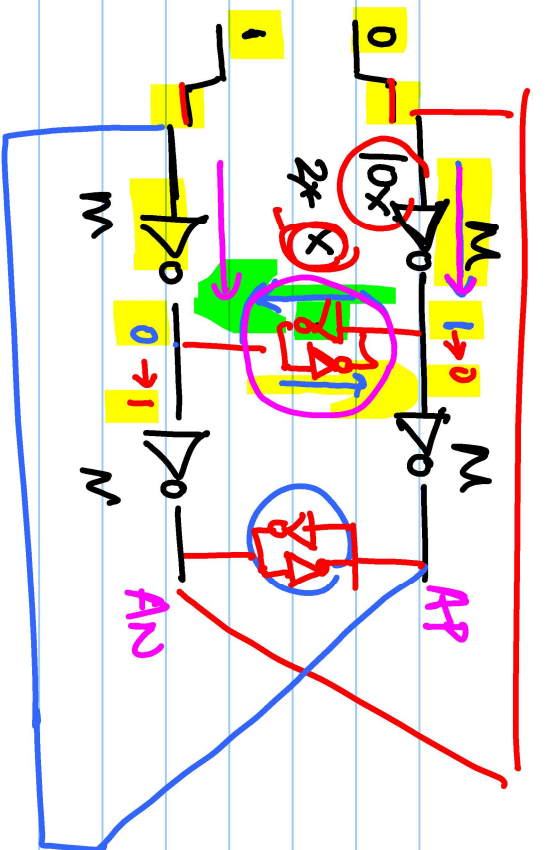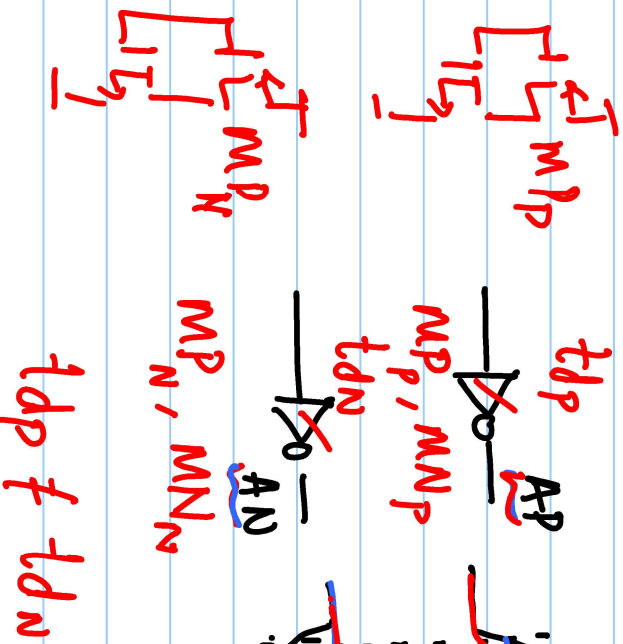


$$t_d \text{ w/o } c < t_d \text{ w/ } c$$


⇒ large size for cross-coupled
as compared to main inv.

$$\text{Noise} \propto \frac{1}{\text{Power}}$$

s_3, t_b, t_r, s_f, t_s

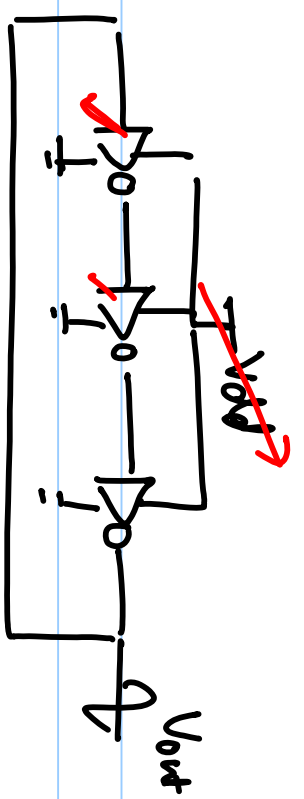

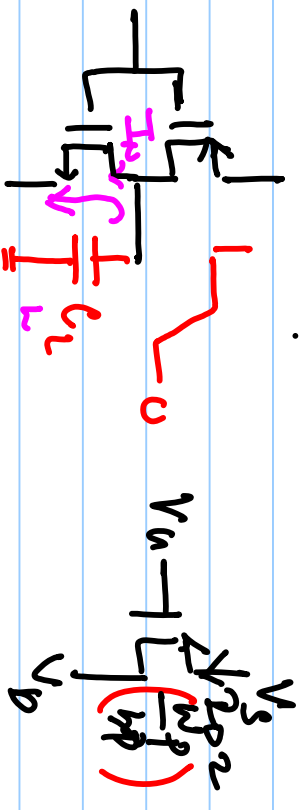
$f_0, \ln(t_t)$: typical corner
 $\frac{W_p}{L_p}, \frac{W_n}{L_n}$





V_s, V_p, V_n, V_d
 $\frac{W_p}{L_p}, \frac{W_n}{L_n}$

$$I_D = \mu_p C_{ox} \frac{W_p}{2L_p} (V_{GS} - V_{tp})^2$$


- Mismatch
 - PVT dependent.

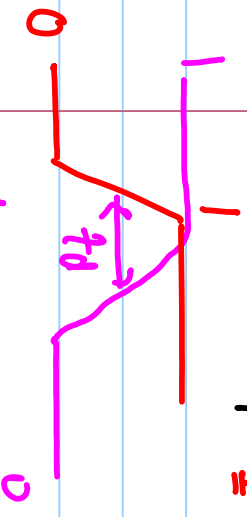


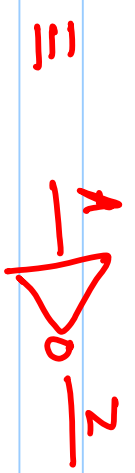
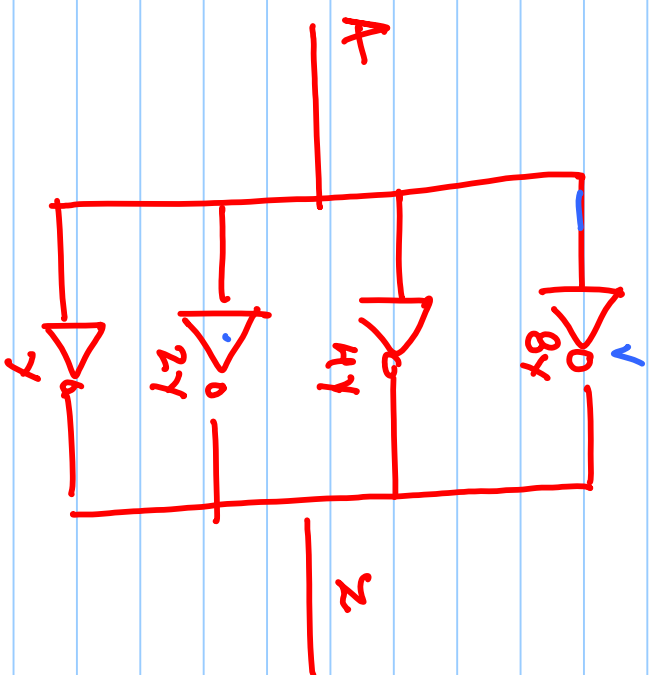
t_d
 $I_L \cdot \Delta t = \Delta V_{out}$
 C_L



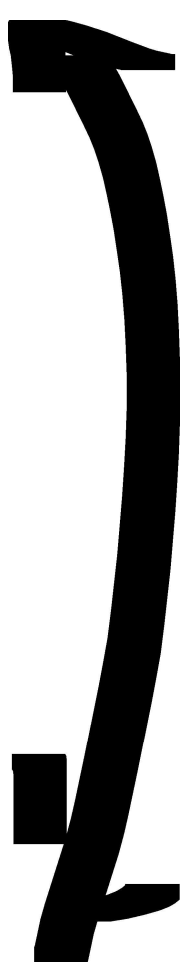
$$\left[\begin{array}{l} Y \rightarrow 15Y \\ 3Y \leftarrow 4Y \rightarrow 15Y \end{array} \right]$$



$V_{GS} - V_{th}$

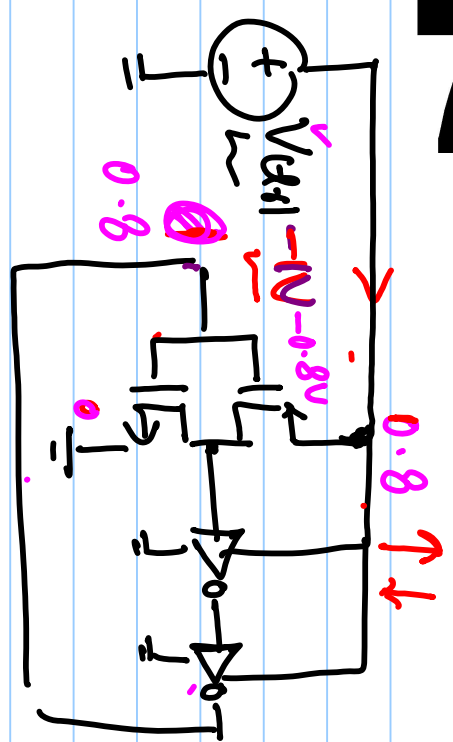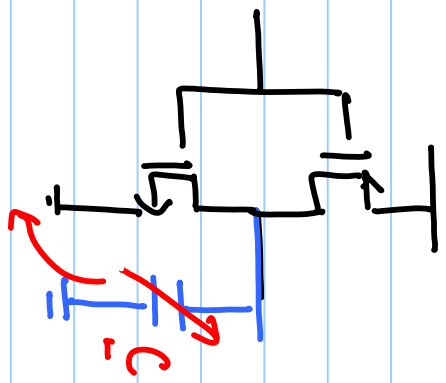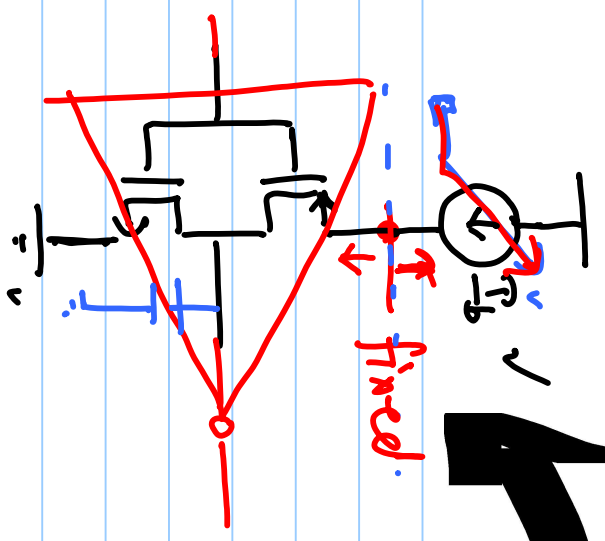

Current-starved inverter

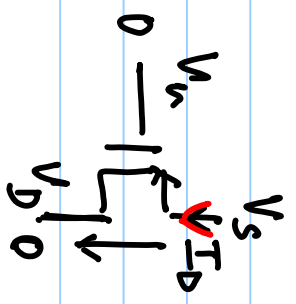

Same

$$I_D = \mu_p C_{ox} \frac{W_p}{2L_p} (V_{GS} - |V_{tp}|)^2$$

50mV 50mV

