
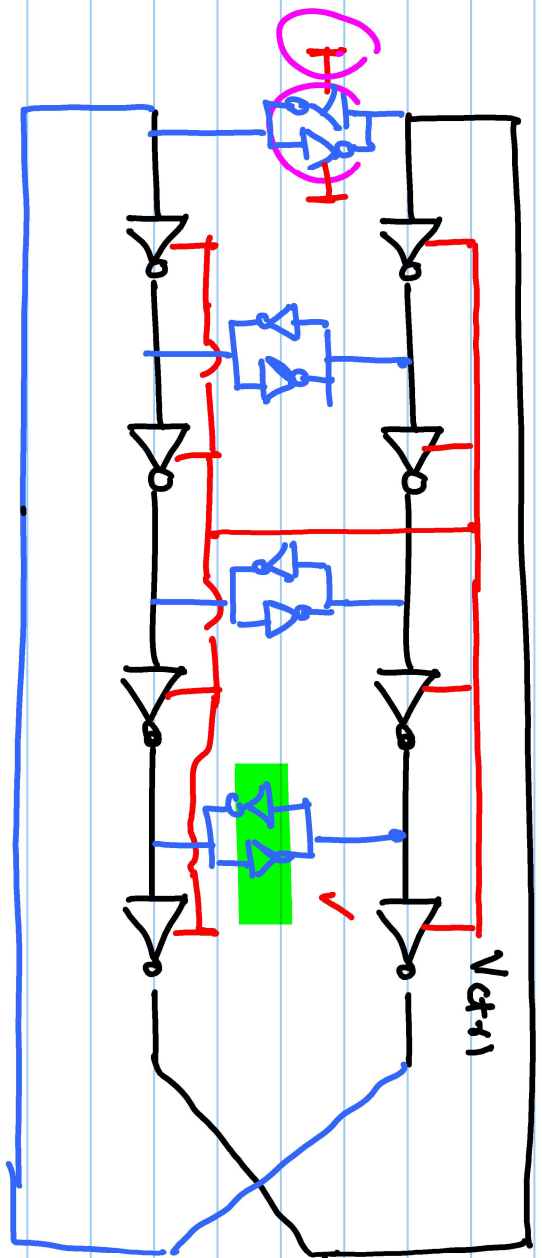






Lecture # 24



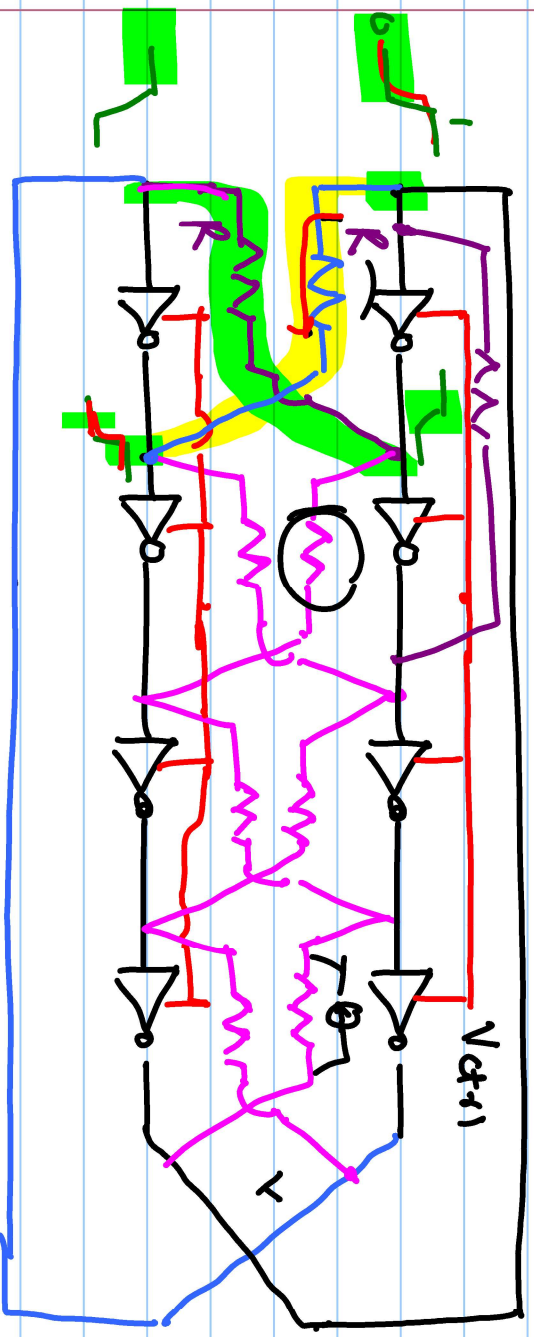


- Power consumption in cross-coupled inv.






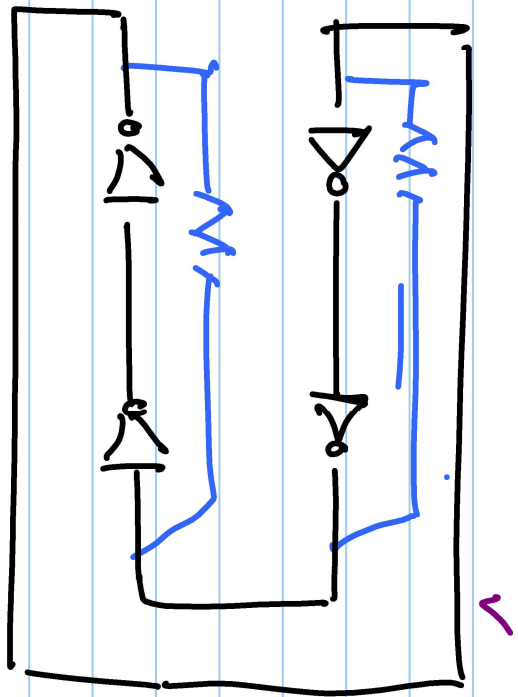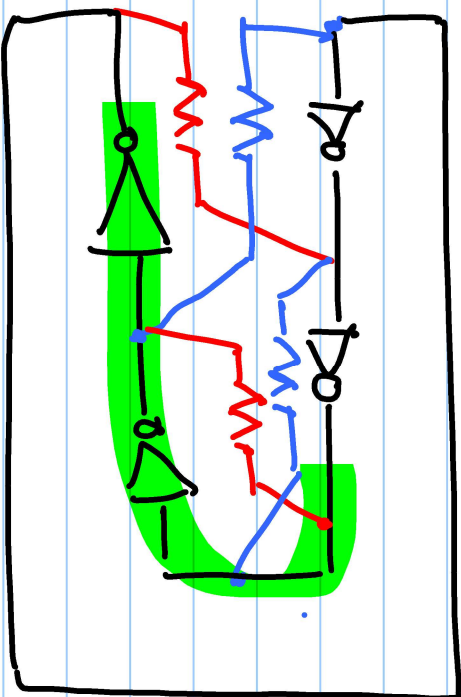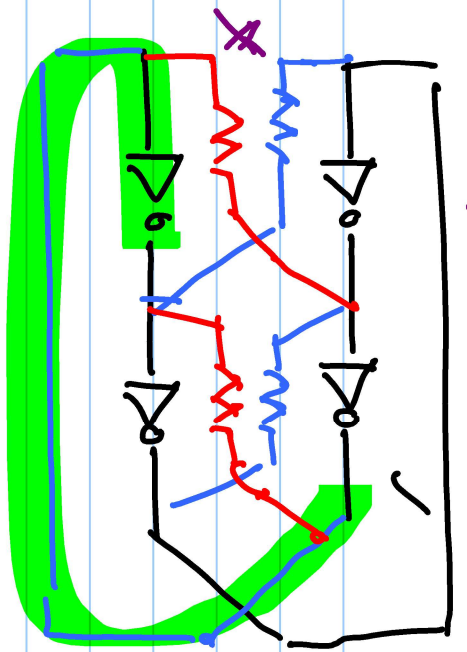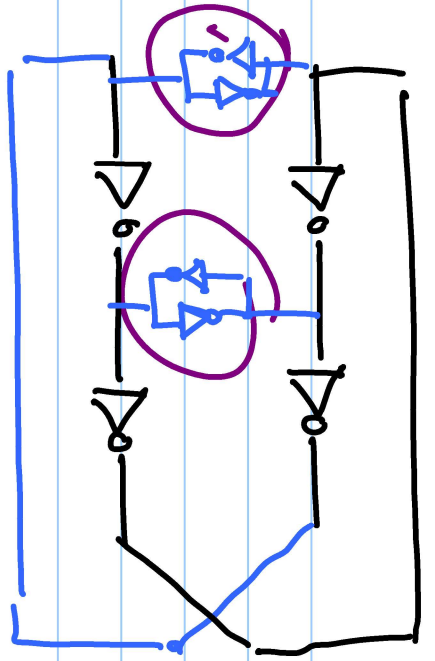- R is small
- r is large.
- R : poly resistor.
- $\pm 20\%$



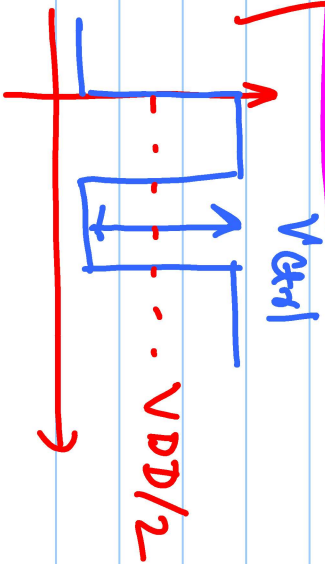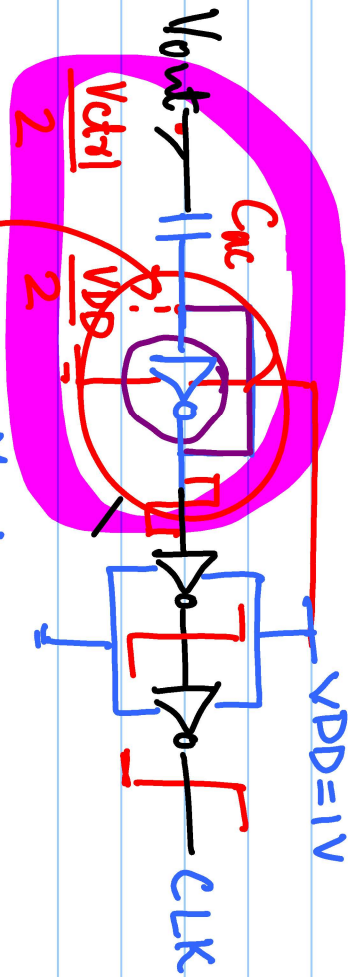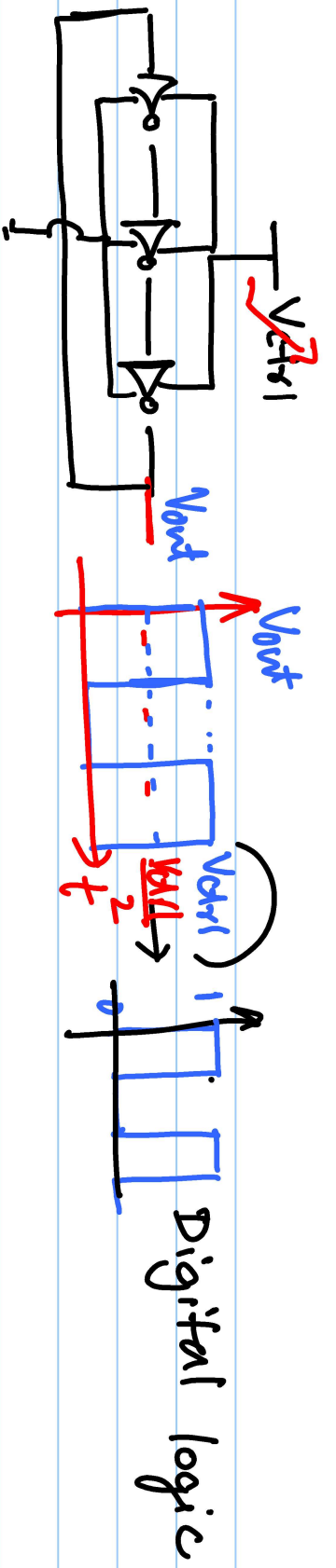
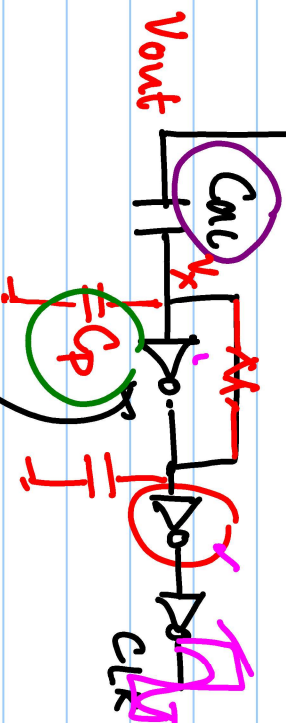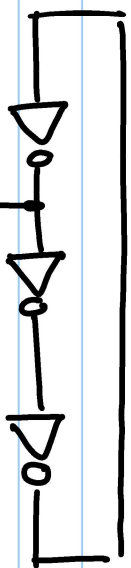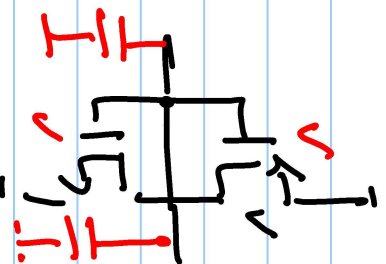
$$\frac{V_o}{V_{out}} = \frac{y_{o11} \frac{1}{sC_p}}{y_{o11} \frac{1}{sC_p} + \frac{1}{sC_{av}}}$$



$$\frac{V_o}{V_{out}} \approx 1$$





$$y_{out} = \frac{1}{g_{mp} + g_{mn}}$$








$$= \frac{\gamma_0 / (1 + \beta C_p \gamma_0)}{1 + \beta C_p \gamma_0 + \beta C_{ac} \gamma_0} = \frac{\beta \gamma_0 C_{ac}}{\beta C_{ac} \gamma_0 + \beta C_p \gamma_0 + 1}$$




$$= \frac{\beta \gamma_0 C_{ac}}{1 + \beta (C_{ac} + C_p) \gamma_0}$$







$$\approx \frac{C_{ac}}{C_{ac} + C_p} \sqrt{1 - 10\% V_{th1} - 10 - 10} \dots 90\% \rightarrow 10 - 10$$

$C_{ac} \gg C_p$

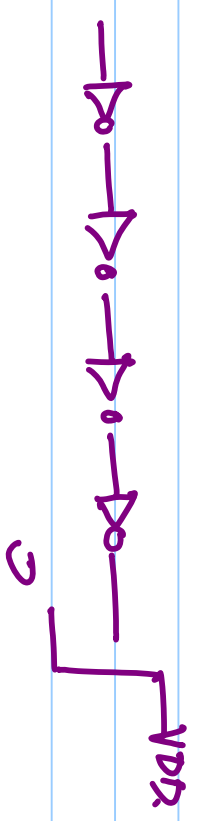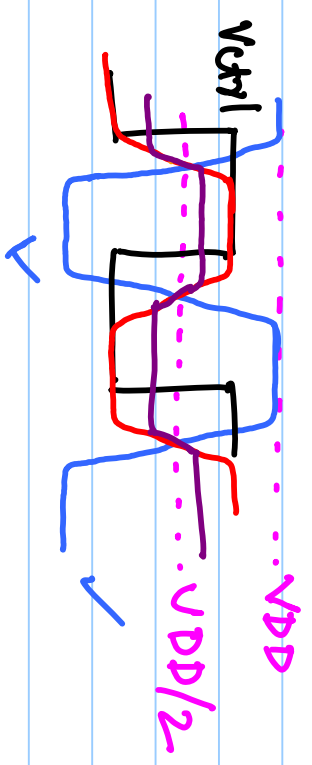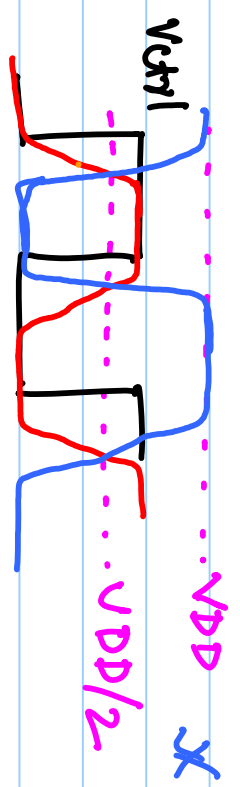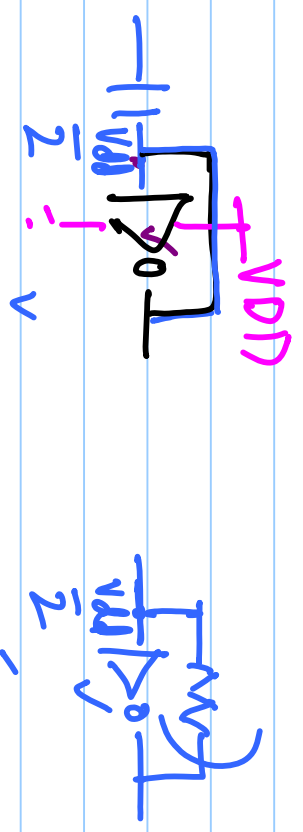

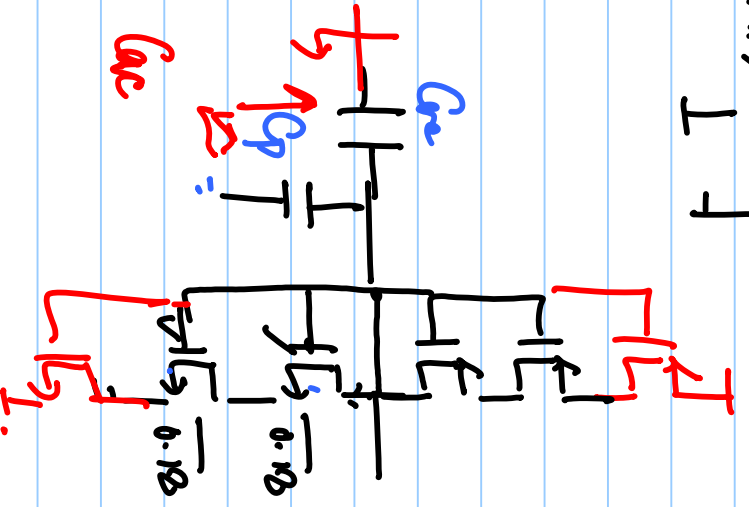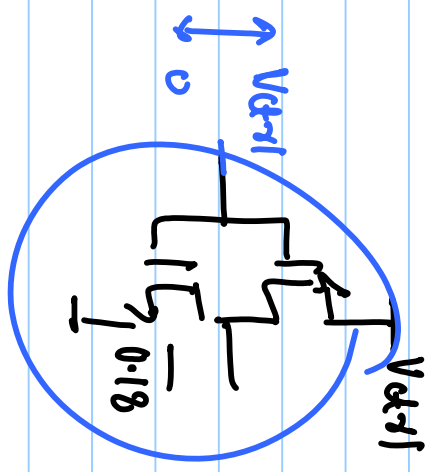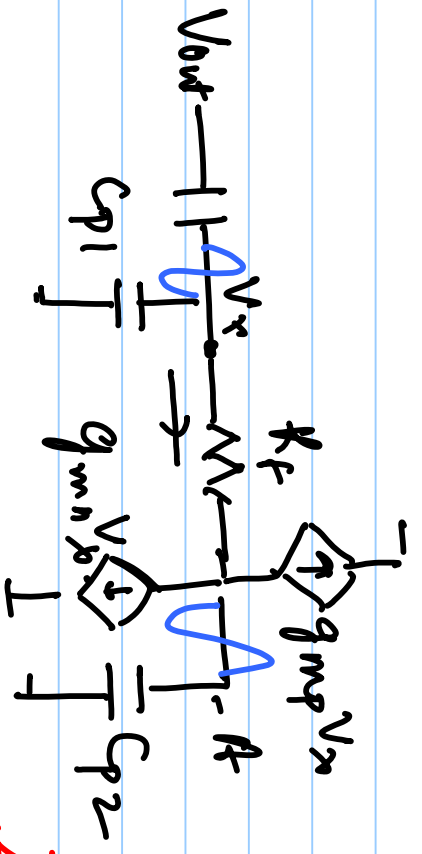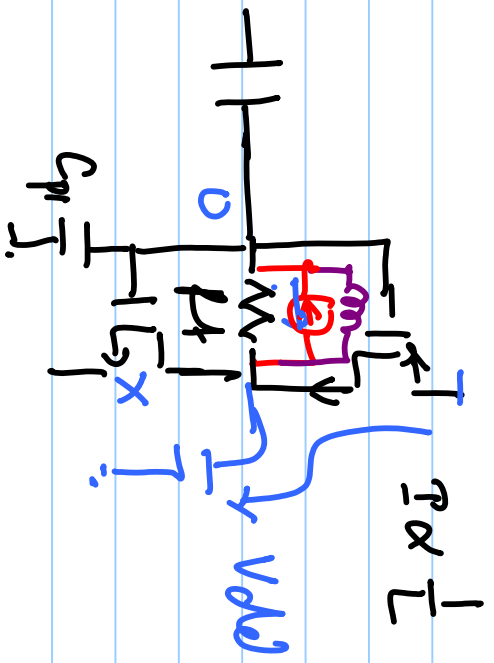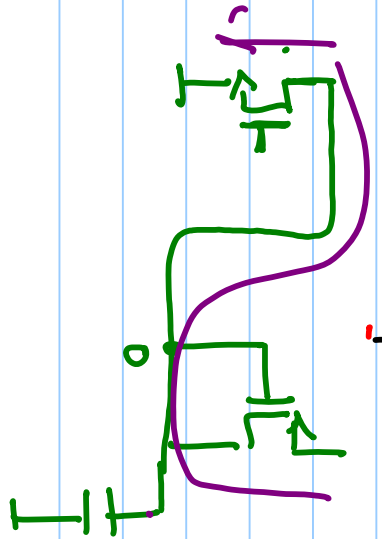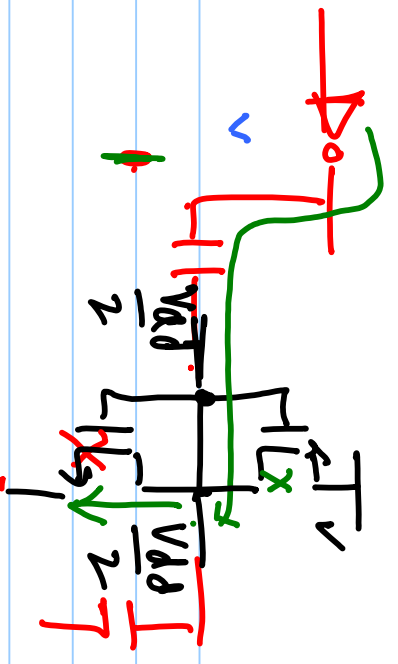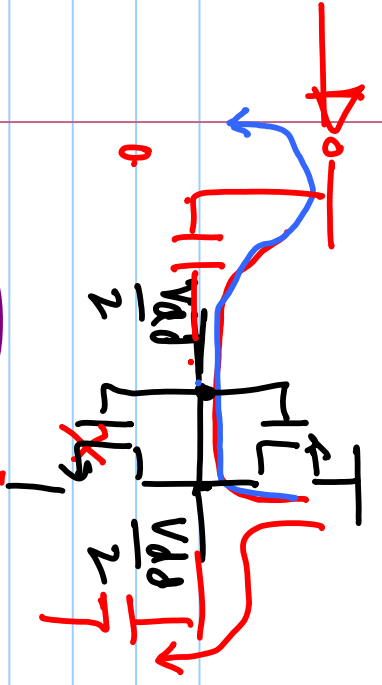

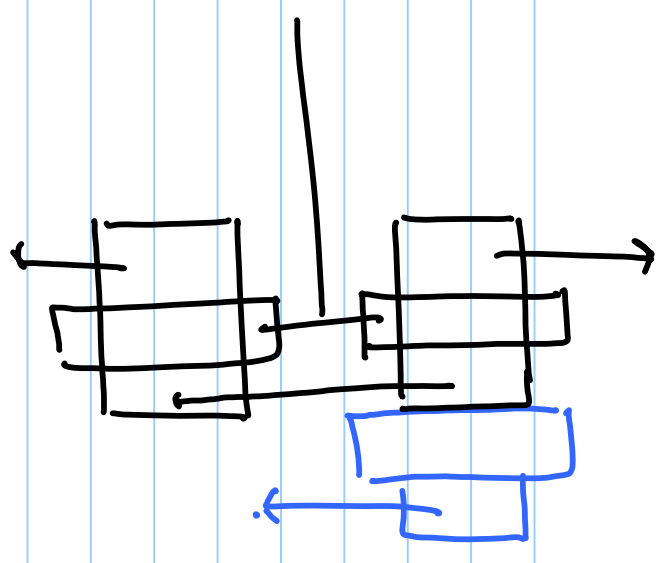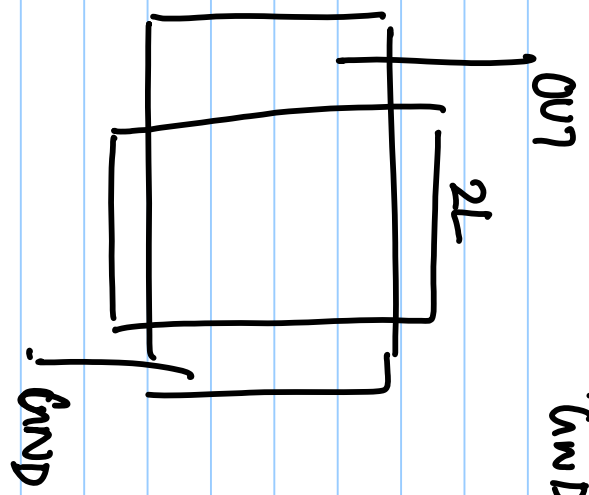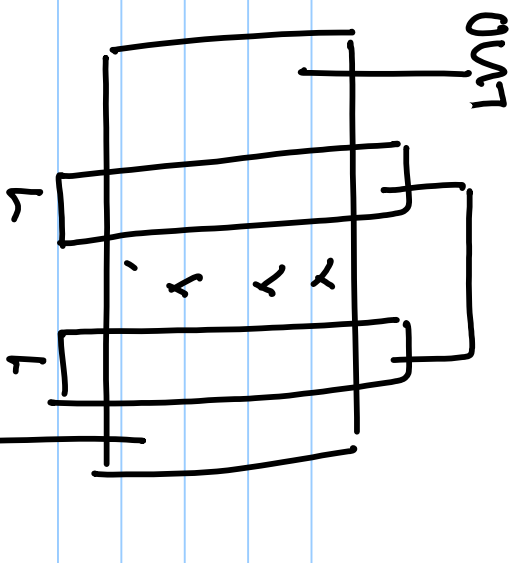

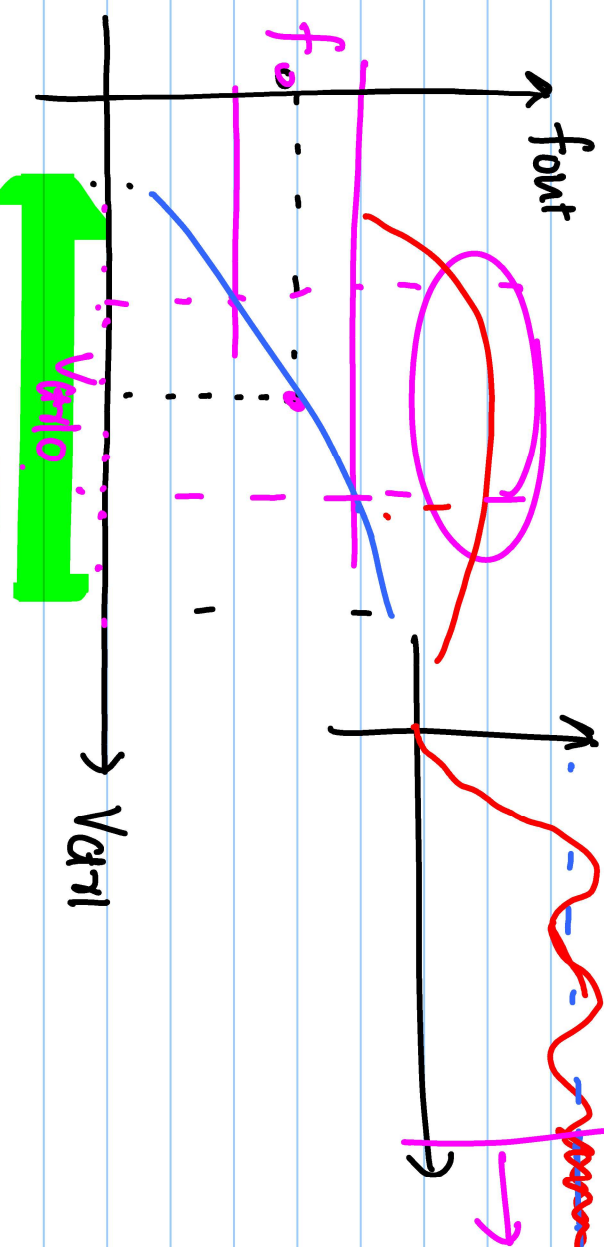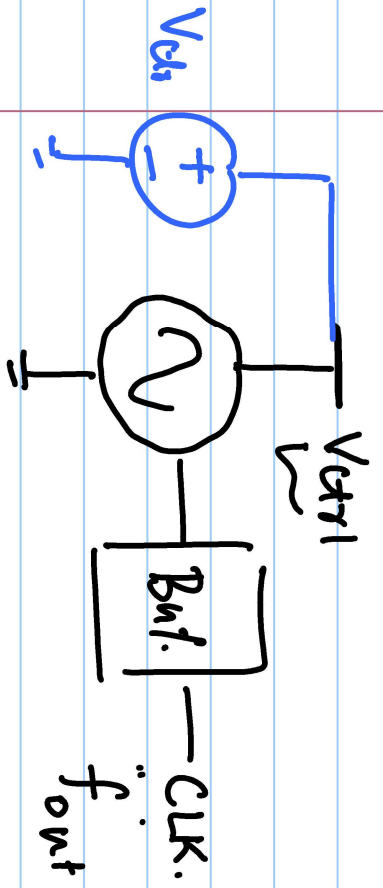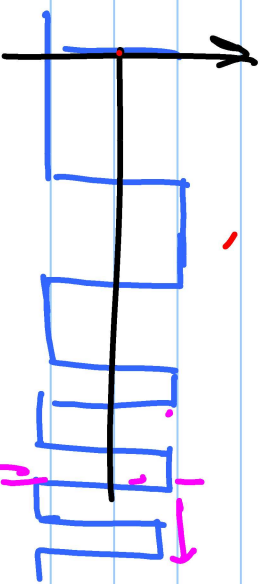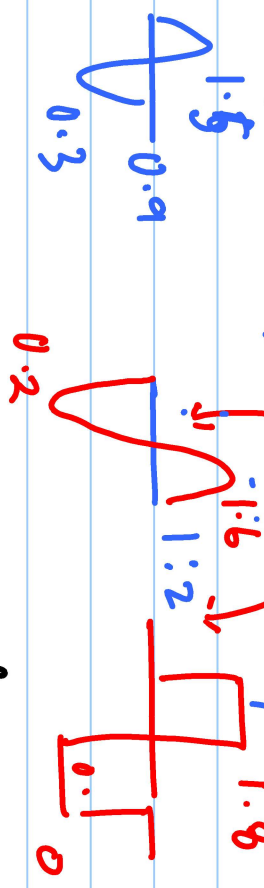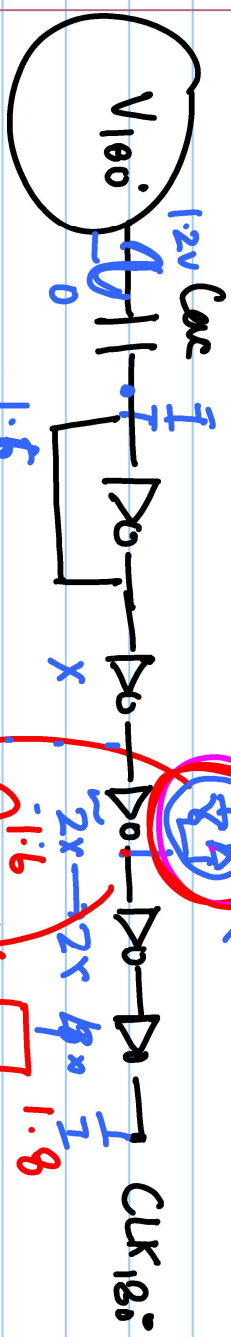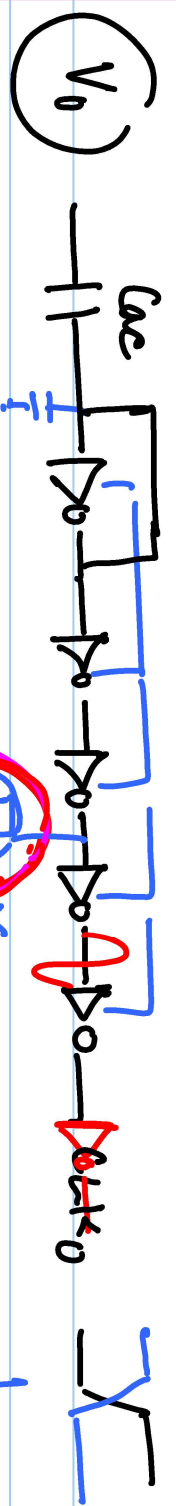

- transient simu.
- freq. / frequency.

$$K_{vfo} = \frac{df_{out}}{dV_{ctrl1}}$$