
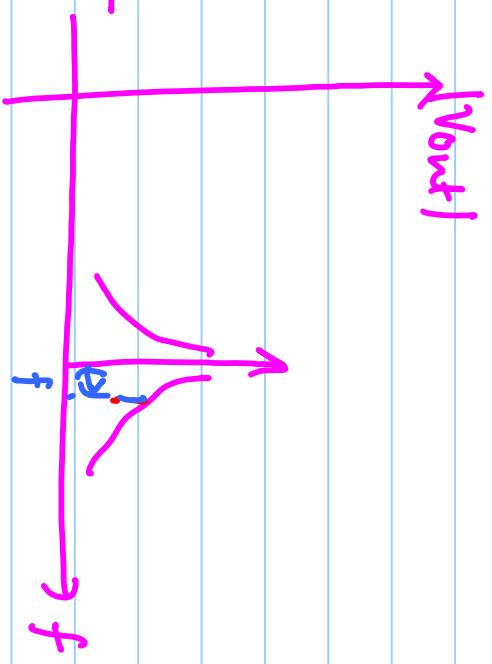



Lecture # 28

Phase Noise in Ring Osc.

$$L(f) = \frac{2fcT}{I} \left(\frac{1}{V_{DD}-V_T} (\gamma_N + \gamma_P) + \frac{1}{V_{DD}} \right) \left(\frac{f_0}{f} \right)^2$$
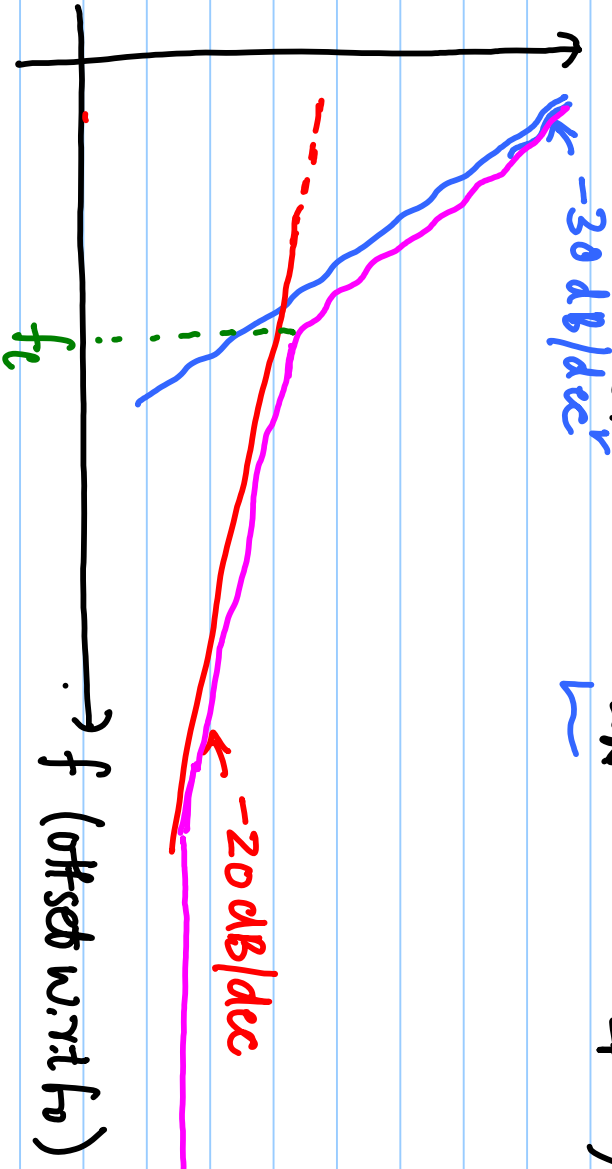
$$+ \frac{C_{ox}}{8MI} \left(\frac{\mu_n K_{tn}}{L_n^2} + \frac{M_p K_{tp}}{L_p^2} \right) \left(\frac{f_0}{f} \right)^3$$



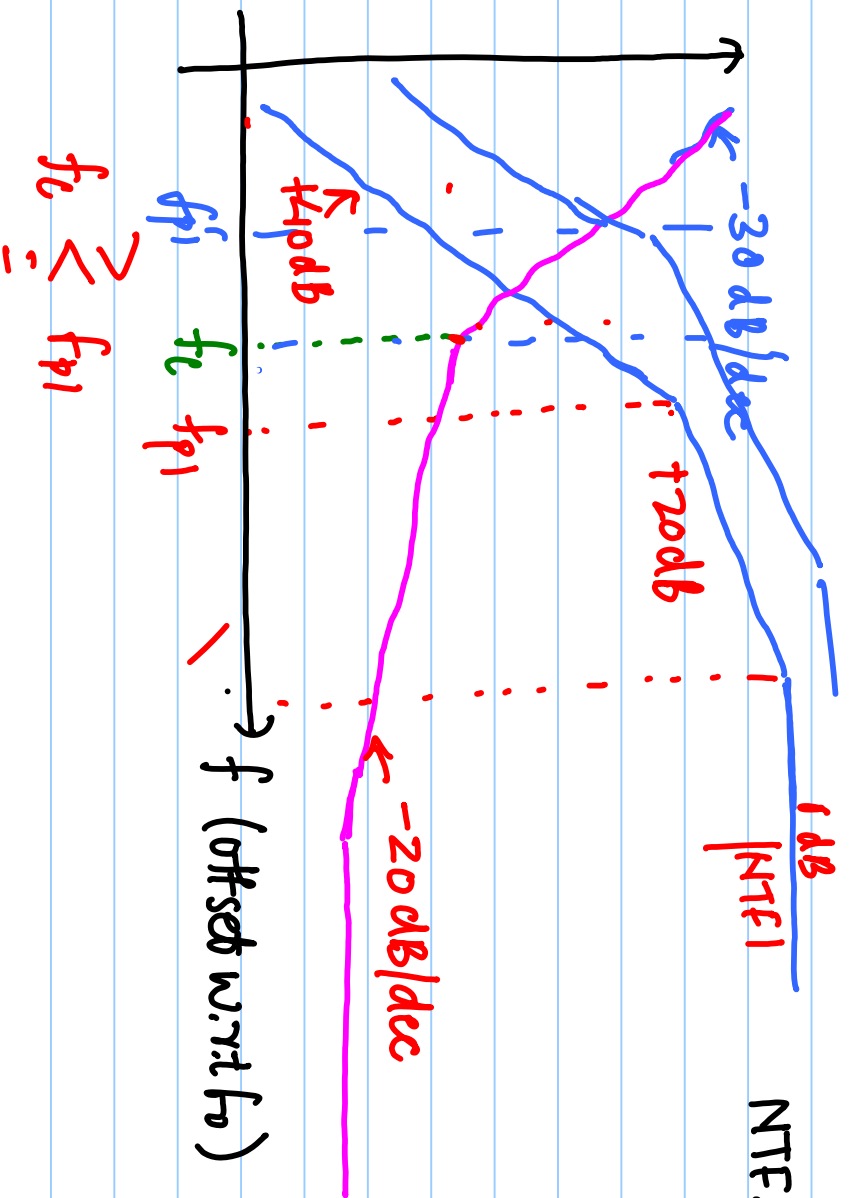

$$NTF_{vco} = \frac{1}{1+Ln}$$

$$= \frac{1}{1 + \frac{I_{cp}}{2\pi} \frac{2\pi K_{vco}}{\omega N} \frac{(1+sRC_1)}{(1+sRC_2/c_1\tau_2)}}$$


$$\approx \frac{1}{\omega(C_1\tau_2)}$$

$$= \omega^2 N (C_1\tau_2) \left(1 + \frac{sRC_1}{c_1\tau_2}\right)$$

$$\frac{(C_1\tau_2) \omega^2 N \left(1 + \frac{sRC_1}{c_1\tau_2}\right) + 2K_{vco} (1+sRC_1)}{}$$

$$\approx \frac{\omega^2 N C_1}{\omega^2 N C_1 + \frac{2K_{vco}}{c_1} (1+sRC_1)}$$

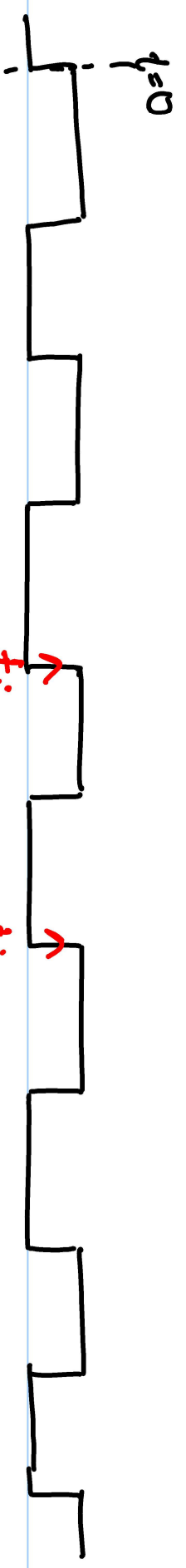
Period Jitter, $\sigma_c^2 = \int_0^\infty S_c(f) df = \int_0^\infty S_q(f) \frac{\sin^2(\pi f/f_0)}{(\pi f_0)^2} df$



N \Rightarrow avg. time period. (T)

Time period $T_i = t_{i+1} - t_i$

$$E[(T_i - T)^2] = \sigma_c^2$$

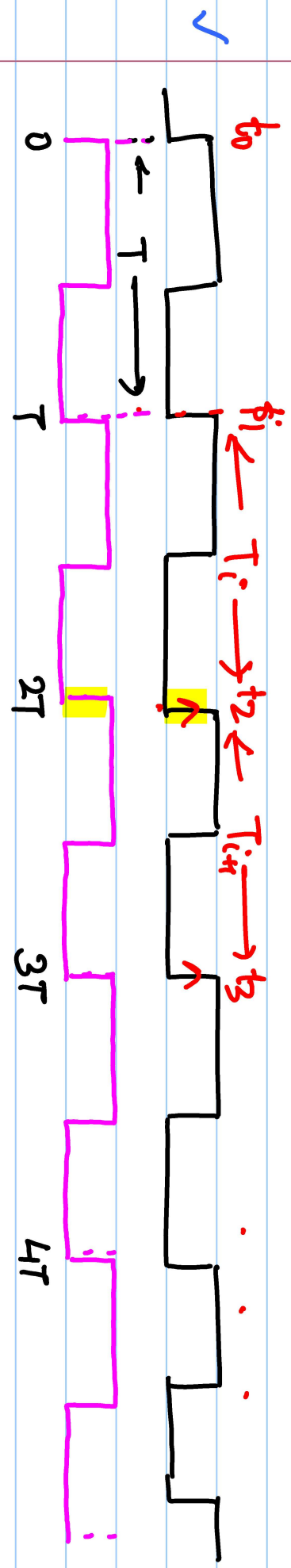

$$\Delta t_i = t_i - i \cdot T \quad (T \text{ I.E: time interval error})$$

$$\sigma^2 = E[\Delta t_i^2] = \int_0^\infty K(f) df \quad (\text{long-term absolute jitter})$$

or accum. v. loked jitter)

Cycle-to-cycle Period Jitter = $E[\Delta t_i^2]$

$$\Delta t_{i_c \rightarrow i_{H,c}} = T_{i_{H+1}} - T_i$$

Sample size.

σ

error $\sigma_n / \sqrt{2N}$

10^1


± 1.282

10^4



± 3.719

10^{12}

± 7.035

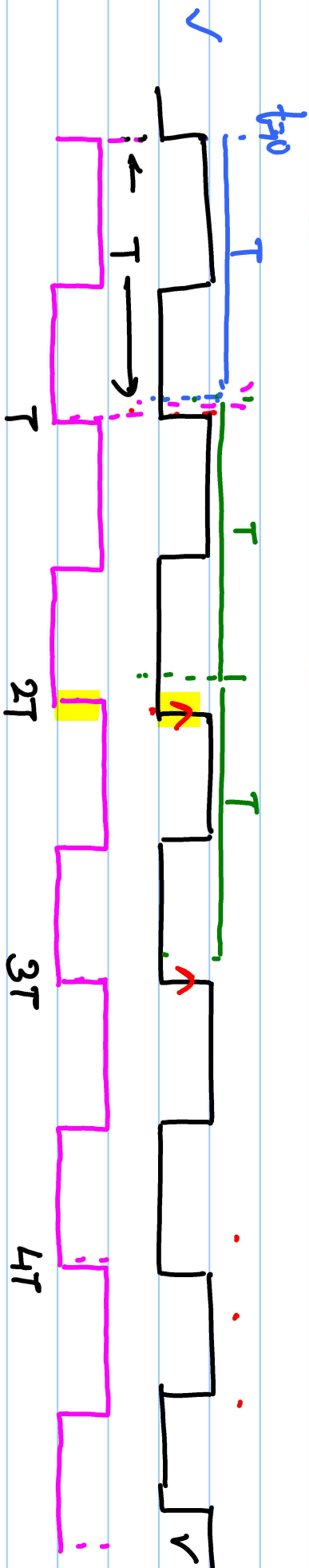

Eye diagram.

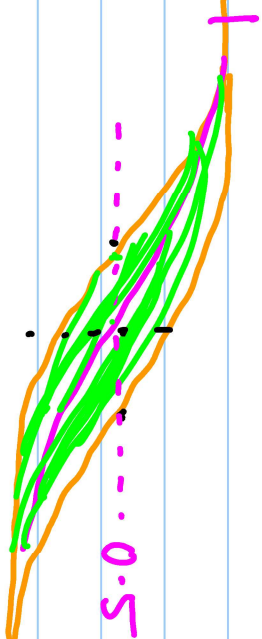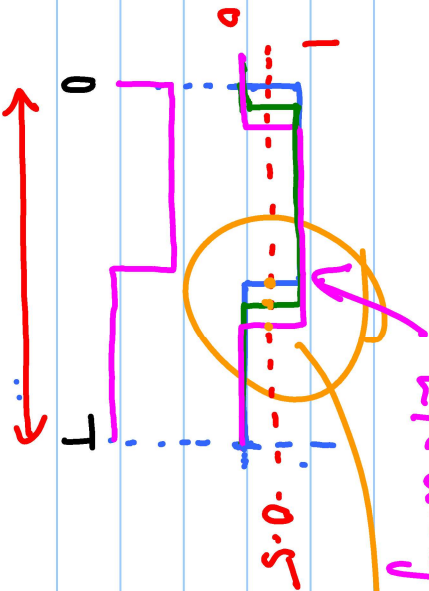



Probability Dist. fn.

$\mu, \sigma, pk-p/c.$




Building Blocks of PLL


- Operating frequency.

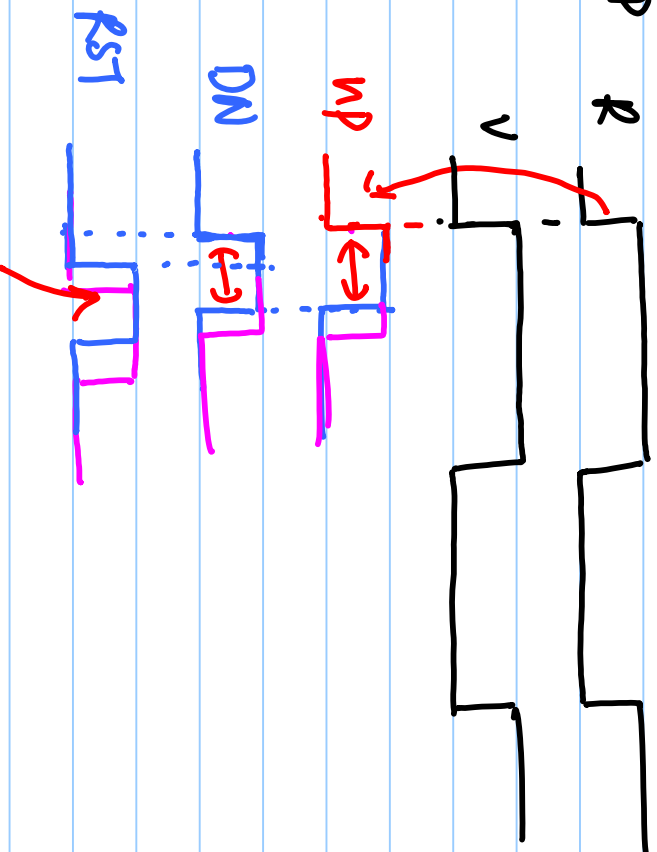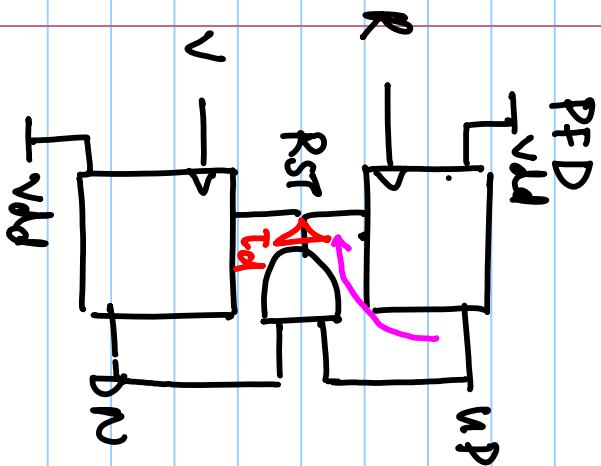

$$T_{RST} = T_{nand2} + T_{RST-Q} + T_d$$
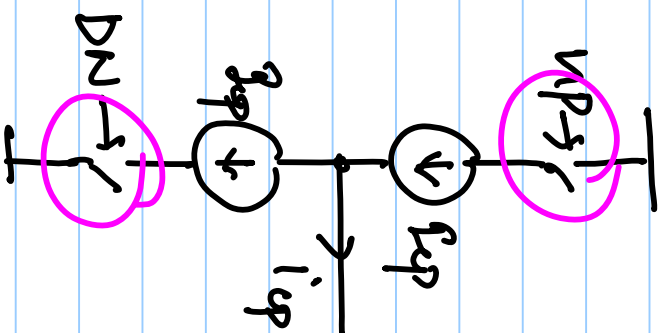
$$T_{low} = T_d T_{nand2} + T_{RST-Q} \gg T_{min}$$




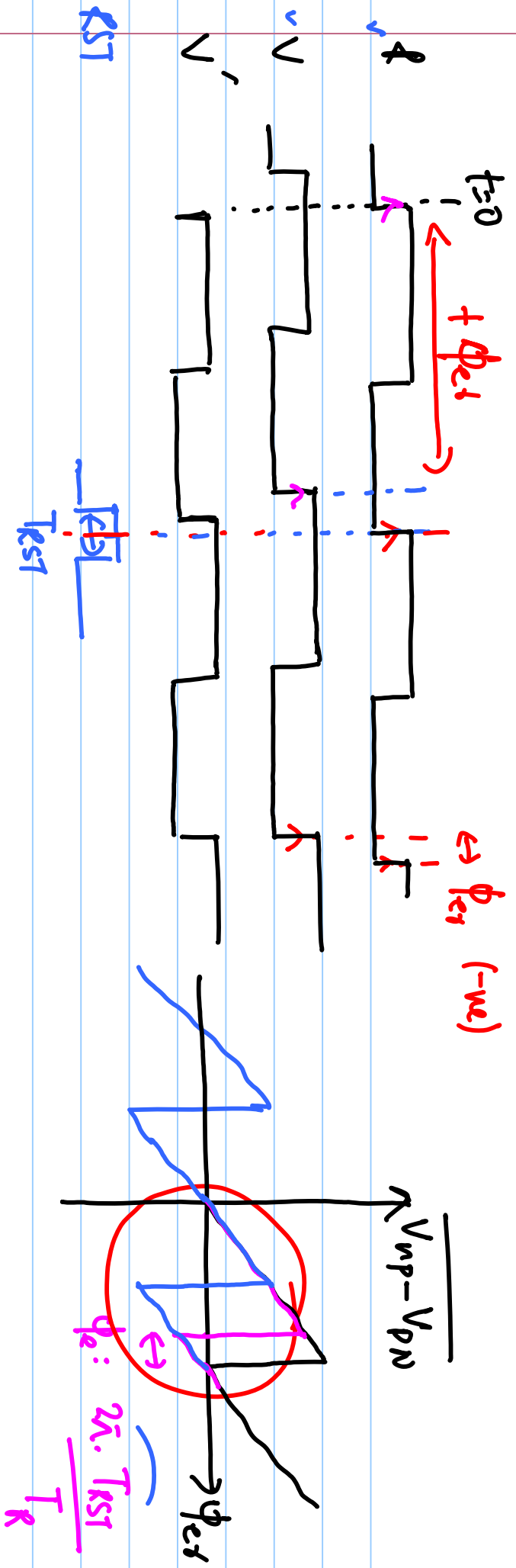


X
transmission

$$\phi_e = 2\pi \cdot \frac{T_{RST}}{T_R}$$


$$T_{RST} < T_R/2$$

$$\Rightarrow f_R < \frac{1}{2T_{RST}}$$

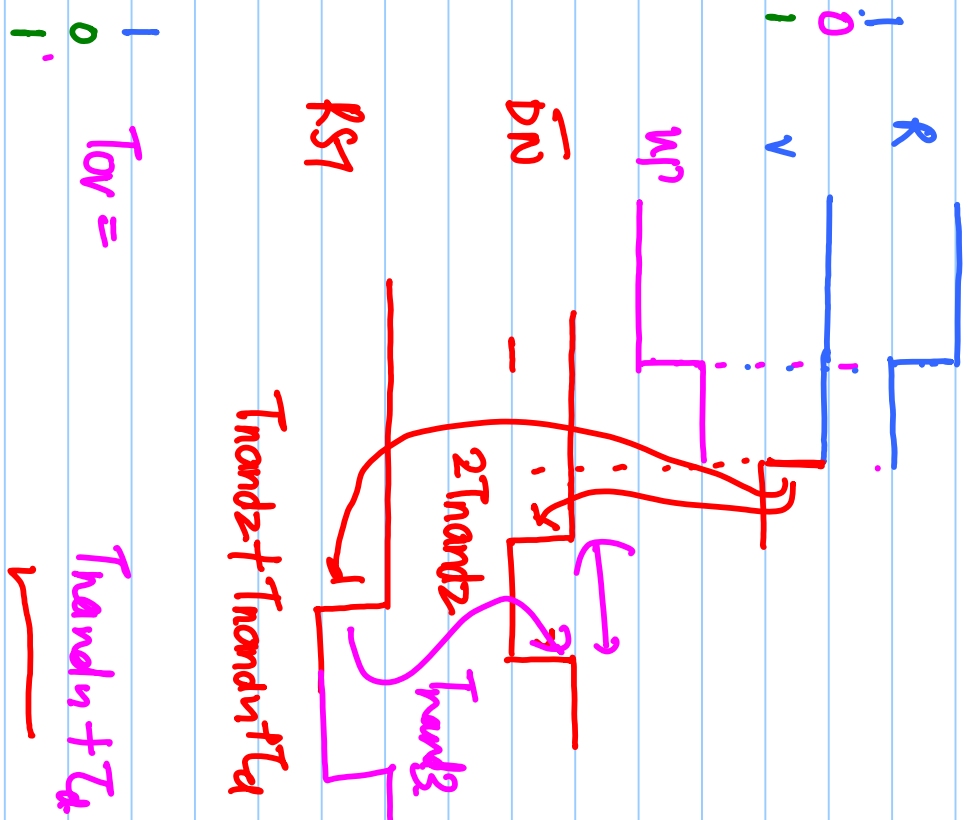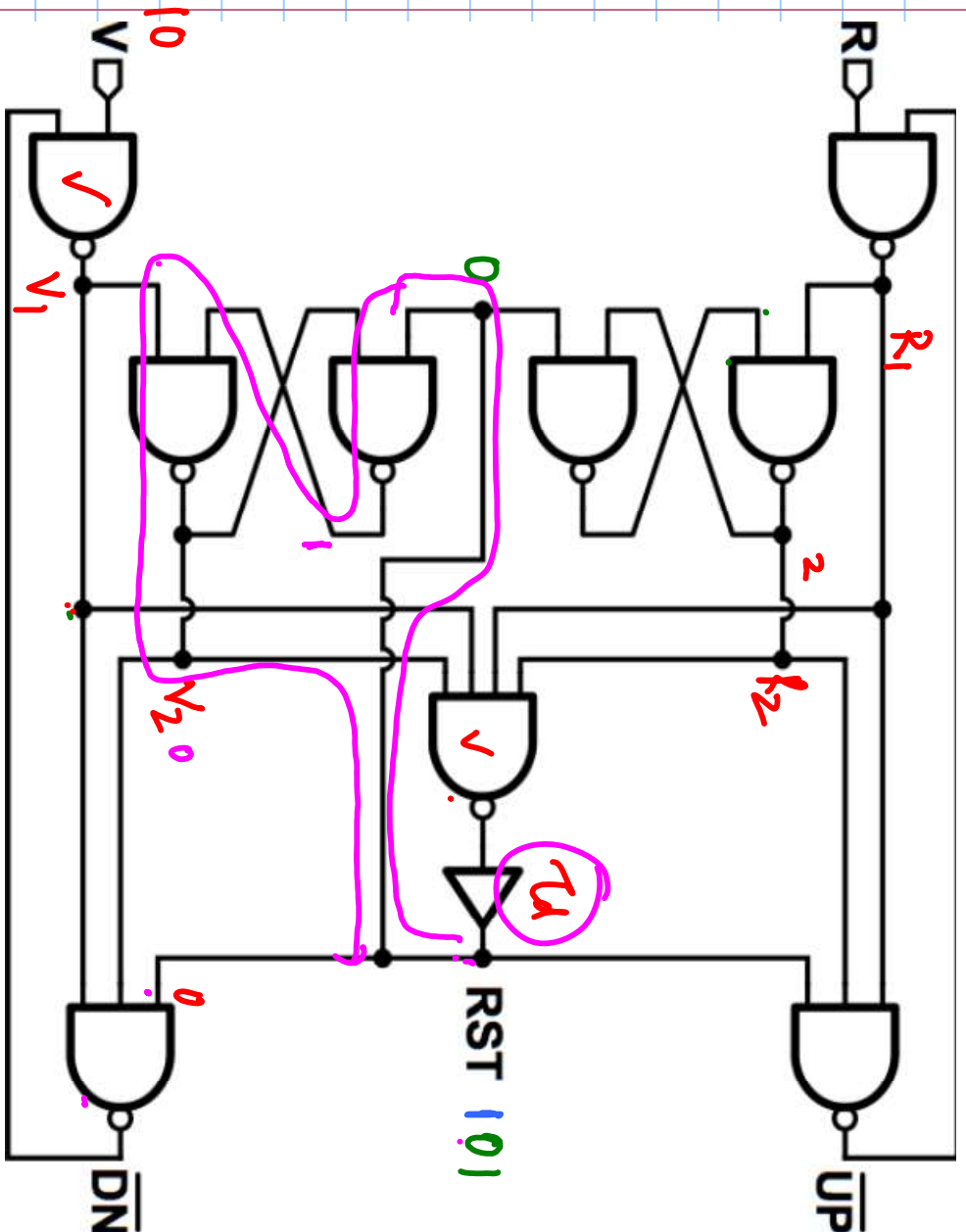

$T_{RST} = 2T_{AND2} + T_{AND4} + T_Q$

$T_{OV} = T_{AND4} + T_Q$

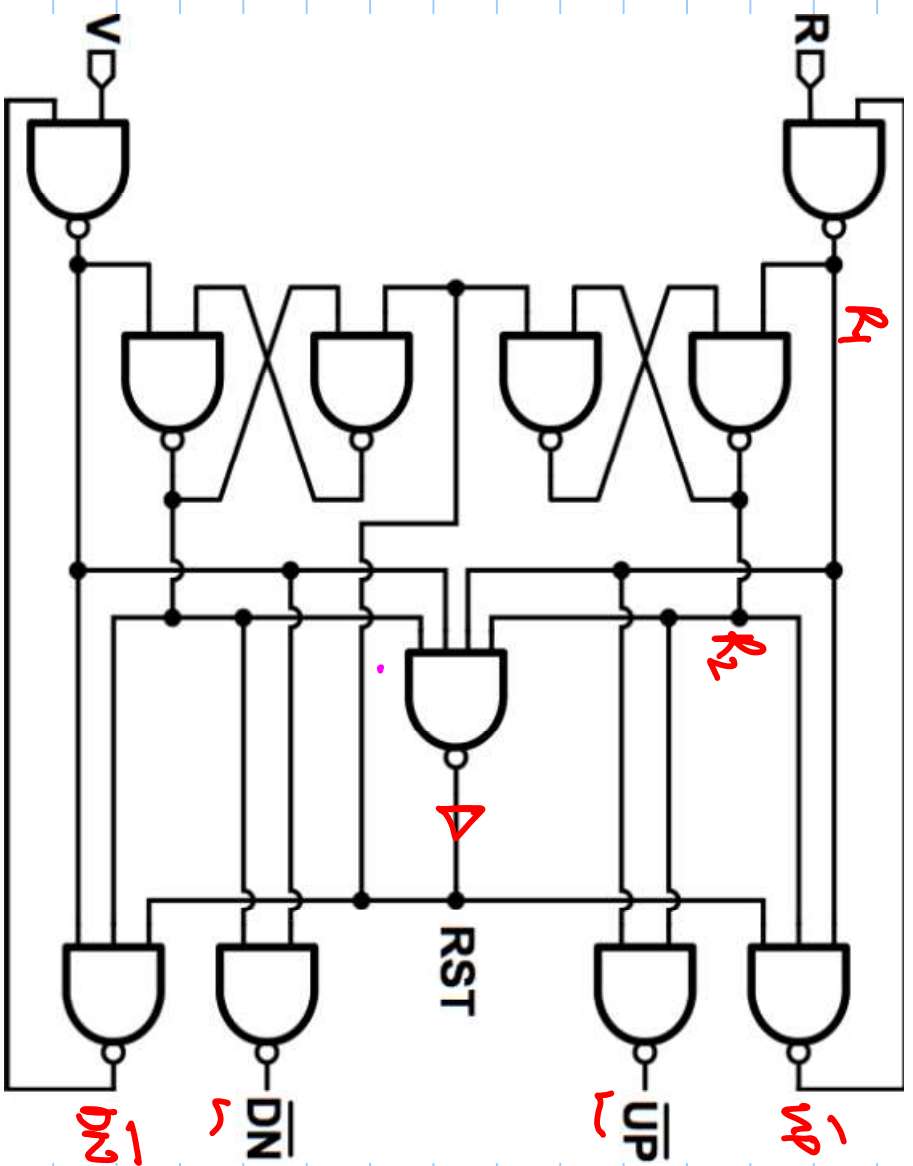

$$T_{OV} \approx 2T_{AND2} + T_{AND1}$$

$$T_{RST} = 2T_{AND2} + T_{AND1}$$