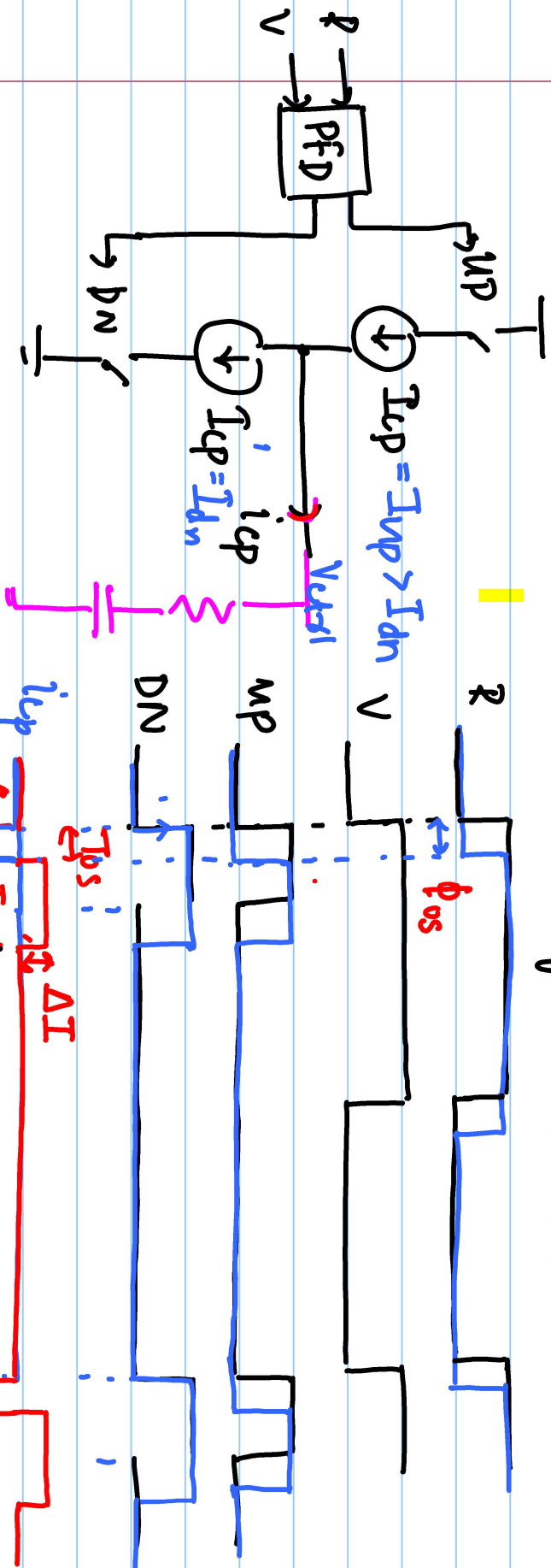


Charge Pump.


- In steady state, $\phi_{es} = 0$



$$\Delta I = I_{up} - I_{dn}$$

$$I_{dn} \cdot T_{os} = \Delta I \cdot T_{ov}$$



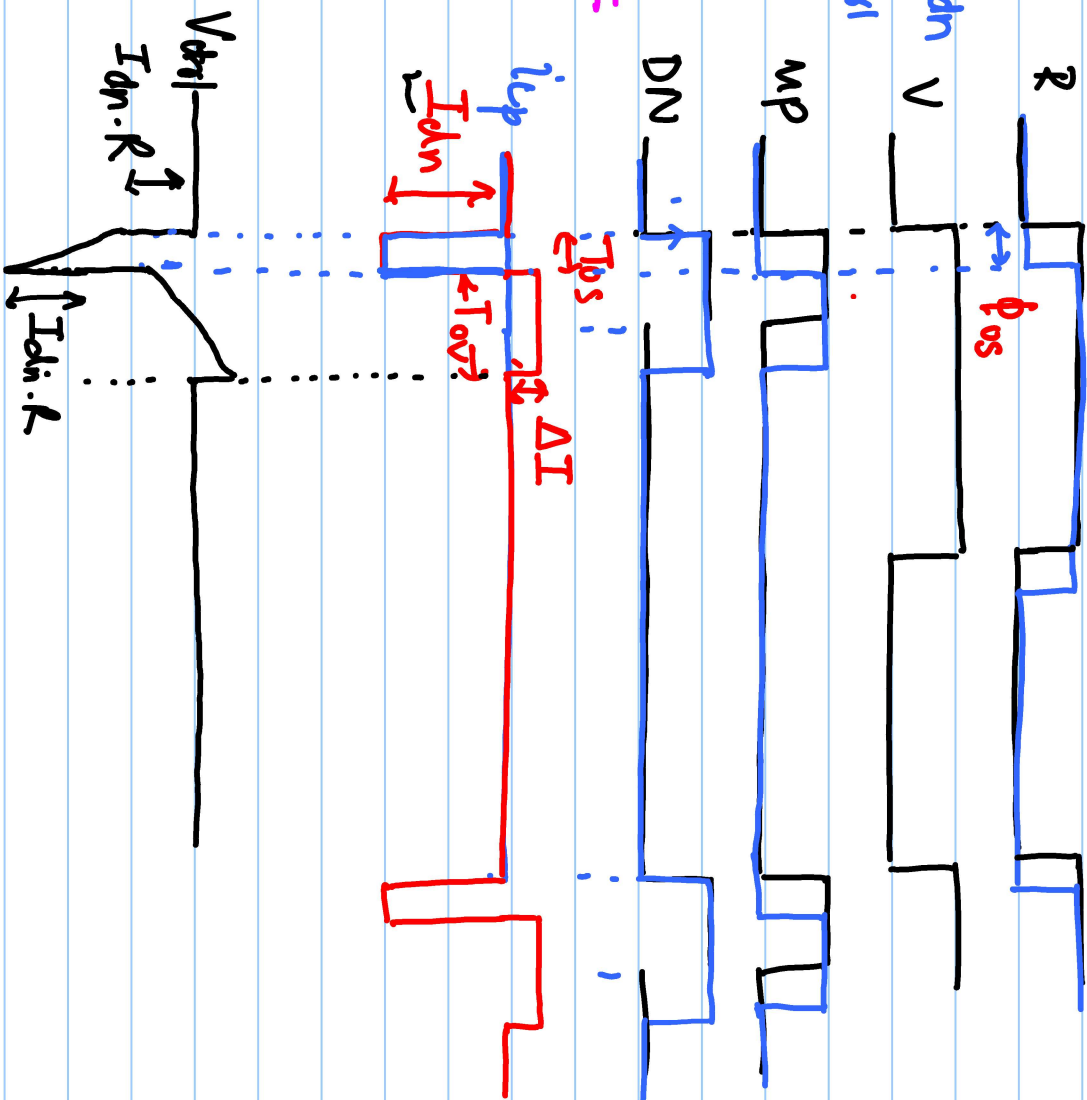
$$T_{os} = \frac{\Delta I}{I_{dn}} \cdot T_{ov}$$



$$2\pi \frac{T_{os}}{T_R} = \frac{\Delta I}{I_{cp}} \quad 2\pi \cdot \frac{T_{ov}}{T_R}$$

$$\phi_{os} = \frac{\Delta I}{I_{cp}} \cdot 2\pi \cdot \frac{T_{ov}}{T_R}$$

$$\frac{1}{T} \int_0^T i_c dt = I_c$$

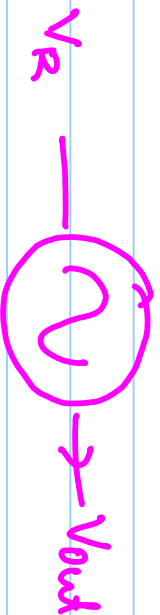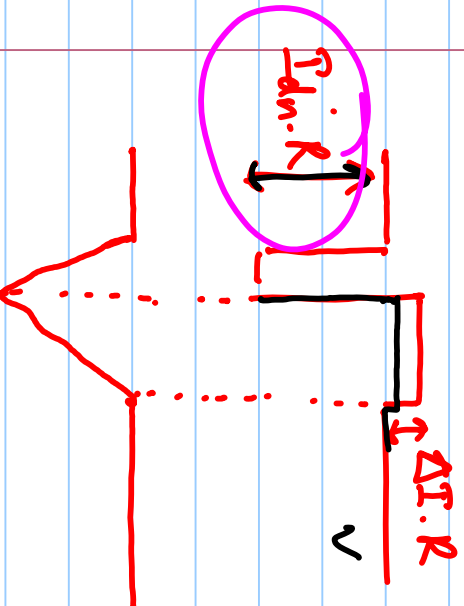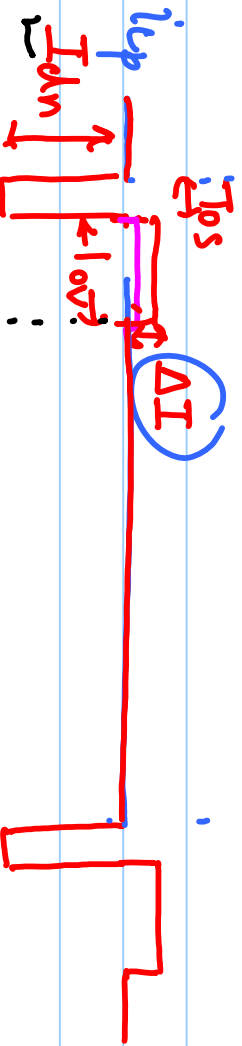


$$f_{vco} = f_0 + K_{vco} \cdot V_c$$

$$V_{c(s)} = i_{cp}R + \frac{1}{C} \int i_{cp} dt$$

$$\frac{1}{C} \int_0^{T_{os}} I_{dn} dt = \frac{1}{C} \int_0^{T_{ov}} \Delta I dt$$
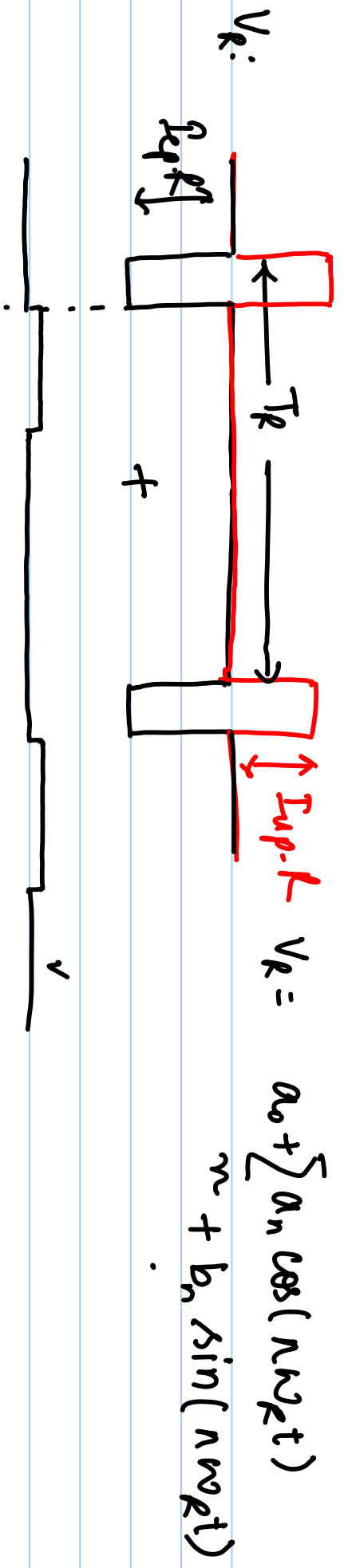
$$V_{out} = \sin(\omega_0 t + \int K_{vco} \cdot V_c dt)$$



$$a_0 = -I_{dn} R \frac{T_{os}}{T_R}$$

$$a_n = -\frac{2I_{dn} \cdot R}{n\pi} \sin\left(n\pi \frac{T_{os}}{T_R}\right)$$

$$V_{RH}(t) \approx -I_{dn} R \frac{T_{os}}{T_R} - \frac{2I_{dn} \cdot R}{\pi} \sin\left(\frac{\pi T_{os}}{T_R}\right) \cos(\omega_R t)$$

$$V_{out} = \sin(\omega_0 t + \underbrace{\int \frac{2I_{up} \cdot R}{\pi} \sin\left(\frac{\pi T_{os}}{T_R}\right) K_{v10} \cdot \cos(\omega_R t) dt}_{\bar{A}})$$


$$= \sin(\omega_0 t + \frac{2I_{up} \cdot R}{\pi} K_{v10} \sin\left(\frac{\pi T_{os}}{T_R}\right) \int \cos(\omega_R t) dt)$$

$$\begin{aligned}
 & : \sin(\omega_0 t + \frac{\beta}{2} \cdot 2 \sin(\frac{\kappa T_{os}}{T_R})) \frac{\sin(\omega_R t)}{\omega_R} \\
 & = \sin(\omega_0 t + \frac{\beta'}{2} \cdot 2 \sin(\frac{\kappa T_{os}}{T_R})) \sin(\omega_R t) \\
 & = \sin(\omega_0 t) \cdot \cos(\frac{\beta'}{2} \cdot 2 \sin(\frac{\kappa T_{os}}{T_R})) \sin(\omega_R t) \\
 & \quad + \cos(\omega_0 t) \sin(\frac{\beta'}{2} \cdot 2 \sin(\frac{\kappa T_{os}}{T_R})) \sin(\omega_R t)
 \end{aligned}$$


$$\approx \sin(\omega_0 t) \cdot 1 + \cos(\omega_0 t) \cdot \frac{\beta'}{2} \cdot 2 \sin(\frac{\kappa T_{os}}{T_R}) \sin(\omega_R t)$$

$\theta \Rightarrow \sin(\theta) \approx \theta, \cos(\theta) = 1$
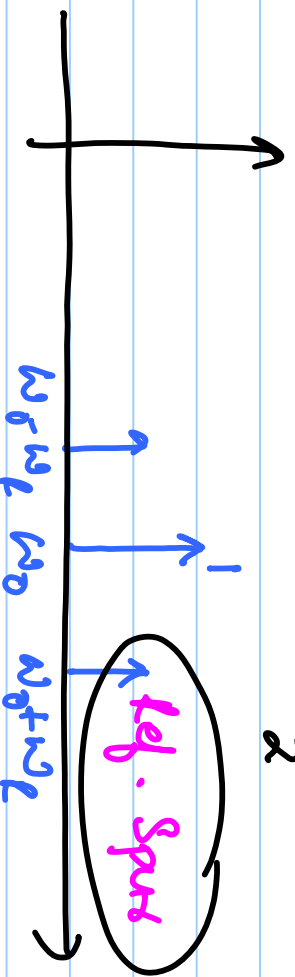
$$= \sin(\omega_0 t) + \frac{\beta'}{2} \cdot \frac{\kappa \cdot T_{os}}{T_R} [\sin(\omega_0 + \omega_R t) - \sin(\omega_0 - \omega_R t)]$$


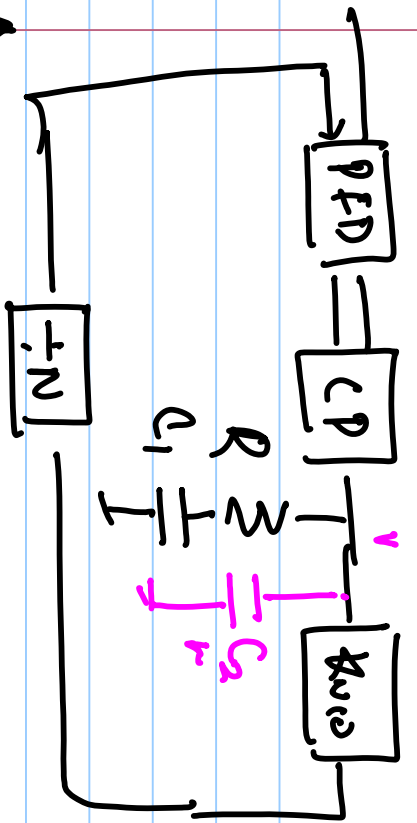
$$\frac{\beta'}{2} \cdot \frac{\kappa \cdot T_{os}}{T_R} = \frac{2 \text{Imp} \cdot R \cdot K_{VCO} \cdot \kappa \cdot T_{os}}{2 \omega_R \cdot T_R}$$




$$= \frac{2f_{up} \cdot R \cdot K_{vco}}{2 \cdot 2\pi f_R} \frac{\phi_{os}}{2}$$

$$= \frac{1}{2} \left(\frac{2f_{up} \cdot R \cdot K_{vco} \cdot \phi_{os}}{2\pi \cdot f_R} \right)$$

$$\rightarrow = \frac{1}{2} \left(\frac{2 \cdot f_{BW} \cdot N \cdot \phi_{os}}{2\pi f_R} \right)$$

Rel. Spur \propto $F_{BW} \propto$ ϕ_{os}

$$\propto \frac{1}{F_R}$$


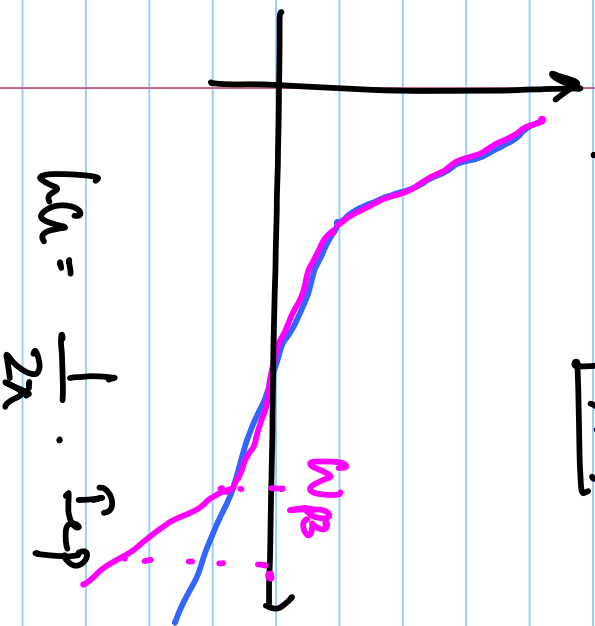


$$W_u = \frac{1}{2\pi} \cdot f_{up} \cdot \left(R + \frac{1}{R_1} \right) \frac{2\pi K_{vco}}{s} \frac{1}{N}$$

$$= \frac{f_{up} (1 + sRC_1) K_{vco}}{s^2 C_1 N} \times \frac{1}{\left(1 + \frac{sRC_1 C_2}{C_1 C_2} \right)}$$

$$|W_u(j\omega_n)| \approx 1 \Rightarrow \frac{f_{up} \cdot (2\pi \cdot R \cdot C_1) K_{vco}}{\omega_n^2 C_1 N} = 1 \Rightarrow \omega_n = \frac{f_{up} K_{vco} \cdot R}{N}$$
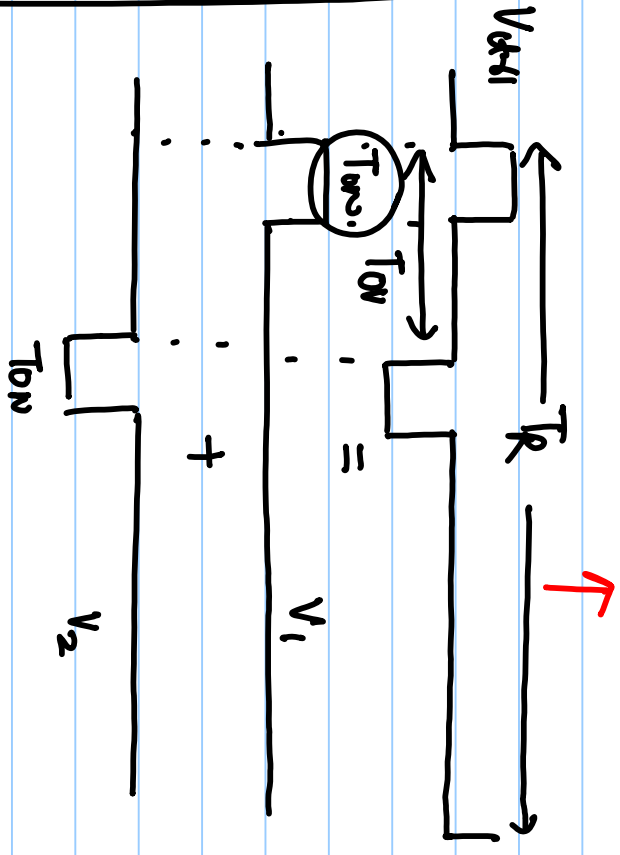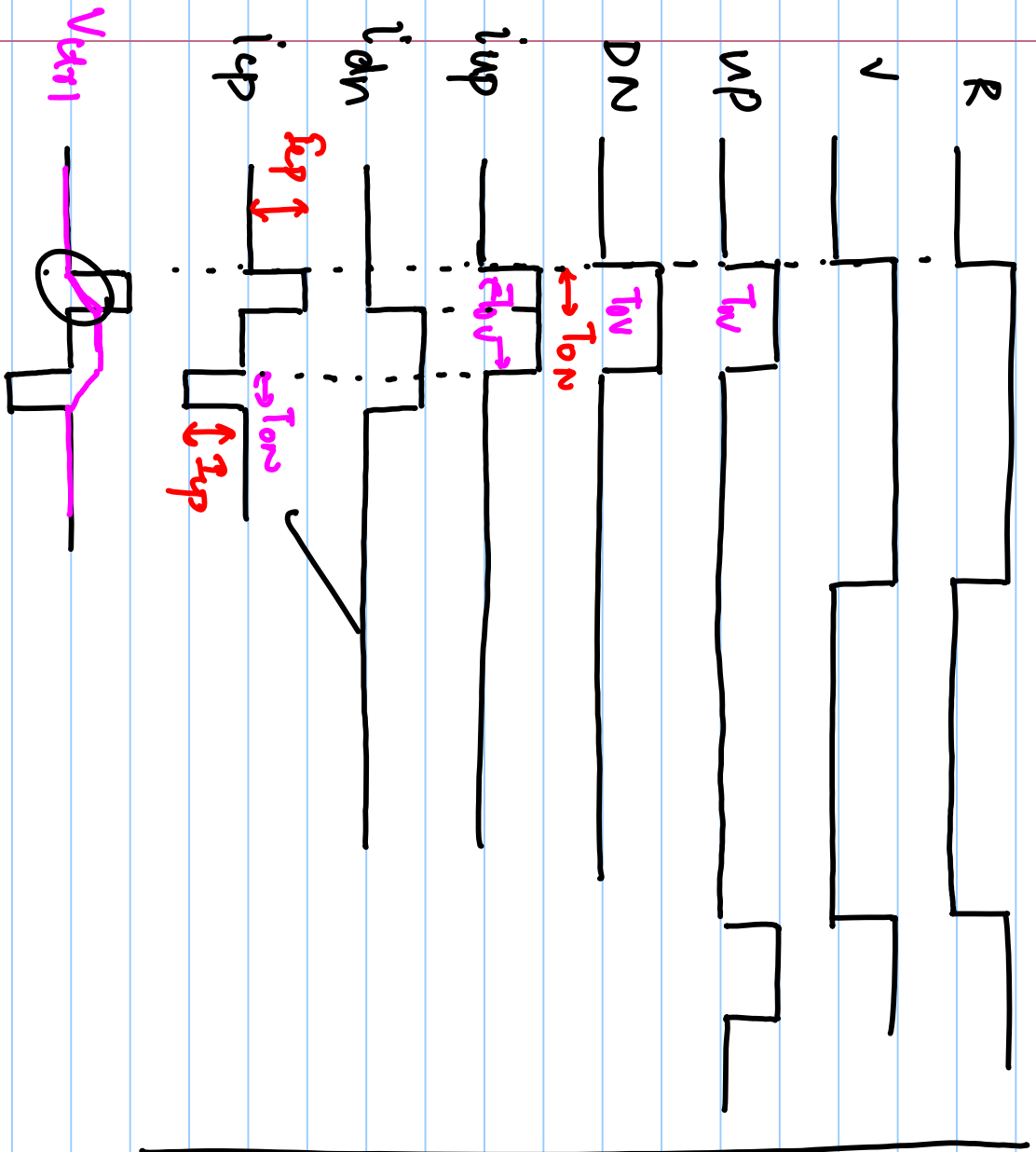
$$S_{pwr} P_{spwr} = 20 \log_{10} \left(\frac{f_{BW}}{F_R} \cdot N \cdot \phi_{os} \right) - 20 \log_{10} \left(\frac{F_L}{F_{P3}} \right)$$



$$V_1(t) = a_0 + \sum a_n \cos(n\omega_c t) + b_n$$

$$V_2 = -V_1(t - T_{ov})$$

$$V_1(t) \rightarrow V_1(s)$$


$$V_2(t) \rightarrow -V_1(s) e^{-sT_{ov}}$$

$$V_1 + V_2 = V_1(s) (1 - e^{-sT_{ov}})$$


$$\approx V_1(x) \left(\frac{\Delta \cdot T_{ov}}{T_r} \right)$$

$$V_1' \left(\frac{\Delta \cdot T_{ov}}{T_r} \right)$$

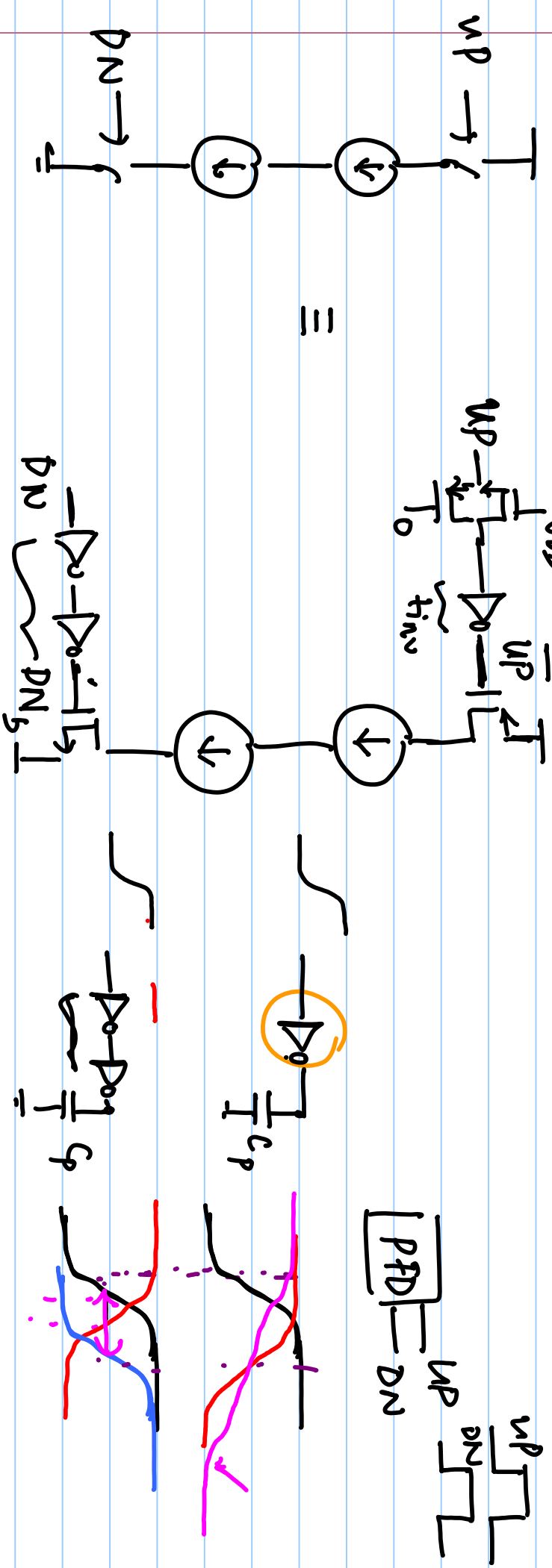
- Mismatch b/w up/dn current source should be minimized.
- Mismatch b/w on time of top/bottom current sources should be minimized.



Source-switched CP

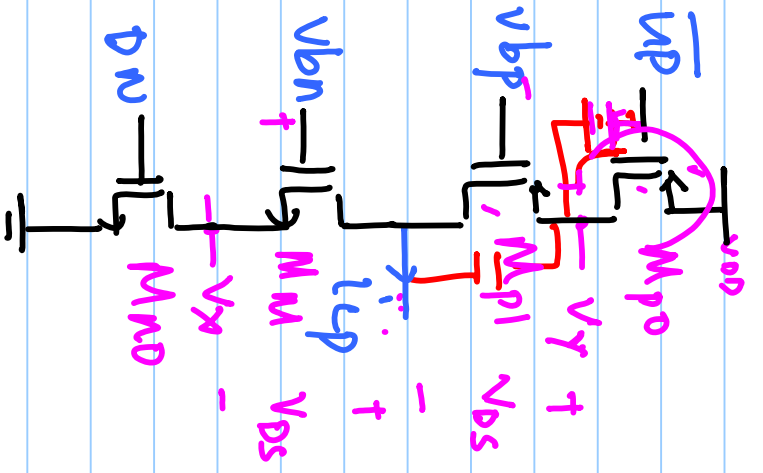

Drain-switched CP

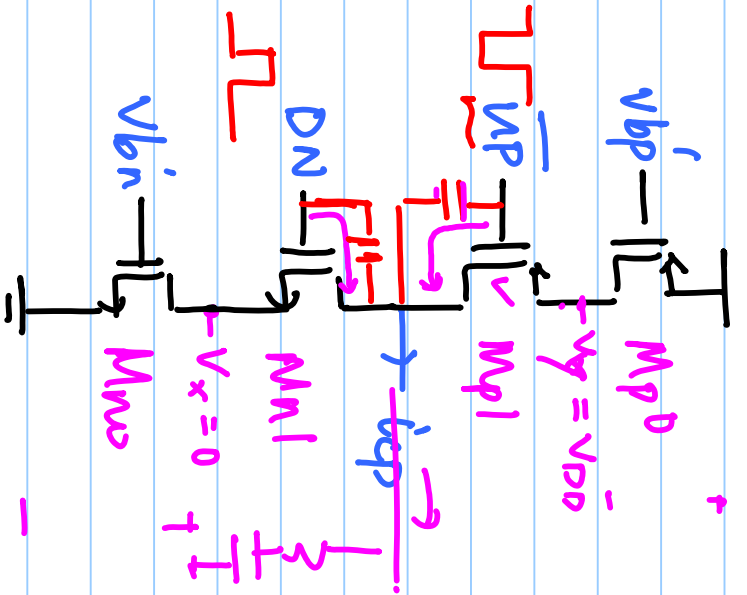

Gate-switched CP

