

EE 110 Basic Electrical Engg - HW I

August 11, 2010

- Use Ohm's law and Kirchoff's law to find the value R in the circuit shown in figure P1.1

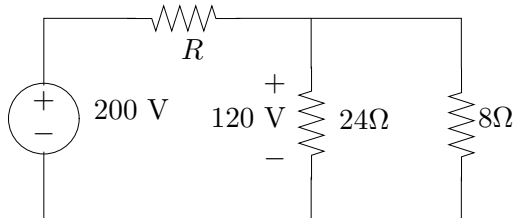


Figure P1.1

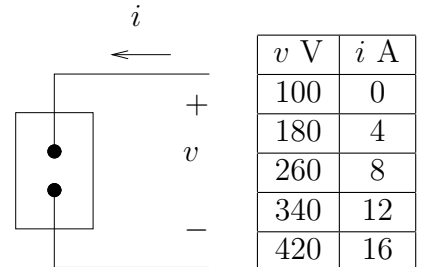


Figure P2.1

- The terminal voltage and terminal current were measured on the device shown in figure P2.1. The values of v and i are as given in the table. Use these to plot v vs. i and compute the equation of the line. Use the equation to construct a circuit model for the device using an ideal voltage source and a resistor. Further, use the model to predict the power that the device will deliver to a 20Ω resistor.
- The voltage and current at the terminals of an automobile battery during a charge cycle are shown in figure P3.1. Calculate the total charge transferred to the battery.

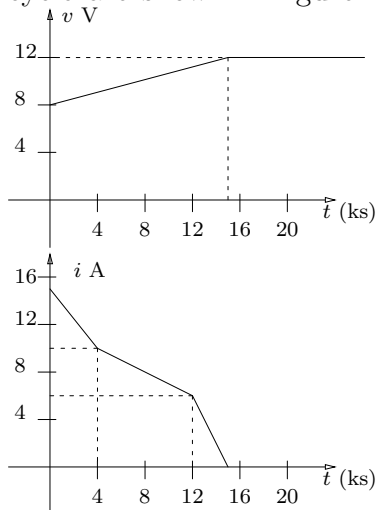


Figure P3.1

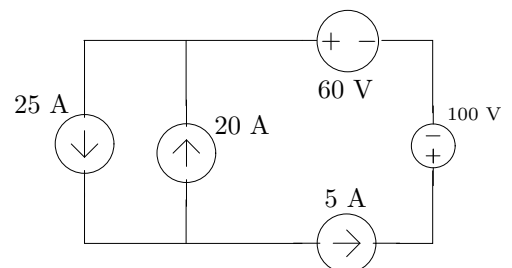


Figure P4.1

- If the interconnection in figure P4.1 is valid, find the total power delivered/consumed by each source in the circuit. If the interconnection is not valid, explain why.

5. For the circuit shown in figure P5.1 determine v_0 . Find the power delivered by (i) the 300 V source and (ii) 10 A source. Check to see if the total power delivered equals the total power consumed.

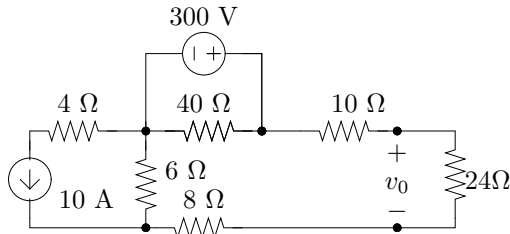


Figure P5.1



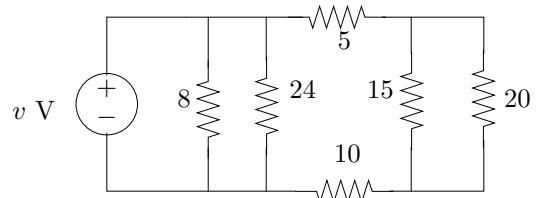


Figure P8.1

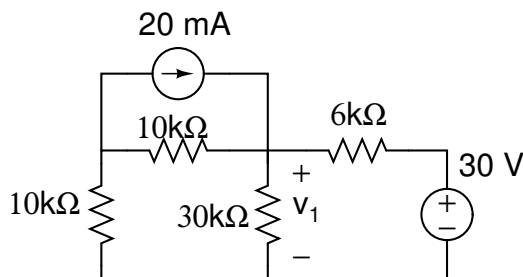6. An electric heater draws 1000 W from a 250-V source. How much power does it take from a 200-V source? What is the value of the resistance of the heater?
7. A blackbox contains an ideal voltage source and an ideal current source connected in parallel. What is the overall behavior of this blackbox? That of a current source? Voltage source? Or, both?
8. For the circuit shown in figure P8.1, find the value v in V that will dissipate 180 W in the 20-Ω resistance. Values of the resistances shown are in Ohms. Further, determine the power delivered by the source.
9. Show how you could connect five 5Ω resistors, to get (a) $R_{eq} = 4 \Omega$, and (b) $R_{eq} = 6 \Omega$, all five resistors being connected in each case.
10. Use the superposition theorem to find the voltage v_1 in fig P10.1(a).
Use the superposition theorem to find the current i_1 in fig P10.1(b).



P10.1 (a)

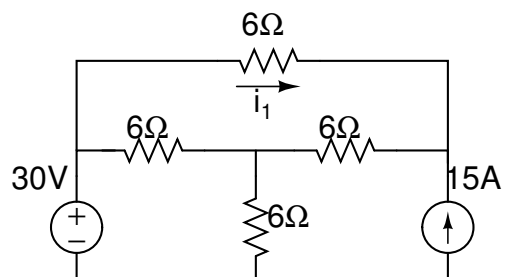

P10.1 (b)

— END —