

# EE2001 - Digital systems lab

## Synthesis and Implementation using an FPGA

Vinita Vasudevan



## Sequential Circuits: Blocking statements

### Shift Register

```

module sr( q, d );
    output [3:0] q;
    reg [3:0] q;
    input d;
    wire clock;

    clock c1( .c(clock) );

    always@(posedge clock)
        begin
            q[0] = d;
            q[1] = q[0];
            q[2] = q[1];
            q[3] = q[2];
        end
endmodule // sr

```

```

module clock( c );
    output c;
    reg c;
    initial
        begin
            c = 0;
        end
    always
        begin
            #5 c = ~c;
        end
endmodule // clock

```

### Wrong output!

0	clk=0	d=0	q = xxxx
4	clk=0	d=1	q = xxxx
5	clk=1	d=1	q = 1111
10	clk=0	d=1	q = 1111
14	clk=0	d=0	q = 1111
15	clk=1	d=0	q = 0000

At the positive edge, the input should be registered only in the first flip-flop. In this case, all flip-flops are set/reset.

## Non-blocking Statements

Solution: Use non-blocking statements.

module sr( q, d );	0	clk=0	d=0	q = xxxx
	4	clk=0	d=1	q = xxxx
output [3:0] q;	5	clk=1	d=1	q = xxx1
reg [3:0] q;	10	clk=0	d=1	q = xxx1
input d;	14	clk=0	d=0	q = xxx1
wire clock;	15	clk=1	d=0	q = xx10
	20	clk=0	d=0	q = xx10
clock c1( .c(clock) );	24	clk=0	d=1	q = xx10
	25	clk=1	d=1	q = x101
always@(posedge clock )	30	clk=0	d=1	q = x101
begin	34	clk=0	d=0	q = x101
q[0] <= d;	35	clk=1	d=0	q = 1010
q[1] <= q[0];	40	clk=0	d=0	q = 1010
q[2] <= q[1];	44	clk=0	d=1	q = 1010
q[3] <= q[2];	45	clk=1	d=1	q = 0101
end	50	clk=0	d=1	q = 0101
endmodule // sr	55	clk=1	d=1	q = 1011

Gather all the righthand side values before the edge and assign them to the left hand side variables after the clock edge. If blocking statements are used, the left hand side variables are assigned sequentially -  $q[1]$  is assigned after  $q[0]$  and so on.

## Counters - Behavioural Model

### Divide-by-two:

```

module clk_divide (Count, clk, reset);
  output Count;
  reg [3:0] Counter; //4 bit counter

  assign Count = Counter[1]; //pick 2nd bit
  always @ (negedge clk)
  begin
    if (!reset)
      begin
        Counter <= 0
      end
    else
      begin
        Counter <= Counter+1;
      end
    end
  end
endmodule

```

0	clk=0	Count=0
5	clk=1	Count=0
10	clk=0	Count=0
15	clk=1	Count=0
20	clk=0	Count=1
25	clk=1	Count=1
30	clk=0	Count=1
35	clk=1	Count=1
40	clk=0	Count=0

## Digital design

- ▶ Specification
- ▶ Modelling using HDLs
- ▶ Functional simulation and testing
- ▶ Timing analysis
- ▶ Mapping to a hardware library/ FPGA (Synthesis)
- ▶ Place and Route
- ▶ Timing analysis.

# Synthesis

Map verilog models to hardware - Bit operators, gates, flipflops


```
assign s = a^b;
```




```
or or1( cout, c1, c2);
```


 
```
always @(posedge clock)
begin
  Q <= D;
end
```



 

```
assign out = (s == 0)? I0:
             (s == 1)? I1:
             (s == 2)? I2:
             (s == 3)? I3: 1'bx;
```


```
module mux4( I0, I1, I2, I3, s, out );
```

```
input I0, I1, I2, I3 ;
input[1:0] s;
output out;
reg out;
```

```
assign t0 = (~s[1] & I0) | (s[1] & I2);
assign t1 = (~s[1] & I1) | (s[1] & I3);
assign out = (~s[0] & t0) | (s[0] & t1);
endmodule
```

```
always@(I0 or I1 or I2 or I3 or s)
begin
case( s )
0: out = I0;
1: out = I1;
2: out = I2;
3: out = I3;
end
```
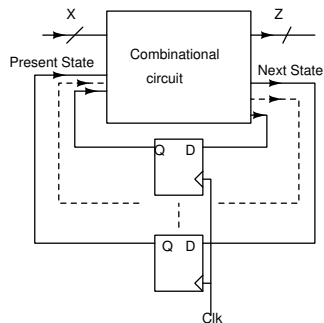
# State Machines: Modelling using Verilog



```
module StateMach( X, Z, clock );
```

```
input X ;
input clock;
output Z;
reg PresentState, NextState;
```

```
always@(posedge clock)
begin
PresentState <= NextState
end
```


```
assign Z = X & PresentState;
```

```
assign NextState = X | PresentState;
```

```
endmodule
```



## Field programmable gate arrays - FPGA

 


- ▶ CLB - Configurable logic blocks
- ▶ IOB - Programmable IO blocks
- ▶ Switch matrix - Programmable interconnects
- ▶ DCM - digital clock management

- ▶ CLBs contain Lookup tables (LUT), multiplexers, D flip flops and fast carry chain
- ▶ CLBs can be programmed to implement logic functions, can act as distributed RAM
- ▶ CLBs can be connected to obtain more complex logic functions using programmable switches and interconnects
- ▶ The IOBs can be programmed to act as input, output, tristate ....
- ▶ DCMs can be programmed to get various clock frequencies, phase shifts ...
- ▶ Block RAMs, multipliers

## Spartan 3E development board



 

SW3 SW2 SW1 SW0  
(N17) (H18) (L14) (L13)

UG230\_c2\_01\_021206

Figure 2-1: Four Slide Switches

```
NET "SW<0>" LOC = "L13"
NET "SW<1>" LOC = "L14"
NET "SW<2>" LOC = "H18"
NET "SW<3>" LOC = "N17"
```

```
NET "LED<7>" LOC = "F9"
NET "LED<6>" LOC = "E9"
NET "LED<5>" LOC = "D11"
NET "LED<4>" LOC = "C11"
NET "LED<3>" LOC = "F11"
NET "LED<2>" LOC = "E11"
NET "LED<1>" LOC = "E12"
NET "LED<0>" LOC = "F12"
```

The slide switches and LEDs are hardwired to certain pins in the FPGA. Must connect the appropriate signal to that pin. Specified in the UCF file.

## Experiment 11

### Decoder, Multiplier and counter the Spartan 3E FPGA

1. Write Verilog code for a 3-to-8 decoder using the case statement. Verify functionality and synthesize the circuit. Download and test on the board.
2. Write Verilog code for a 2-bit multiplier using gates.
3. Implement a clock divider that divides the 50MHz input clock to approximately 1Hz
4. Implement a 3-bit up/down counter using the 1Hz clock. Use a slide switch to indicate up/down. Display the number using an appropriate number of LEDs. Get the pin location of the clock from the user guide.

In both cases, the inputs are to be given using the switches present in the FPGA board and the result should be displayed using LEDs.