

# EE2001 - Digital systems lab

Vinita Vasudevan



## 2s complement

- ▶ The decimal value of a n-bit binary number is  $\sum_{i=0}^{n-1} a_i 2^i$ .
- ▶ If a negative number is represented in the two's complement form, its decimal value is  $-(2^n - \sum_{i=0}^{n-1} a_i 2^i)$ .
- ▶ In practice it is obtained by first subtracting the number from  $2^n - 1$  (each bit is complemented) and then adding 1 to the number.
- ▶ For a positive number  $a_{n-1} = 0$  and for a negative number  $a_{n-1} = 1$ .

- ▶ Positive number the decimal value is  $\sum_{i=0}^{n-2} a_i 2^i$ . Negative


$$\text{number: } -(2^n - 2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i) = -2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$$

## 2s complement

- ▶ In general, the value is  $-a_{n-1}2^{n-1} + \sum_{i=0}^{n-2} a_i 2^i$
- ▶ if  $A$  is an  $n$  bit number  $a_{n-1}a_{n-2} \cdots a_0$ , we need  $A - A = 0$ . If the sum is also  $n$  bits, throw away the carry out from the MSB
- ▶ If the sum is  $n + 1$  bits? Do a sign extension. Verify that the decimal value of the number does not change with sign extension.
- ▶ How do you deal with fractions?
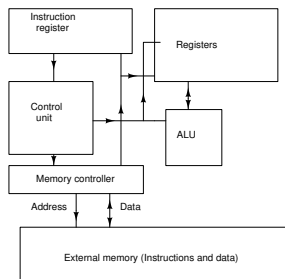
## Functional Simulation: Behavioural Modelling


High level model specifying circuit function, without getting into actual implementation



Need to verify functionality/execution behaviour of various instructions, before going to gate level or even data flow level modelling. Easier to write a C programme to verify functionality, using loops, case statements etc.

Behavioural modelling also useful for components.

Example: Multiplexer

 

$$Out = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$

C program

```

if (!S0 && !S1)
{
    Out = I0
}
else if (!S0 && S1)
{
    Out = I1
}
else if (S0 && !S1)
{
    Out = I2
}
else
{
    Out = I3
}

```

# Data flow modelling using Verilog

```
module mux4( l0, l1, l2, l3, s, out );
```

```
input l0, l1, l2, l3 ;  
input[1:0] s;  
output out  
wire t0, t1;
```

```
assign t0 = (~s[1] & l0) | (s[1] & l2);  
assign t1 = (~s[1] & l1) | (s[1] & l3);  
assign out = (~s[0] & t0) | (s[0] & t1);
```

```
endmodule
```

```
module mux4( l0, l1, l2, l3, s, out );
```

```
input l0, l1, l2, l3 ;  
input[1:0] s;  
output out;
```

```
assign out = (s == 0)? l0:  
             (s == 1)? l1:  
             (s == 2)? l2:  
             (s == 3)? l3: 1'bx;
```

```
endmodule
```

# Behavioural Modelling

```
module mux4( l0, l1, l2, l3, s, out );
```

```
input l0, l1, l2, l3 ;  
input[1:0] s;  
output out;  
reg out;
```

```
always@(l0 or l1 or l2 or l3 or s)
```

```
begin  
  if (s == 0)  
    out = l0;  
  else if (s == 1)  
    out = l1;  
  else if (s == 2)  
    out = l2;  
  else if (s == 3)  
    out = l3;  
end
```

```
endmodule
```

- ▶ Code is similar to C
- ▶ The arguments to the always block constitute the sensitivity list. Any change in these inputs will cause the always block to execute
- ▶ The statements within the always block are executed sequentially
- ▶ In order to assign values to it, “out” has to be declared as “reg” (similar to what we did in test benches).

## Can mix models

```
module circuit( l0, l1, l2, l3, s, a, b, c, d);
```


```
input l0, l1, l2, l3 ;
input a, b;
input[1:0] s;
output c, d;
reg out;
```

```
always@(l0 or l1 or l2 or l3 or s)
begin
case( s )
0: out = l0;
1: out = l1;
2: out = l3;
3: out = l3;
end
```

```
assign c = out & a;
```

```
xor x1(d, out, b);
```

```
endmodule
```

 



## Experiment 3: Behavioural modelling using Verilog

Objective: Model circuits using behavioural models.

- ▶ Try out the behavioural and data flow model of a 4-to-1 MUX.
- ▶ Model a 1-to-4 demultiplexer using a behavioural model.
- ▶ Repeat the experiment using a data-flow model model.
- ▶  $A$  and  $B$  are 4-bit inputs and the output of the circuit is  $MAX(A, B)$ . You can use a mix of data flow and behavioural models if you wish.

In all three cases, write a test bench to test the circuit.