

# EE2001 - Digital systems lab

Vinita Vasudevan




## Objectives

- ▶ Practical aspects of digital design - Augment the theory course
- ▶ In the theory course - study gates at functions/logic level.
- ▶ Logic '0' and '1' are represented by voltages. Components have nonzero input and output currents.
- ▶ Each component has a datasheet detailing input and output behaviour.
- ▶ How do you design using these datasheets?
 
## Practical aspects

- ▶ What is the range of voltages representing a logic high and low?
- ▶ What is the maximum number of gates that can be connected to the output of a gate? (Fanout)
- ▶ Propagation delay
- ▶ Power consumed

Range of voltages corresponding to logic high and low levels - different for different logic families. You will be using TTL or LSTTL gates.




- ▶ Typical output high and low voltages ( $V_{OH}$  and  $V_{OL}$ )
- ▶ Lowest output voltage that will be regarded as a logic 1 at the input. ( $V_{IH}$ )
- ▶ Highest output voltage that will be regarded as a logic 0 ( $V_{IL}$ )

Noise margins:


$$NM_H = V_{OH} - V_{IH},$$

$$NM_L = V_{IL} - V_{OL}$$

## Voltage transfer characteristics


 


 Static characteristics - input voltage is changed slowly.



## Practical gates - 74xx LSTTL

	MIN	NOM	MAX	Units
Supply Voltage $V_{CC}$	4.75	5	5.25	V
High level output current $I_{OH}$			-400	$\mu A$
Low level output current, $I_{OL}$			8	mA
Operating free air temperature	0		70	$^{\circ}C$

  

	MIN	NOM	MAX	Units
High level input voltage $V_{IH}$	2			V
Low level input voltage $V_{IL}$			0.8	V
High level output voltage $V_{OH}$	2.7	3.4		V
Low level output voltage $V_{OL}$		0.25	0.5	V
High level input current, $I_{IH}$			20	$\mu\text{A}$
Low level input current, $I_{IL}$			-0.4	mA

# Output characteristics

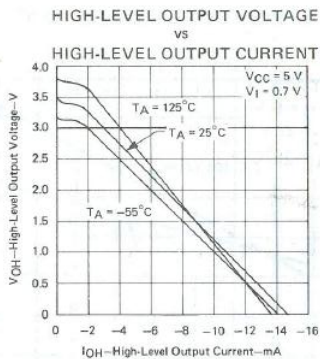


FIGURE D2


 



FIGURE D3

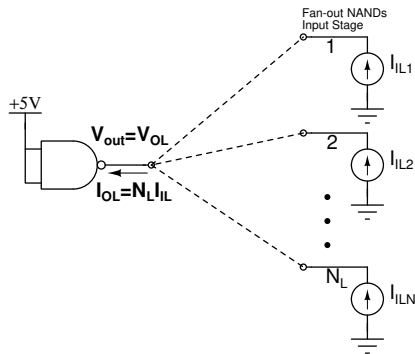

# Maximum number of gates that can be connected when output voltage is low


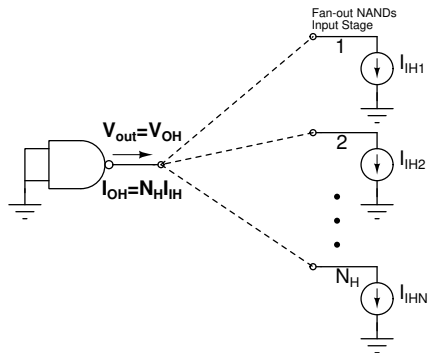
# Maximum number of gates that can be connected when output voltage is high



Fan-out of the gate is the minimum of  $(N_H, N_L)$ .

# Practical Gates: Data sheets

## recommended operating conditions

	54 FAMILY 74 FAMILY	SERIES 54 SERIES 74	SERIES 54H SERIES 74H	SERIES 54L SERIES 74L	SERIES 54LS SERIES 74LS	SERIES 54S SERIES 74S	UNIT
		'00, '04, '10, '20, '30	'H00, 'H04, 'H10, 'H20, 'H30	'L00, 'L04, 'L10, 'L20, 'L30	'LS00, 'LS04, 'LS10, 'LS20, 'LS30	'S00, 'S04, 'S10, 'S20, 'S30, 'S133	
		MIN NOM MAX	MIN NOM MAX	MIN NOM MAX	MIN NOM MAX	MIN NOM MAX	
Supply voltage, $V_{CC}$	54 Family 74 Family	4.5 5 5.5 4.75 5 5.25	4.5 5 5.5 4.75 5 5.25	4.5 5 5.5 4.75 5 5.25	4.5 5 5.5 4.75 5 5.25	4.5 5 5.5 4.75 5 5.25	V
High-level output current, $I_{OH}$	54 Family 74 Family	-400 -400	-500 -500	-100 -200	-400 -400	-1000 -1000	$\mu$ A
Low-level output current, $I_{OL}$	54 Family 74 Family	16 -16	20 20	2 3.6	4 8	20 20	mA
Operating free-air temperature, $T_A$	54 Family 74 Family	-55 125 0 70	-55 125 0 70	-55 125 0 70	-55 125 0 70	-55 125 0 70	$^{\circ}$ C

# Practical gates: Data sheets

electrical characteristics over recommended operating free-air temperature range (unless otherwise noted)

PARAMETER	TEST FIGURE	TEST CONDITIONS†	SERIES 54	SERIES 54H	SERIES 54L	SERIES 54LS	SERIES 54S	UNIT		
			SERIES 74	SERIES 74H	SERIES 74L	SERIES 74LS	SERIES 74S			
			'00, '04, '10, '20, '30	'H00, 'H04, 'H10, 'H20, 'H30	'L00, 'L04, 'L10, 'L20, 'L30	'LS00, 'LS04, 'LS10, 'LS20, 'LS30	'S00, 'S04, 'S10, 'S20, 'S30, 'S133			
		MIN	TYP‡	MAX	MIN	TYP‡	MAX	MIN	TYP‡	MAX
$V_{IH}$ High-level input voltage	1, 2		2	2	2	2	2	V		
$V_{IL}$ Low-level input voltage	1, 2	54 Family	0.8	0.8	0.7	0.7	0.8	V		
		74 Family	0.8	0.8	0.7	0.8	0.8	V		
$V_{IK}$ Input clamp voltage	3	$V_{CC} = \text{MIN}, I_I = 5$	-1.5	-1.5		-1.5	-1.2	V		
$V_{OH}$ High-level output voltage	1	$V_{CC} = \text{MIN}, I_{OH} = \text{MAX}, V_{IL} = V_{IL \text{ max}}$	54 Family 2.4 3.4	2.4 3.5	2.4 3.3	2.5 3.4	2.5 3.4	V		
		74 Family	2.4 3.4	2.4 3.5	2.4 3.2	2.7 3.4	2.7 3.4	V		
$V_{OL}$ Low-level output voltage	2	$V_{CC} = \text{MIN}, V_{IH} = 2 \text{ V}$	54 Family 0.2 0.4	0.2 0.4	0.15 0.3	0.25 0.4	0.5	V		
		$I_{OL} = \text{MAX}$	74 Family 0.2 0.4	0.2 0.4	0.2 0.4	0.25 0.5	0.5	V		
		$I_{OL} = 4 \text{ mA}$	Series 74LS			0.4		V		
$I_I$ Input current at maximum input voltage	4	$V_{CC} = \text{MAX}$	$V_I = 5.5 \text{ V}$ 1	1	0.1		1	mA		
			$V_I = 7 \text{ V}$		0.1		0.1	mA		
$I_{IH}$ High-level input current	4	$V_{CC} = \text{MAX}$	$V_{IH} = 2.4 \text{ V}$ 40	50	10		10	$\mu\text{A}$		
			$V_{IH} = 2.7 \text{ V}$			20	50	$\mu\text{A}$		
$I_{IL}$ Low-level input current	5	$V_{CC} = \text{MAX}$	$V_{IL} = 0.3 \text{ V}$ -1.6	-2	-0.18		-0.4	mA		
			$V_{IL} = 0.4 \text{ V}$					mA		
			$V_{IL} = 0.5 \text{ V}$				-2	mA		
$I_{OS}$ Short-circuit output current‡	6	$V_{CC} = \text{MAX}$	54 Family -20 -55	-40 -100	-3 -15	-20 -100	-40 -100	mA		
			74 Family -18 -55	-40 -100	-3 -15	-20 -100	-40 -100	mA		
$I_{CC}$ Supply current	7	$V_{CC} = \text{MAX}$	See table on next page					mA		


# Experiment 4 - Input and Output characteristics of LSTTL gates

## Objectives

1. To get familiar with data sheets of TTL logic gates
2. To understand various static logic gate characteristics: typical output high and low voltages, noise margins, input and output current levels and fanout.
 
## Transfer characteristics

Using the following circuit , measure the output voltage while changing the magnitude of the input voltage slowly.





(1)
  
## Output characteristics


Using circuit (3), measure the output current as a function of the output voltage when both the inputs of the NAND gate are in logic-1 state.

Using circuit (4), measure the output current as a function of the output voltage, when both the inputs are in logic 0 state.


 
## Input Characteristics

Using the following circuit, measure the input current as a function of the input voltage.



From these experiments find the fan-in and fanout of the NAND gate



## General Instructions for all experiments

- ▶ First download datasheets for all components and get pin diagrams.
- ▶ Must strictly use a colour code for the wiring. For eg. use red wires for  $V_{CC}$ , black for ground and green for signals. This will make it easier to debug.
- ▶ Use the two vertical bars on the edges of the breadboard for  $V_{CC}$  and Ground.
- ▶ A circuit should have a single reference voltage. All Grounds should be connected together, including that of the measuring instrument
- ▶ Connect  $V_{CC}$  and Ground of all components and do a simple functional check of each component before you start wiring.
- ▶ All wires should be cut to the required length.

- ▶ Plan the layout of the circuit in such a way that there is enough free space for wiring and probing. Ensure that open ends of multiple wires do not touch each other.
- ▶ Check the wiring before powering up the circuit.
- ▶ Make any modifications after **disconnecting/switching off** the power supply.
- ▶ In case the outputs are different from the expected values, as a primary step in debugging, check if the  $V_{CC}$  and  $GND$  pins get their appropriate values in all the ICs used in the circuit.
- ▶ You should design and wire up the circuit on Monday. The lab session on Tuesday is meant for testing, debugging and understanding results.
- ▶ Each group should have a lab notebook that has the circuit design and a record of the results obtained. At the end of each session, get it signed by the teaching assistant.