

# EE2001 - Digital systems lab

## Critical paths and maximum frequency of operation


Vinita Vasudevan




- ▶ Functional simulation - Verilog/C
- ▶ Timing analysis - Critical paths

## Static and dynamic behaviour



### Static Characteristics

 

### Dynamic Characteristics

 


## Propagation delays

  


Due to

- ▶ Delays in turning transistors ON/OFF.
- ▶ Charging and discharging capacitors (wiring/parasitic/input capacitances of transistors and gates).

## Propagation delays

 


$$t_{pd} = \frac{t_{pHL} + t_{pLH}}{2}$$

 

Finite delay between arrival of inputs and arrival of outputs. How quickly can the inputs change?



## Static timing analysis

 

- ▶ Inputs to a gate can arrive at arbitrary times. Arrival depends on all the gate preceding it.
- ▶ Delays are input dependent. Take the worst case delay
- ▶ Separate function from timing.
- ▶ Longest path problem in a graph. Use SUM and MAX.

## Critical paths - Static timing analysis

All primary inputs available at  $t=0$ .

  

$$\text{Gate delay} = \text{MAX}(d_1, d_2)$$


The next set of inputs must arrive at  $t > 8.5$  units.



## Measured propagation delays - Test structures

Due to manufacturing variations, delays vary greatly from circuit to circuit. Measure on-chip delays.

### Ring Oscillator

 


- ▶ After 3 propagation delays ( $t_{pd}$ ), voltage at X goes from  $V_{OL}$  (logic 0) to  $V_{OH}$  (logic 1)
- ▶ View the signal X on the oscilloscope and measure the frequency.
- ▶  $3t_{pd} = \frac{T}{2}$


## 7483 - Carry lookahead adder

AC CHARACTERISTICS ( $T_A = 25^\circ\text{C}$ )

Symbol	Parameter	Limits			Unit	Test Conditions
		Min	Typ	Max		
t <sub>PLH</sub> t <sub>PHL</sub>	Propagation Delay, C <sub>0</sub> Input to any $\Sigma$ Output		16 15	24 24	ns	V <sub>CC</sub> = 5.0 V C <sub>L</sub> = 15 pF Figures 1 and 2
t <sub>PLH</sub> t <sub>PHL</sub>	Propagation Delay, Any A or B Input to $\Sigma$ Outputs		15 15	24 24	ns	
t <sub>PLH</sub> t <sub>PHL</sub>	Propagation Delay, C <sub>0</sub> Input to C <sub>4</sub> Output		11 15	17 22	ns	
t <sub>PLH</sub> t <sub>PHL</sub>	Propagation Delay, Any A or B Input to C <sub>4</sub> Output		11 12	17 17	ns	

 

## Propagation delay of the adder

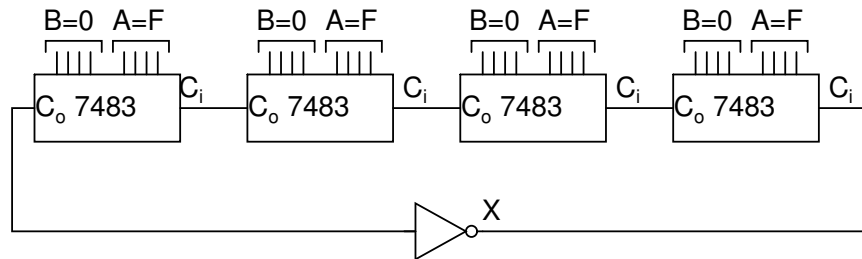

- ▶ In an adder chain, the last input to arrive is usually the carry input.
- ▶ The critical path is the carry path.

## Experiment 7

- ▶ Learn how to use the oscilloscope - TAs will give a demo
- ▶ Wire up the ring oscillator using inverters and measure the oscillation frequency. If you cannot measure it, increase the (odd) number of inverters in the loop. Estimate the propagation delay.
- ▶ Connect four 4-bit adders (7483) and an inverter so that it oscillates. Estimate the propagation delay of the 7483.
- ▶ Using XOR and AND gates design a multiplier that multiplies two 2 bit numbers. Identify the critical path and measure the critical path delay.