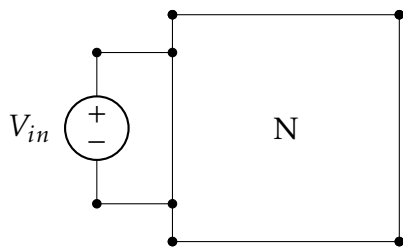


# Lecture 11: Driving Point Functions & Network Function


Lecturer: Dr. Vinita Vasudevan

Scribe: Shashank Shekhar

**Driving Point Functions:** Impedence and admittance measured at the same port of the network with assumption is LTI i.e. zero initial condition and no independent sources other than the input.



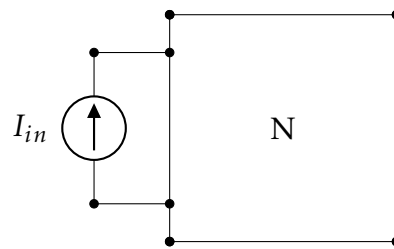
$$Y_{in}(s) = \frac{I_{in}(s)}{V_{in}(s)}$$




$$Z_{in}(s) = \frac{V_{in}(s)}{I_{in}(s)}$$

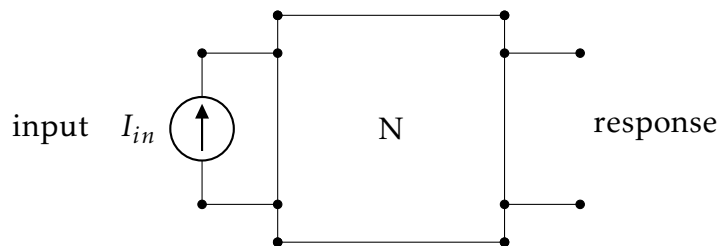**Transfer Function:** It is the ratio of laplace transform of input and response at different port with assumption is LTI i.e. zero initial condition and no independent sources other than the input.



### Example 1:

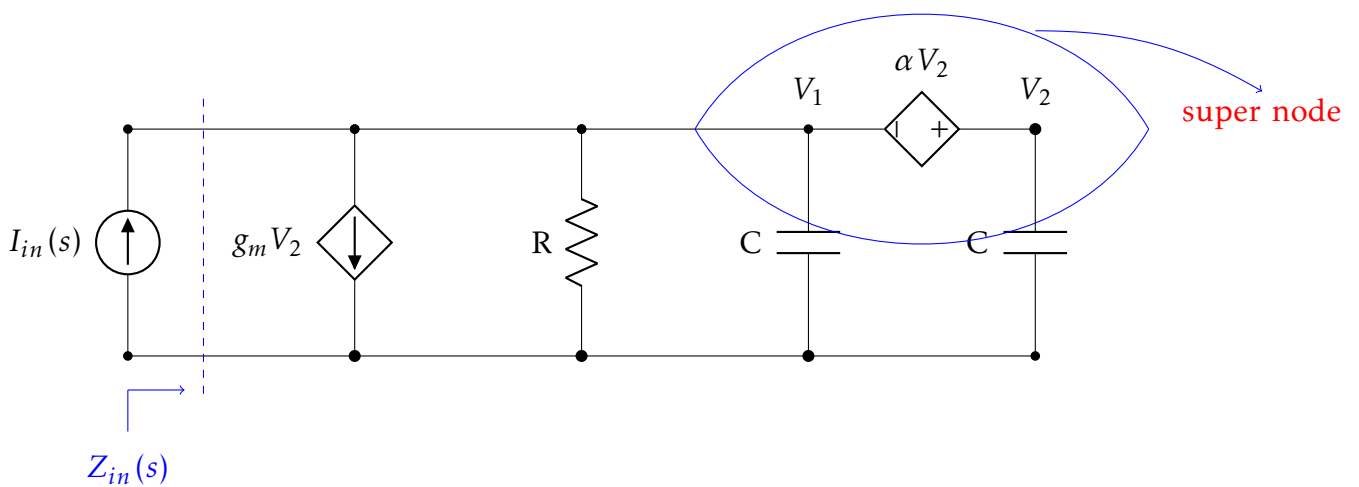

$$V_1 \left( \frac{1}{R} + sC \right) + V_2 (sC) + V_2 g_m = I_{in}(s)$$

$$V_1 - V_2 = \alpha V_2$$

$$\begin{bmatrix} \frac{1+sRC}{R} & g_m+sC \\ 1 & -(1+\alpha) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{in} \\ 0 \end{bmatrix}$$

The inverse for  $2 \times 2$  matrix is given as:

$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{D} \begin{bmatrix} -(1+\alpha) & -(g_m+sC) \\ -1 & \frac{1+sRC}{R} \end{bmatrix} \begin{bmatrix} I_{in} \\ 0 \end{bmatrix}$$

where,

$$\frac{1}{D} = \frac{-R}{(1+g_mR+\alpha)+sRC(2+\alpha)}$$

$$V_1(s) = \frac{-(1+\alpha)I_{in}}{D}$$

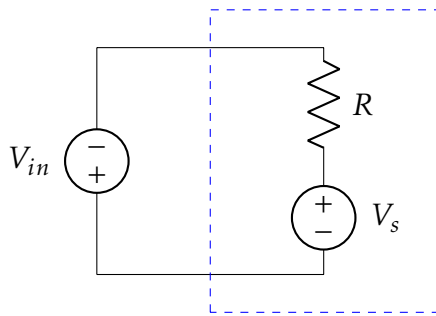
$$Z_{in}(s) = \frac{R(1+\alpha)}{(1+g_mR+\alpha)+sRC(2+\alpha)}$$



$$I = \frac{V_{in} - V_s}{R}$$

Not linear

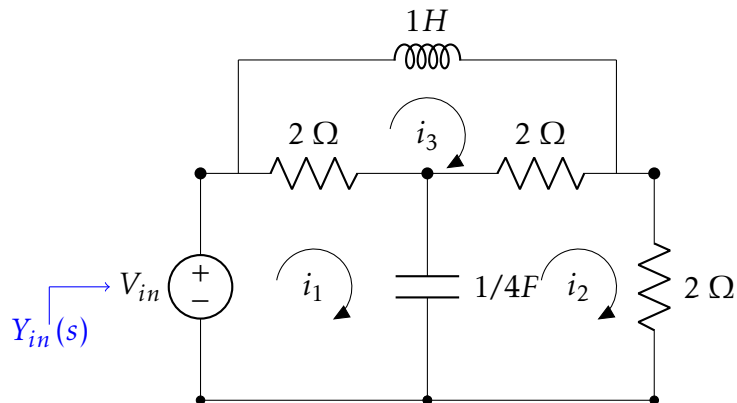**Example 2:** Find admittance  $Y_{in}(s)$



$$\begin{bmatrix} 2(s+2/s) & -4/s & -2 \\ -4/s & 4\frac{s+1}{s} & -2 \\ -2 & -2 & 4+s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_{in} \\ 0 \\ 0 \end{bmatrix}$$

$$Det = \frac{8(s+2)^2}{s}$$


Use Cramer's rule to solve

$$I_1(s) = V_{in}(s) \frac{4(s^2 + 4s + 4)/s}{8(s+2)^2/s}$$

$$Y_{in}(s) = 1/2$$

Note that poles and zeros cancel. But it is a second order system with repeated root  $s = -2$ .

**Example 3:**

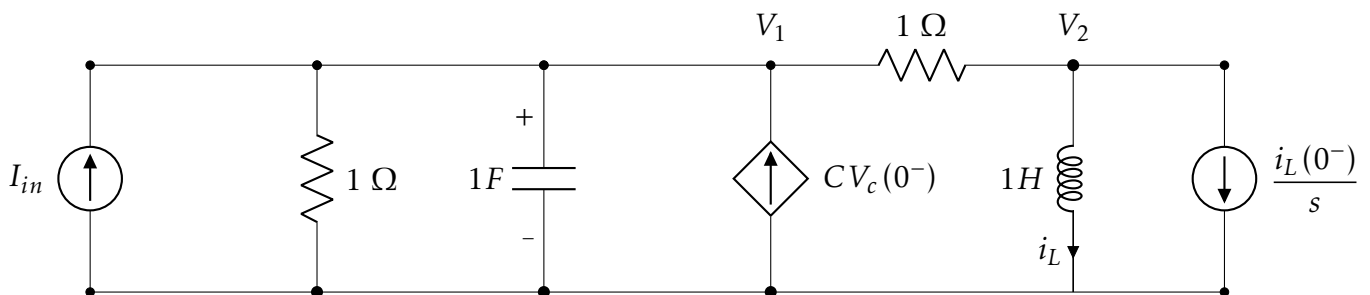

$$\begin{bmatrix} s+2 & -1 \\ -1 & 1/s+1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{in} + CV_c(0^-) \\ -i_L(0^-)/s \end{bmatrix}$$

**Initial value and final value theorem**


$$\begin{aligned} \mathcal{L}\left[\frac{df}{dt}\right] &= sF(s) - f(0^-) = \int_{0^-}^{\infty} \frac{df}{dt} e^{-st} dt \\ \lim_{s \rightarrow \infty} (sF(s) - f(0^-)) &= \lim_{s \rightarrow \infty} \int_{0^-}^{0^+} \frac{df}{dt} e^{-st} dt + \lim_{s \rightarrow \infty} \int_{0^+}^{\infty} \frac{df}{dt} e^{-st} dt \\ RHS &= \lim_{s \rightarrow \infty} \int_{0^-}^{0^+} \frac{df}{dt} = f(0^+) - f(0^-) \\ & \lim_{s \rightarrow \infty} sF(s) = f(0^+) \end{aligned}$$

## Final Value

$$\begin{aligned} \lim_{s \rightarrow 0} (sF(s) - f(0^-)) &= \int_{0^-}^{\infty} \frac{df}{dt} dt \\ &= \lim_{t \rightarrow \infty} \int_{0^-}^t \frac{df}{d\tau} d\tau \\ &= \lim_{t \rightarrow \infty} f(t) - f(0^-) \\ \lim_{s \rightarrow 0} sF(s) &= \lim_{t \rightarrow \infty} f(t) \end{aligned}$$

**Note:** Final value theorem will give steady state solution only if there is a steady state. It works only if all poles are in the LHP and you have at most one simple pole at the origin  
 e.g.  $\lim_{s \rightarrow 0} \frac{s \cdot s}{s^2 + \omega^2} = 0$ . Not correct as  $\lim_{t \rightarrow \infty} \cos \omega t \neq 0$

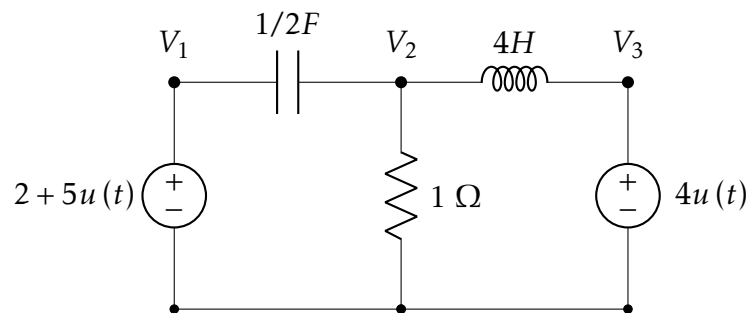**Exercise :** Find  $V_2(s), V_2(t)$  for circuit given below



Use initial value theorem and find  $v_2(0^+)$  from  $V_2(s)$  and final value theorem to find  $\lim_{t \rightarrow \infty} v_2(t)$