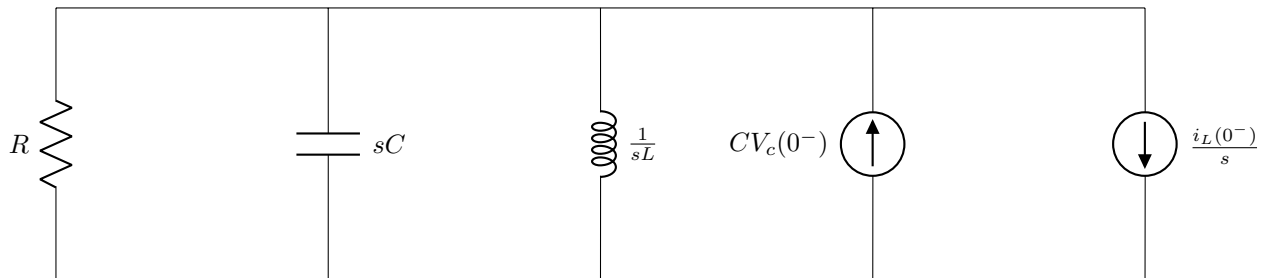


## Lecture 14: Parallel RLC network

Lecturer: Dr. Vinita Vasudevan

Scribe: Pradeep

Assuming we know  $V_C(0^-)$ ,  $I_L(0^-)$ , the s-domain circuit is as follows



Applying KCL at top node we get the following equation:

$$\begin{aligned}
 V(s)\left[\frac{1}{R} + \frac{1}{sL} + sC\right] &= \frac{-i_L(0^-)}{s} + CV_C(0^-) \\
 V(s) &= \frac{[CV_C(0^-) - \frac{i_L(0^-)}{s}]}{R + sL + s^2RLC} sLR \\
 &= \frac{\left[CV_C(0^-) - \frac{i_L(0^-)}{s}\right]}{RLC \left[s^2 + \frac{s}{RC} + \frac{1}{LC}\right]} sLR \\
 V(s) &= \frac{[CV_C(0^-) - \frac{i_L(0^-)}{s}]}{C[s^2 + \frac{s}{RC} + \frac{1}{LC}]} s
 \end{aligned}$$

The natural frequencies are determined by the roots of the denominator polynomial

$$s_1, s_2 = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\alpha = \frac{1}{2RC} \rightarrow \text{frequency; damping factor}$$

$$w_0 = \frac{1}{\sqrt{LC}} \Rightarrow \text{resonant frequency}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - w_0^2}$$

This gives us 3 cases:

**Case1:**  $\alpha^2 > w_0^2$

denominator has two distinct roots  $s_1, s_2$

$s_1, s_2$  are real values

The solution will be of form  $A_1 e^{s_1 t} + A_2 e^{s_2 t}$

since  $\sqrt{\alpha^2 - w_0^2} < \alpha$

The solution is an exponentially decaying function, one time constant larger than the other.  
It is an over damped situation.

**Case2:**  $\alpha^2 = w_0^2$

In this case denominator has two equal real roots.

$$s_1, s_2 = -\alpha$$

The solution will be of form  $A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$

It is a critically damped situation.

**case3:**  $\alpha^2 < w_0^2$

In this case the denominator has complex roots.

$$\text{let } w_\alpha = \sqrt{w_0^2 - \alpha^2}$$

$$s_1, s_2 = -\alpha \pm jw_\alpha$$

$$\begin{aligned} \text{denominator} &= (s + \alpha + jw_\alpha)(s + \alpha - jw_\alpha) \\ &= (s + \alpha)^2 + w_\alpha^2 \end{aligned}$$

The solution will be of form  $e^{-\alpha t}[A_1 \cos(w_\alpha t) + A_2 \sin(w_\alpha t)]$


This is an under damped system.

$$\text{'Q' Quality factor} = \frac{w_0}{2\alpha}$$

$$\text{over damped; } w_0 < \alpha \implies Q < \frac{1}{2}$$

$$\text{critically damped; } w_0 = \alpha \implies Q = \frac{1}{2}$$
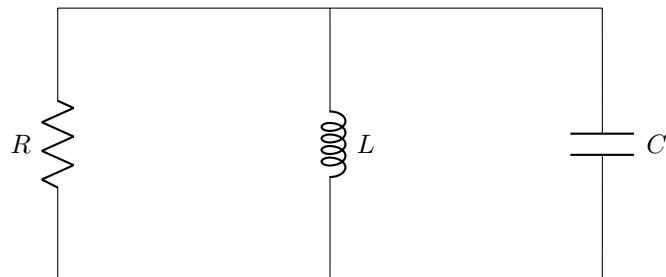
$$\text{under damped; } w_0 > \alpha \implies Q > \frac{1}{2}$$



For high quality factor, R should be large