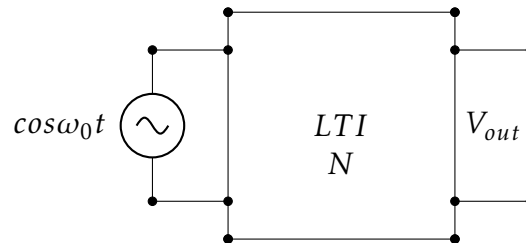


Lecture 25: Sinusoidal Steady State

Lecturer: Dr. Vinita Vasudevan

Scribe: Shashank Shekhar

Since power supply is 50 Hz sinusoids, we are interested in steady state voltage/current.



Assume poles of 'N' are in LHP; no poles in $j\omega$ axis. One way to analyze this is to use Laplace transforms and let $t \rightarrow \infty$.

$$V_{out}(s) = H(s) \frac{s}{s^2 + \omega_0^2} \quad \{\text{Effectively input is } \cos \omega_0 t u(t)\}$$

$$= \frac{A_1}{s + \alpha_1} + \frac{A_2}{s + \alpha_2} + \dots + \frac{B_1 s + B_2}{s^2 + \omega_0^2}$$

Natural response

Since poles are in LHP there are transient that will die out in times $\gg \max_i \left\{ \frac{1}{\alpha_i} \right\}$

Steady state solution (forced solution) is due to $\frac{B_1 s + B_2}{s^2 + \omega_0^2}$

Find B_1 & B_2 ; multiply both sides by $s^2 + \omega_0^2$ and substitute $s = \pm j\omega_0$

$$H(j\omega_0) \cdot j\omega_0 = B_1(j\omega_0) + B_2$$

$$H(-j\omega_0) \cdot (-j\omega_0) = B_1(-j\omega_0) + B_2$$

$$B_1 = \text{Re}\{H(j\omega_0)\}$$

$$B_2 = -\omega_0 \text{Im}\{H(j\omega_0)\}$$

$$\therefore \frac{B_1 s + B_2}{s^2 + \omega_0^2} \longleftrightarrow \text{Re}\{H(j\omega_0)\} \cos \omega_0 t - \text{Im}\{H(j\omega_0)\} \sin \omega_0 t$$

$$= |H(j\omega_0)| \cos(\omega_0 t + \theta)$$

where

$$\theta = \tan^{-1} \left[\frac{\text{Im}\{H(j\omega_0)\}}{\text{Re}\{H(j\omega_0)\}} \right]$$

The other way to look at is the eigenfunction approach

$$e^{j\omega t} \rightarrow H(j\omega) e^{j\omega t}$$

Note that this is a steady state response after all transients have died out. If we find the response to $e^{j\omega t} u(t)$, we will also get the transient response (Not an eigenfunction)

$$e^{-j\omega t} \rightarrow H(-j\omega) e^{-j\omega t}$$

Superposition

$$\cos \omega t \rightarrow \text{Re}\{H(j\omega) e^{j\omega t}\}$$

Same as steady state response obtained using Laplace transforms. So to find response to $\cos \omega_0 t$ all we need is $H(j\omega_0)$

Input is $Ae^{j\omega t}$; where, A is complex. Linearity \Rightarrow Output is $AH(j\omega)e^{j\omega t}$
 Actual input is $\text{Re}\{Ae^{j\omega t}\}$ where $A = |A|e^{j\theta}$. So actual input is $= |A|\cos(\omega t + \theta)$.

Phasors: The complex coefficient multiplying $e^{j\omega t}$.

$$e^{j\omega t} \rightarrow 1 \angle 0$$

$$Ae^{j\theta} e^{j\omega t} \rightarrow A \angle \theta$$

To get response to $\sin \omega_0 t$;

$$\begin{aligned} \frac{e^{j\omega t} - e^{-j\omega t}}{2j} &\rightarrow \frac{H(j\omega) e^{j\omega t} - H(-j\omega) e^{-j\omega t}}{2j} \\ &= \text{Im}\{H(j\omega) e^{j\omega t}\} \\ &= \text{Re}\{-jH(j\omega) e^{j\omega t}\} \\ &= \text{Re}\{H(j\omega) e^{-j\pi/2} e^{j\omega t}\} \\ -\sin \omega_0 t &\rightarrow 1 \angle -\pi/2 \end{aligned}$$

All response in a circuit can be written as a (Phasor) $e^{j\omega t}$.


Denote currents as $Ie^{j\omega t}$; I complex, voltages as $Ve^{j\omega t}$; V complex

KCL: $\sum_k I_k e^{j\omega t} = 0$ at each node.

$$\begin{aligned} e^{j\omega t} &\neq 0 \\ \Rightarrow \sum_k I_k &= 0 \quad \{\text{can be written directly using phasors}\} \end{aligned}$$


KVL: $\sum_k V_k = 0$

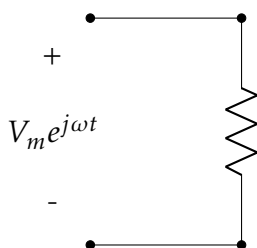Branch constitutive relationship Initial conditions are of no consequence as we are looking at steady state solutions after all transients have died out. System is stable; all transients due to initial conditions have also died out.



$$I = \frac{V_m}{R} e^{j\omega t}$$
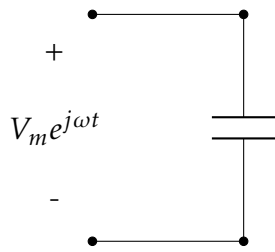
$$I = \frac{V_m}{R} \text{ (Phasor Current)}$$




$$I = \underbrace{j\omega C V_m}_{I_m} e^{j\omega t}$$

$$V_m = |V_m| e^{j\theta}$$

$$\Rightarrow I_m = \omega C |V_m| e^{j(\theta + \pi/2)}$$

Current leads voltage by $\pi/2$

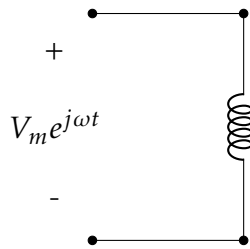

$$I = \frac{1}{L} \int V_m e^{j\omega t} dt$$


$$= \frac{1}{j\omega L} V_m \cdot e^{j\omega t} dt$$

$$\Rightarrow I_m = \frac{|V_m|}{\omega L} e^{-j\pi/2}$$


Current lags voltage by $\pi/2$

Impedance: $\frac{V_m}{I_m} = Z$ **Admittance:** $\frac{I_m}{V_m} = Y$ Both Z and Y are complex numbers.

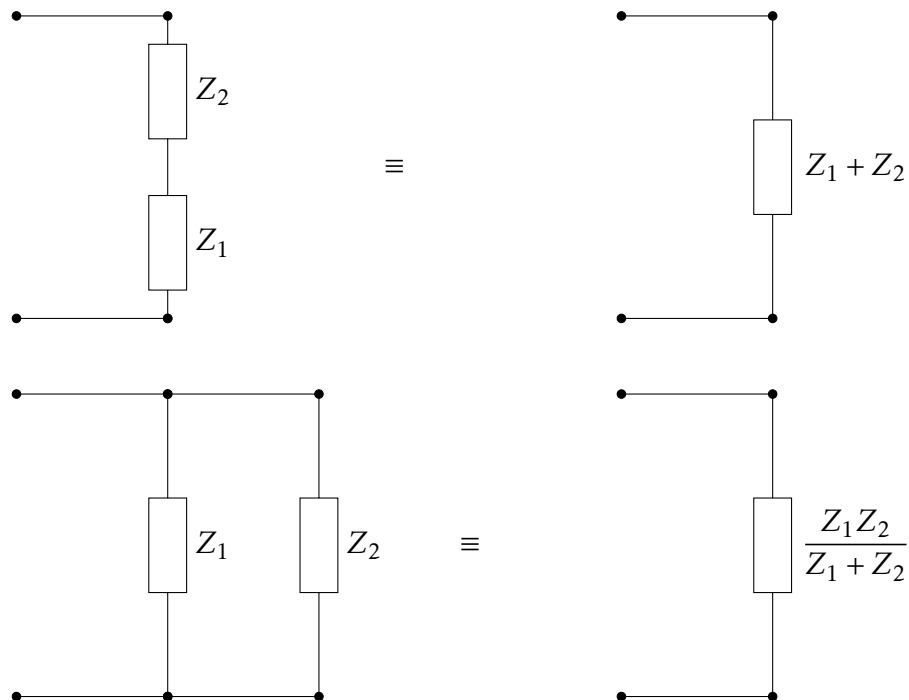Series and Parallel connections of impedance



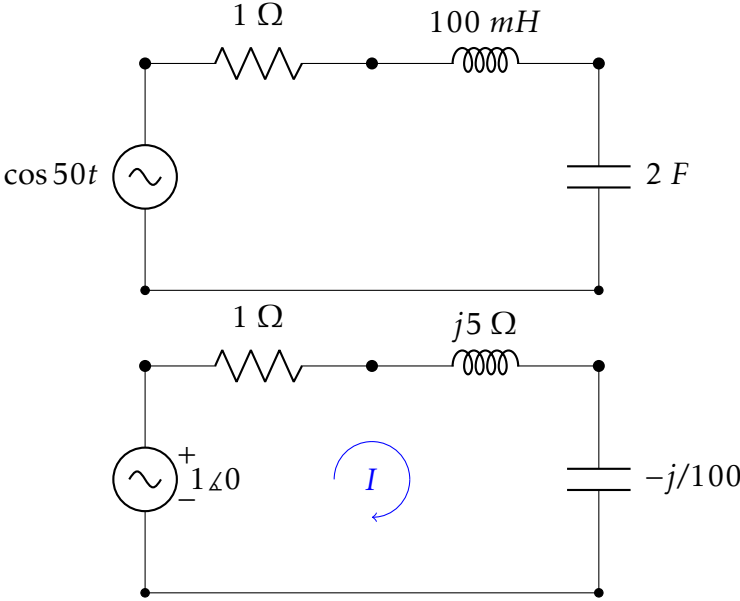Example find steady state response of the following circuit



$$I \left(1 + j5 - \frac{j}{100} \right) = 1 + j0$$