
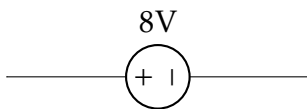


## Lecture 3: Component Models (Contd...)


Lecturer: Dr. Vinita Vasudevan

Scribe: Shashank Shekhar

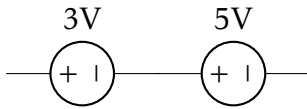
### Series and Parallel connection of Ideal Sources




Series Connection: Same current

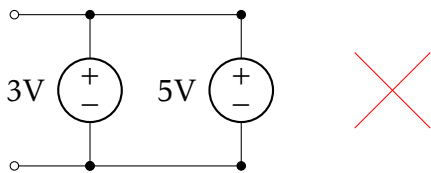

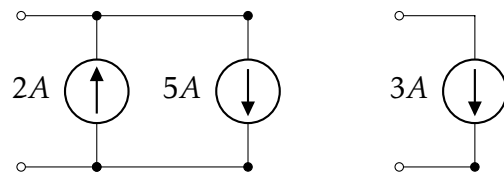Ideal voltage sources can **not** be added in parallel.




Parallel Connection: Same Voltage

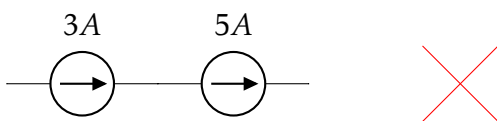




Ideal current sources can **not** be added in series.
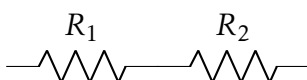
### Series and Parallel connection of Resistors




$$v(t) = (R_1 + R_2) i(t)$$

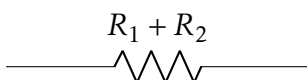

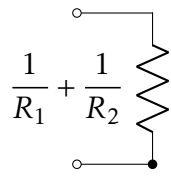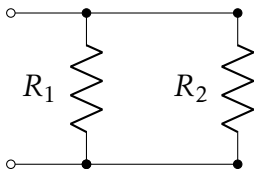

$$i(t) = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v(t)$$

### Capacitor

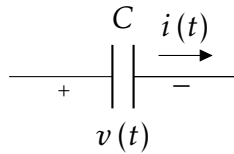

$q = CV$ , where  $V$  is voltage drop across the capacitor


$$\begin{aligned} i(t) &= \frac{dq}{dt} = \frac{d}{dt}(CV) \\ &= C \frac{dV}{dt} + V \frac{dC}{dt} \end{aligned}$$

For a LTI capacitor, value of capacitance is invariant of time  $\frac{dC}{dt} = 0$


hence,

$$i(t) = C \frac{dV}{dt}$$


### Example 1:

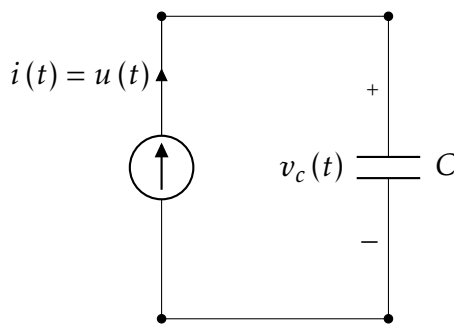

$$\begin{aligned} i(t) &= C \frac{dV}{dt} \\ \Rightarrow v_c(t) &= v_c(0) + \frac{1}{C} \int_0^t i(t) dt \\ v_c(t) &= \frac{t}{C} \end{aligned}$$

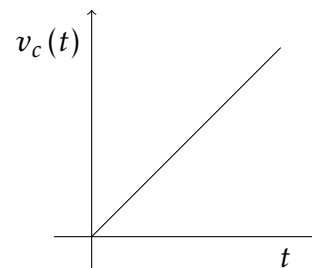

**Example 2:**

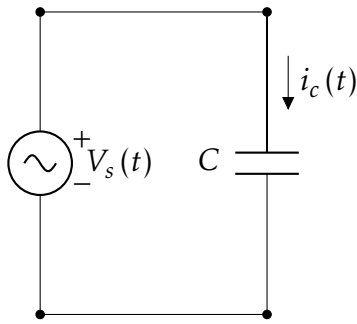


$$V_s(t) = A \cos \omega t$$

$$i(t) = C \frac{dV}{dt}$$

$$= -\omega AC \sin \omega t$$

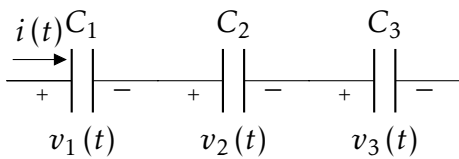**Series and Parallel connection of Capacitors**



$$v_1(t) = v_1(0) + \frac{1}{C_1} \int_0^t i(t) dt$$

$$v_2(t) = v_2(0) + \frac{1}{C_2} \int_0^t i(t) dt$$

$$v_3(t) = v_3(0) + \frac{1}{C_3} \int_0^t i(t) dt$$

$$v(t) = v_1(t) + v_2(t) + v_3(t)$$


$$= \sum_{i=1}^3 v_i(0) + \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) \int_0^t i(t) dt$$

So,

$$C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

with,

$$v_{eq}(0) = \sum_{i=1}^3 v_i(0)$$

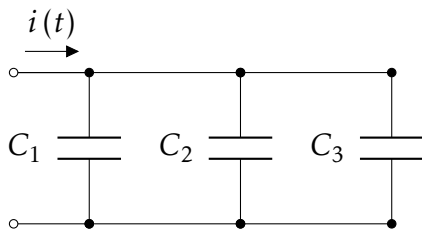

$$i(t) = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + C_3 \frac{dV}{dt}$$


$$= (C_1 + C_2 + C_3) \frac{dV}{dt}$$

So,

$$C_{eq} = (C_1 + C_2 + C_3)$$

The initial voltage on all capacitors is the same.

## Inductor

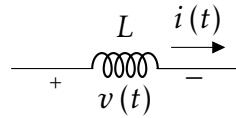

$\phi = Li$ , where  $\phi$  is magnetic flux and  $i$  is current through inductor


$$\begin{aligned} v(t) &= \frac{d\phi}{dt} = \frac{d}{dt}(Li) \\ &= L \frac{di}{dt} + i \frac{dL}{dt} \end{aligned}$$

For a LTI capacitor, value of inductance is invariant of time  $\frac{dL}{dt} = 0$

hence,

$$v(t) = L \frac{di}{dt}$$

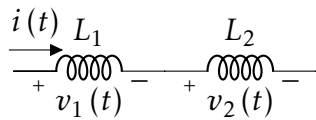
## Series and Parallel connection of Resistors



$$\begin{aligned} v(t) &= v_1(t) + v_2(t) \\ &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} \end{aligned}$$

So,

$$L_{eq} = (L_1 + L_2)$$

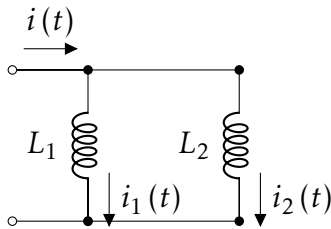


$$\begin{aligned} i(t) &= i_1(t) + i_2(t) \\ &= i_1(0) + \frac{1}{L_1} \int_0^t v(t) dt + i_2(0) + \frac{1}{L_2} \int_0^t v(t) dt \\ &= \sum_{k=1}^2 i_k(0) + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t v(t) dt \end{aligned}$$


So,

$$L_{eq} = \left( \frac{1}{L_1} + \frac{1}{L_2} \right)$$

## Example 3:

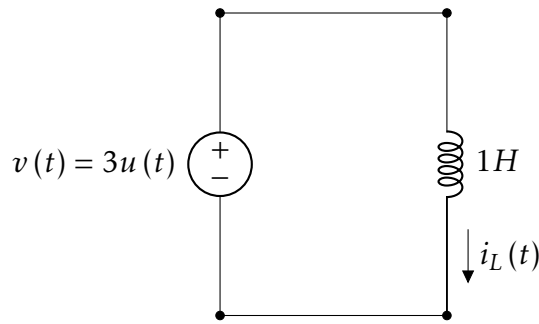

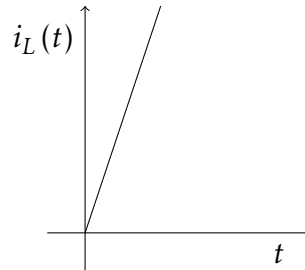
$$\begin{aligned}
 i_L(t) &= i_L(0) + \frac{1}{L_1} \int_0^t v(t) dt \\
 &= i_L(0) + \int_0^t 3u(t) dt \\
 &= i_L(0) + 3t
 \end{aligned}$$



Assume initial current is zero

$$i_L(t) = 3t$$


**Example 4:**

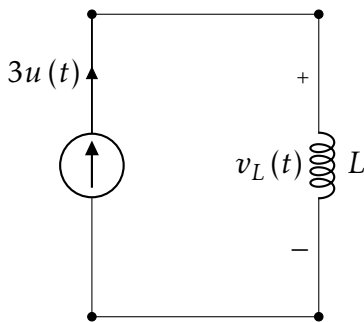

$$\begin{aligned}
 v_L(t) &= L \frac{di}{dt} \\
 &= 3L \frac{du}{dt} \\
 &= 3L\delta(t)
 \end{aligned}$$

A sudden change in current causes a impluse voltage across the inductor which is not practically possible,Therefore current through an inductor can not change instantaneously.

**Example 5:**

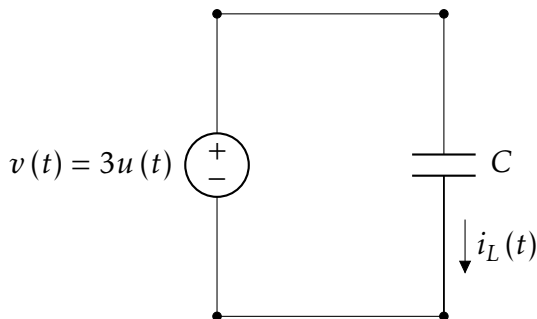

$$\begin{aligned}
 i_C(t) &= C \frac{dv}{dt} \\
 &= 3C \frac{du}{dt} \\
 &= 3C\delta(t)
 \end{aligned}$$

A sudden change in voltage causes a impluse current through the capacitor which is not practically possible,Therefore voltage across a capacitor can not change instantaneously.