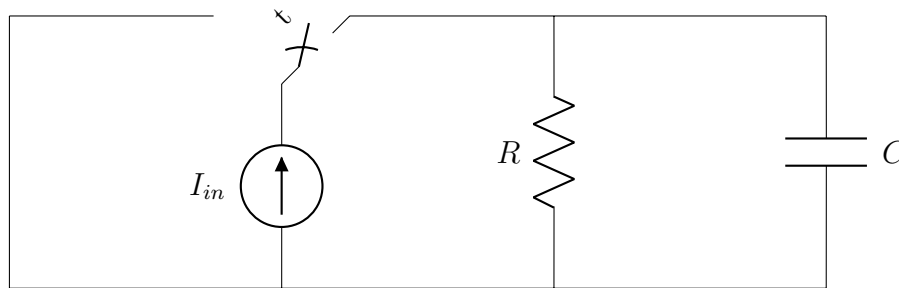



# Class Notes - Lectures 9 and 10. Scribe: Jadhav Pradeep

September 1, 2018

## 1 20-08-18



$V_c(0) = 1V$  find  $V_c(t)$

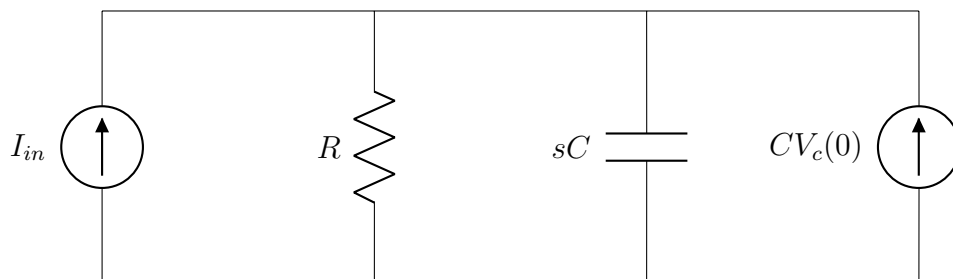

$$I_{in}(s) + CV_c(s) = \left(\frac{1}{R} + sC\right)V_c(s)$$


$$V_c(s) = \frac{RI_{in}(s)}{1 + sCR} + \frac{RCV_c(0^-)}{1 + sCR}$$

$V_c(s)$  = zero state equation + zero input solution


Zero Input :  
that means current source open  
Applying KCL

$$C \frac{dV_c}{dt} + \frac{V_c}{R} = 0$$

$$V_c = V(0^-) e^{-\frac{t}{RC}}$$

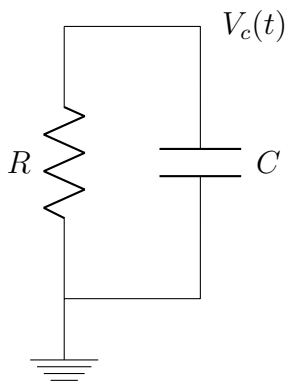

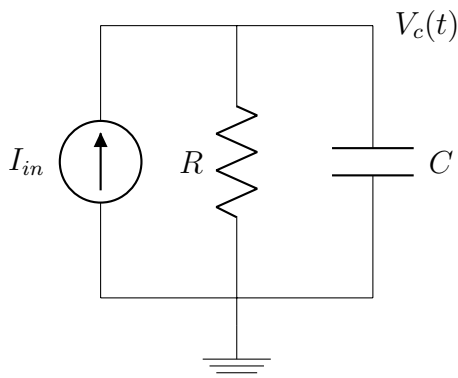Zero state response: The circuit is linear. First find the impulse response.



$$I_{in}(t) = \delta(t)$$

The claim is the entire current  $\delta(t)$  must go through the capacitor. Show this by contradiction. If a fraction  $F\delta(t)$  of the current goes through the resistor, we have

$$\begin{aligned} i_R &= F\delta(t) \\ V_R &= RF\delta(t) \\ &= V_c \\ i_C &= CRF \frac{d\delta(t)}{dt} \end{aligned}$$

At  $t=0$ , if we apply KCL at the node, we have

$$-\delta(t) + F\delta(t) + CF\dot{\delta}(t) = 0$$

KCL cannot be satisfied as there is no term to cancel  $\dot{\delta}(t)$ . Only possible solution at  $t=0$  that satisfies KCL is  $i_c(0) = \delta(t)$ . At  $t=0$

$$\delta(t) = C \frac{dV_c}{dt}$$

Therefore,


$$V_c(0^+) - V_c(0^-) = \frac{1}{c} \int_{0^-}^{0^+} \delta(t) dt$$

As  $V_C(0^-) = 0$

$$V_c(0^+) = \frac{1}{C}$$

The current impulse dumps charges onto the capacitor  $\implies$  step changes in the voltages across the capacitor

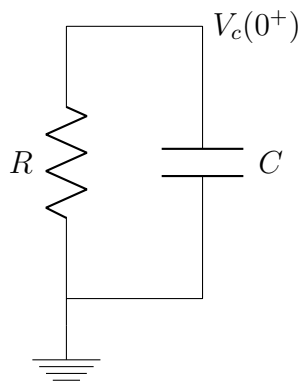For  $t > 0$ , once again the input is equal to zero. Therefore, the circuit is as follows




$$\begin{aligned} C \frac{dV_c}{dt} + \frac{V}{R} &= 0 \\ V_c(t) &= V_c(0^+) e^{\frac{-t}{RC}} u(t) \\ &= \frac{1}{C} e^{\frac{-t}{RC}} u(t) \\ &= h(t) \end{aligned}$$

For any arbitrary input current,

$$\begin{aligned} V_c(t) &= \int_0^t h(\tau) I_{in}(t - \tau) d\tau \\ h(t) &= \frac{1}{C} e^{\frac{-t}{RC}} \frac{\Omega}{s} \end{aligned}$$

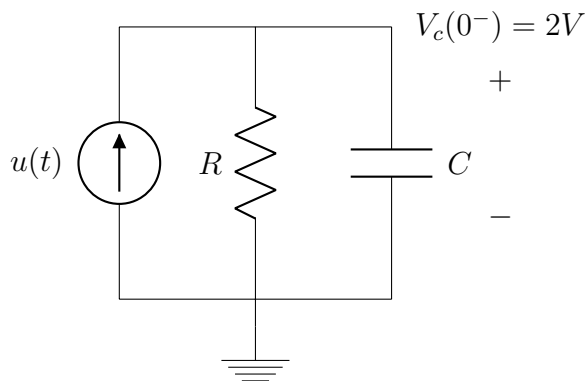If  $I_{in} = u(t)$  and  $V_C(0^-) = 2V$



Zero input solution :  $V_C(t) = 2e^{\frac{-t}{RC}} u(t)$


Zero state:

$$\begin{aligned}
 V_c(t) &= \int_0^\infty u(t-\tau) \frac{1}{C} e^{-\frac{\tau}{RC}} d\tau \\
 &= \int_0^t \frac{1}{C} e^{-\frac{\tau}{RC}} d\tau \\
 &= R(1 - e^{-\frac{t}{RC}})
 \end{aligned}$$

Total Solution :  $V_c(t) = 2e^{-\frac{t}{RC}} + R(1 - e^{-\frac{t}{RC}})$ , for  $t > 0$ .

As  $t \rightarrow \infty$  capacitor is an open ckt and  $V_c(t) \rightarrow R V$

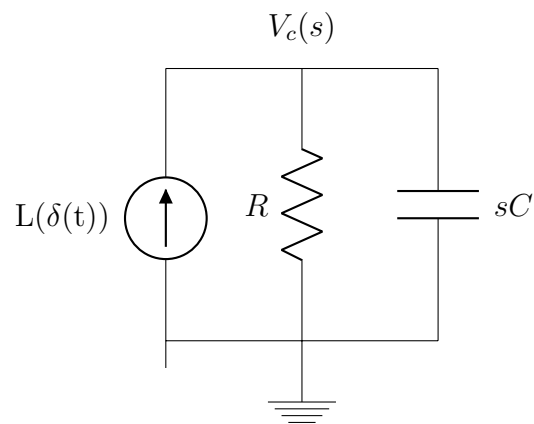We can also get the impulse response as the inverse Laplace transform of the transfer function.




$$L(\delta(t)) = 1$$

$$\begin{aligned}
 V(s) \left( \frac{1}{R} + sC \right) &= 1 \\
 &= \frac{R}{1 + sCR} \\
 H(s) &= \frac{V_c(s)}{I_{in}(s)} \\
 &= \frac{R}{1 + sCR} \\
 h(t) &= \frac{1}{C} e^{-\frac{t}{RC}} u(t)
 \end{aligned}$$


## 2 21-08-18

$$V_c(0^-) = V_{c0}$$

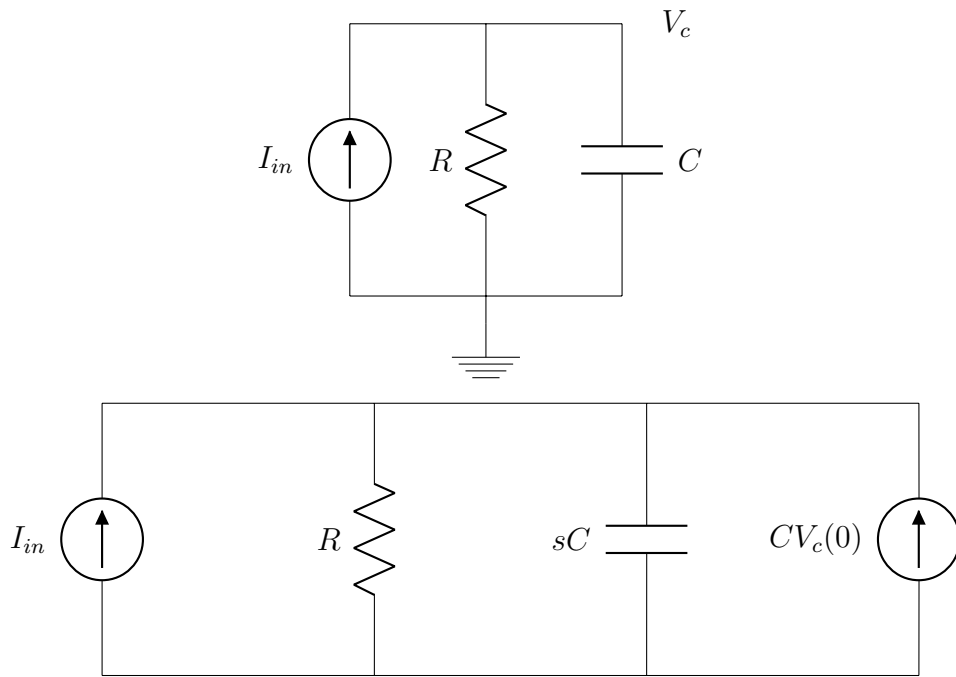


$$\begin{aligned}
 I_{in}(s) + CV_c(s) &= \left(\frac{1}{R} + sC\right)V_c(s) \\
 V_c(s) &= \frac{RI_{in}(s)}{1 + sCR} + \frac{RCV_c(0^-)}{1 + sCR} \\
 H(s) &= \frac{V_c(s)}{I_{in}(s)} \\
 &= \frac{R}{1 + sCR} \\
 h(t) &= \frac{1}{C}e^{-\frac{t}{RC}}u(t)
 \end{aligned}$$

Zero input Solution :

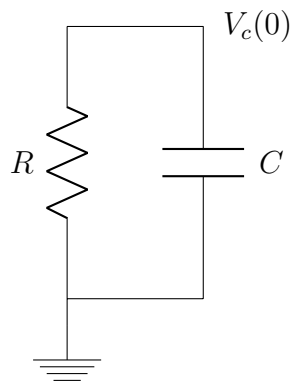


$$\begin{aligned}
 C\frac{dv_c}{dt} + \frac{v}{R} &= 0 \\
 V_c(t) &= V_c(0)e^{-\frac{t}{RC}}u(t)
 \end{aligned}$$

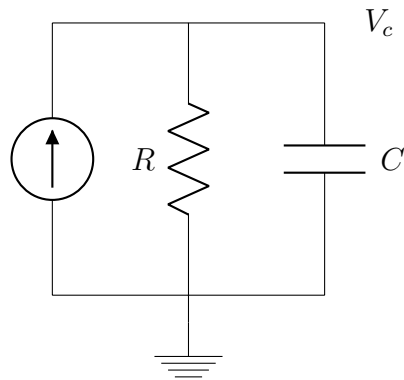
Zero State:  
 $C \frac{dV_c}{dt} = \delta(t)$



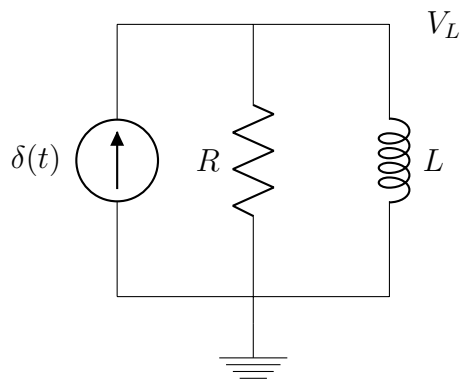No current/voltage can be  $\propto \dot{\delta}(t)$



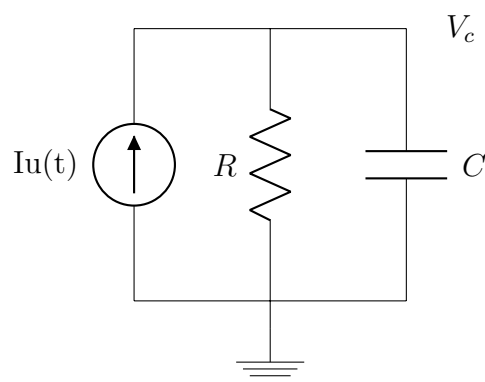If  $i_L \propto \delta(t)$ ,  $V_L \propto \dot{\delta}(t)$  and KCL not satisfied. The only way you can satisfy KCL at  $t=0$  is if  $i_R = \delta(t)$  and  $V_L = R\delta(t) = L \frac{di_L}{dt}$




$$\begin{aligned}
 V_c(t) &= V_{c0} e^{-\frac{t}{RC}} + \mathcal{L}^{-1}\left(\frac{IR}{s(1+sCR)}\right) \\
 &= V_{c0} e^{-\frac{t}{RC}} + IR(1 - e^{-\frac{t}{RC}})t > 0
 \end{aligned}$$

As  $t \rightarrow \infty$  capacitor is open ckt  $V_c(t) \rightarrow IR$ .

Natural response (complementary function) + Forced response (particular integral solution)

$$[V_{c0}e^{-\frac{t}{RC}} - IR e^{-\frac{t}{RC}}] + IR$$

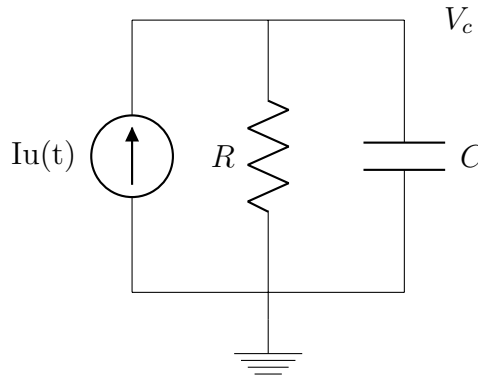Transient Solution (terms containing time constants of the circuit) + Steady state (IR).



KCL in time domain can be written as

$$C \frac{dv_c}{dt} + \frac{v_c}{R} = Iu(t)$$

$$\frac{dv_c}{dt} + \frac{v_c}{CR} = \frac{Iu(t)}{C}$$

Homogeneous solution

$$\frac{dv_c}{dt} + \frac{v_c}{CR} = 0 \tag{1}$$

Guess the solution as  $V_{cn}(t) = Ae^{\xi t}$  and substitute in equation (1)

$$A\left(\xi + \frac{1}{RC}\right)e^{\xi t} = 0$$

$$\xi = \frac{-1}{RC}$$

Therefore the natural response =  $Ae^{-\frac{t}{RC}}$ . The solution to the characteristic equation are the natural frequencies of the system.

Particular Solution or the forced solution is the steady state solution after the input is applied. After a long time, since the input is a constant, the guess for the solution is also a constant. Assume  $v_{cp} = K$  and substitute guessed solution in differential equation and solve for K. In this case,  $K = IR$ . Therefore the total solution is  $V_c(t) = Ae^{-\frac{t}{RC}} + IR$ . Solve for A by applying initial conditions at  $t = 0^+$  (after the input is applied).

$$V_c(0^+) = A + IR$$

Since  $V_c(0^+) = V_c(0^-)$ , we have  $V_c(t) = (V_{c0} - IR)e^{-\frac{t}{RC}} + IR$ .

### Question

Assume  $I_{in}(t) = e^{-2t}u(t)$ ,  $R = 1\Omega$ ,  $C = 1F$ ,  $V_{c0} = 1V$

- 1 solve in transform domain; draw circuit in s domain, Solve and find inverse transform
- 2 use  $h(t)$  and convolve with input to get zero state solution

**3** Natural + Forced response

**Answer**

**1**

$$V_c(s) = \frac{1}{s+1} + \frac{1}{(s+1)(s+2)}$$
$$v_c(t) = e^{-t} + (e^{-t} + e^{-2t}), t > 0$$

**2**  $h(t) = e^{-t}$  ; convolve with  $e^{-2t}$  to get the output. **3** Natural response :  $Ae^{-t}$  The forced response requires steady state solution of

$$\frac{dv_c}{dt} + V_c = e^{-2t}$$

Guess solution as  $Be^{-2t}$  and substitute in the differential equation. This gives  $B = -1$ . Therefore,  $V_c(t) = Ae^{-t} - e^{-2t}$ . To apply initial conditions, note that at  $t = 0^+$ ,  $V_c(0^+) = 1$ . Therefore,  $A = 2$  and  $V_c(t) = 2e^{-t} - e^{-2t}$