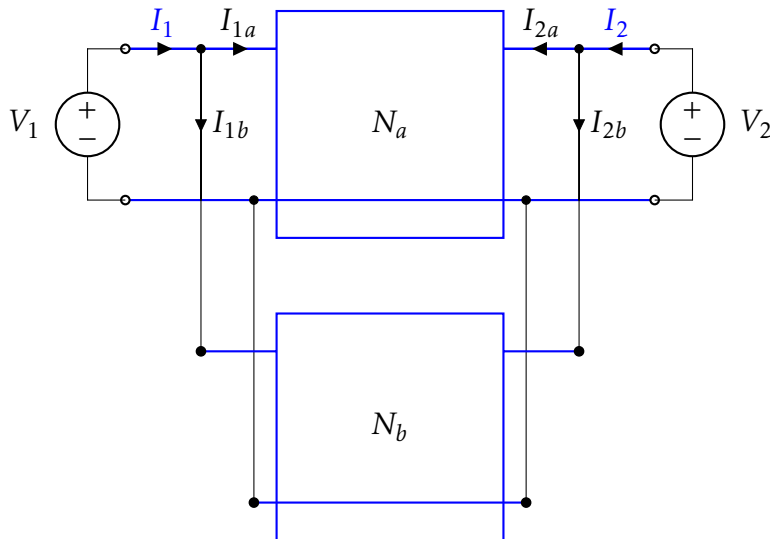


## Two port Networks - parallel and series connections.

Vinita Vasudevan

### Parallel connection



Connecting  $N_b$  to  $N_a$  should not alter the port currents in  $N_a$  when a voltage source is connected to the port. We see that  $I_1 = I_{1a} + I_{2a}$  and  $I_2 = I_{2a} + I_{2b}$ . If  $V_2 = 0$ , both  $N_a$  and  $N_b$  have port 2 shorted and an input voltage  $V_1$  at port 1.

Hence,


$$y_{11} = \frac{I_1}{V_1} = \frac{I_{1a} + I_{1b}}{V_1} = y_{11a} + y_{11b}$$

and


$$y_{21} = \frac{I_2}{V_1} = \frac{I_{2a} + I_{2b}}{V_1} = y_{21a} + y_{21b}$$

The other two parameters add in a similar fashion.

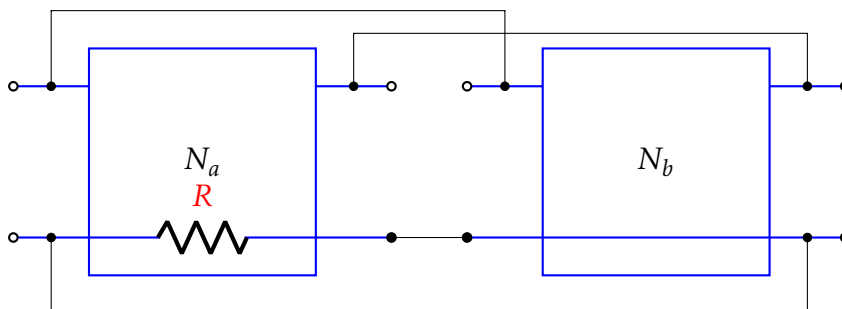This addition will not work in the following parallel connection due to the presence of the resistor  $R$ . When  $N_b$  is connected, the resistor gets shorted out altering the  $y$  parameters of  $N_a$ .



### Series connection

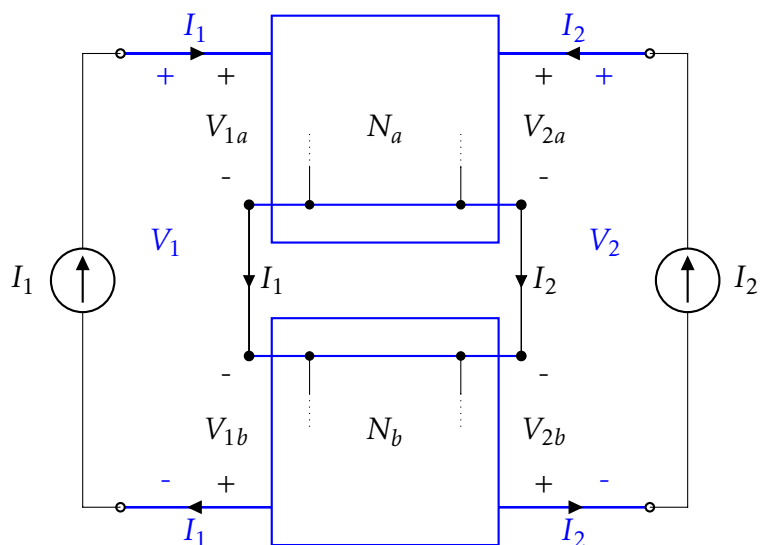

Connecting  $N_b$  to  $N_a$  should not alter the port currents in either network when a current source is connected. Note the polarities of the port voltages in  $N_b$ . The  $z$  parameters of the combined network is equal to the sum of the  $z$  parameters of  $N_a$  and  $N_b$ .


Lets say we set  $I_2 = 0$  and measure  $z_{11}$  and  $z_{21}$ . We have  $V_1 = V_{1a} - V_{1b}$  and  $V_2 = V_{2a} - V_{2b}$ . For  $N_b$ , the current  $I_1$  leaves port 1, so that  $z_{11_b} = \frac{V_{1b}}{I_1} = \frac{V_{1b}}{-I_1}$ .

$$z_{11} = \frac{V_1}{I_1} = \frac{V_{1a} - V_{1b}}{I_1} = z_{11_a} + z_{11_b}$$

$$z_{21} = \frac{V_2}{I_1} = \frac{V_{2a} - V_{2b}}{I_1} = z_{21_a} + z_{21_b}$$

The other two parameters add in a similar fashion.

### Series-Parallel connections

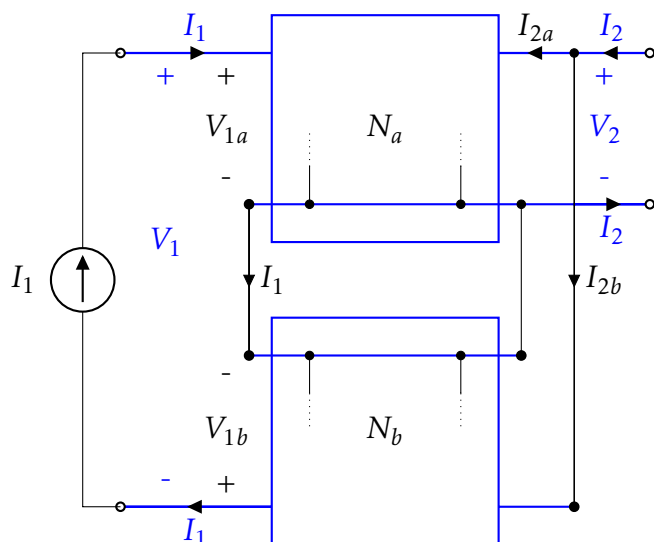

Note that  $h_{11_b} = \frac{V_{1b}}{-I_1}$  and  $h_{21_b} = \frac{I_{2b}}{-I_1}$ . Therefore,

$$V_1 = V_{1a} - V_{1b}$$

$$I_2 = I_{2a} + I_{2b}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} = h_{11_a} + h_{11_b}$$



$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} = \frac{I_{2a} + I_{2b}}{I_1} = h_{21_a} - h_{21_b}$$

Similarly  $h_{22} = h_{22_a} + h_{22_b}$  and  $h_{12} = h_{12_a} - h_{12_b}$ .

Parallel-series connections can be done similarly with  $g$ -parameters as the preferred parameters. They will add similar to  $h$ -parameters.
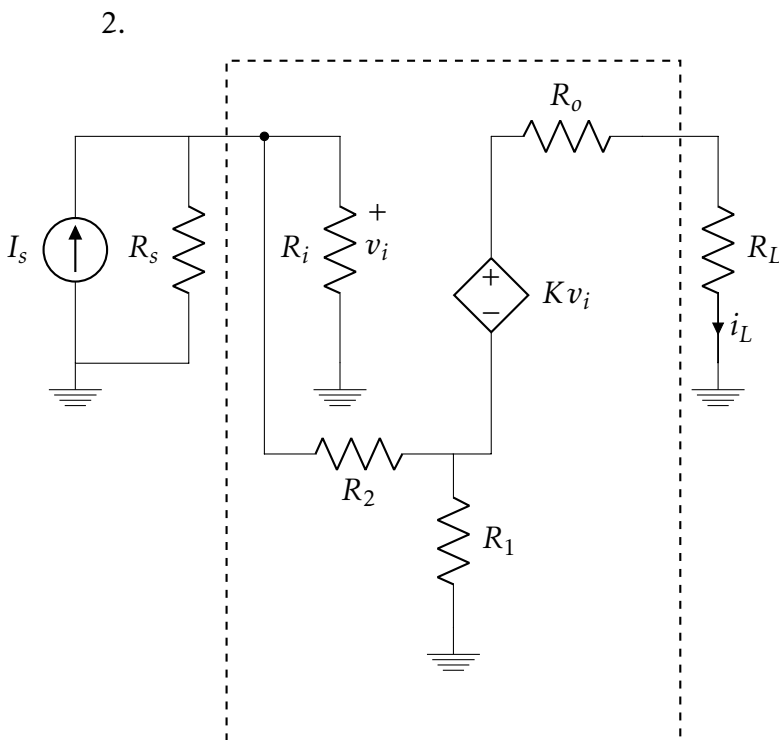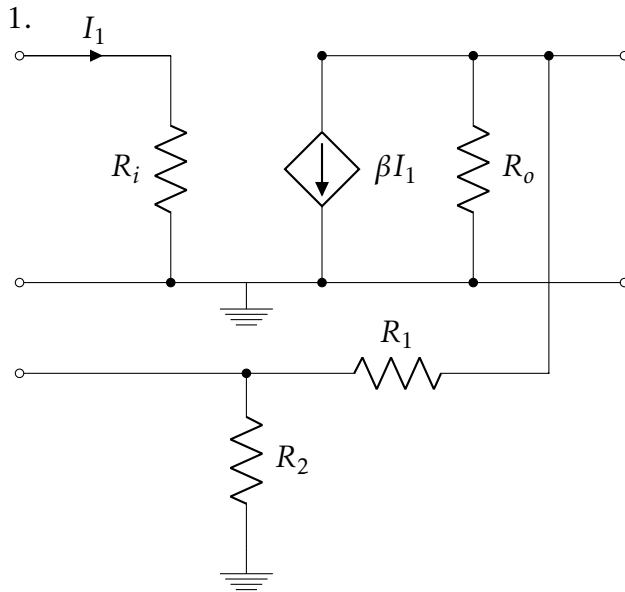
### Exercises

Which parameters are most suitable for analysis of the following networks? In each case, find the parameters of the individual and combined network.



Get the parameters for the circuit within the dashed box and find the overall current gain.