




EE2025




Lecture 3/4



Sudharsanan Srinivasan

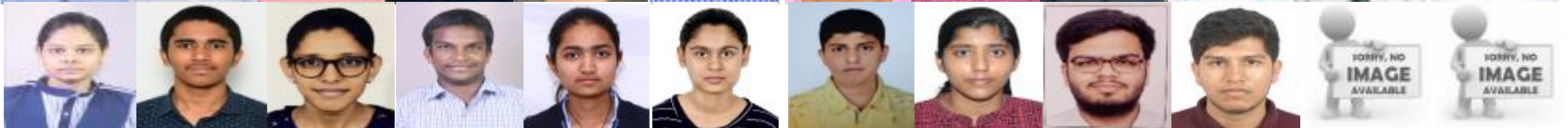

Telegraph equations

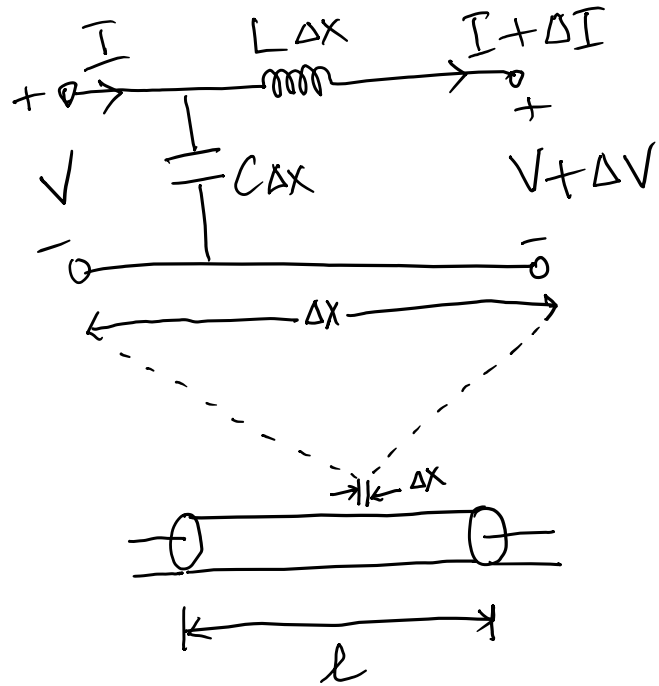

$$\Delta V = -L \Delta x \frac{\partial I}{\partial t} \Rightarrow \frac{\Delta V}{\Delta x} = -L \frac{\partial I}{\partial t}$$

$$\Delta I = -C \Delta x \frac{\partial V}{\partial t} \Rightarrow \frac{\Delta I}{\Delta x} = -C \frac{\partial V}{\partial t}$$


In the limit $\Delta x \rightarrow 0$

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t}$$

Telegraph
Equations

Impedance and delay

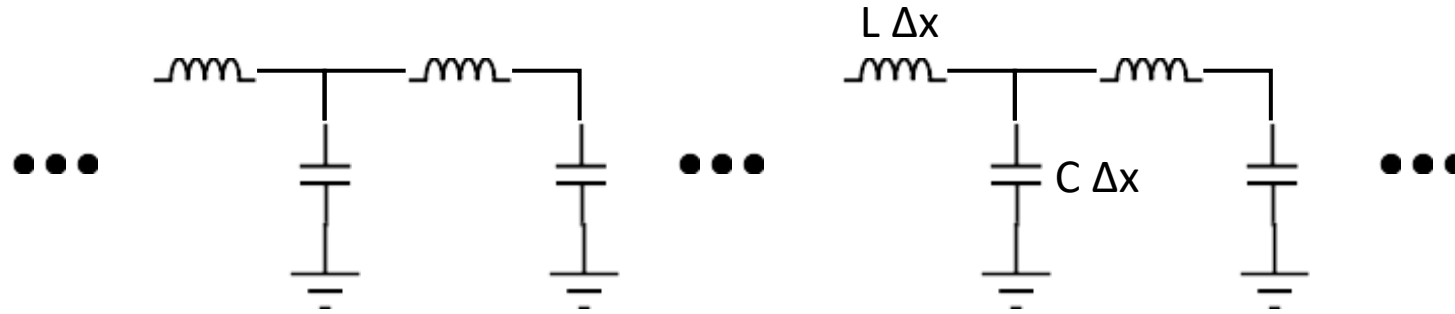


$$V(x, t) = V^+(t - x/v) + V^-(t + x/v)$$

$$I(x, t) = \frac{V^+(t - x/v)}{Z_0} - \frac{V^-(t + x/v)}{Z_0}$$

where $Z_0 = \sqrt{\frac{L}{C}}$ and $v = \frac{1}{\sqrt{LC}}$

Impedance and delay

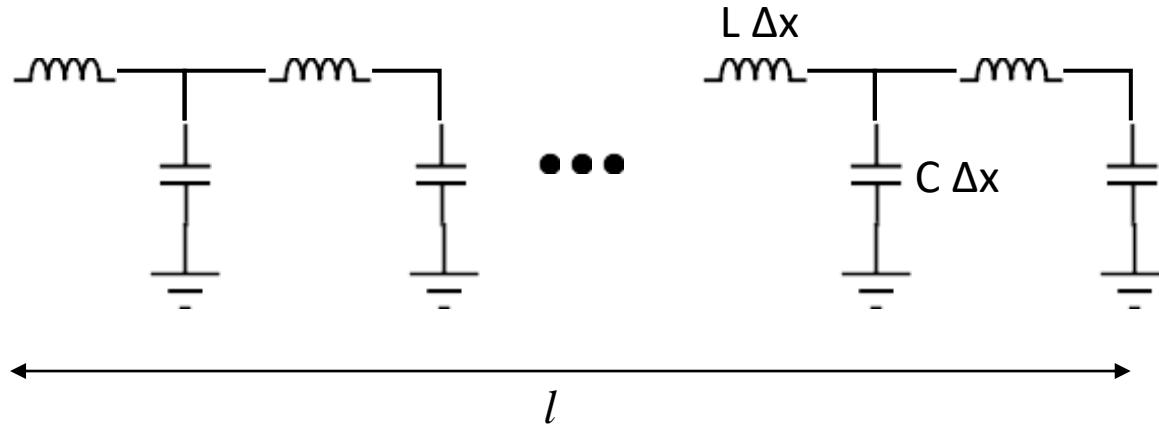


$$C_{\text{length}} = \frac{l}{Z_0}$$

$$\tau = \frac{l}{v} = \text{"speed of light delay"}$$

$$L_{\text{length}} = \tau Z_0$$


Reflection coefficient

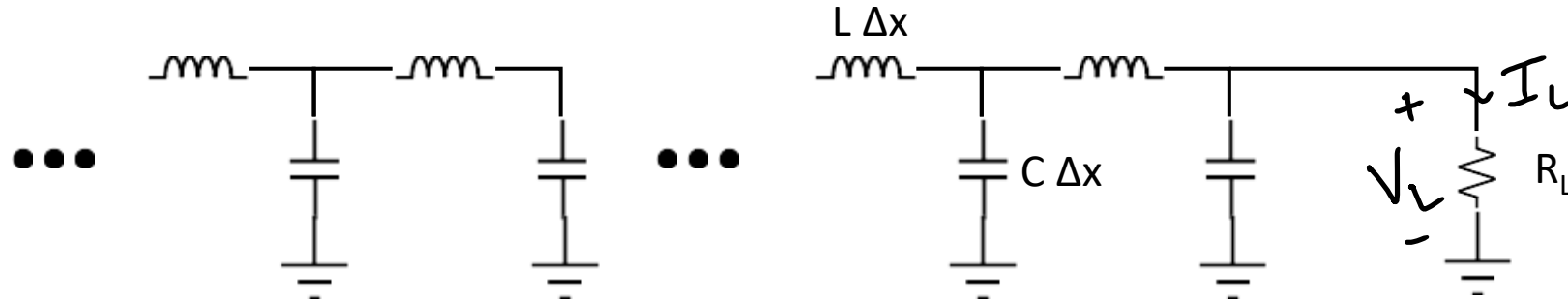

$$\Gamma_L = \frac{R_L - z_0}{R_L + z_0} = \frac{V^-}{V^+}$$

$$\Gamma_L = \frac{2R_L}{R_L + z_0} = 1 + \Gamma_L = \frac{V_L}{V^+}$$

Reflection coefficient

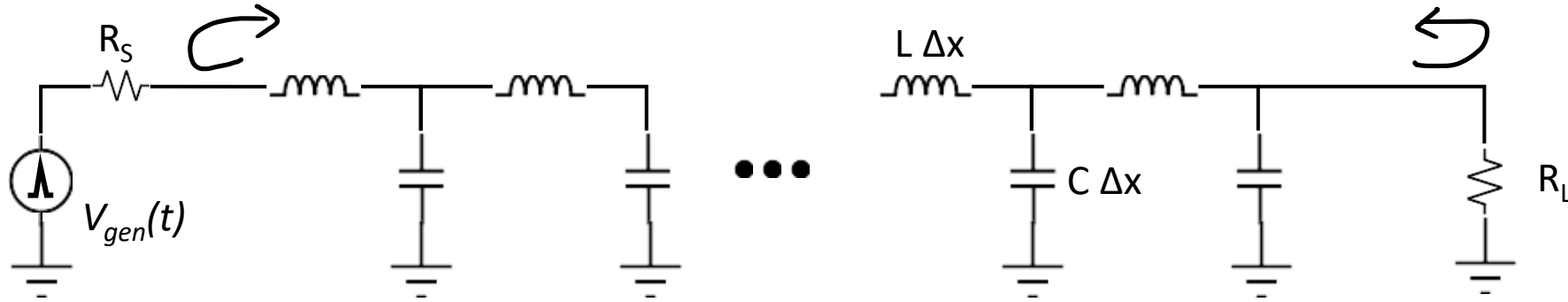

At end of line:

$$V^- = \Gamma_L V^+$$


At beginning of line:

$$V^+ = \Gamma_s V^- + T_s V_{gen}$$

$$T_s = \frac{Z_0}{Z_0 + R_s}$$


T-lines in the time domain

Lattice/Echo diagrams

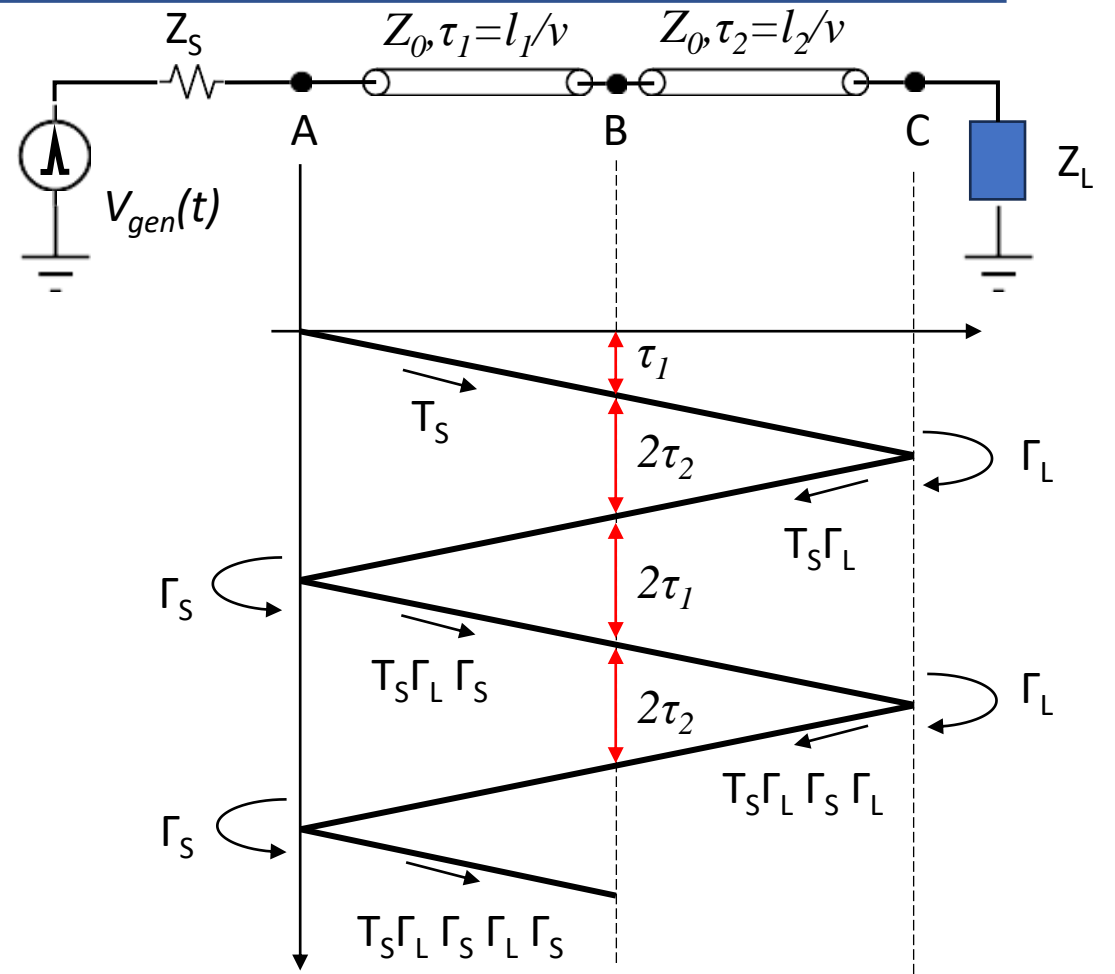


Two outcomes

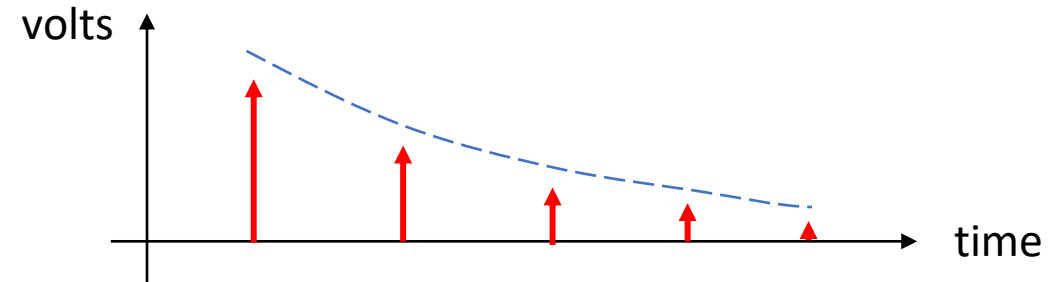If $\Gamma_L \Gamma_S$ is positive, impulse response decays exponentially



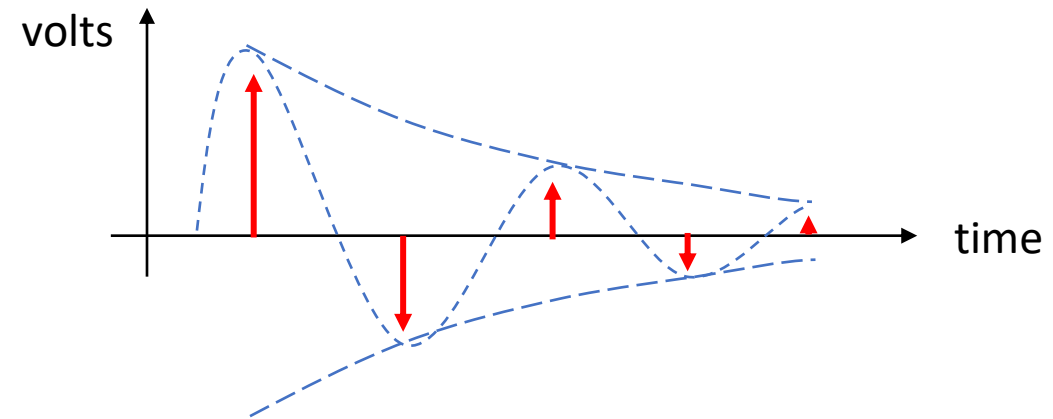
If $\Gamma_L \Gamma_S$ is negative, impulse response alternates sign \rightarrow ringing



Similar to RLC ringing, but why?

T-lines in the frequency domain
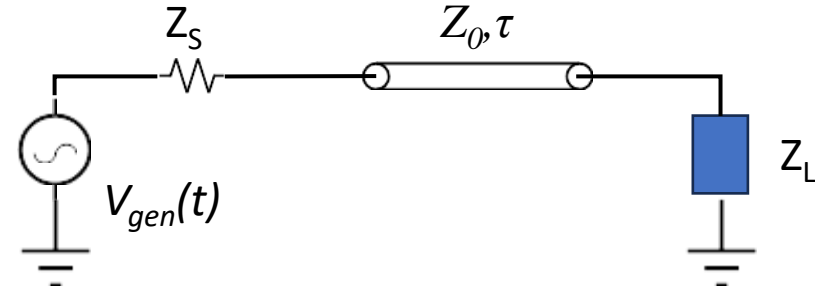
$$V_{\text{gen}}(t) = \text{Re} [V_0 e^{j\omega t}]$$



Why would we want to do this analysis?


Time-domain analysis:

- Intuitive and clear: pulses bouncing back and forth. Very difficult with reactive (L, C) load or generator impedances

Frequency-domain analysis:

- Less intuitive.
- Easy with reactive (L, C) load or generator impedances
 - (1) standing waves
 - (2) Smith Chart

Generalized distributed model

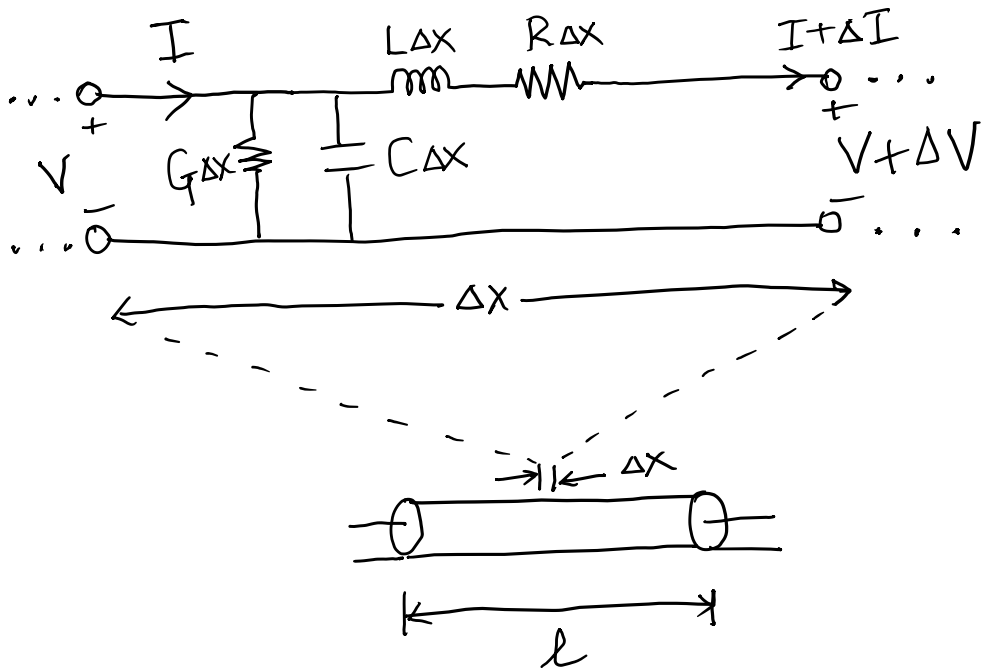

$$\Delta V = -(R + j\omega L)I \Delta x$$

$$\Delta I = -(G + j\omega C)V \Delta x$$

$$\frac{d^2 V}{dx^2} = \gamma^2 V$$

$$\frac{d^2 I}{dx^2} = \gamma^2 I$$

where

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\gamma = \alpha + j\beta$$

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$



$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

Extra


Back-up on digital lines




Low Z_0

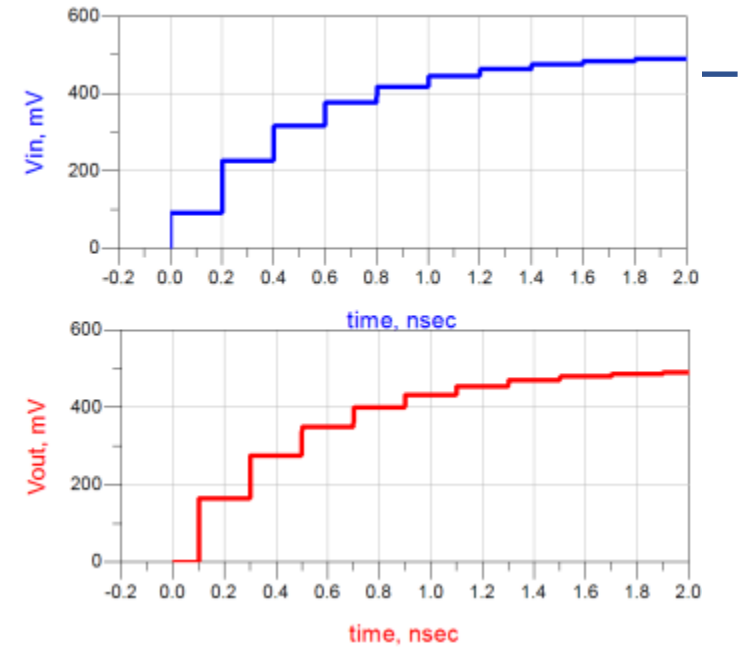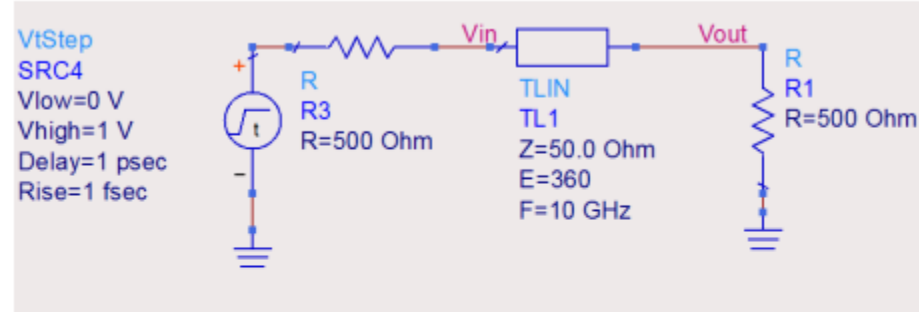

$$L = Z_0 \tau, C = \tau / Z_0$$

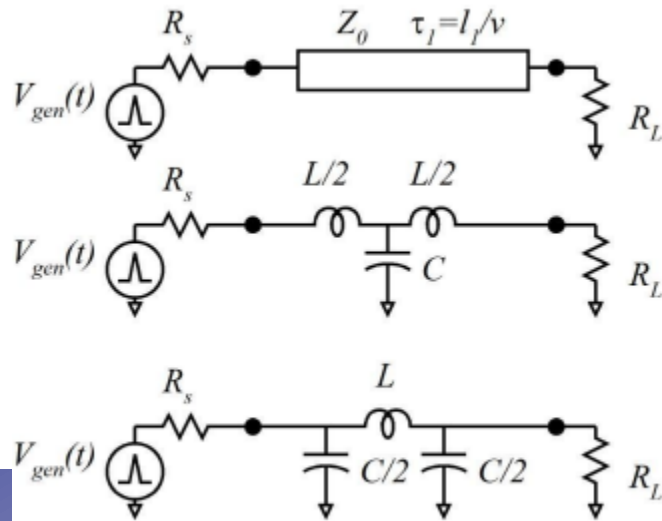

Approximate model



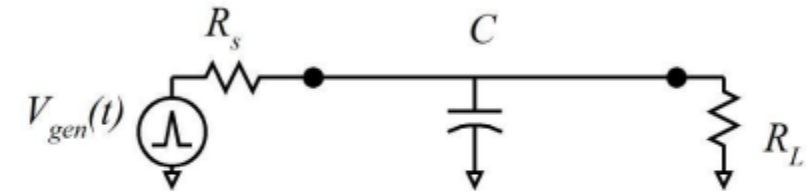


$$L / (R_L + R_s) \ll (R_L \parallel R_s) C$$


→ neglect inductor

RC circuit → charging.


High Z_0

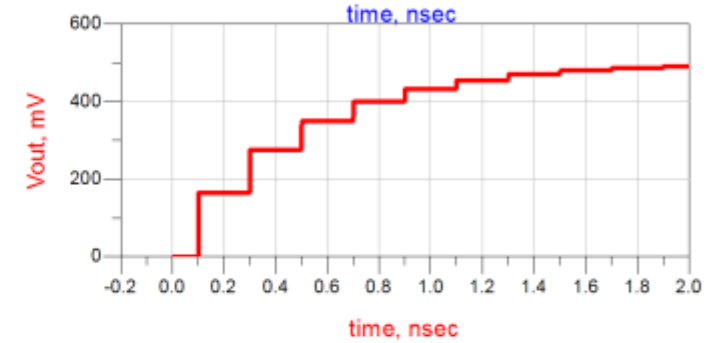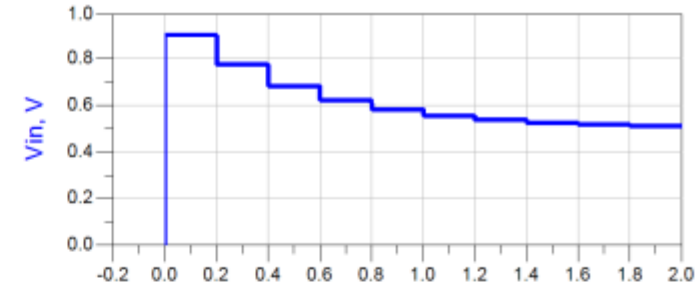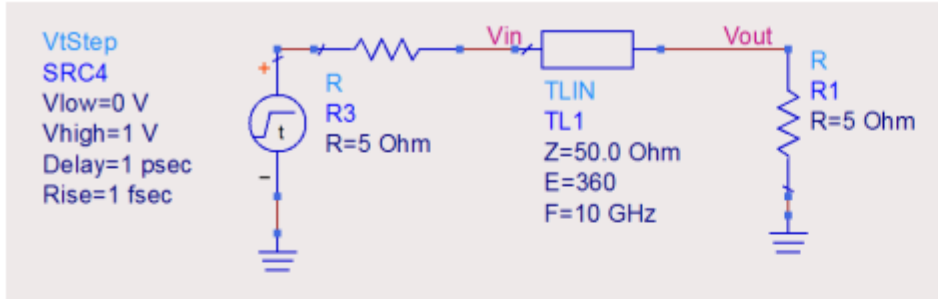

$$L = Z_0 \tau, C = \tau / Z_0$$

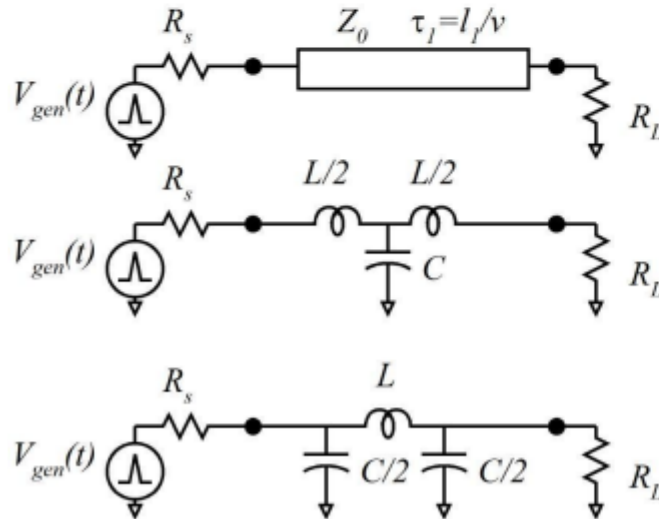

Approximate model


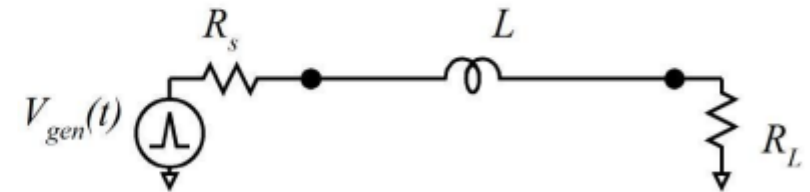


$$L / (R_L + R_s) \gg (R_L \parallel R_s) C$$


→ neglect capacitor

RL circuit → charging.


$$R_L \ll R_S$$

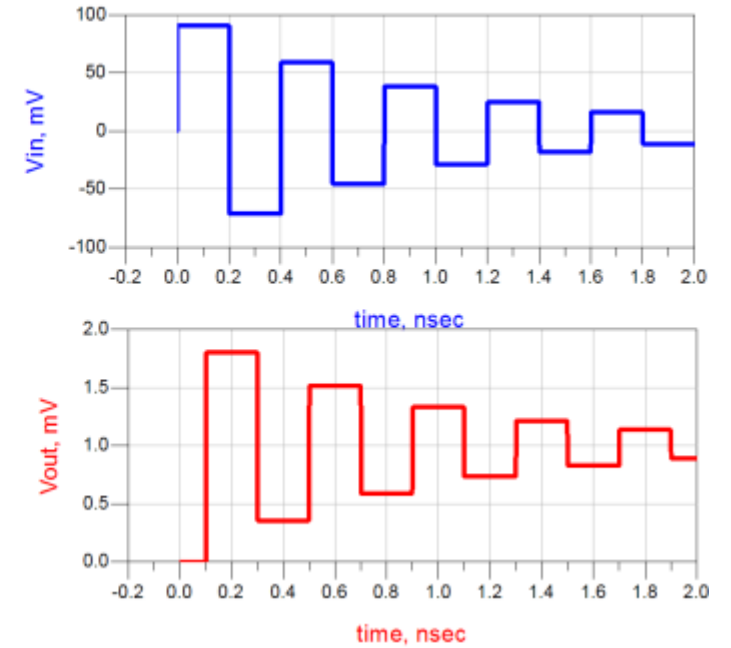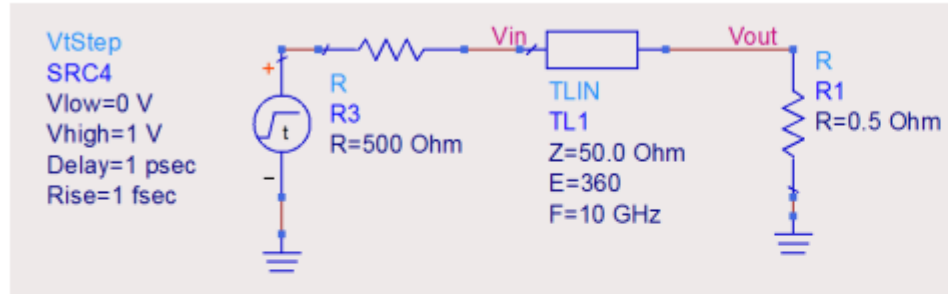

$$L = Z_0 \tau, C = \tau / Z_0$$

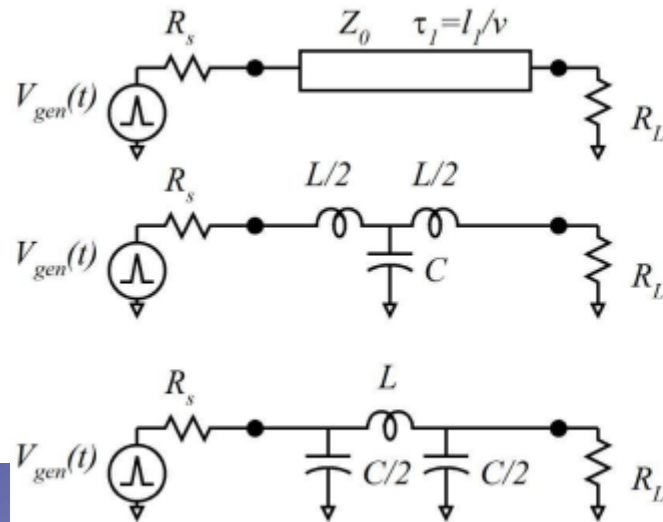

Approximate model

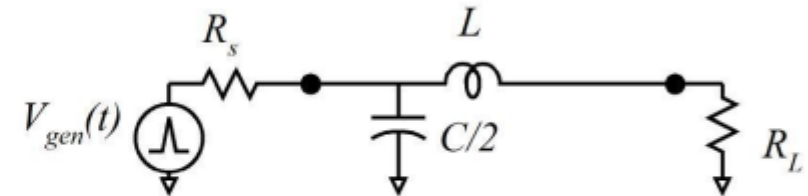

$$R_L C / 2 \ll R_S C / 2$$

→ neglect 2nd capacitor

RLC circuit → ringing

