



# EE2025



# Lecture 5



Sudharsanan Srinivasan




# Summary


- Since the electromagnetic field underlying voltage and current signals travel at a finite speed, a delay is induced in carrying information from the source to the load over a finite piece of a transmission line.
- A lossless transmission line can be modeled using a distributed LC ladder circuit.
- The model leads to wave-like solutions ( $t \pm x/v$ ) traveling in opposite directions
- The transmission line is characterized by an impedance  $Z_0 = \sqrt{L/C}$ , and the delay  $\tau = \ell \sqrt{LC}$
- When there is a discontinuity in the transmission line, reflections occur causing echoes on the line.
- The reflection and transmission coefficient characterizes the voltages and currents at the junction.
- Since reflection and transmission are local events they are not influenced by non-local impedances.

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$

$$T_s = \frac{Z_0}{Z_0 + R_s}$$

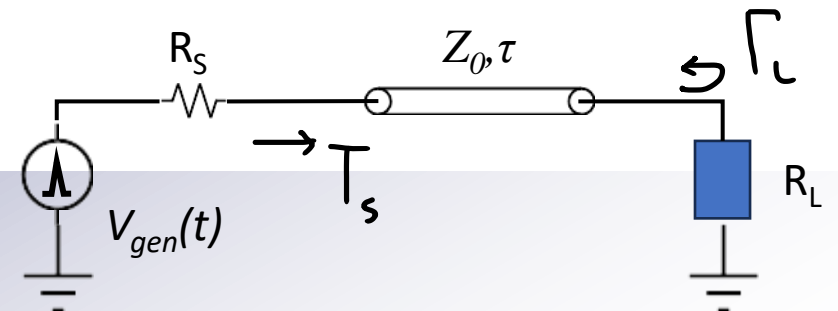

# Generalized distributed model

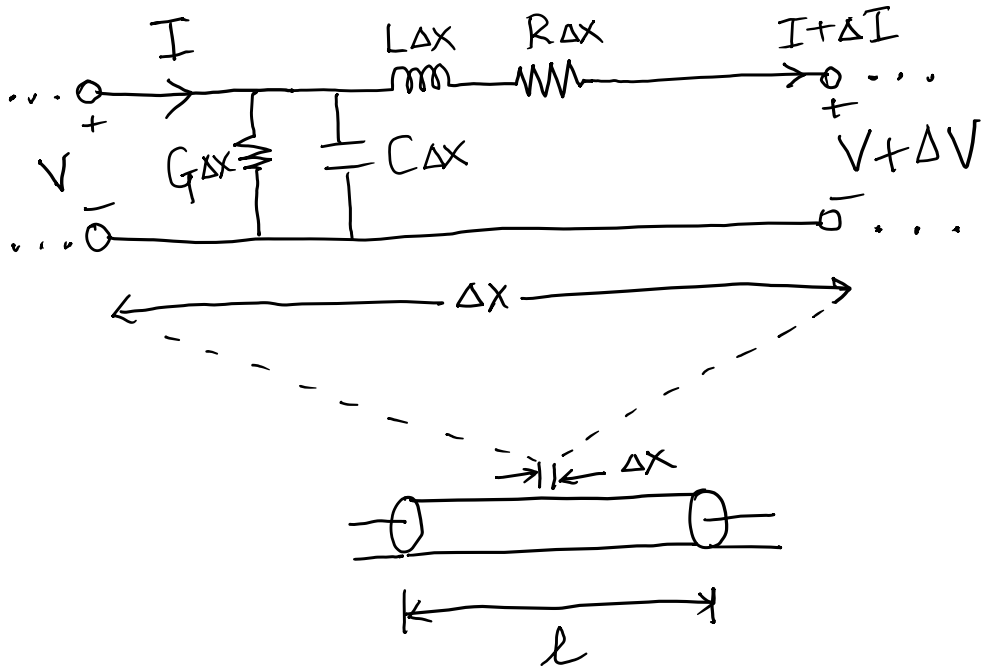

$$V(t) = \text{Re} [V e^{j\omega t}]$$

$$I(t) = \text{Re} [I e^{j\omega t}]$$

$$\left. \begin{aligned} \Delta V &= -(R + j\omega L) \Delta x I \\ \Delta I &= -(G + j\omega C) \Delta x V \end{aligned} \right\} \Rightarrow \begin{aligned} \frac{dV}{dx} &= -(R + j\omega L) I \\ \frac{dI}{dx} &= -(G + j\omega C) V \end{aligned}$$

$$\frac{d^2 V}{dx^2} = \gamma^2 V$$

$$\frac{d^2 I}{dx^2} = \gamma^2 I$$

where

$$\gamma^2 = (R + j\omega L)(G + j\omega C)$$

$$\gamma = \alpha + j\beta$$

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

where is the  $(t - \frac{x}{v})$ ?



# Phase and attenuation constant

$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x} \quad \text{where} \quad \gamma^2 = (R + j\omega L)(G + j\omega C) = (\alpha + j\beta)^2$$
$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

$$V(t) = \text{Re} \left[ V^+ e^{-\alpha x} e^{j(\omega t - \beta x)} + V^- e^{-\alpha x} e^{j(\omega t + \beta x)} \right] \quad \left( \text{Comparing to } \left( t - \frac{x}{v} \right) \right)$$

$e^{j\omega \left( t - \frac{\beta x}{\omega} \right)} \Rightarrow v = \frac{\omega}{\beta}$

Phase  $\phi_{V^+} = \angle V^+ + \omega t - \beta x$

$$\beta \Delta x = 2\pi \Rightarrow \Delta x = \frac{2\pi}{\beta} = \lambda \quad \text{or} \quad \beta = \frac{2\pi}{\lambda} \quad \left( \frac{\text{rads}}{\text{m}} \right)$$

Amplitude =  $|V^+| e^{-\alpha x}$        $\alpha$   $\left( \frac{\text{neper}}{\text{m}} \text{ or } \frac{\text{dB}}{\text{m}} \right)$



# Wave amplitudes and Impedance

$$\frac{dV}{dx} = -(R + j\omega L)I$$

$$\frac{dI}{dx} = -(G + j\omega C)V$$


$$V = V^+ e^{-\gamma x} + V^- e^{\gamma x}$$

$$I = I^+ e^{-\gamma x} + I^- e^{\gamma x}$$

$$\frac{V^+}{I^+} = -\frac{V^-}{I^-} = Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$V = V^+ e^{-\gamma x} + V^- e^{+\gamma x}$$
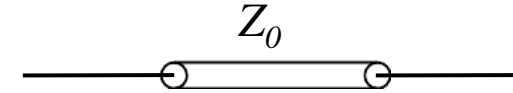
$$I = \frac{V^+}{Z_0} e^{-\gamma x} - \frac{V^-}{Z_0} e^{\gamma x}$$



Check  $R = G = 0$

$$Z_0 = \sqrt{\frac{L}{C}}$$

# Reflection coefficient

$$\begin{aligned}\Gamma(l) &= \frac{V^- e^{\gamma(-l)}}{V^+ e^{-\gamma(-l)}} \\ &= \Gamma(0) e^{-2\gamma l}\end{aligned}$$


$$\Gamma(0) = \Gamma_L$$

$$\begin{aligned}V(l) &= V^+ e^{\gamma l} [1 + \Gamma(l)] \\ I(l) &= \frac{V^+}{Z_0} e^{\gamma l} [1 - \Gamma(l)]\end{aligned}$$

$$Z(l) = Z_0 \left[ \frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right]$$

$$\text{or } \Gamma(l) = \frac{Z(l) - Z_0}{Z(l) + Z_0}$$
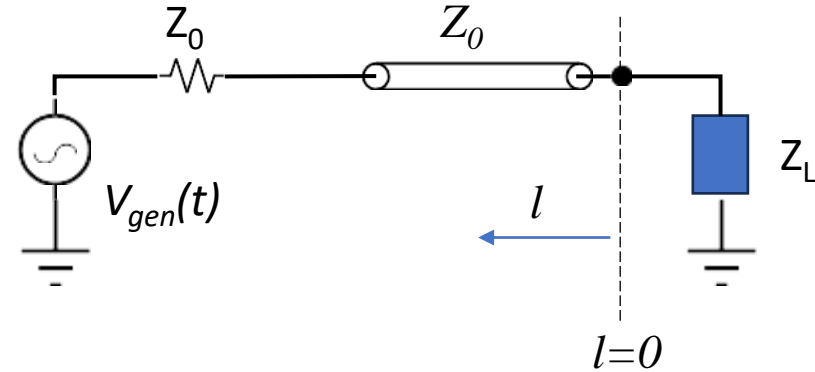
$$\Rightarrow \Gamma_L = \Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0}$$



# Impedance transformation

$$Z(l) = Z_0 \left[ \frac{1 + \Gamma(l)}{1 - \Gamma(l)} \right]$$

$$\Gamma(0) = \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= Z_0 \left[ \frac{1 + \Gamma(0) e^{-2\gamma l}}{1 - \Gamma(0) e^{-2\gamma l}} \right]$$


$$Z(l) = Z_0 \left[ \frac{Z_L \cosh(\gamma l) + Z_0 \sinh(\gamma l)}{Z_L \sinh(\gamma l) + Z_0 \cosh(\gamma l)} \right]$$

*normalized impedance*

$$\bar{Z}(l) = \frac{Z(l)}{Z_0} = \frac{\bar{Z}_L \cosh(\gamma l) + \sinh(\gamma l)}{\bar{Z}_L \sinh(\gamma l) + \cosh(\gamma l)}$$

where  $\bar{Z}_L = \frac{Z_L}{Z_0}$

*nothing special about this pt.*

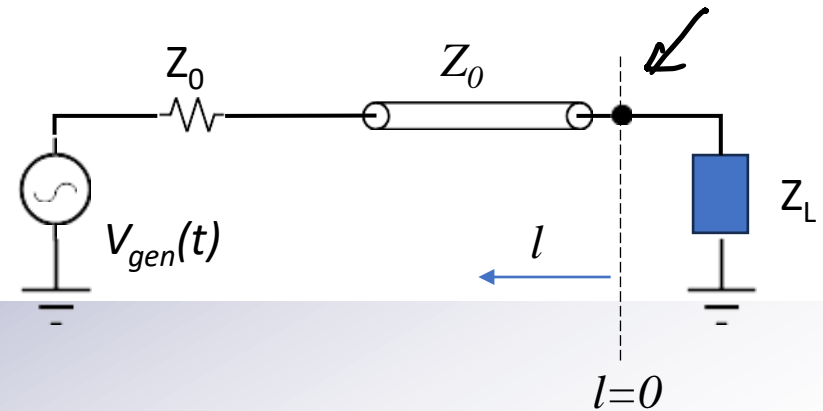

# Loss-less and low loss transmission lines

$$\text{Loss-less : } R = G = 0 \Rightarrow \gamma = j\omega\sqrt{LC} \Rightarrow \alpha = 0, \beta = \omega\sqrt{LC}$$

$$\text{Low-loss : } R \ll \omega L, G \ll \omega C$$

$$v = \frac{1}{\sqrt{LC}} = \frac{\omega}{\beta}$$

$$\gamma = \sqrt{j\omega L \left(1 + \frac{R}{j\omega L}\right) j\omega C \left(1 + \frac{G}{j\omega C}\right)}$$

$$= j\omega\sqrt{LC} \left\{ 1 - \frac{jR}{2\omega L} - \frac{jG}{2\omega C} \right\}$$

$$\beta = \omega\sqrt{LC} \quad \alpha = \left[ \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} \right]$$

$$\alpha \ll \beta$$





# VSWR

$$\text{Loss-less} \Rightarrow \alpha = 0 \quad \gamma = j\beta = j\omega\sqrt{LC}$$

$$V(l) = V^+ e^{j\beta l} + V^- e^{-j\beta l}$$

$$I(l) = \frac{V^+}{Z_0} e^{j\beta l} - \frac{V^-}{Z_0} e^{-j\beta l}$$

$$\Gamma(l) = \frac{V^-}{V^+} e^{-2j\beta l} = \Gamma_L e^{-2j\beta l}$$

(No other source for  $V^-$  other than refl. @ load.)

$\Gamma_L$  is complex in general  $\Gamma_L = |\Gamma_L| e^{j\phi}$

$$V(l) = V^+ e^{j\beta l} [1 + |\Gamma_L| e^{j(\phi - 2\beta l)}]$$

$$I(l) = \frac{V^+}{Z_0} e^{j\beta l} [1 - |\Gamma_L| e^{j(\phi - 2\beta l)}]$$

when  $(\phi - 2\beta l) = 2m\pi$   
 $m \in \mathbb{Z}$

$V$  is maximum  
 $I$  is minimum

when  $\phi - 2\beta l = (2n+1)\pi$   
 $n \in \mathbb{Z}$

$V$  is min  
 $I$  is max



# VSWR (contd...)

$$V_{\max} = |V^+| (1 + |\Gamma_L|)$$

$$V_{\min} = |V^+| (1 - |\Gamma_L|)$$

$$I_{\min} = \frac{|V^+|}{Z_0} (1 - |\Gamma_L|)$$

$$I_{\max} = \frac{|V^+|}{Z_0} (1 + |\Gamma_L|)$$

$$VSWR (P) = \frac{V_{\max}}{V_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

$$\text{or } |\Gamma_L| = \frac{P - 1}{P + 1}$$

# Impedance transformation on loss-less line

$$Z(l) = \frac{V(l)}{I(l)} = Z_0 \left[ \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}} \right]$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$Z(l) = Z_0 \left[ \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{j Z_L \sin \beta l + Z_0 \cos \beta l} \right]$$

$$\bar{Z}(l) = \frac{Z(l)}{Z_0} = \left[ \frac{\bar{Z}_L \cos \beta l + j \sin \beta l}{j \bar{Z}_L \sin \beta l + \cos \beta l} \right]$$

↑  
normalized

$$Z(l)_{\max} = \frac{V_{\max}}{I_{\min}} = Z_0 \left[ \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \right], R_{\max} = Z_0 \rho$$

$$Z(l)_{\min} = \frac{V_{\min}}{I_{\max}} = \frac{Z_0}{\rho} = R_{\min}$$



# Periodicity

$$Z(l) = Z_0 \left[ \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{j Z_L \sin \beta l + Z_0 \cos \beta l} \right]$$

## Case II

put  $l \rightarrow l + \lambda/4$

$$\cos \beta \left( l + \frac{\lambda}{4} \right) = -\sin \beta l$$

$$\sin \beta \left( l + \frac{\lambda}{4} \right) = \cos \beta l$$

$$\frac{Z(l)}{Z_0} = \frac{-Z_L \sin \beta l + j Z_0 \cos \beta l}{j Z_L \cos \beta l - Z_0 \sin \beta l} =$$

## Case I

put  $l \rightarrow l + \frac{\lambda}{2}$

$$\cos \beta \left( l + \frac{\lambda}{2} \right) = -\cos \beta l$$

$$\sin \beta \left( l + \frac{\lambda}{2} \right) = -\sin \beta l$$

$$\Rightarrow \boxed{Z \left( l + \frac{\lambda}{2} \right) = Z(l)}$$

(remember  $\beta = \frac{2\pi}{\lambda}$ )

$$\frac{j Z_L \sin \beta l + Z_0 \cos \beta l}{Z_L \cos \beta l + j Z_0 \sin \beta l} = \frac{Z_0}{Z(l)}$$

Impedance  
inverts  
itself



# $Z_0$

---

$$Z(l) = Z_0 \left[ \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{j Z_L \sin \beta l + Z_0 \cos \beta l} \right]$$

when  $Z_L = Z_0$

$$Z(l) = Z_0 \quad \forall l$$

$$\Gamma(l) = 0 \quad \forall l$$

} "Matched load"