




# EE2025





# Lecture 6/7



Sudharsanan Srinivasan

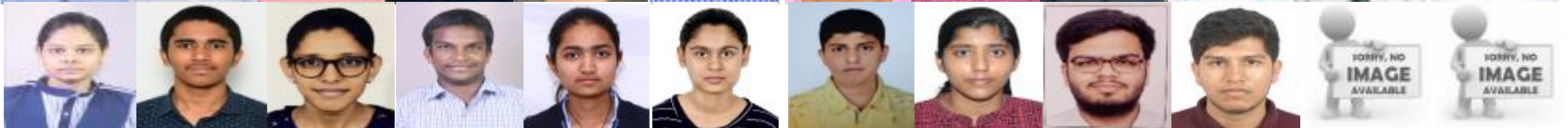

# How to find $V^+$ ?

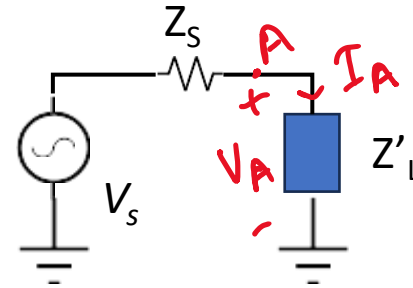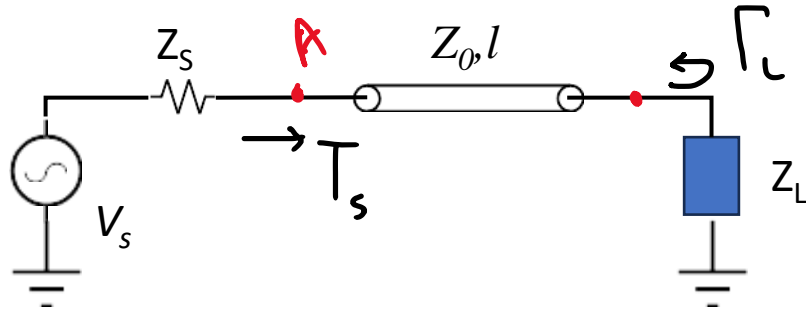

# Power transfer

@ LOAD  $P_L = \frac{1}{2} \operatorname{Re}(VI^*)$  why?

$$V = V^+ + V^- = V^+ e^{j\beta l} [1 + \Gamma_L e^{-2j\beta l}]$$

$$I = I^+ + I^- = \frac{V^+}{Z_0} e^{j\beta l} [1 - \Gamma_L e^{-2j\beta l}]$$

$$l=0 \quad P_L = \frac{1}{2} \operatorname{Re} \left[ \frac{|V^+|^2}{Z_0} (1 + \Gamma_L)(1 - \Gamma_L) \right]$$

$$= \frac{1}{2} \frac{|V^+|^2}{Z_0} \{1 - |\Gamma_L|^2\}$$

# Power transfer

---

$$P_{inc} = \frac{1}{2} \operatorname{Re} [V^+ I^{+*}]$$

$$= \frac{|V^+|^2}{2Z_0}$$

$$P_{refl} = \frac{1}{2} \operatorname{Re} [V^- I^{-*}]$$

$$= - |\Gamma_L|^2 \frac{|V^+|^2}{2Z_0}$$

↑  
traveling  
back to source

$$P_L = P_{inc} + P_{refl} = \frac{|V^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

# Power transfer

Power anywhere along the line

$$\begin{aligned}\text{Complex power } P(l) &= \frac{1}{2} V(l) I(l)^* \\ &= \frac{1}{2} \left[ V^+ e^{j\beta l} (1 + \Gamma_L e^{-2j\beta l}) \right] \left[ \frac{V^+}{Z_0} e^{j\beta l} (1 - \Gamma_L e^{-2j\beta l}) \right]^* \\ &= \frac{1}{2} \frac{|V^+|^2}{Z_0} \left\{ 1 - |\Gamma_L|^2 + \text{Im}(\Gamma_L e^{-2j\beta l}) \right\}\end{aligned}$$

$$\text{Re}[P(l)] = \frac{|V^+|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

"independent of 'l' "

$$\text{Im}(P(l)) = \frac{|V^+|^2}{2Z_0} \text{Im}(\Gamma_L e^{-2j\beta l})$$

"reactive power"

