
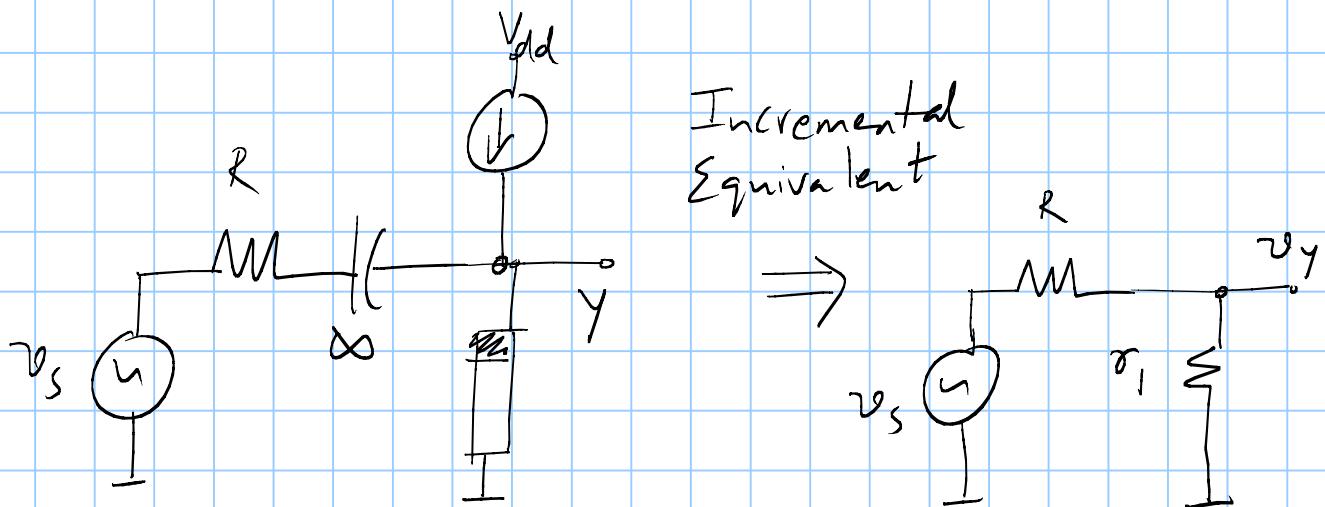


SOLUTIONS TO QUIZ 1

Note Title

9/23/2007

Problem 1

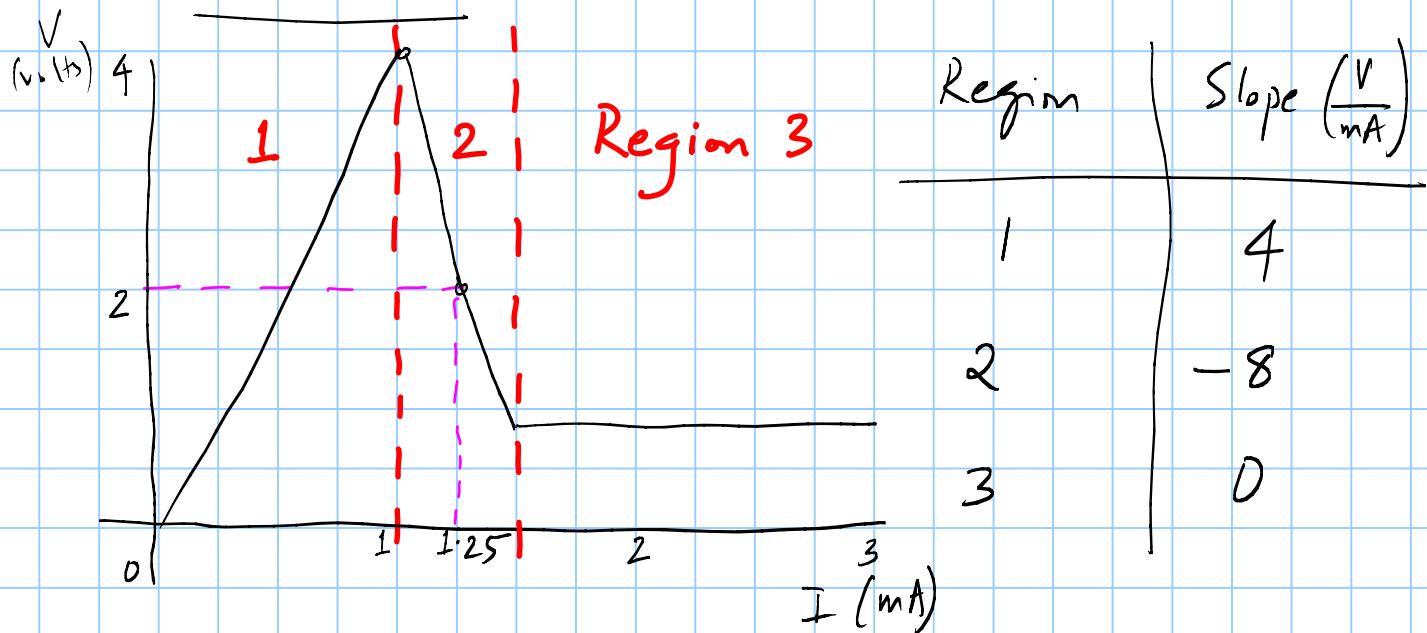

Amplifier

r_i is the incremental resistance of the wormister

$$\text{Incremental gain} = \frac{v_y}{v_s} = \frac{r_i}{r_i + R}$$

Part (a) : To get incremental gain, r_i must be
NEGATIVE

\Rightarrow Must bias the wormister in Region 2

Part (b) : Want gain of -4

$$\Rightarrow -4 = \frac{r_1}{r_1 + R} \Rightarrow -4r_1 - 4R = r_1 \\ \Rightarrow R = -1.25 r_1$$

From the V-I characteristics, $r_1 = -8\text{ k}\Omega$

$$\Rightarrow R = 10\text{ k}\Omega$$

Part (c) : Swing limit computation

The incremental gain is -4

Let V_o be the quiescent voltage at Y

The total voltage at Y is

$$\underbrace{V_o}_{\text{Quiescent}} + \underbrace{(-4)v_s}_{\text{Incremental}}$$

To maximize output swing without distorting,
the output sinewave must JUST begin to clip
at BOTH extremes

$$\Rightarrow V_o + 4v_A = 0.8 \text{ Volts}$$

$$\Delta V_o - 4v_A = 4 \text{ Volts}$$

$$\Rightarrow V_o = \frac{0.8 + 4}{2} = 2.4 \text{ Volts}$$


A quiescent voltage of 2.4 Volts maximizes
output swing. This corresponds to a quiescent

$$\text{current of } 1\text{mA} + \frac{(2.4 - 4)}{-8\text{V/mA}} = 1.2\text{mA}$$

$I = 1.2\text{mA}$ maximizes the output swing

Part (d)

Incremental 2 port parameters

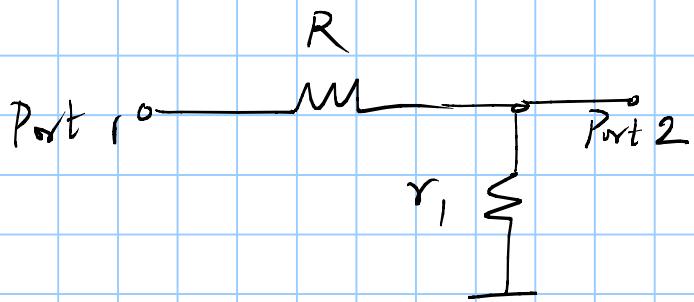

Denote

$$G = 1/R, g_1 = 1/r_1$$

$$Y_{11} = G$$

$$Y_{12} = -G$$

$$Y_{21} = -G$$


$$Y_{22} = g_1 + G$$

$$\Rightarrow Y_{11} = 0.1\text{mS} \quad Y_{12} = -0.1\text{mS} \quad Y_{21} = -0.1\text{mS}$$

$$Y_{22} = -0.125\text{mS} + 0.1\text{mS} = -0.025\text{mS}$$

$$Y = \begin{bmatrix} 0.1\text{mS} & -0.1\text{mS} \\ -0.1\text{mS} & -0.025\text{mS} \end{bmatrix}$$


Problem 2:

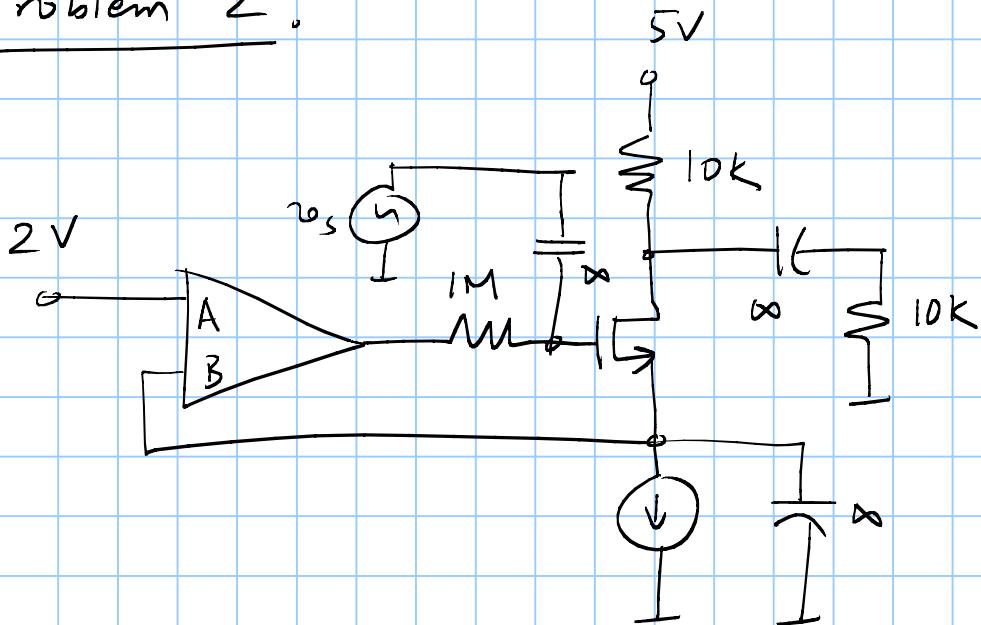

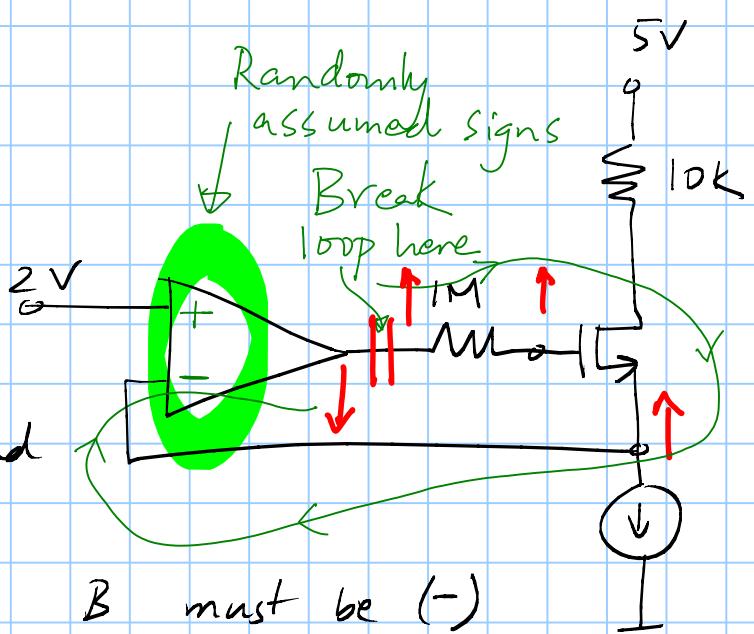
Part (a)

Determining the signs on
the opamp

Break loop at a
convenient location and
go around the loop
 \Rightarrow A must be (+)



Part (b)

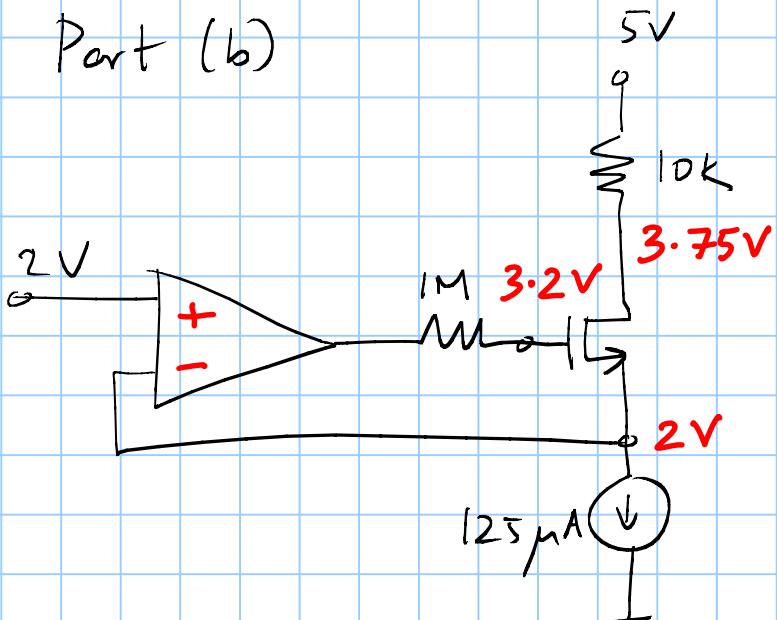

Circuit for Calculating
operating point

$$V_T = 0.7 \text{ V} \quad \frac{W}{L} = 10$$

$$K = 100 \text{ mA/V}^2$$

$\mu_{n\text{Cox}}$


$$\frac{1}{2} \frac{100 \mu A}{V^2} 10 (V_{GS} - 0.7)^2 = 125 \mu A$$

$$\Rightarrow (V_{GS} - 0.7)^2 = \frac{125}{500} \Rightarrow V_{GS} = 0.7 + 0.5 \text{ V}$$

$$\Rightarrow V_G = 2 \text{ V} + V_{GS} = 3.2 \text{ V}$$

$$V_D = 5 \text{ V} - 125 \mu A \cdot 10 \text{ k} = 3.75 \text{ V}$$

Part (b) Incremental equivalent circuit

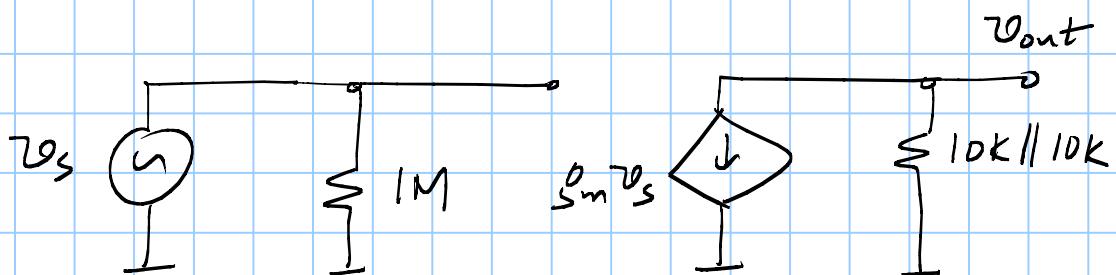

$$\text{Incremental gain} = \frac{V_{out}}{V_s} = -\text{gm} (5 \text{ k})$$

$$\text{gm} = \frac{2I}{V_{GS} - V_T} = \frac{250 \mu A}{0.5 \text{ V}} = 500 \mu S$$

$$\Rightarrow \frac{V_{out}}{V_s} = -2.5$$

Part (c) Limit for cutoff

$$V_{max,1} = \frac{I}{\text{gm}} = \frac{125 \mu A}{500 \mu S} = 0.25 \text{ Volts}$$

Limit for saturation

$$\begin{aligned} \text{Total drain voltage} &= 3.75 - 2.5 V_A \sin \omega t \\ \text{Total gate voltage} &= 3.2 + V_A \sin \omega t \end{aligned}$$

$$\Rightarrow 3.75 - 2.5 v_A = 3.2 + v_A - V_T$$

$$\Rightarrow v_A = \frac{3.75 + 0.7 - 3.2}{3.5} = \frac{1.25}{3.5} \approx 0.3 \text{ Volts}$$

\Rightarrow Maximum input amplitude for distortion free operation is

$$\underline{\min \{ 0.25 \text{ Volts}, 0.3 \text{ Volts} \} = 0.25 \text{ Volts}}$$