
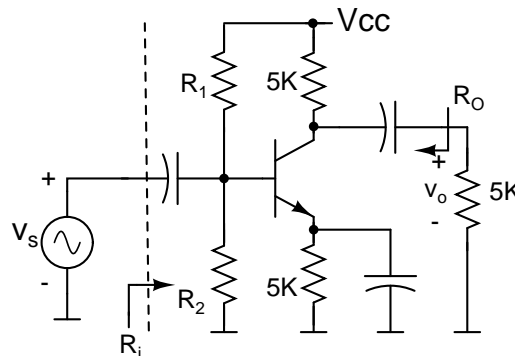


ANALOG CIRCUITS : PROBLEM SET 4a

shanthi@ee.iitm.ac.in

Problem 1

For the transistor shown $\frac{\eta kT}{q} = 40 \text{ mV}$, $\beta = 99$, $V_{BE} = 0.65 \text{ V}$ nominal. Find V_{CEQ} , R_i , R_o , A_v and the incremental power gain. Assume $v_L = (1 \text{ mV}) \sin \omega t$.

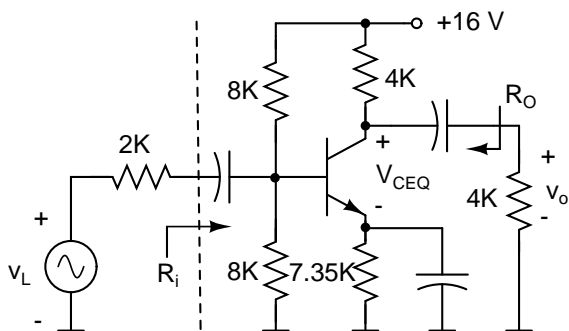


Problem 3

ANSWERS:

$V_{CEQ} = 4.65 \text{ V}$, $R_i = 2 \text{ K}$, $R_o = 4 \text{ K}$, $A_v = -24.75$, Power gain = 1225.125

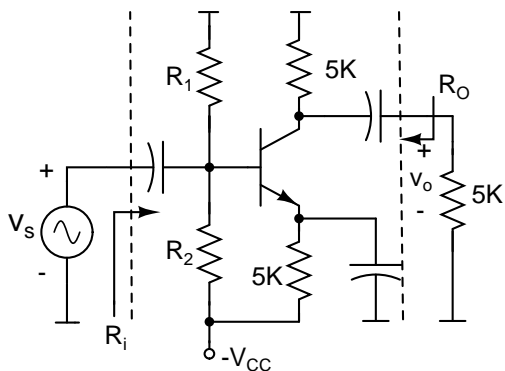Problem 2


In the circuit shown, use $\alpha = 0.995$, $V_T = 25 \text{ mV}$. V_{CEQ} must be 5 V and R_i - the resistance presented by the circuit to the driving region v_s must be 1.5 K. Use $V_{BE} = 0.7 \text{ V}$ nominally. Calculate V_{CC} , R_1 & R_2 to get a small signal gain of -200.




ANSWERS :

$V_{CC} = 25.101 \text{ V}$, $R_1 = 8.822 \text{ K}$, $R_2 = 6.609 \text{ K}$

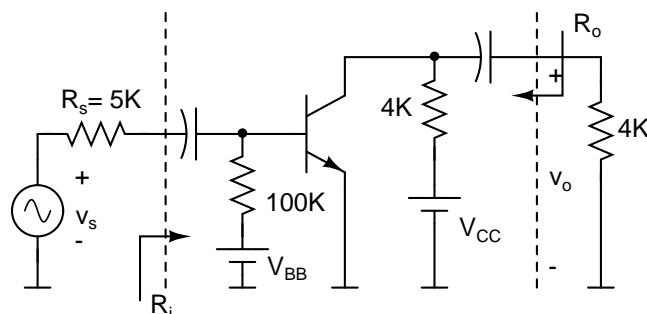How would the answers be affected for the following circuit



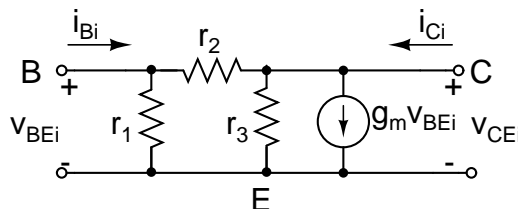
The input signal is small. A more comprehensive linear small-signal incremental equivalent circuit for the transistor is given in the form show below, where r_1 , r_2 , r_3 , g_m are 4 K Ω , 8 M Ω , 100 K Ω & 50 mS. Calculate R_i , R_o and $\frac{v_o}{v_s}$.



ANSWERS :

$R_i = 3.671 \text{ K}$, $R_o = 3.654 \text{ K}$, $\frac{v_o}{v_s} = -41.499$

Problem 4

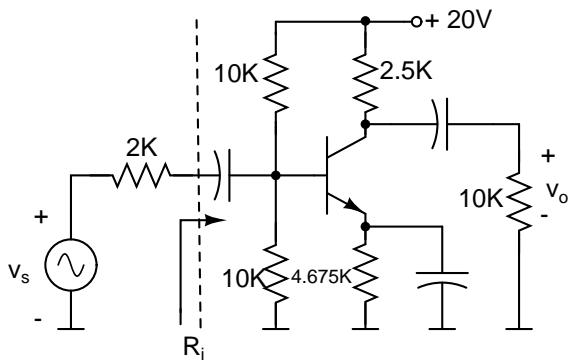


The applied signal is very small. Calculate R_i and $\frac{v_o}{v_s}$ using the approximate equivalent circuit for the transistor. V_T and β are 30 mV and 199 respectively.

ANSWERS :

$$R_i = 1.875 \text{ K}, \frac{v_o}{v_s} = -64.194$$

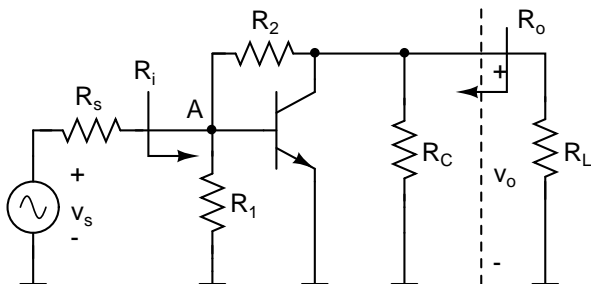Problem 5

The signal picture of a CE amplifier is as shown.




Find R_i , R_o and $\frac{v_o}{v_s}$ in terms of g_m , β and r_o . Find their limits when $\beta \rightarrow \infty$. The signal is small.

Problem 6

Assume in the figure shown that g_m is high enough to make the incremental voltage gain $\frac{v_o}{v_s}$ independent of the device. Assume all capacitors are large. Also assume that $aR \parallel (1-a)R \ll (1+\beta)R$. Take $V_{EB} = 0.7$ normally; $I_{EQ}R_e = 4.3\text{V}$.


A gain of -4 is needed with the circuit being just capable of handling a maximum amplitude of 2V for the input sinusoid v_s . V_{ee} should be minimum possible for the specified $I_{EQ}R_e$. Calculate R_1 , R_e , V_{ee} and a .

Next remove the external load of 12K. What will the limiting swings possible for v_o on either side now? To what maximum amplitude will you have to restrict v_s if v_o is to be a full undistorted sine wave?

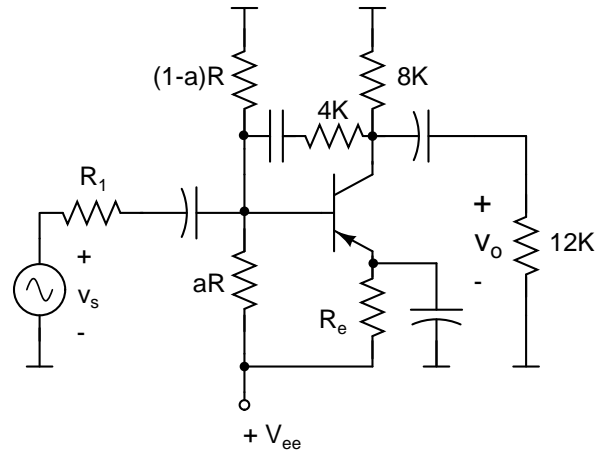

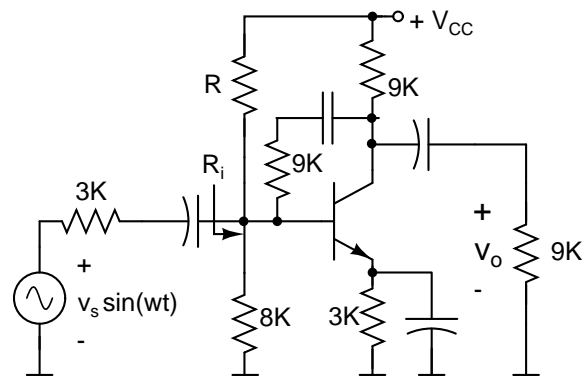Problem 7

The input sine wave has $v_s = 2.5 \text{ V}$. To get an undistorted output within swing limits, calculate V_{CC} and R . Take V_{BE} nominal = 0.65V. Also calculate R_i for small signals given that $\beta = 100$ and $V_T = 25 \text{ mV}$.




ANSWERS :

$$V_{CC} = 38.15 \text{ V}, R = 29.448 \text{ K}, R_i = 29.5 \Omega$$

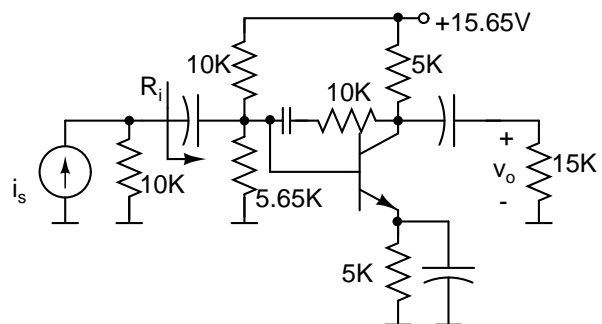Problem 8

$V_{BE} = 0.65 \text{ V}$ nominally. $V_T = 25 \text{ mV}$. For small signals, find R_i and $\frac{v_o}{i_s}$. Assume $\beta = 250$.





ANSWERS :

$$R_i = 87.914 \Omega, \frac{v_o}{i_s} = -9445.43 \Omega$$

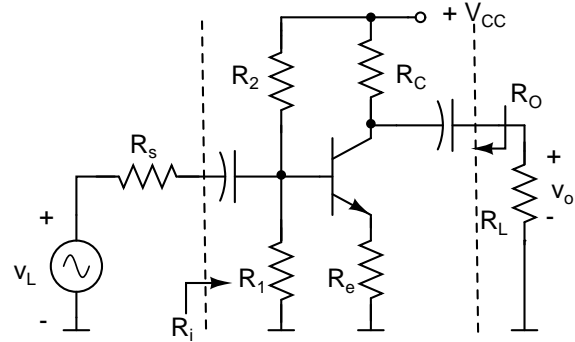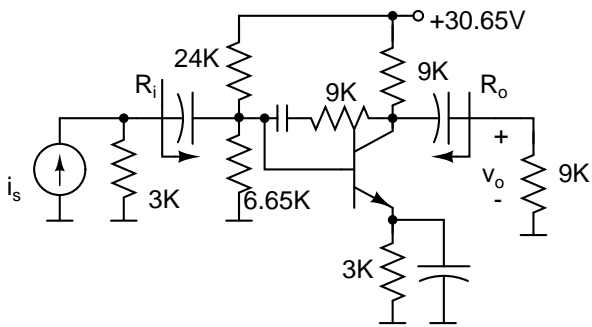Problem 9


Assuming the signal to be very small calculate R_i , R_o and exact value of $\frac{v_o}{i_s}$. $\beta = 200$ and $r_o = 50 \text{ K}$.




Calculate for small signals R_i , R_o and v_o/v_s . (This is just circuit analysis). Give the limits for R_i , R_o and the conditions to be satisfied to make gain independent of the device. When $g_m \rightarrow \infty$, what type of a controlled source does the amplifier act like ?

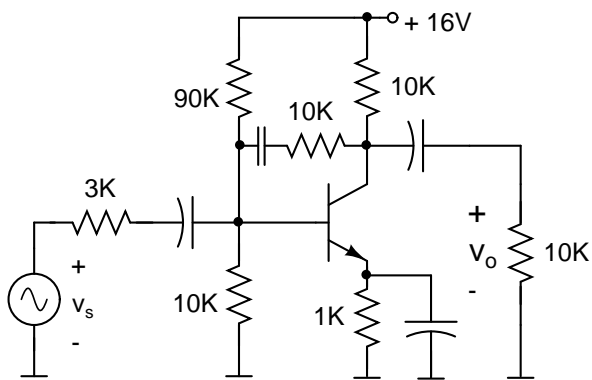Problem 10

Take $V_T = 25 \text{ mV}$, $\beta = 99$ and $V_{BE} = 0.6$ nominally. Determine $\frac{v_o}{v_s}$, R_i , R_o and the output swing limits.



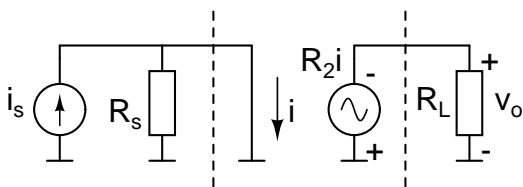This configuration acts like a current controlled voltage source (low input and output impedance) when $g_m \rightarrow \infty$.



Answers:


$$v_{o\max} = 4.4 \text{ V}, v_{o\min} = -3.333 \text{ V}, R_i = 72.581 \Omega, R_o = 377.113 \Omega$$

Problem 11

Yet another configuration of a CE amplifier is a shown.

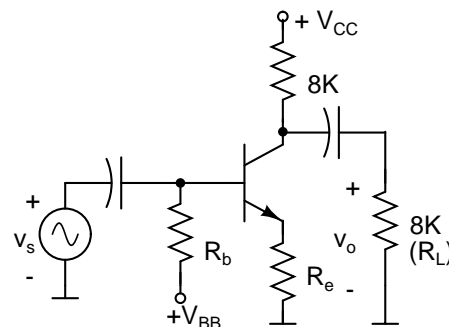Problem 12

The capacitances are very large. v_o , the output sinusoid, is to be linked with the input sinusoid by a device independent gain factor of 2, with a limiting amplitude of 8 V before clipping sets in. v_o should just begin to distort at both the extremes.



Find V_{CC} , V_{BB} and R_e . V_{BE} is 0.7V, nominally. Given that $R_b \ll (\beta_{DC} + 1)R_e$, comment on the stability of the transistor operating point - that is, compute the change in emitter current when the nominal V_{BE} changes by $\pm 0.1 \text{ V}$ due to device variability and/or ambient temperature.

Now let $R_L \rightarrow \infty$. What are the limiting swings now possible for v_o on the either side? To what value will you restrict the amplitude of v_s to get an undistorted sinusoidal output?


ANSWERS :

$$V_{CC} = 32.7 \text{ V}; V_{BB} = 4.7 \text{ V}; R_e = 2 \text{ K}. \text{ when } R_L \rightarrow \infty : v_{o\max} = 16 \text{ V}, v_{o\min} = -9.6 \text{ V}, v_{s\max} = 2.4 \text{ V}$$

Problem 13

Take $V_{BE} = 0.6 \text{ V}$ nominally. Use the approximate equivalent circuit with $\frac{\eta k T}{q} = 24 \text{ mV}$ and $\alpha = 0.99$. Calculate R_i

and R_o for small signals.

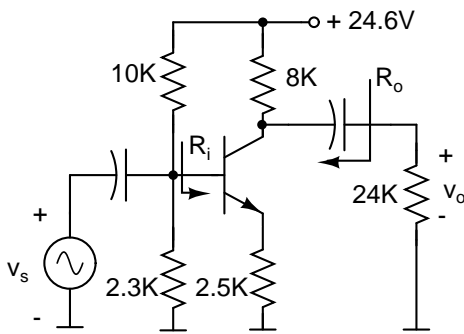

In the large signal case, if v_o is to be free of distortion determine the maximum possible positive and negative value of the input waveform.

ANSWERS :


$V_{smax} = 2.11 \text{ V}, v_{smin} = -4 \text{ V}, R_i = 251.5 \text{ K}, R_o = 8 \text{ K}.$

Problem 14

Design a circuit to get a gain of -2, independent of the device and free of distortion. $V_{omax} = 10 \text{ V}$, with output being a sinusoid. The waveform of V_o should just begin to distort at both extremes. R_i should be in the range of 5K, R_s is given to be 20Ω and R_L is 10K.

Problem 15


(Common Collector amplifier)

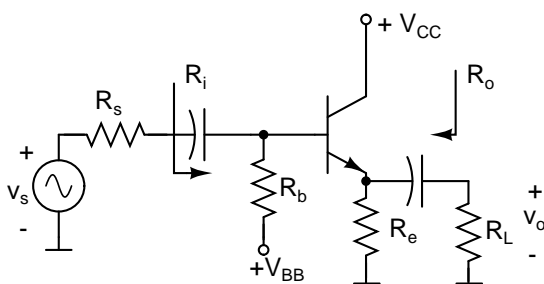

Calculate for small signals R_i, R_o and $\frac{v_o}{v_s}$. (Once again circuit analysis). Give the limits for R_i, R_o and the conditions to be satisfied to make gain independent of the device. What type of a controlled source does this amplifier act like when $g_m \rightarrow \infty$.

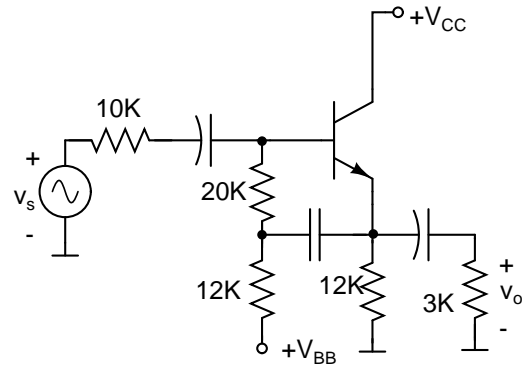Problem 16

The transistor has very high β . With minimum possible V_{BB} and V_{CC} , the circuit should be able to handle the given drive of 5V maximum amplitude. Calculate the values of V_{BB} and V_{CC} required.




When the 3K lead is removed, determine the swing possible for v_o on either side, and the maximum amplitude to which v_s must now be restricted if v_o is to be a full undistorted sine wave. Take $V_{BE} = 0.7 \text{ V}$, nominally. Assume all capacitances are large.

ANSWERS :

$V_{CC} = 35.7 \text{ V}, V_{BB} = 30.7 \text{ V}, V_{omax} = 5 \text{ V}, V_{omin} = -15 \text{ V}$
 v_s can have an amplitude of 5 V.

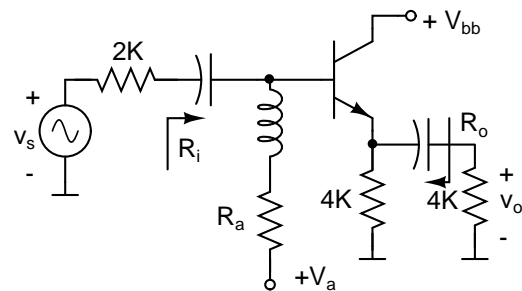Problem 17

For small signals calculate R_i, R_o and $\frac{v_o}{v_s}$. The device has equivalent small signal y-parameters as follows :
 $y_{11} = 0.4 \text{ mS}, y_{12} = 0, y_{21} = 40 \text{ mS}, y_{22} = 25\mu\text{S}$
 These parameters are with emitter as common terminal.




ANSWERS :

$R_L = 194.881 \text{ K}, R_o = 44.015, \frac{v_o}{v_s} = 0.97714$

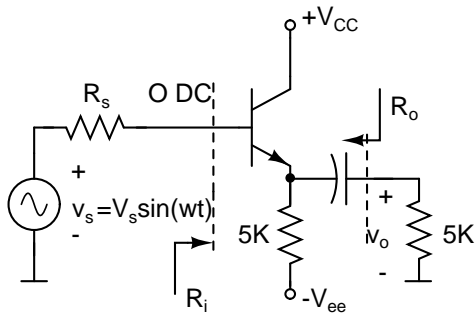Problem 18

V_s is 6V. Calculate the values of V_{CC} and V_{ee} which will give a v_o waveform with distortion just commencing at positive and negative extremes.




With the values found for V_{CC} and V_{ee} , use the approximate equivalent circuit for the transistor and determine R_i , R_o and v_o/v_s for small signals. Take $V_T = 25 \text{ mV}$, $\beta = 199$.

ANSWERS :

$V_{CC} = 6 \text{ V}, V_{ee} = 12.65 \text{ V}, R_L = 502.083 \text{ K}, R_o = 35.168, \frac{v_o}{v_s} = 0.986$

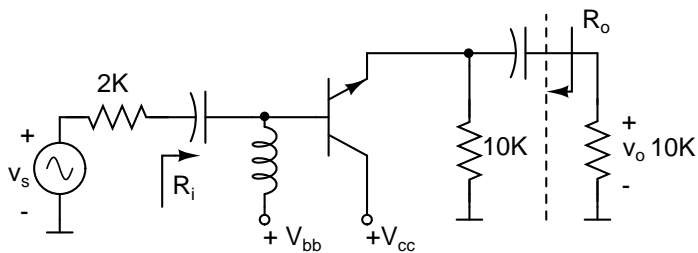Problem 19

Calculate R_i and R_o ; the value of V_{CC} and V_{bb} which, with minimum input DC power to the stage, enable it to just handle the specified inout drive without distortion in v_o . Calculate also the small signal $\frac{v_o}{v_s}$. Take $V_{BE} = 0.7 \text{ V}$ nominally, $r_e = 20 \Omega$, $\alpha = 0.992$ and $V_S = 10 \text{ V}$. In all cases, take the inductance and capacitors to be very large in value.




ANSWERS :

$V_{CC} = 30 \text{ V}, V_{bb} = 20.7 \text{ V}, R_i = 627.5 \text{ K}, R_o = 99.01 \text{ Ohms}, \frac{v_o}{v_s} = 0.9804$

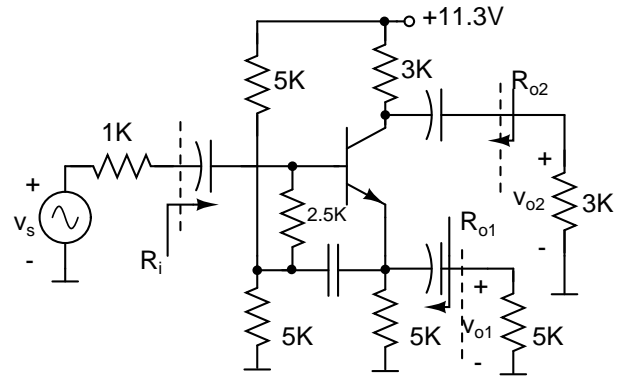Problem 20

All the coupling capacitors are very large in value. Take $V_T = 25 \text{ mV}$, $\alpha = 0.99$. Find for small signals R_i , R_{o1} as seen from the output terminal 1, R_{o2} as seen from output terminal 2, v_{o1}/v_s and v_{o2}/v_s .



ANSWERS :

$R_i = 64.375 \text{ K}, R_{o2} = 3 \text{ K}, R_{o1} = 43.39, \frac{v_{o1}}{v_s} = 0.9656, \frac{v_{o2}}{v_s} = -1.1358$

Problem 21


For very small signals, find v_o/v_s with the proper sign. Take $V_{BE} = 0.65 \text{ V}$, nominally, $V_T = 30 \text{ mV}$, $\alpha = 0.995$ for all transistors. Also determined which transistor controls the upper limit of swing and which the lower one.

ANSWERS :

$\frac{v_o}{v_s} = 14609$, T_5 controls lower swing limit - gets cut off when $v_o = -1.46 \text{ V}$ & T_4 controls upper swing limit - gets cut off when $v_o = 3.90 \text{ V}$

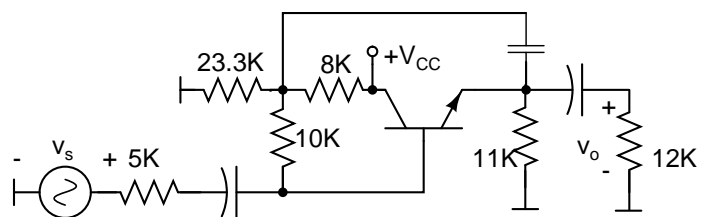Problem 22

$V_{BE} = 0.65 \text{ V}$ nominally. $V_T = 25 \text{ mV}$. Calculate R_i for small signals. Also find the positive and negative limits for v_o if it is to be free from distortion. Take $\beta = 200$, $V_{CC} = 15.65 \text{ V}$.



ANSWERS :

$R_i = 455.7 \text{ K}, V_{omax} = 4 \text{ V}, V_{omin} = -2.923 \text{ V}$

Problem 23

(COMMON BASE CONFIGURATION)


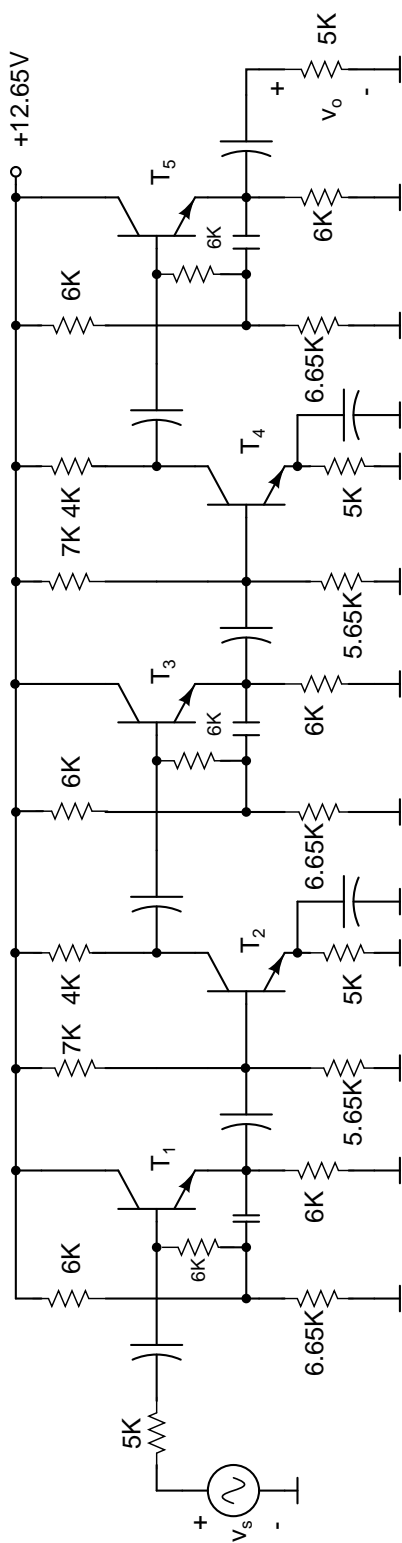



Figure 1: Circuit for Problem 21

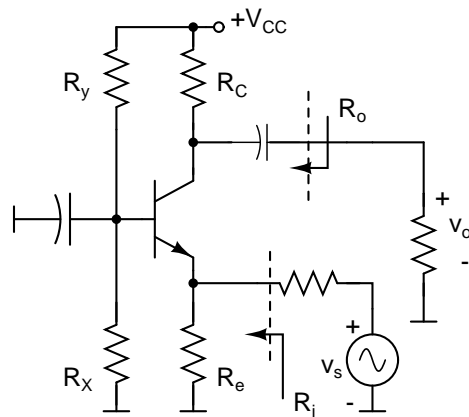

Calculate for small signals R_i , R_o and v_o/v_s . Give the limits for R_i , R_o and the conditions to be satisfied to make v_o/v_s independent of device and free of distortion even for large signal case. What type of a controlled source does this amplifier act like when $g_m \rightarrow \infty$?


Problem 24

For the circuit shown below, let $R_s = R_e = 4\text{ K}$, $R_C \parallel R_L = 20\text{ K}$. Calculate i_o/i_s given that $h_{ib} = 20\Omega$, $h_{rb} = 10^{-4}$, $h_{fb} = -0.99$ and $1/h_{ob} = 2\text{ M}\Omega$. Also, calculate R_i and R_o for the circuit. Finally, calculate i_o/i_s for the direct connection of the Norton equivalent and the load, without the transistor in between. Take $R_C = R_L$. To find R_o , take R_C to be part of load.

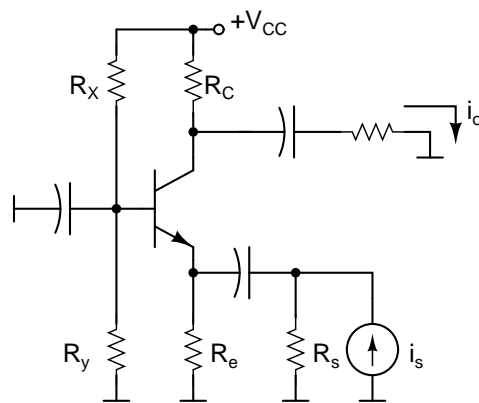

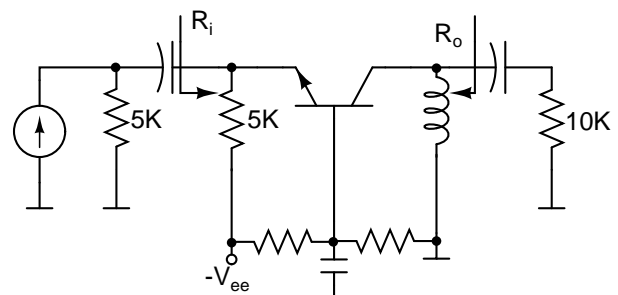Problem 25

For small signals, find R_i and R_o , given that $r_\pi = 2\text{ K}$, $\beta = 200$, $r_o = 30\text{ K}$




ANSWERS :

$R_i = 13.206 \text{ Ohms}, R_o = 3.364 \text{ M}\Omega$

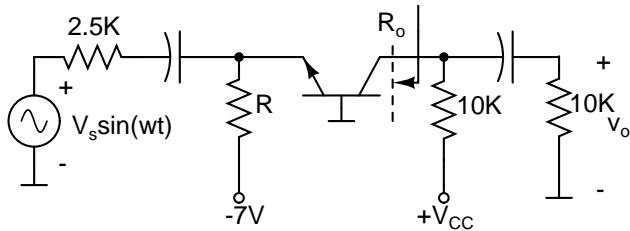Problem 26

The input is a sine wave with $V_S = 3.75\text{V}$. To get an undistorted output sine wave within swing limits, Calculate V_{CC} and R .



If $V_T = 25 \text{ mV}, \beta = 200, r_o = 40 \text{ K}$, Calculate R_o . Take $V_{BE} = 0.65 \text{ V}$ nominally.

ANSWERS :

$V_{CC} = 22.5 \text{ V}, R = 4.233 \text{ K}, R_o = 2.596 \text{ M}$