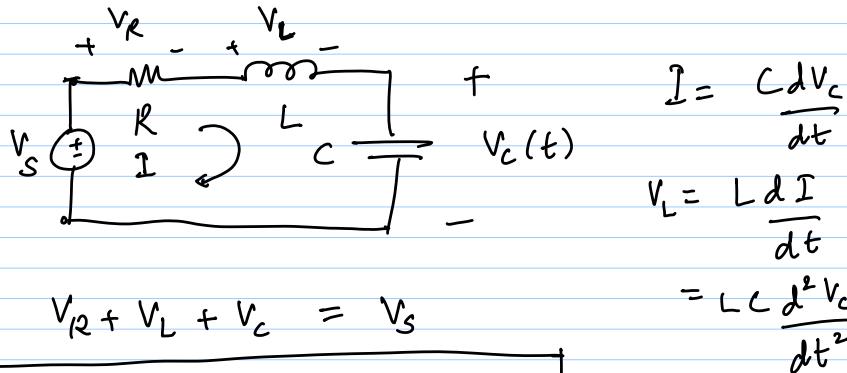


19/3/15

Lec 27Second Order SystemsNatural response: $V_s = 0$

$$LC \frac{d^2V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = 0$$

$$V_C = V_p \exp(pt)$$

$$(LC\cdot p^2 + RC\cdot p + 1) V_p \exp(pt) = 0$$

$$= 0$$

$$LC \cdot p^2 + RC \cdot p + 1 = 0$$

2nd order
dct

$$p = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC}$$

1st order:


$$RC \frac{dV_C}{dt} + V_C = 0$$

$$V_C = V_p \exp(pt) : (RCp + 1) \cdot V_p \exp(pt) = 0$$

$$p = -\frac{1}{RC}$$

$$p = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= p_1 \text{ & } p_2$$

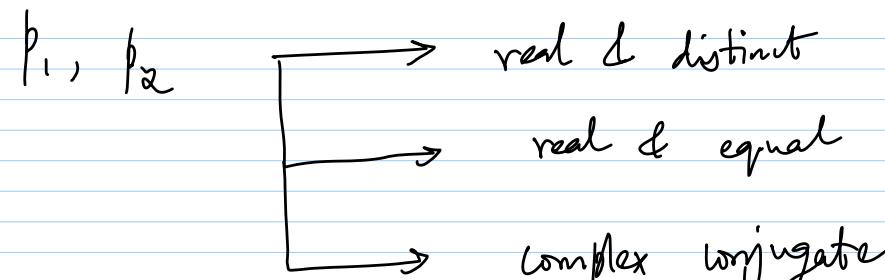

$$\underline{\text{Real & distinct}} \Rightarrow \left(\frac{R}{2L}\right)^2 > \frac{1}{LC} \Rightarrow R^2 > \frac{4L}{C}$$

$$V_C(t) = A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$$

$$A_1, A_2 \rightarrow \text{from initial conditions}$$

$$V_C(0) \quad I_L(0)$$

$$\text{Real & equal} \Rightarrow \left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \Rightarrow R^2 = \frac{4L}{C}$$

$\rho_1 = \rho_2 = \rho$

$$V_c(t) = (A_1 + A_2 t) \exp(\rho t)$$

$$\text{complex conjugate} \Rightarrow R^2 < 4L/C$$

$$\rho_{1,2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \quad \boxed{\rho_r \pm j\rho_i}$$

$$V_c(t) = A_1 \exp(\rho_r t) + A_2 \exp(\rho_i t)$$

$$A_I = A_r^*$$

Sinusoidal solution, with amplitude exponentially decreasing over time.

$$LC \frac{d^2 V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s$$

$$\frac{d^2 V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{V_c}{LC} = \frac{V_s}{LC}$$

$$\text{std. form} \rightarrow \frac{d^2 V_c}{dt^2} + 2\zeta \omega_n \frac{dV_c}{dt} + \omega_n^2 V_c = \omega_n^2 V_s$$

↓
'2eta'

$$V_c(t) = A_r \exp(\rho_r t) + A_i^* \exp(\rho_i t)$$

real + imag } 2 initial conditions

$$\rho_{1,2} = \rho_r \pm j\rho_i \quad \xrightarrow{\text{A}_0 \cos(\rho_i t + \phi)}$$

$$V_c(t) = A_r \exp(\rho_r t) \exp(j\rho_i t) + A_i^* \exp(\rho_r t) \cdot \exp(-j\rho_i t)$$

ζ = damping factor

ω_n = natural frequency

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\frac{d^2 V_c}{dt^2} + \frac{\omega_n}{Q} \cdot \frac{dV_c}{dt} + \omega_n^2 V_c = \omega_n^2 V_s$$

$$Q = \text{quality factor} = \frac{1}{2\zeta} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Characteristic polynomial

$$LC \cdot p^2 + RL \cdot p + 1 = 0$$

$$p^2 + 2\zeta\omega_n p + \omega_n^2 = 0$$

if

$$p^2 + \frac{\omega_n}{Q} \cdot p + \omega_n^2 = 0$$

$$p_{1,2} = \omega_n \left[-\zeta \pm \sqrt{\zeta^2 - 1} \right]$$

$$= \omega_n \left[-\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 - 1} \right]$$

$p_{1,2}$ → real & distinct

$$\zeta > 1 ; Q < \frac{1}{2}$$

overdamped system

real & equal

$$\zeta = 1 , Q = \frac{1}{2}$$

critically damped system

complex conjugate

$$\zeta < 1 ; Q > \frac{1}{2}$$

underdamped system

