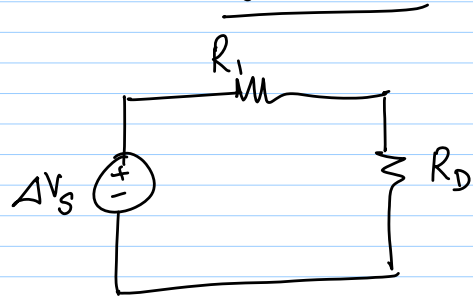


24/2/15


lec 19



Incremental equivalent ckt

$$R_D = \frac{1}{f'(V)|_{V_0}}$$

example

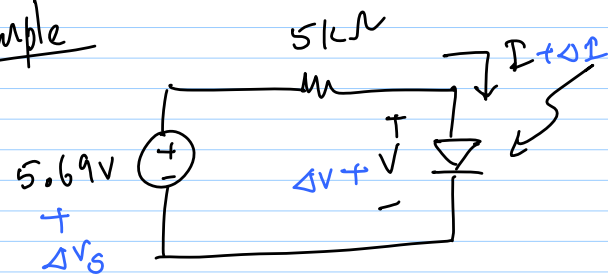

$I_S = 10^{-15} A$
 $T = 300K$
 $V = 0.69V$
 $I = 1mA$

I	V
100μA	630mV
1mA	690mV
10mA	750mV

$$R_D = \frac{1}{f'(V)|_{V_0}}$$

$$I = I_S \left[\exp\left(\frac{V}{V_T}\right) - 1 \right]$$


$$I_0 = I_S \left[\exp\left(\frac{V_0}{V_T}\right) - 1 \right] \approx I_S \exp\left(\frac{V_0}{V_T}\right)$$

$$f'(V) = \frac{I_S}{V_T} \exp\left(\frac{V}{V_T}\right)$$

$$R_D = \frac{1}{f'|_{V_0}} = \frac{V_T}{I_S \exp\left(\frac{V_0}{V_T}\right)} \approx \frac{V_T}{I_0}$$

$$R_D = \frac{V_T}{I_0}$$

here $R_D = \frac{25mV}{1mA} = 25\Omega$



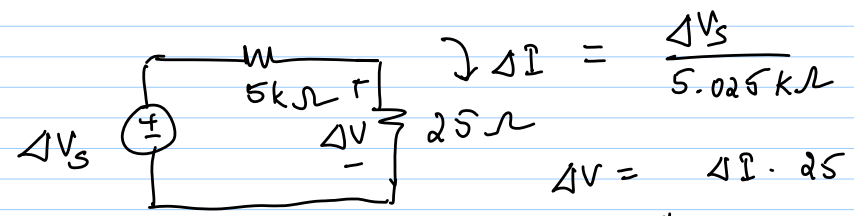


"incremental" or "small-signal" analysis

* Incremental Ckt

- has the same graph as org. ckt
- branch voltages = ΔV_k
- branch currents = ΔI_k
- Linear elements remain the same
- independent sources replaced with source of same type; value = increment/change in value
- Nonlinear elements: replace with resistance of value $r = \frac{1}{f'(V)}$

$$\{\Delta V_k = r \Delta I_k\}$$

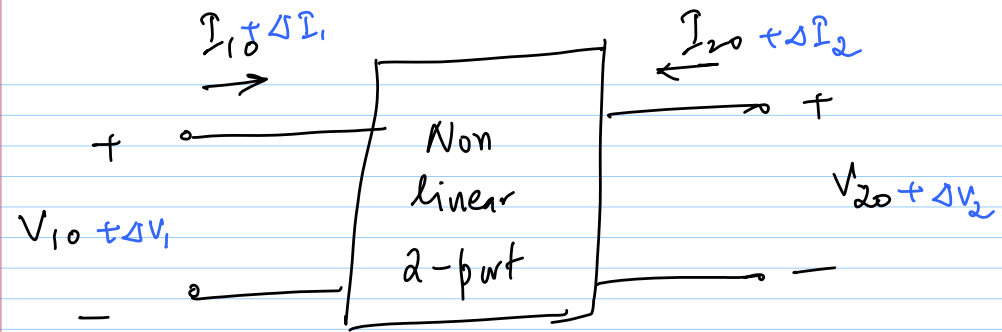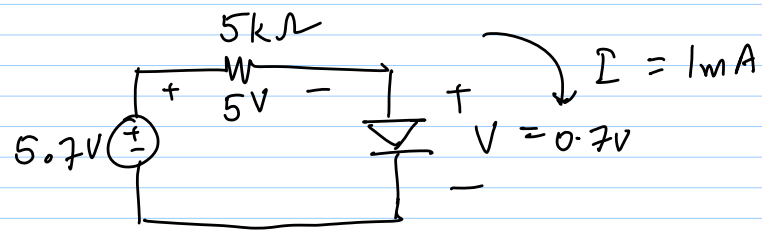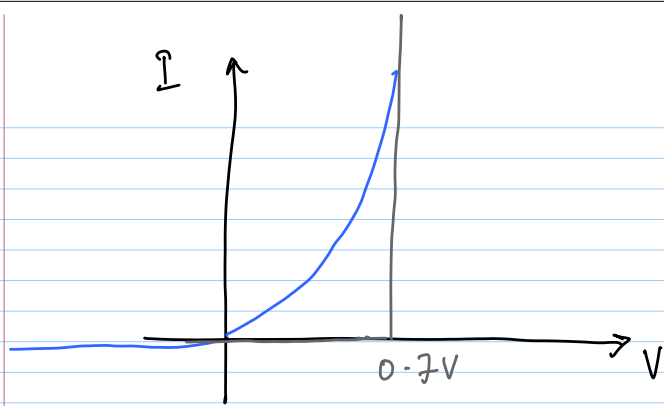

Incremental
y-parameters

$$I_1 = f_1(V_1, V_2); \quad I_2 = f_2(V_1, V_2)$$

$$\Delta I_1 = \left. \frac{\partial f_1}{\partial V_1} \right|_{op} \cdot \Delta V_1 + \left. \frac{\partial f_1}{\partial V_2} \right|_{op} \cdot \Delta V_2$$

$$+\Delta I_2 = \left. \frac{\partial f_2}{\partial V_1} \right|_{op} \cdot \Delta V_1 + \left. \frac{\partial f_2}{\partial V_2} \right|_{op} \cdot \Delta V_2$$

$$\Delta I_1 = y_{11} \Delta V_1 + y_{12} \Delta V_2$$

$$+\Delta I_2 = y_{21} \Delta V_1 + y_{22} \Delta V_2$$