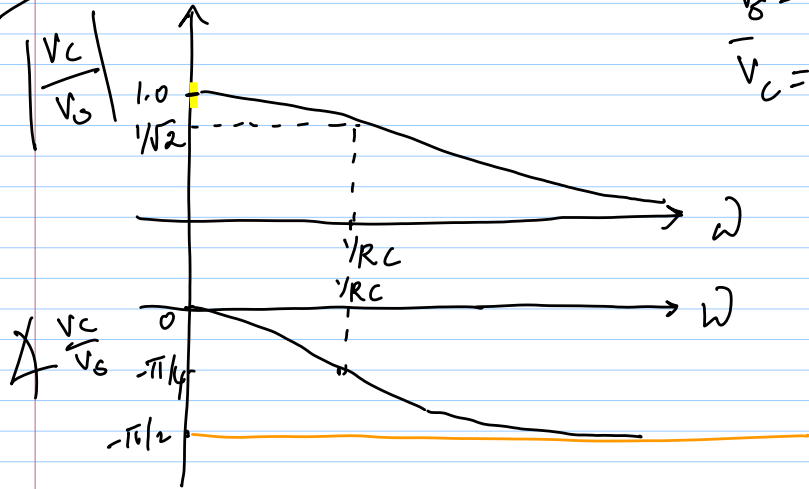


30/3/15

Lec 32

$$\bar{V}_s = V_p \angle 0$$

$$\bar{V}_c = \frac{1}{1+j\omega RC} \cdot \bar{V}_s$$



Logarithmic Scale

$$\frac{\bar{V}_c}{\bar{V}_s} = \frac{1}{1+j\omega RC}$$

$$\log_{10} \left| \frac{\bar{V}_c}{\bar{V}_s} \right| = \log_{10} \left| \frac{1}{\sqrt{1+\omega^2 C^2 R^2}} \right|$$

$$\left| \frac{\bar{V}_c}{\bar{V}_s} \right|_{\text{linear}} = \frac{1}{\sqrt{1+\omega^2 C^2 R^2}}$$

$\omega \ll \frac{1}{RC}$	$    = 1$
$\omega = \frac{1}{RC}$	$    = \frac{1}{\sqrt{2}}$
$\omega \gg \frac{1}{RC}$	$    = \frac{1}{\omega RC}$

$\log_{10}$	dB
0	0
-0.15	-3 dB
$-\log_{10}(\omega RC)$	$-20 \log_{10}(\omega RC)$

$$\text{decibel (dB)} \Big|_{\text{power}} = 10 \log_{10}(P)$$

$$\text{decibel (dB)} \Big|_{\text{Voltage}} = 20 \log_{10}(V)$$


@  $\omega \gg \frac{1}{RC}$


$$20 \log_{10} \left| \frac{\bar{V}_c}{\bar{V}_s} \right| = -20 \log_{10}(\omega) - 20 \log_{10}(RC)$$

@  $\omega_1$  :  $-20 \log_{10}(\omega_1) - 20 \log_{10}(RC)$

dB normally used for ratios of quantities

Bode Plots

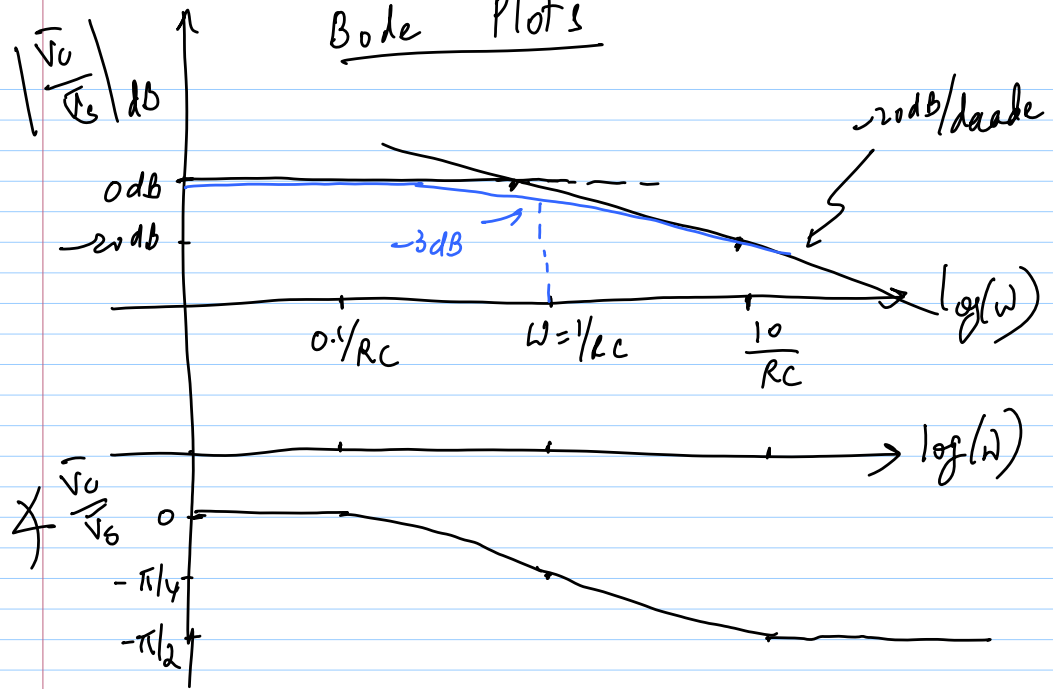

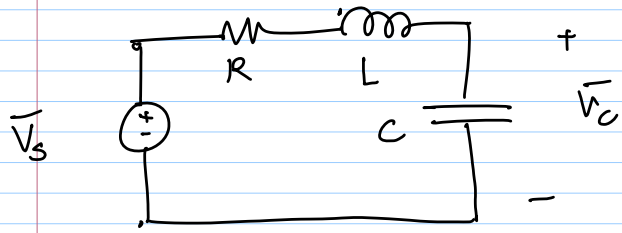

$$\frac{\bar{V}_c}{\bar{V}_s} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{1}{(1 - \omega^2 LC) + j\omega CR}$$