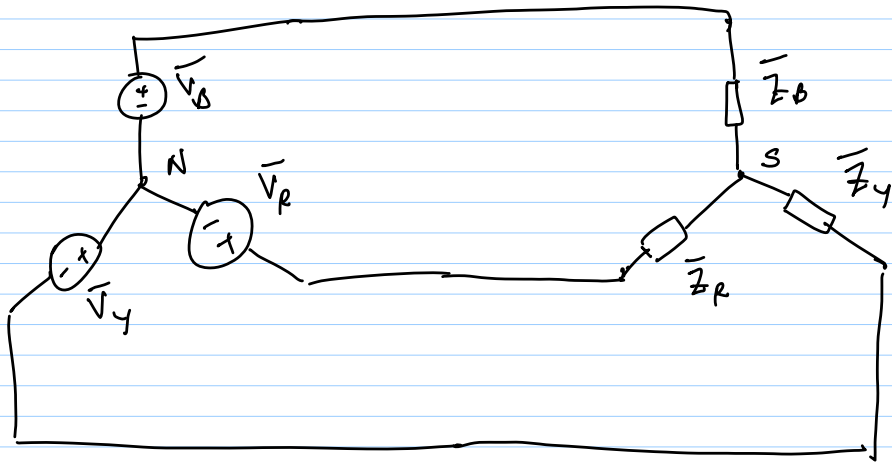


27/4/15

Lec 42


Symmetrical Components



$$Z_{RY} = \frac{\sum Z_R Z_Y}{Z_B} \leftarrow \text{star to delta conversion}$$

$$Z_R = \frac{Z_{RY} Z_{BR}}{\sum Z_{RY}} \leftarrow \text{delta to star conv.}$$

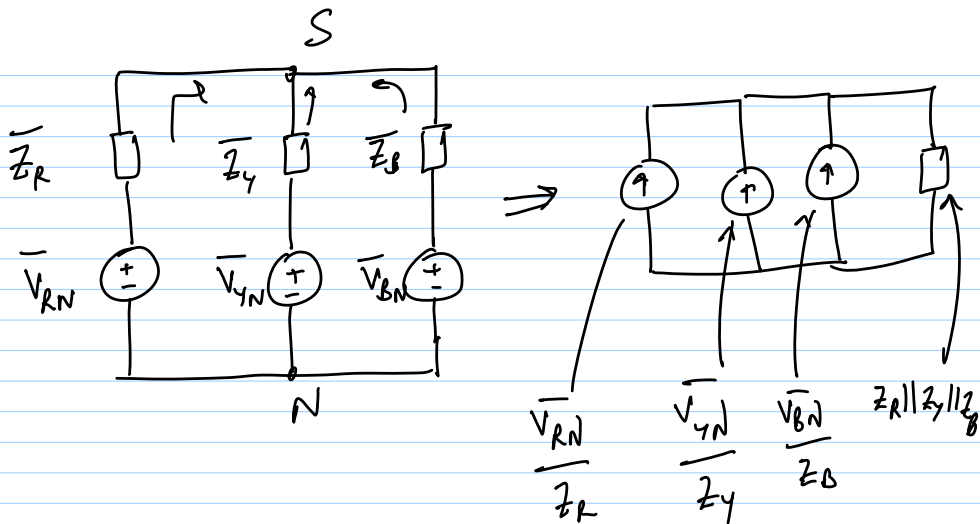
$$\left. \begin{matrix} \bar{V}_{RS} \\ \bar{V}_{YS} \\ \bar{V}_{BS} \end{matrix} \right\} = ? \quad \bar{V}_{SN}$$




$$\bar{V}_{SN} = \frac{\sum \bar{V}_{RN} / Z_R}{\sum 1/Z_R} ; \quad \bar{V}_{RS} = \bar{V}_{RN} - \bar{V}_{SN}$$

$$V_1 = \frac{V_1 + V_2}{2} + \frac{V_1 - V_2}{2}$$
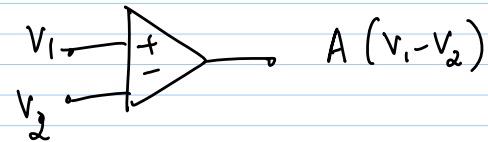
$$V_2 = \frac{V_1 + V_2}{2} - \frac{V_1 - V_2}{2}$$



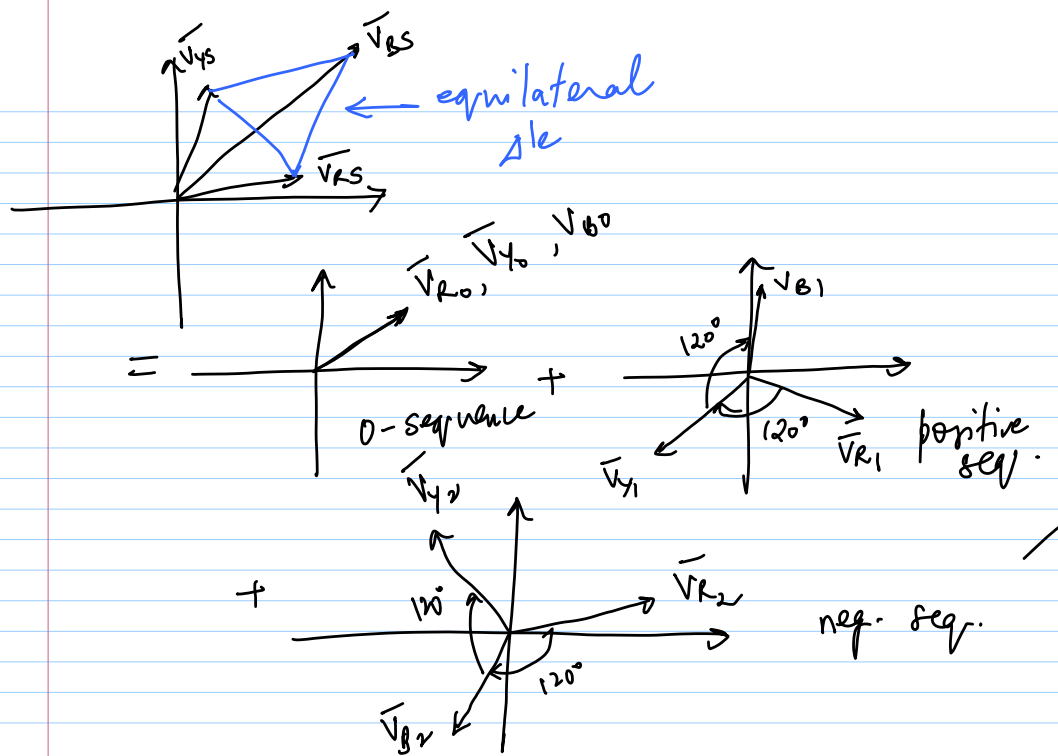

### AC power measurement

$$V_p \cos \omega t$$

$$I_p \cos(\omega t + \phi)$$

$$p(t) = V_p I_p \cos \omega t \cdot \cos(\omega t + \phi)$$


$$= \frac{V_p I_p}{2} \cos \phi \text{ average power}$$

$$+ \frac{V_p I_p}{2} \cos(2\omega t + \phi)$$

$$\bar{P} = \frac{V_p I_p}{2} \cos \phi$$

$$pf = \frac{\text{Re}(P)}{|P|}$$

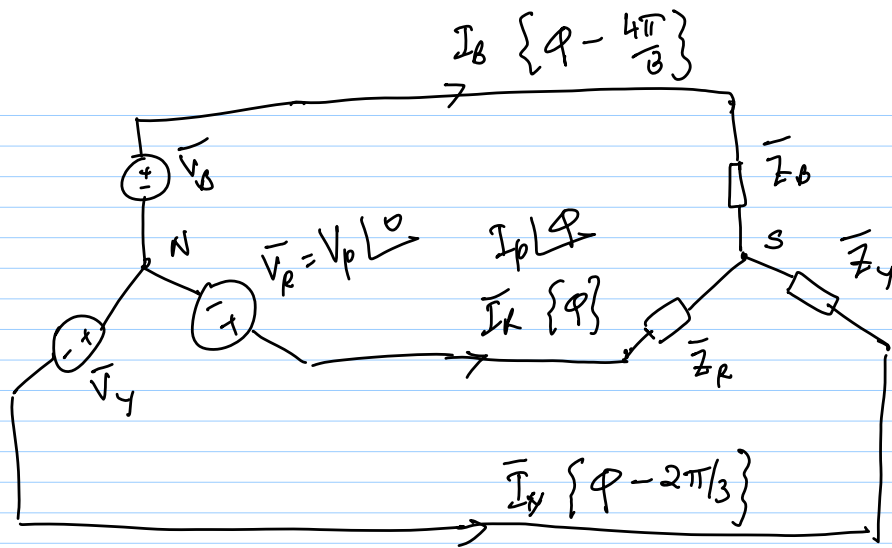avg. power      reactive power      osc. power



$$Z_L: p(t) = \frac{V_p I_p}{2} \cos \phi + \frac{V_p I_p}{2} \cos 2\omega t \cos \phi$$

$$- \frac{V_p I_p}{2} \sin(2\omega t) \sin \phi$$

$$Z_Y: p(t) = \frac{V_p I_p}{2} \cos \phi$$

$$+ \frac{V_p I_p}{2} \cos \phi \cdot \cos(2\omega t - \frac{4\pi}{3})$$

$$- \frac{V_p I_p}{2} \sin \phi \sin(2\omega t - \frac{4\pi}{3})$$


$$\bar{Z}_b = \dots$$

$$P_{avg.} = \frac{3V_p I_p \cos \phi}{2}$$




$$PF = \frac{V_p I_p / 2 \cos \phi}{P \text{ per phase}}$$

per phase

Wattmeter

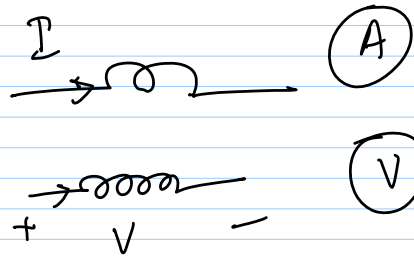

Wattmeter

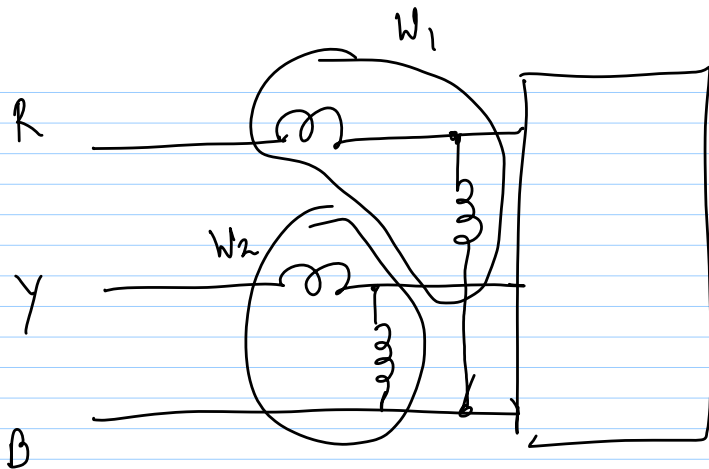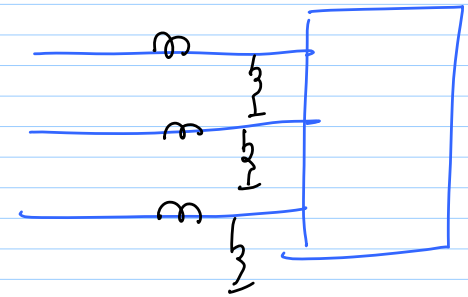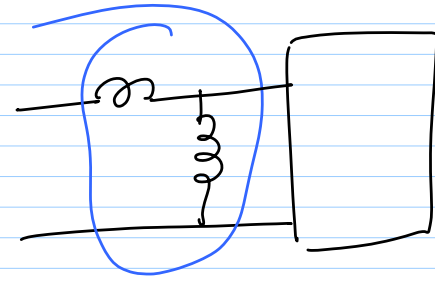

$$\sum V_k I_k$$