

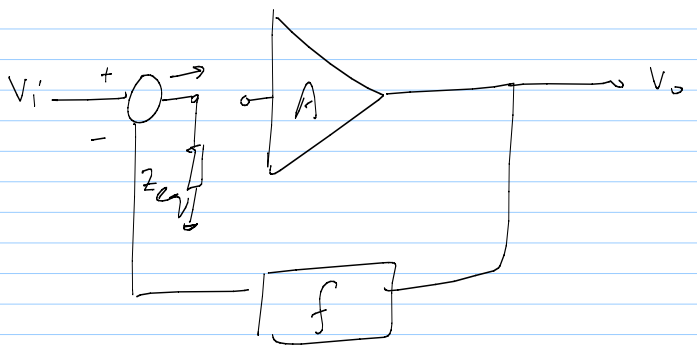
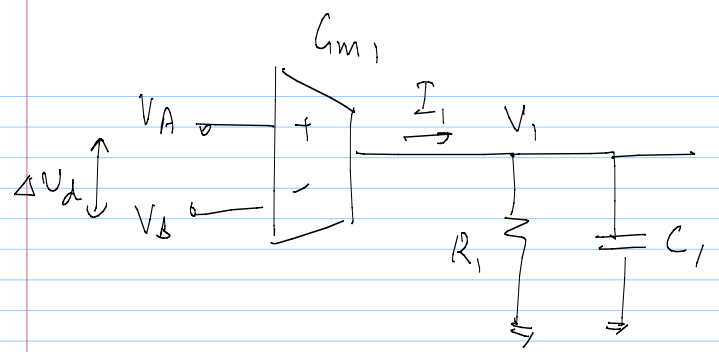
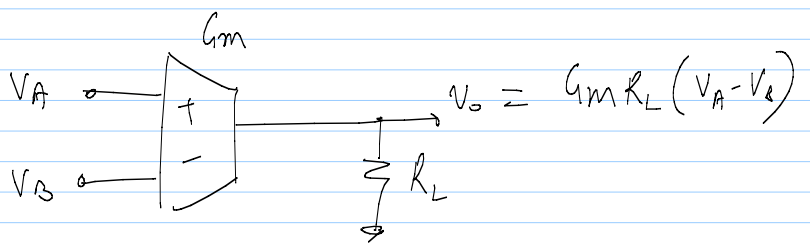
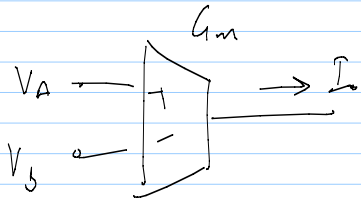
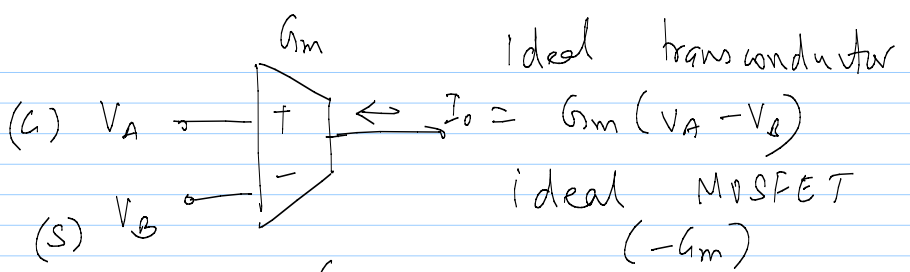


26/8/14

lec 13

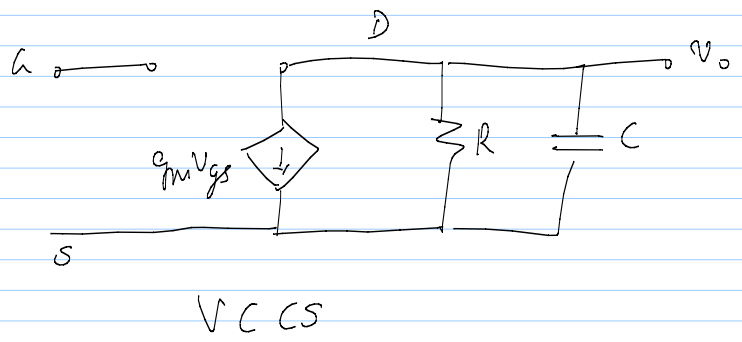

2-stage MOSFET opamp

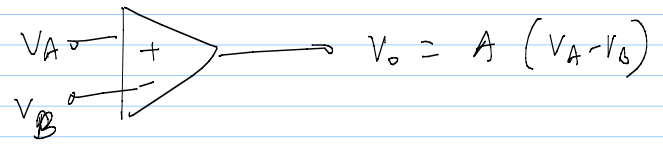

$\frac{V_o}{V_A - V_B} (a) = ?$


$I_1 = G_{m1} \cdot V_d$

$V_1 = I_1 \cdot Z_1 = I_1 \cdot \frac{R_1}{1 + sC_1R_1}$


$$\frac{V_1}{V_A} = \frac{G_{m1} R_1}{1 + sC_1 R_1} = \frac{A_o}{1 + s/\omega_p}$$

$$A_o = G_{m1} R_1$$

$$\omega_p = \frac{1}{R_1 C_1}$$

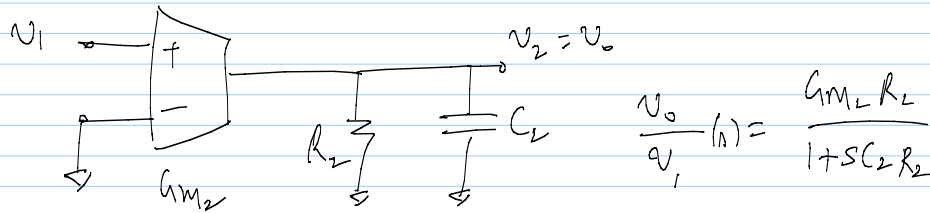
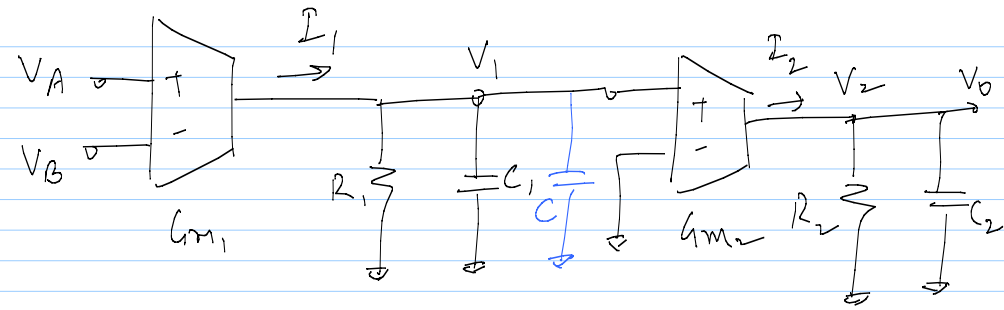
$$\frac{V_o}{V_1}(s) = \frac{G_{m2} R_2}{1 + sC_2 R_2}$$




$$A(s) = \frac{V_o}{V_A - V_B}(s) = \frac{G_{m1} R_1}{1 + sC_1 R_1} \cdot \frac{G_{m2} R_2}{1 + sC_2 R_2}$$

$$A_o = G_{m1} R_1 \cdot G_{m2} R_2$$

$$\omega_{p1} = \frac{1}{R_1 C_1}; \quad \omega_{p2} = \frac{1}{R_2 C_2} \quad \text{say } \omega_{p1} \ll \omega_{p2}$$

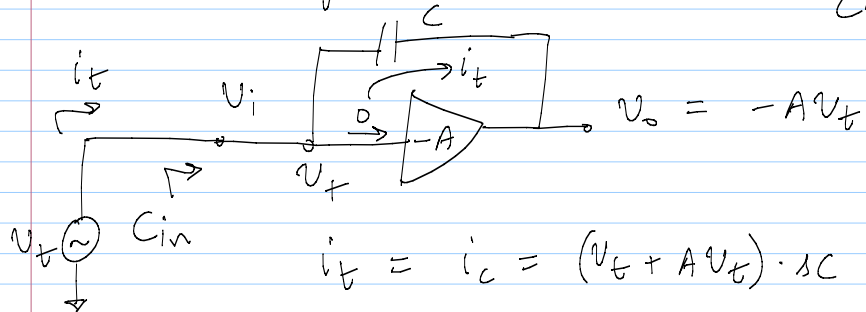
* We want to move ω_{p1} to ω_d
 * R_1 is already large due to $A_{o,max}$
 $\Rightarrow \uparrow C_1 \Rightarrow$ add C in parallel with C_1
 e.g. $C = 50 \times C_1 \Rightarrow$ very large Cap.




$$i_t = i_c = (V_t + AV_t) \cdot sC$$

$$sC_{in} = \frac{i_t}{V_t} = (1 + A) sC$$
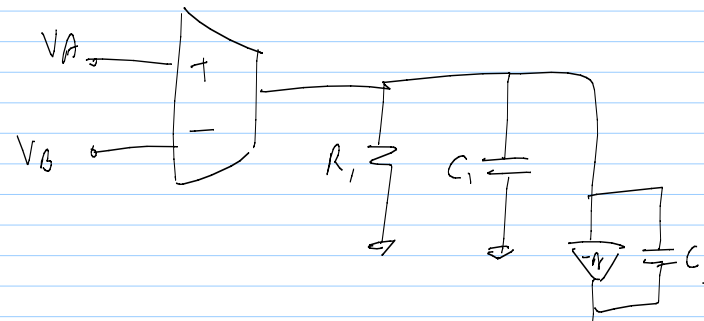
$$\Rightarrow C_{in} = (1 + A) C \quad \text{"Miller Effect"}$$



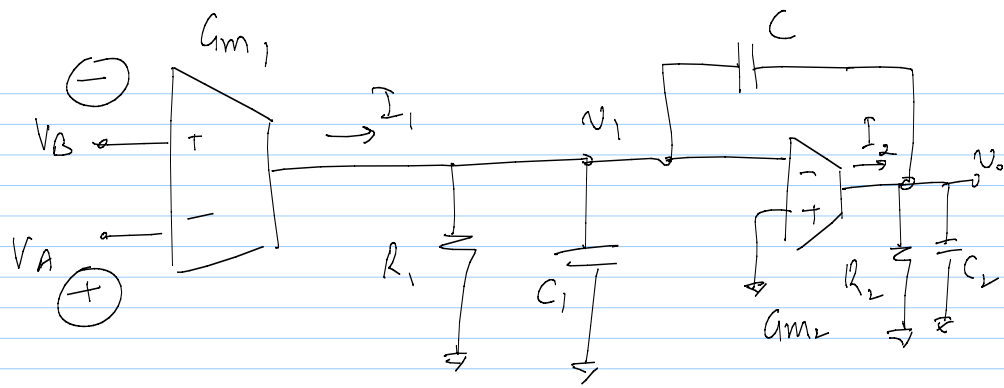

ideal G_m 's (no R_i, C_i)

$$I_1 = G_{m1} (V_B - V_A) \rightarrow \text{flows thro' } C$$

$$V_1 = 0$$

$$V_0 = \frac{-I_1}{sC}$$

$$\frac{V_0}{V_a - V_b} = \frac{G_{m1}}{sC} \quad \text{integrator}$$

