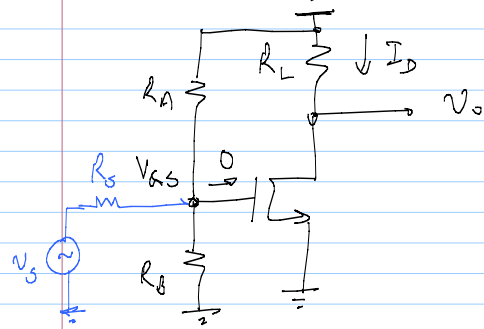


2/9/14

lec 16


$$V_{DD} = V_{DS} + I_D R_L$$



$$V_{gs} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

* cannot connect $V_s - R_s$ directly to gate
 $\Rightarrow V_{gs}$ will change

$$\text{to } \frac{R_B || R_s}{R_A + R_B || R_s} \cdot V_{DD} \quad \times$$

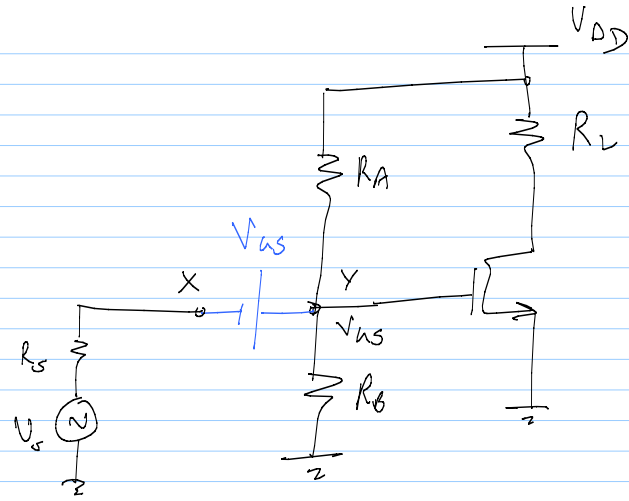


DC voltage
 @ $X = 0$
 @ $Y = V_{gs}$

$$1) V_x \text{ --- } \equiv V_x^+ \text{ --- } C$$


if current drawn from cap = 0

$$2) V_x \text{ --- } \equiv V_x^+ \text{ --- } \infty$$


even if current is drawn

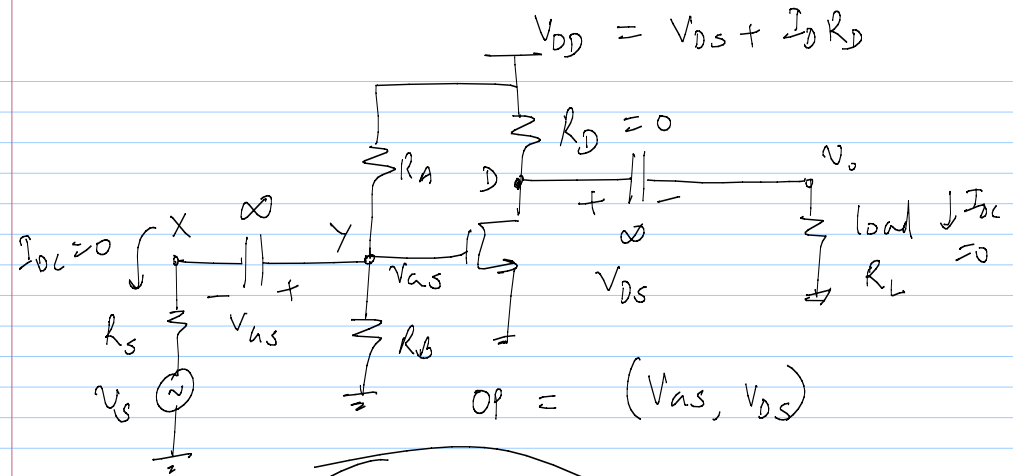

$$OP = (V_{gs}, V_{DS})$$

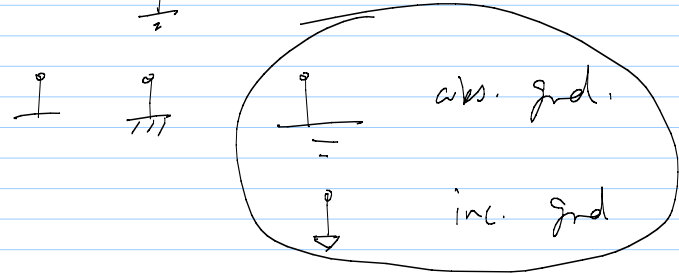

Small-signal equivalent

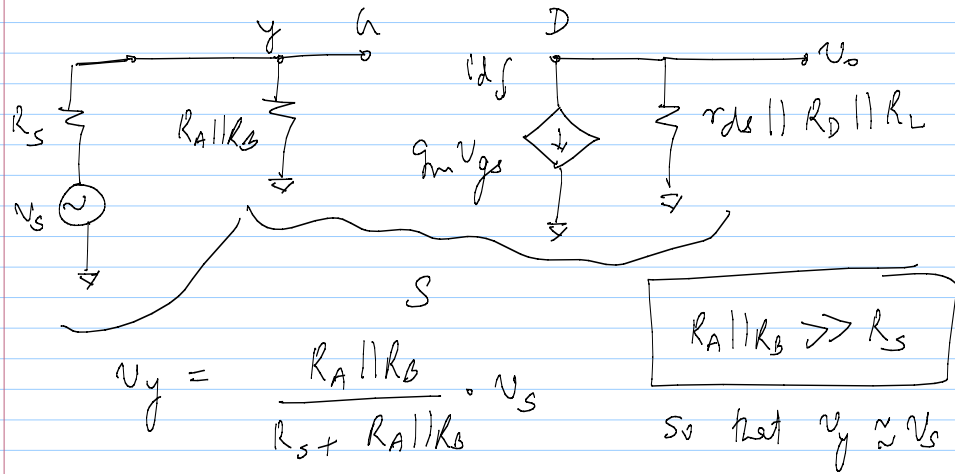

$$v_y = v_{gs}$$

$$i_d = g_m v_{gs}$$

$$= g_m v_s$$

$$v_o = -i_d \cdot (r_{ds} || R_D || R_L)$$

$$= -g_m (r_{ds} || R_D || R_L) \cdot v_s$$

$$\frac{v_o}{v_s} = -g_m (r_{ds} || R_D || R_L)$$