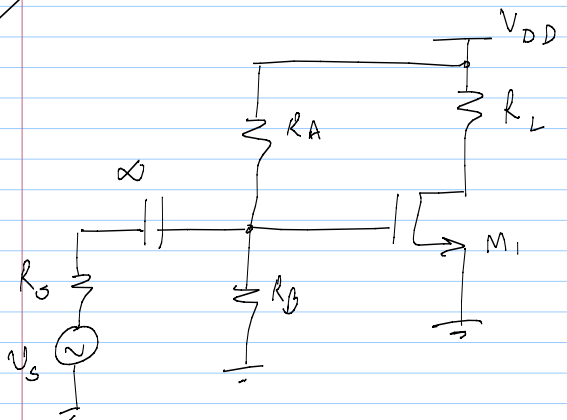


9/9/14

lec 19

Issues

- \* Nonlinearity - swing limits
- \*  $\infty$  caps
  - we caps that are large enough dep. on  $\omega, R_s$
- \*  $V_{GS1}, I_{D1}, g_m, h$  are functions of device parameters



$\mu_n, C_{ox}, V_T$  ←  
 fn. of Temp ←  $R_s$  tolerance

$$V_{GS1} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$

- \* Ratio of resistances remains almost the same on a particular IC even if absolute values may be diff. from designed value

$$\frac{R_B}{R_A + R_B} \text{ will not change}$$

⇒  $V_{GS1}$  stays the same

$$I_D = f(V_{GS1} - V_T)$$


varies

- \* MOSFETs on the same IC are identical

$$g_m = f(I_D)$$

$$V_{GS1} = f(I_D)$$

We want to maintain constant  $I_D$

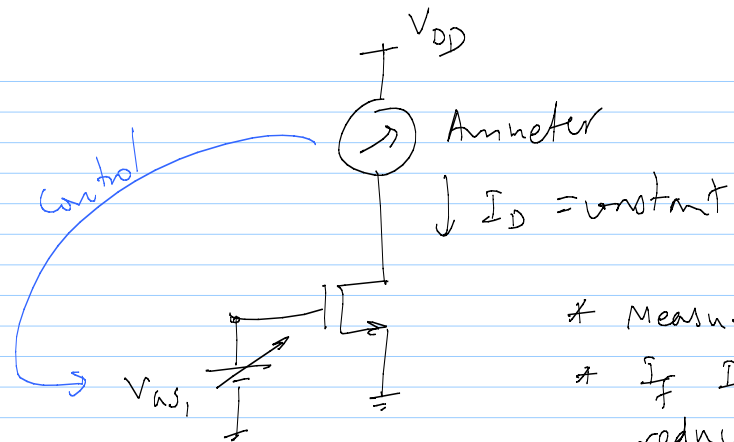

e.g.  $I_D = 1mA$


"Negative Feedback"

- \* Measure  $I_D$
- \* If  $I_D > 1mA$ , reduce  $V_{GS1}$
- \* If  $I_D < 1mA$ , increase  $V_{GS1}$

Compare  $I_D$  &  $I_0$


$\Rightarrow (I_D - I_0)$

drive  $(I_D - I_0)$  to 0

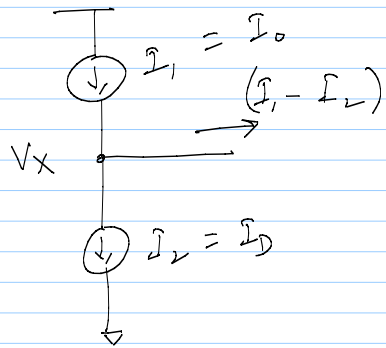

If  $I_1 > I_2, V_x \downarrow$


$I_1 < I_2, V_x \downarrow$

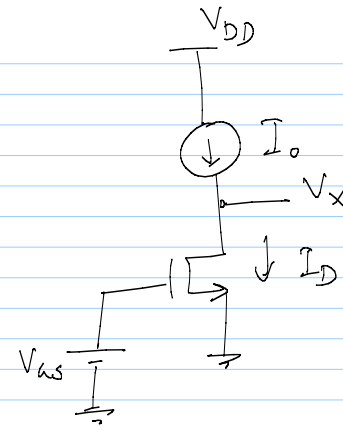

\*  $I_0 > I_D$ , we want to inc.  $V_{bs}$  ( $V_x$  increases)

\*  $I_0 < I_D$ , we want to del.  $V_{bs}$  ( $V_x$  decreases)

Why not connect  $x$  to  $b$ !

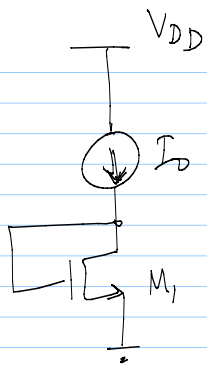


$V_{bs}$  will adjust to a value so that  $I_D = I_0$

$I_0 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{bs} - V_T)^2$

$\Rightarrow$  will set  $V_{bs}$

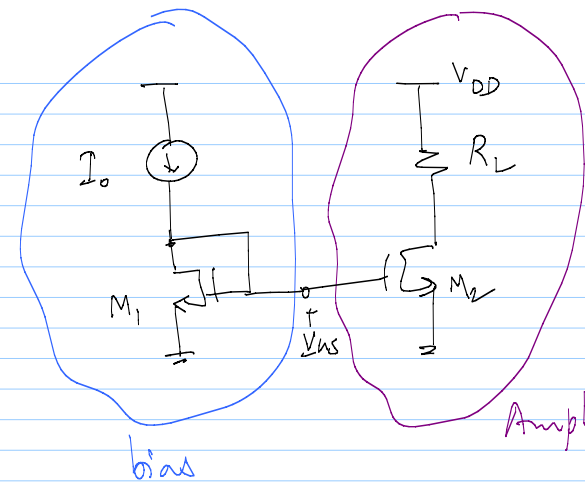$V_{DS} = V_{bs}$  )  $M_1$  is in saturation



"CURRENT MIRROR"

\*  $M_1$  &  $M_2$  should be in sat.

