
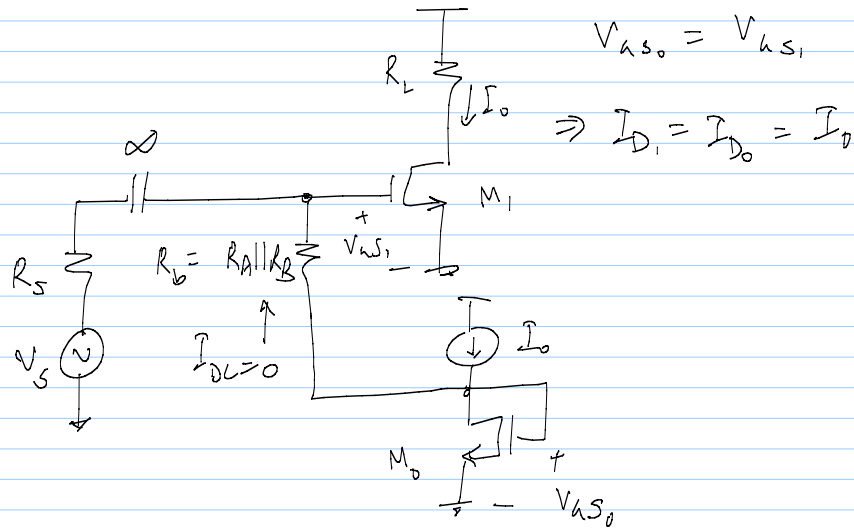


10/9/14

lec 20

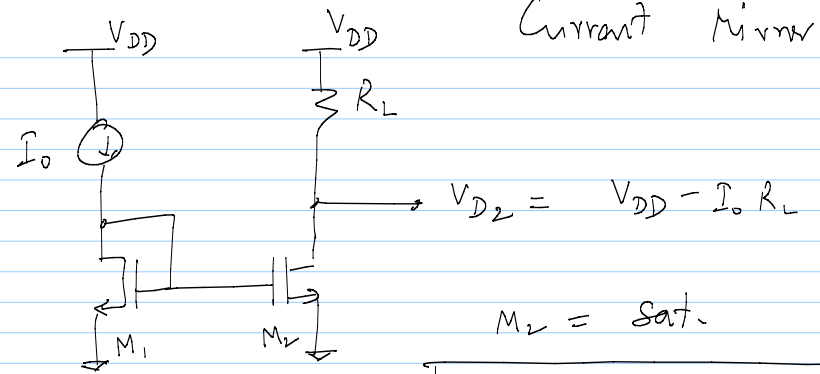


"Current Mirror"



$M_2 = \text{sat.}$


$V_{DD} - I_0 R_L > V_{as_1} - V_T$

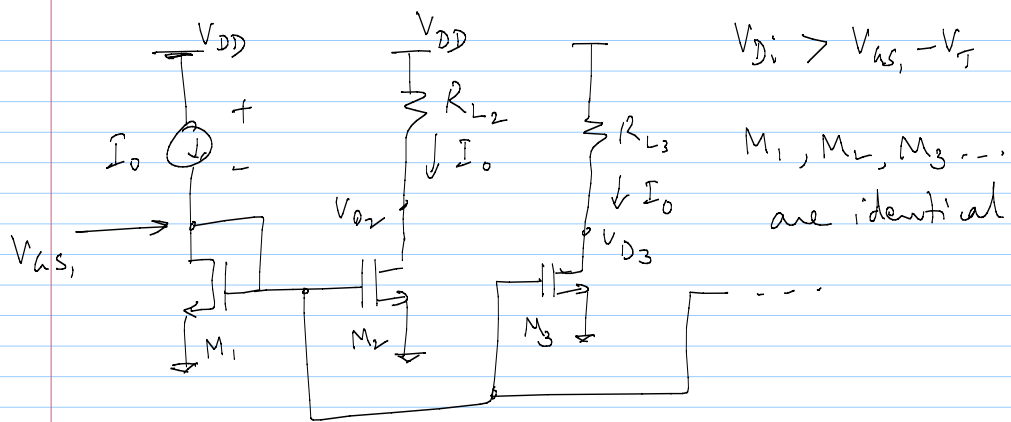
$V_{as_1} = V_{as_2}$
 $\Rightarrow I_{D_1} = I_{D_2} = I_0$



If we want to generate $2I_0$, make

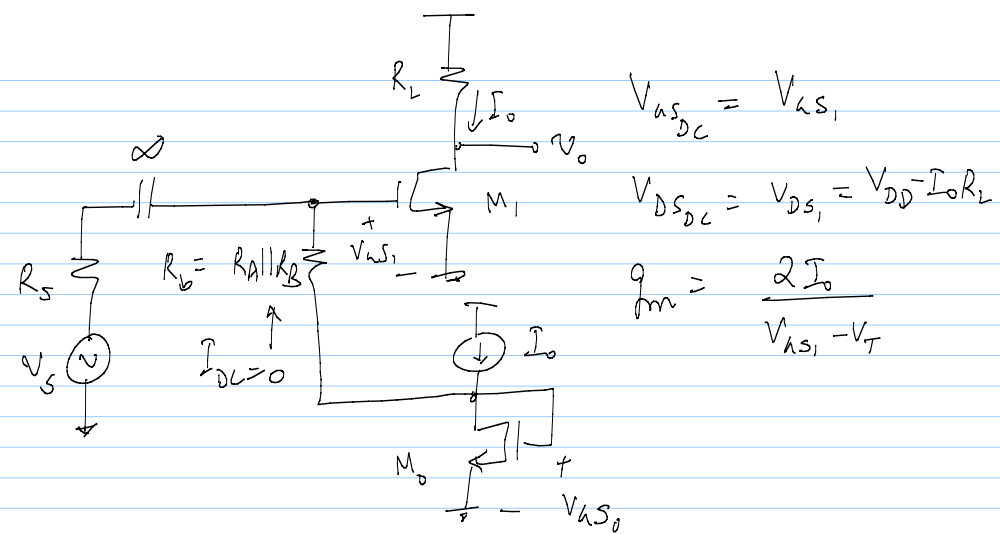$\left(\frac{W}{L}\right)_{M_2} = 2 \left(\frac{W}{L}\right)_{M_1}$



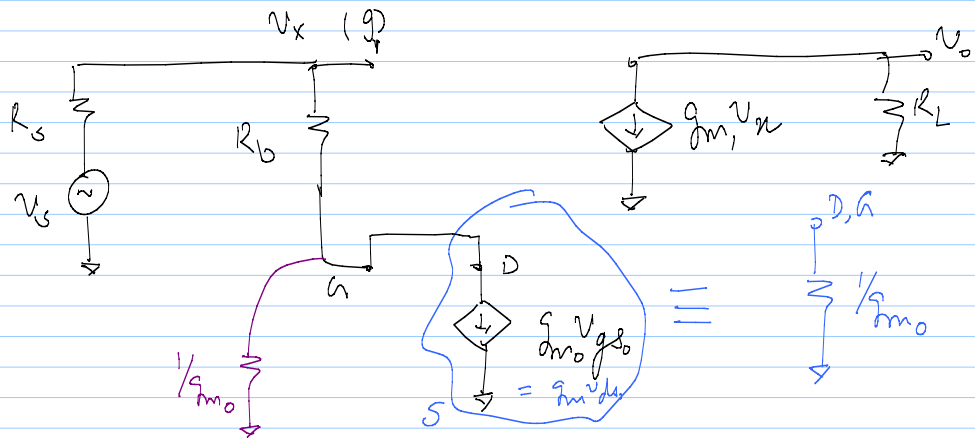

$$v_x = \frac{R_b + 1/g_{m0}}{R_s + R_b + 1/g_{m0}} v_s \approx v_s \text{ if } R_b + 1/g_{m0} \gg R_s$$

$$\frac{v_o}{v_s} = -g_m R_L$$


$V_{as,1} =$ same as before

$I_D =$ "


$V_{DS,1} =$ "

$G =$ "

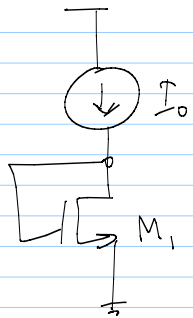\therefore Swing limits } = same as before




DC

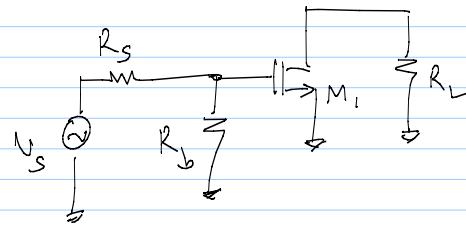



AC

1)

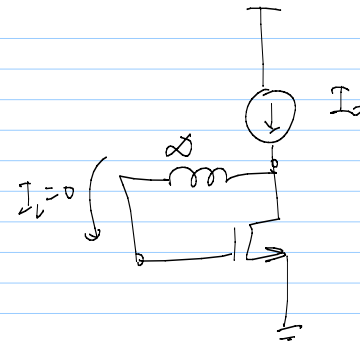


+ inductors are bulky X

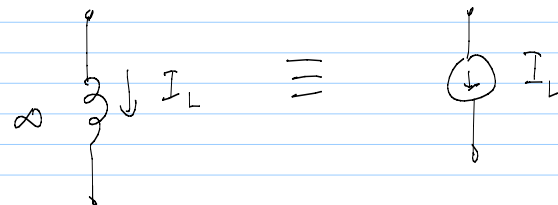


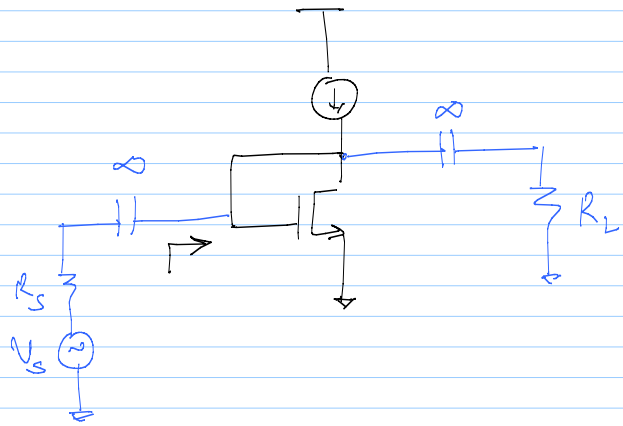
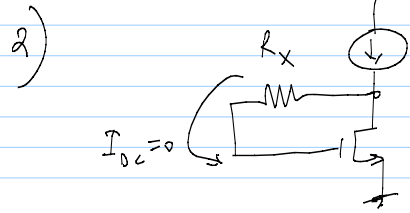
$$\frac{v_o}{v_s} = \frac{R_L \parallel \frac{1}{g_m}}{R_L \parallel \frac{1}{g_m} + R_s}$$



$$v_{as,DC} = V_{DS,DC}$$

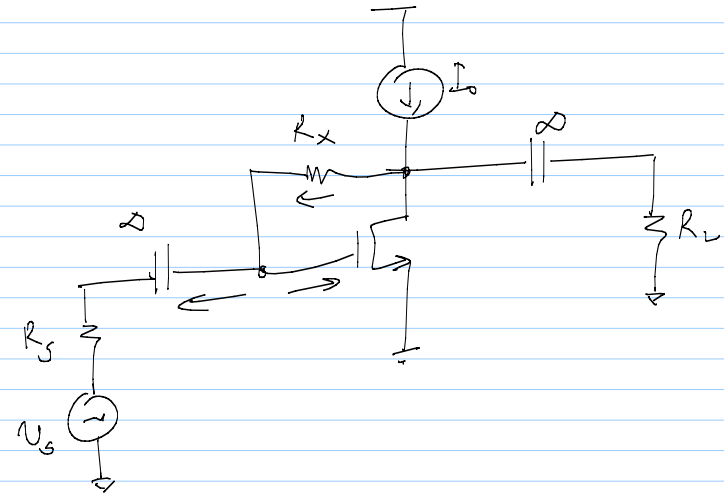

Small-signal:

