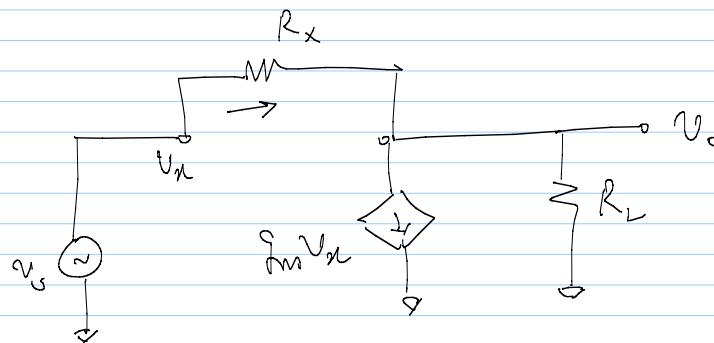


11/9/14

lec 21



$$V_x = V_s$$

$$\frac{V_s - V_o}{R_x} = g_m V_s + \frac{V_o}{R_L}$$

Negative f.b. to stabilise bias point

I_{ref} = desired bias current

- 1) Measure I_D (I_s)
- 2) Compare I_D (I_s) with I_{ref}
- 3) If $I_D > I_{ref}$, reduce V_{AS} (V_u or V_s)
- 4) If $I_D < I_{ref}$, increase V_{AS} (V_u or V_s)

\Rightarrow 4 ways of using -ve f.b. to stabilize bias point

$$V_o (h_L + h_x) = V_s (h_x - g_m)$$



$$\frac{V_o}{V_s} = \left(\frac{h_x - g_m}{h_x + h_L} \right) = \frac{-g_m}{h_L} \left[\frac{1 - h_x/g_m}{1 + h_x/h_L} \right]$$

* $g_m \gg h_L$ for large gain

* Choose $h_x \ll h_L \Rightarrow h_x \ll g_m$

$$R_x \gg R_L$$


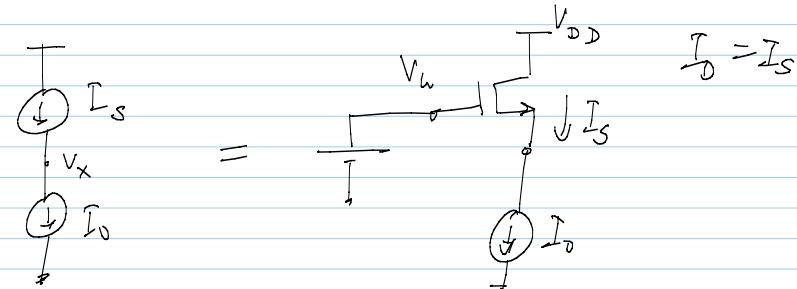
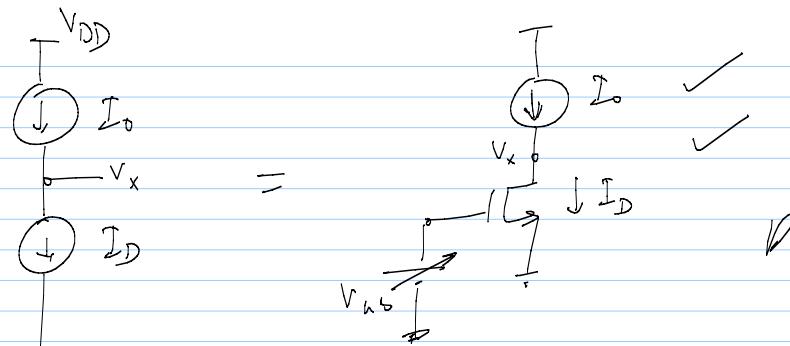
- * Swing limits: 1) $I_D = I_0$ (ut off limit is the same)
- 2) $V_{D_{DC}} = V_{A_{DC}}$ \Rightarrow triode limit is different (+/w)



* V_{AS} tunes I_S (or I_s)


\Rightarrow keep V_S constant & tune V_A (or)

keep V_A constant & tune V_S

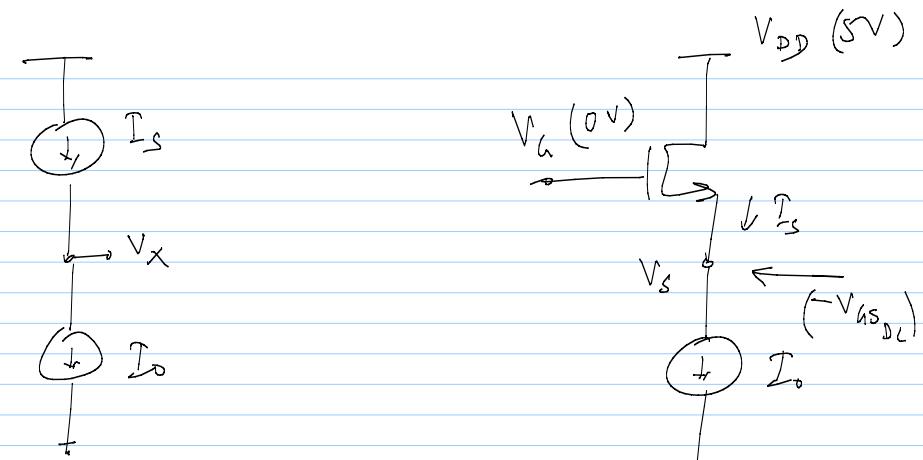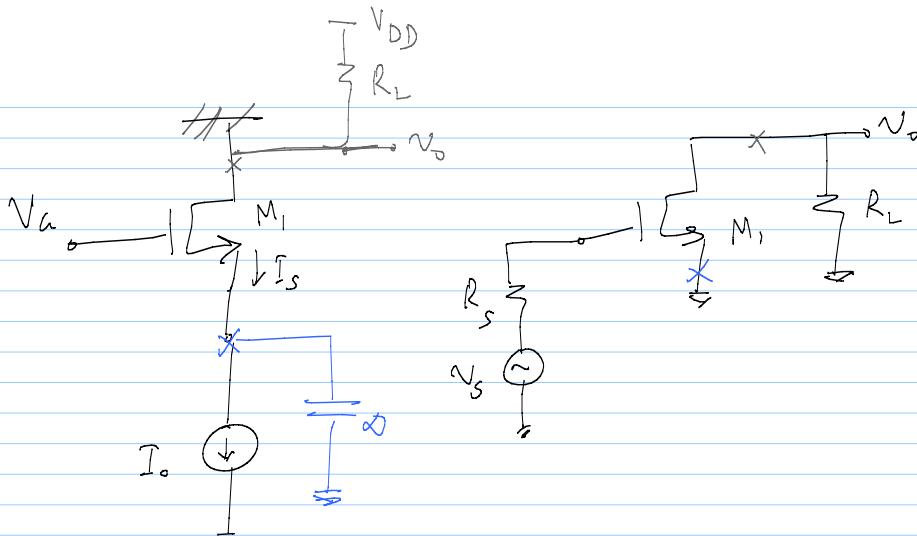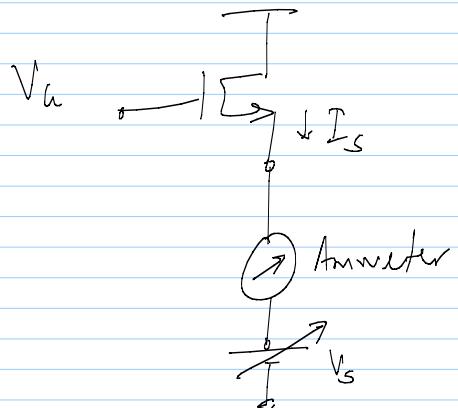

$$\text{If } I_s > I_o \Rightarrow V_X \uparrow \left\{ \begin{array}{l} V_S \uparrow \\ V_{AS} \uparrow \end{array} \right\}$$
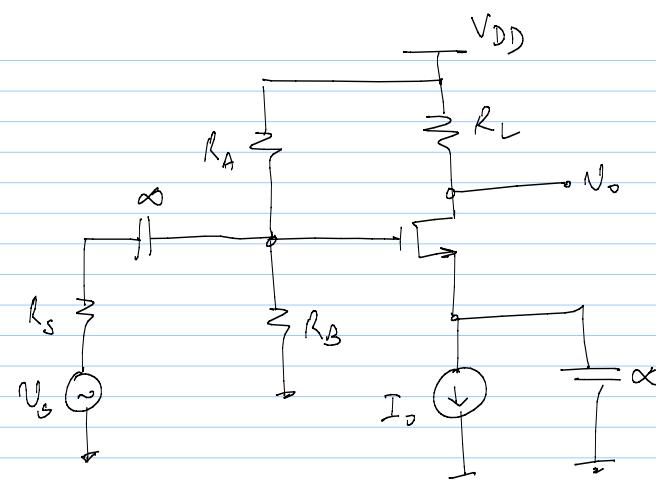
$$I_s < I_o \Rightarrow V_X \downarrow \left\{ \begin{array}{l} V_{AS} \uparrow \\ V_S \downarrow \end{array} \right\}$$



$$V_{AS,DC} = \frac{R_B}{R_A + R_B} \cdot V_{DD}$$