

17/9/14


lec 23

Measured values



- $I_D$
- $I_S$
- $I_B$
- $I_S$

Driven values


- $V_A$  ✓
- $V_S$  ✓
- $V_S$
- $V_A$

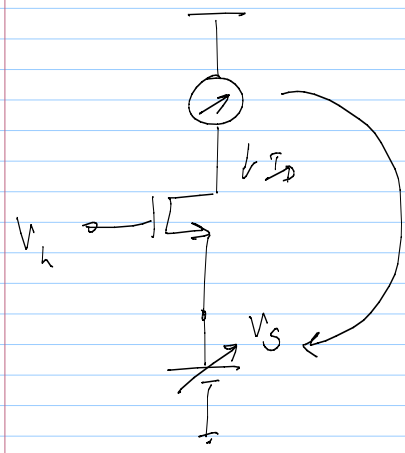

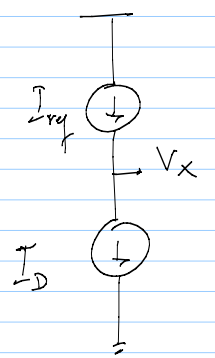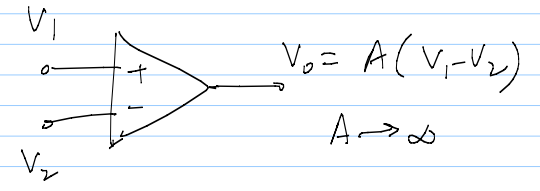$I_D > I_{ref} \Rightarrow \uparrow V_S$   
 $I_D < I_{ref} \Rightarrow \downarrow V_S$



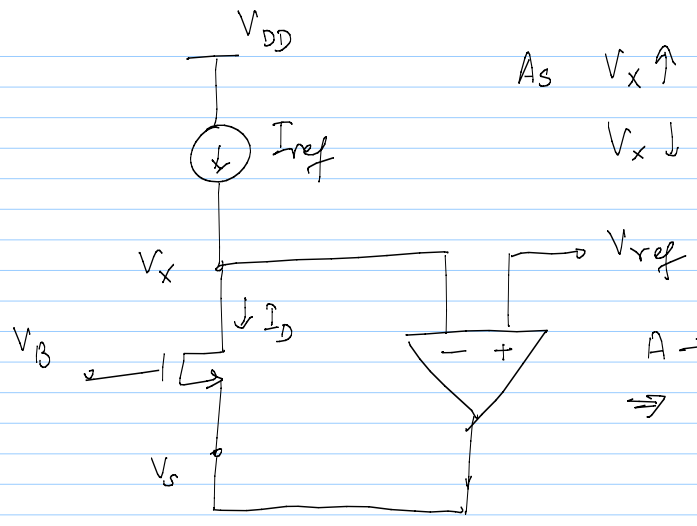$I_D > I_{ref} \Rightarrow V_x \downarrow$   
 $I_D < I_{ref} \Rightarrow V_x \uparrow$





As  $V_x \uparrow \Rightarrow V_S \downarrow$   
 $V_x \downarrow \Rightarrow V_S \uparrow$

$A \rightarrow \infty$   
 $\Rightarrow V_x \rightarrow V_{ref}$

For sat. operation  $\Rightarrow V_D > V_A - V_T$   
 $V_{ref} > V_B - V_T$


$$V_S = V_B - V_{as} |_{I_{ref}} = V_D - \left[ V_T + \sqrt{\frac{2I_{ref}}{\mu_n \text{box} \left(\frac{W}{L}\right)}} \right]$$

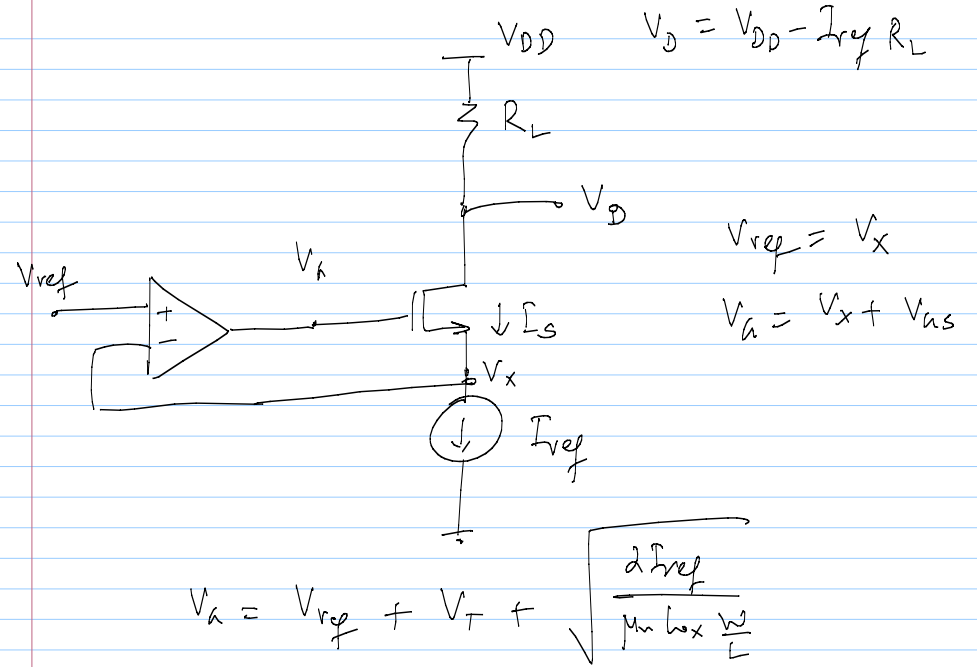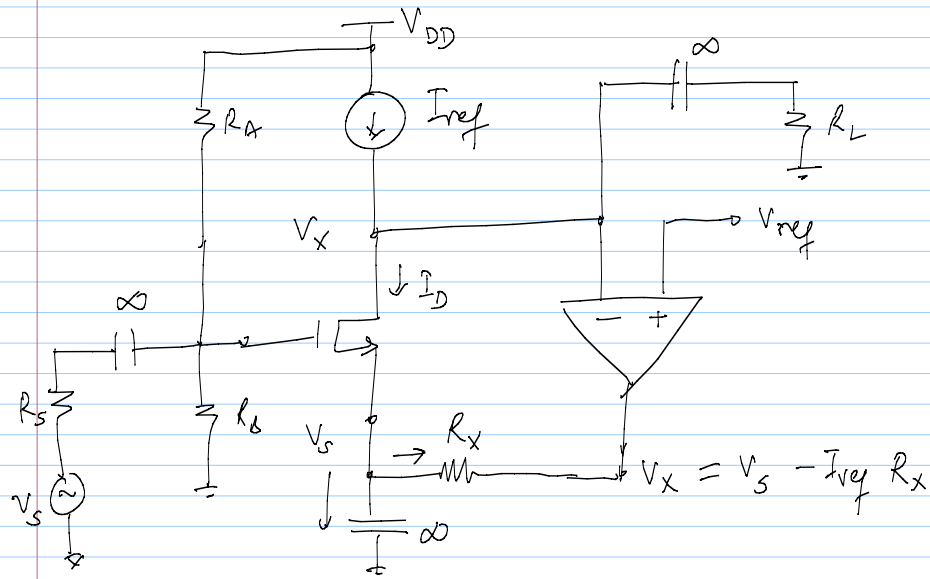

### Controlled Sources

	$Z_{in}$	$Z_{out}$
VCCS	$\infty$	0
VCCS	$\infty$	$\infty$
CCVS	0	0
CCCS	0	$\infty$

### Opamp

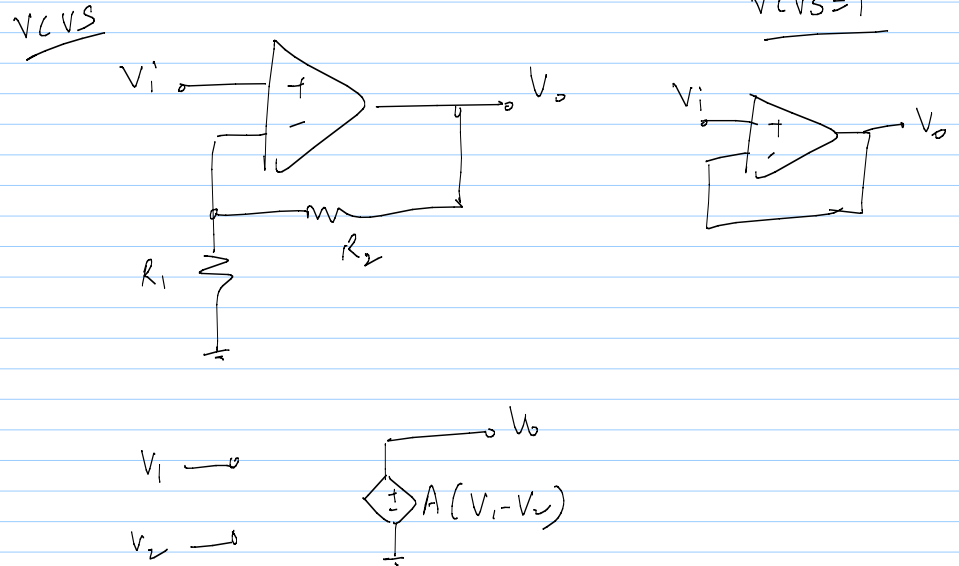


CCVS



We have }  $I_{in}$

We want }  $V_{out} = R I_{in}$

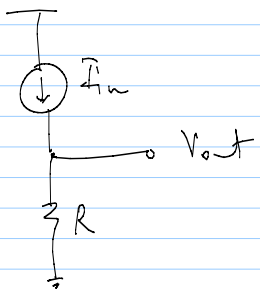we want  
 $Z_{in} = 0$   
 $Z_{out} = 0$


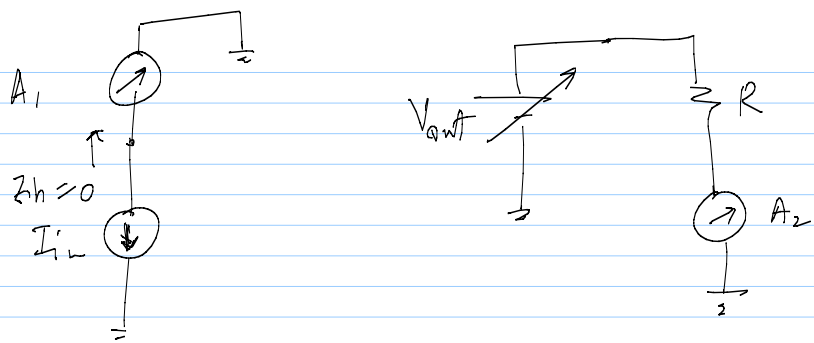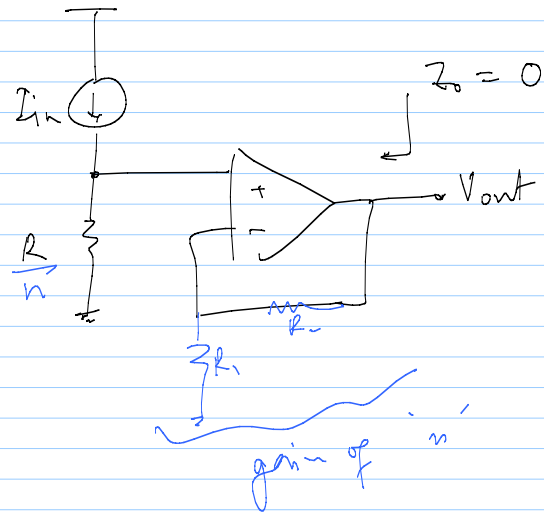
$$V_{out} = R I_{in} \Rightarrow I_{in} = \frac{V_{out}}{R}$$



Compare  $A_1$  &  $A_2$   
 Drive  $V_{out}$  such that  $A_1 = A_2$

→ put them in series

